

# Overcoming Offset

Prof. Kofi Makinwa

Electronic Instrumentation Laboratory / DIMES

Delft University of Technology

Delft, The Netherlands

email: [k.a.a.makinwa@tudelft.nl](mailto:k.a.a.makinwa@tudelft.nl)





# Motivation

- The offset of amplifiers realized in standard IC technologies is typically in the **millivolt** range
- However, many analog circuits e.g. opamps, comparators, ADCs and DACs require amplifiers with **microvolt** offsets
- Also, many sensors (e.g. thermopiles, bridges, hall-effect sensors etc.) output DC signals that need to be processed with **microvolt** precision
- This tutorial will focus on **dynamic** offset-cancellation (DOC) techniques, with which offset can be reduced to the **microvolt** level.

# Outline

- Differential amplifiers
  - Offset and  $1/f$  noise
- Dynamic Offset Cancellation (DOC)
  - Auto-zeroing
  - Correlated Double-Sampling (CDS)
  - Chopping
- Summary
- References

# What is Offset?

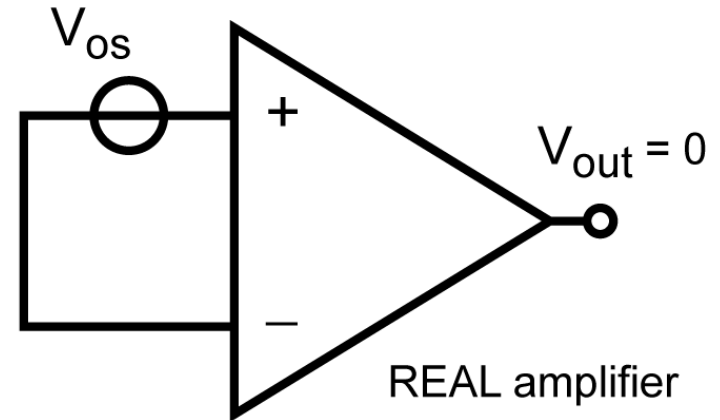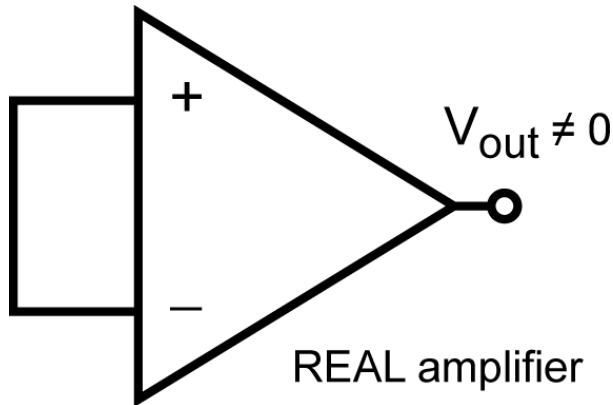


- When the input of a REAL amplifier is shorted,  $V_{out} \neq 0$ !
- The **offset**  $V_{os}$  is the input voltage required to make  $V_{out} = 0$ . It is typically in the range:  $100\mu\text{V}$  to  $10\text{mV}$ .
- Note: In CMOS, input offset currents are negligible.

# Differential Amplifiers

Differential amplifiers are often used to amplify DC signals.

Their balanced structure is

 - Nominally offset free
- Rejects common-mode and power supply interference
- Easily realized in both CMOS and bipolar technologies



# Offset in Differential Amplifiers

Component mismatch


e.g.  $R_1 \neq R_2$ ,  $M_1 \neq M_2 \Rightarrow$  **offset**

Mismatch is mainly due to

- Doping variations
- Lithographic errors
- Packaging & local stress

All things being equal

 
- Bipolar  $\Rightarrow V_{os} \sim 0.1\text{mV}$
- CMOS  $\Rightarrow V_{os}$  is 10 -100x worse!


 
# Amplifier Behaviour Near DC

Characterized by

- Offset
- Drift
- $1/f$  (flicker) noise
- Thermal noise
- $1/f$  corner frequency



# What to Do?

Offset and  $1/f$  noise are part of life!

But we can reduce offset “enough” by

1. Using “large” devices and good layout<sup>1</sup>  $\Rightarrow$  1mV
2. Trimming  $\Rightarrow$  100 $\mu$ V drift over temperature (MOS)
3. Dynamic offset-cancellation (DOC) techniques  $\Rightarrow$  1 $\mu$ V

DOC techniques also


- Reduce drift and  $1/f$  noise
- Improve PSRR and CMRR



# Mismatch


Determined by:

 1. Lithographic accuracy e.g.  $R = \rho L/W$   
 $\Rightarrow \Delta R/R \sim \Delta L/L + \Delta W/W$   
 $\Rightarrow$  Matching improves with area!




2. Doping Variations  $\Rightarrow \Delta R/R$  limited to 0.1% even for large neighboring resistors
3. Mechanical stress due to metal lines or packaging

# Good Layout Helps!

 

Bad Layout

Dummy elements

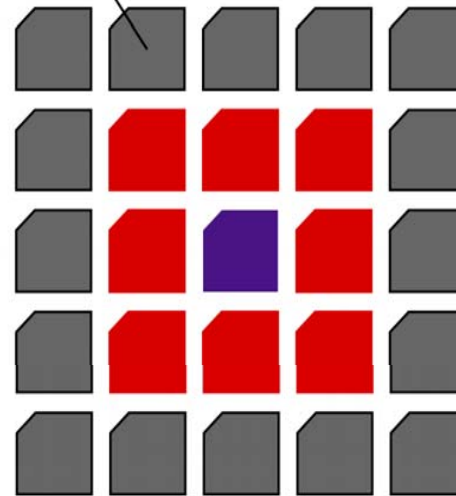

Good Layout

**Good layout**  $\Rightarrow$

- Large Devices
- Exclusive use of unit cells (and dummies)
- Currents in unit cells flow in the same direction

# Trimming

⇒ Cancel offset by adjusting an on-chip component

- ✓ Low circuit complexity
- ✓ Minimal effect on circuit bandwidth
  
- ✗ Requires test equipment
- ✗ Does not reduce drift or  $1/f$  noise
- ✗ Requires an analog memory, e.g.
  - Fusible links (Zener diodes)
  - Laser-trimmed resistors
  - PROM + DAC (component array)

# Trimming a BJT Differential Amp


$$V_{os} = V_T \left( \frac{\Delta R}{R} + \frac{\Delta I_S}{I_S} \right)$$

$$V_T = kT/q = 26\text{mV} @ 300\text{K}$$

- $V_{OS} \sim 0.1\text{mV}$  is possible!

After trimming (via  $\Delta R$ )

 - $V_{OS} \sim 0$
- Also temperature coefficient of  $V_{OS}$  ( $\text{TC}V_{os}$ )  $\sim 0$



# Trimming a MOSFET Diff. Amp (1)


$$V_{os} = \Delta V_{TH} + \frac{I_D}{g_m} \left( \frac{\Delta R}{R} + \frac{\Delta \beta}{\beta} \right)$$

where  $\beta = \mu C_{ox}(W/L)$

- $\Delta V_{TH} \sim 1\text{mV}$   
and temp. independent
- $I_D/g_m$  is temp. dependent

After trimming

 - $V_{OS} \sim 0$  but  $TCV_{OS} \sim 1\mu\text{V}/^\circ\text{C}$
- Much worse than bipolar!



# Trimming a MOSFET Diff. Amp (2)


$$V_{os} = \Delta V_{TH} + \frac{I_D}{g_m} \left( \frac{\Delta R}{R} + \frac{\Delta \beta}{\beta} \right)$$

where  $\beta = \mu C_{ox}(W/L)$

Better trimming

- Trim  $V_{TH}$  &  $\beta$  *independently* at room temperature!  
 $\Rightarrow TCV_{OS} \sim 0.33\mu V/^{\circ}C$  ( $3\sigma$ )

M. Bolatkale et al., ISSCC 08

 

# Trimming: Summary

- Simple, does not limit BW
- Does not reduce drift or  $1/f$  noise
- Requires test equipment and an analog memory
  
- Works very well with BJT diff. amps since it nulls both  $V_{OS}$  and  $TCV_{OS}$
- Works less well with MOSFET diff. pairs poorly defined  $TCV_{OS} \Rightarrow 100\mu V$  drift over temp.
  
- Higher performance  $\Rightarrow$  Dynamic offset cancellation

# Dynamic Offset Cancellation (DOC)


Two basic methods<sup>2</sup>

1. Measure the offset somehow and then subtract it from the input signal  $\Rightarrow$  Auto-zeroing
2. Modulate the offset away from DC and then filter it out  $\Rightarrow$  Chopping

Both methods also reduce low frequency noise and improve common-mode & power supply rejection




# Auto-zero Principle (1)

 

Auto-zero phase

- $S_1, S_2$  closed,  $S_3$  open  $\Rightarrow V_{out} = V_{os}$   
 $\Rightarrow$  offset stored on  $C_{az}$
- Amplifier is unavailable


# Auto-zero Principle (2)

 

Amplification phase:

- $S_1, S_2$  open,  $S_3$  closed  $\Rightarrow V_{in}$  is amplified
- *Finite* voltage gain  $A \Rightarrow$  error in sampled offset  $\Rightarrow$  input-referred residual offset  $V_{res} = V_{os}/(A+1)$
- Charge injection is also a problem ...

# Charge Injection (1)

 


Consists of two components

1. Channel charge,  $Q_{ch} = WLC_{ox}(V_{GS} - V_t)$
2. Charge transfer via the overlap capacitance between gate and source/drain  $\Rightarrow$  clock feed-through

Problematic when a MOSFET switches **OFF**.

# Charge Injection (2)


 


CI error voltage  $\Delta V_{inj}$  depends on many factors<sup>3,4</sup>


- Source voltage and impedance
- Clock amplitude & slew rate
- Transistor area (WL) (smaller  $\Rightarrow$  better)
- Value of  $C_{az}$  (larger  $\Rightarrow$  better)
- In  $0.7\mu\text{m}$  CMOS, minimum-size NMOS,  $2.5\text{V}$  step &  $10\text{pF} \Rightarrow \Delta V_{inj} \sim 250\mu\text{V}$
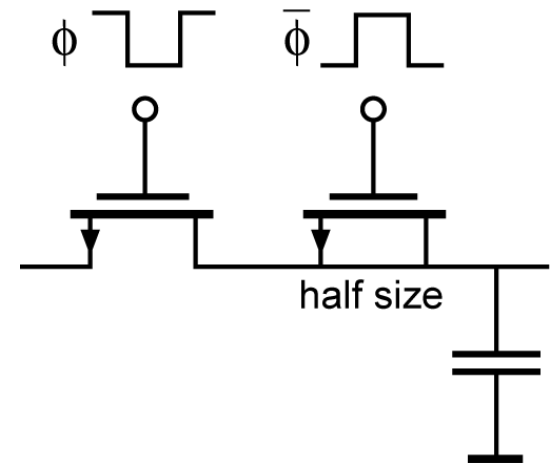 
# Mitigating Charge Injection (CI)

- Use differential topologies
  - ⇒ CI is a common-mode signal
  - ⇒ 1<sup>st</sup> order cancellation
- Use small switches & big caps (subject to noise & BW requirements)
- For single-ended topologies dummy switches help<sup>3,4</sup>
- **But** area of main switch will be ~2x minimum size ⇒ more CI ⇒ limited benefit




# Sampling the offset: $kT/C$ noise

 

- Thermal noise of  $R_{on}$  is filtered by  $C_{az}$
- When the switch is opened the instantaneous noise voltage is held on  $C_{az}$
- Total noise power =  $kT/C_{az}$  (10pF @ 300K  $\Rightarrow$  20.3 $\mu$ V)
- Large capacitance  $\Rightarrow$  accurate sampling of  $V_{os}$

# Output-Referred Auto-zeroing

 

$$V_{\text{res}} = \Delta V_{\text{inj}}/A_1$$

- Amplifier's offset is now completely cancelled<sup>5,6</sup>
- Gain of 1<sup>st</sup> amplifier reduces effects of charge injection and  $kT/C$  noise  $\Rightarrow$  sampling capacitors can be smaller
- **But** too much gain  $\Rightarrow$  clipping!  $\Rightarrow A_1$  is typically  $< 200$

# Residual Offset of Auto-zeroing

Determined by

- Charge injection
- Leakage on  $C_{az}$
- Finite amplifier gain

In practice

- Minimum size switches
- $C_{az}$  as large as possible (sometimes external)
- Multi-stage amplifier topologies

Results in residual offsets of 1-10 $\mu$ V



# Residual Noise of Auto-zeroing (1)

$$V_{n,az}(f) = V_n(f) * (1 - H(f))$$


$H(f)$  is the frequency response of the S&H

$H(f) = \text{sinc}(\pi f/f_s) \Rightarrow$  LPF


$\Rightarrow 1 - H(f)$  is a HPF

$\Rightarrow$  reduction of both offset and  $1/f$  noise

 $\Rightarrow$  but sampled thermal noise will fold back to DC





# Residual Noise of Auto-zeroing (2)

 


- **Noise** bandwidth  $B > f_s$  (due to settling considerations)  $\Rightarrow$  input noise will fold back (alias) to DC
- The result is then LP filtered by the  $\text{sinc}(\pi f/f_s)$  function

# Residual Noise of Auto-zeroing (3)

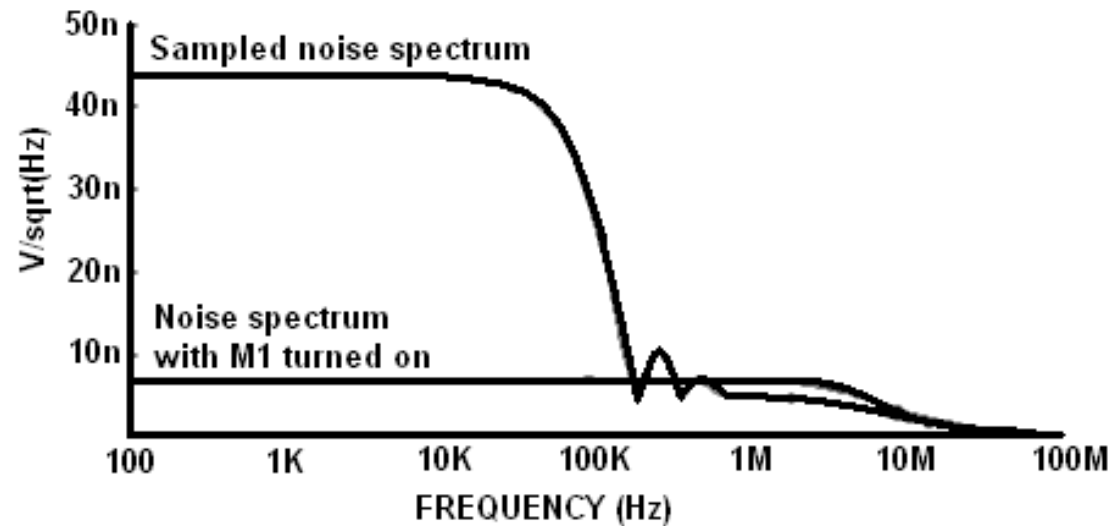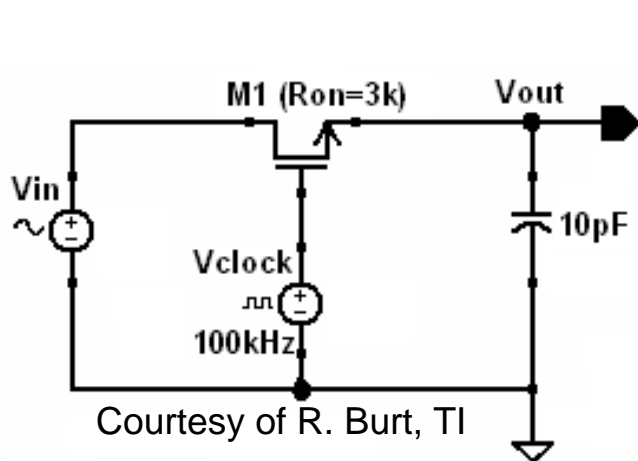

- S&H with 100kHz clock & 50% duty-cycle
- Noise aliasing  $\Rightarrow$  6x increase in LF noise voltage!
- Notches at multiples of  $2f_{\text{clock}}$  due to 50% duty cycle<sup>2</sup>
- Sampled noise spectrum obtained with  $P_{\text{noise}}^{9,10}$

# Residual Noise of Auto-zeroing (4)

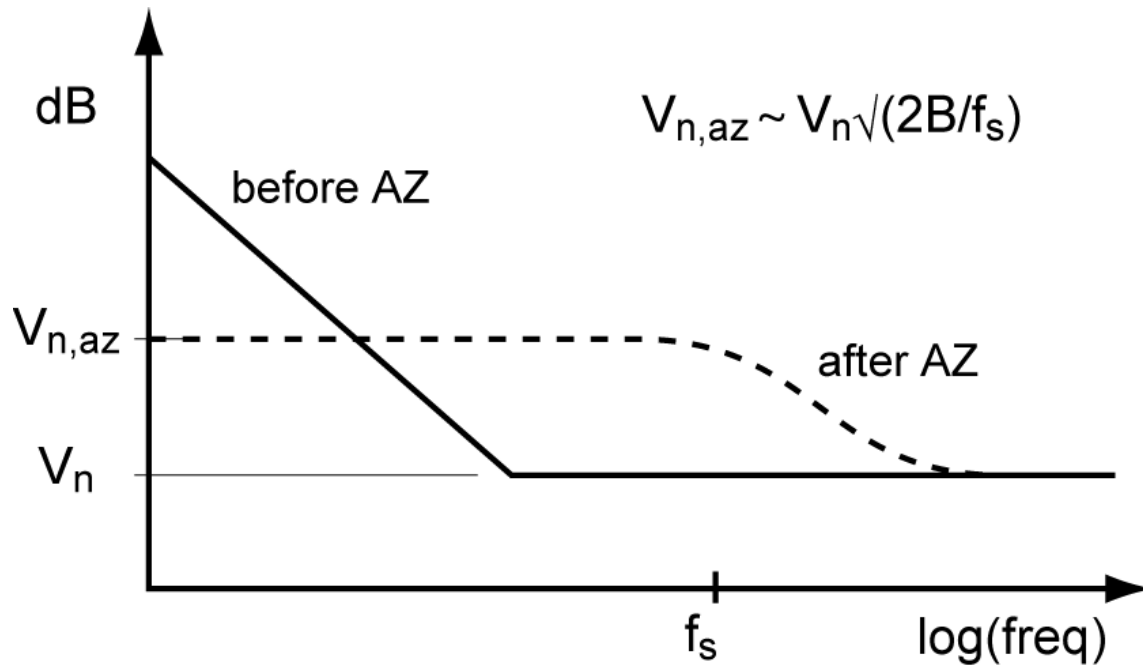

- Detailed analysis<sup>2</sup>  $\Rightarrow$  significant reduction of  $1/f$  noise **IF**  $f_s \gg 1/f$  corner frequency
- Noise aliasing  $\Rightarrow$  LF power increased by the under-sampling factor (USF) =  $2B/f_s \Rightarrow$  factor 3 to 6 in volts

# Continuous Output


- Basic auto-zero principle  $\Rightarrow$  the amplifier is not continuously available

## Solutions

- Two AZ'ed amplifiers connected in parallel  
 $\Rightarrow$  Ping-pong architecture
- An AZ'ed amplifier nulls the offset of another amplifier  
 $\Rightarrow$  Offset stabilization
 
# AZ Ping-Pong Amplifier


- Input signal “bounced” between two auto-zeroed amplifiers<sup>11,12</sup>
- Output  $V_{out}$  is then a quasi-continuous signal
- But switching spikes limit performance
- Randomized switching reduces spikes<sup>13</sup>



# Offset Stabilization (OS)

Negative feedback  
⇒ offset visible at input


High bandwidth  
main amplifier

 

- Also called continuous-time AZ
- Low bandwidth, low offset compensating amplifier  
⇒ Auto-zeroed or chopped

 
# AZ Offset-Stabilized Amplifier

- Auto-zeroed nulling amp cancels the offset of main amplifier<sup>14,15</sup>
- Continuous output and less spikes
- But poor overload performance, i.e. when  $V_+ - V_- > V_{os}$
- Amplifier cannot be used as a comparator






# Correlated Double Sampling (CDS)

 

- Sometimes only a signal **difference** is required e.g. in image sensors
- Phase 1:  $V_1 = A( V_{in1} + V_{os} )$
- Phase 2:  $V_2 = A( V_{in2} + V_{os} )$
- $\Rightarrow (V_1 - V_2) = A(V_{in1} - V_{in2})$
- CDS also suppresses  $1/f$  noise

# CMOS Image Sensors

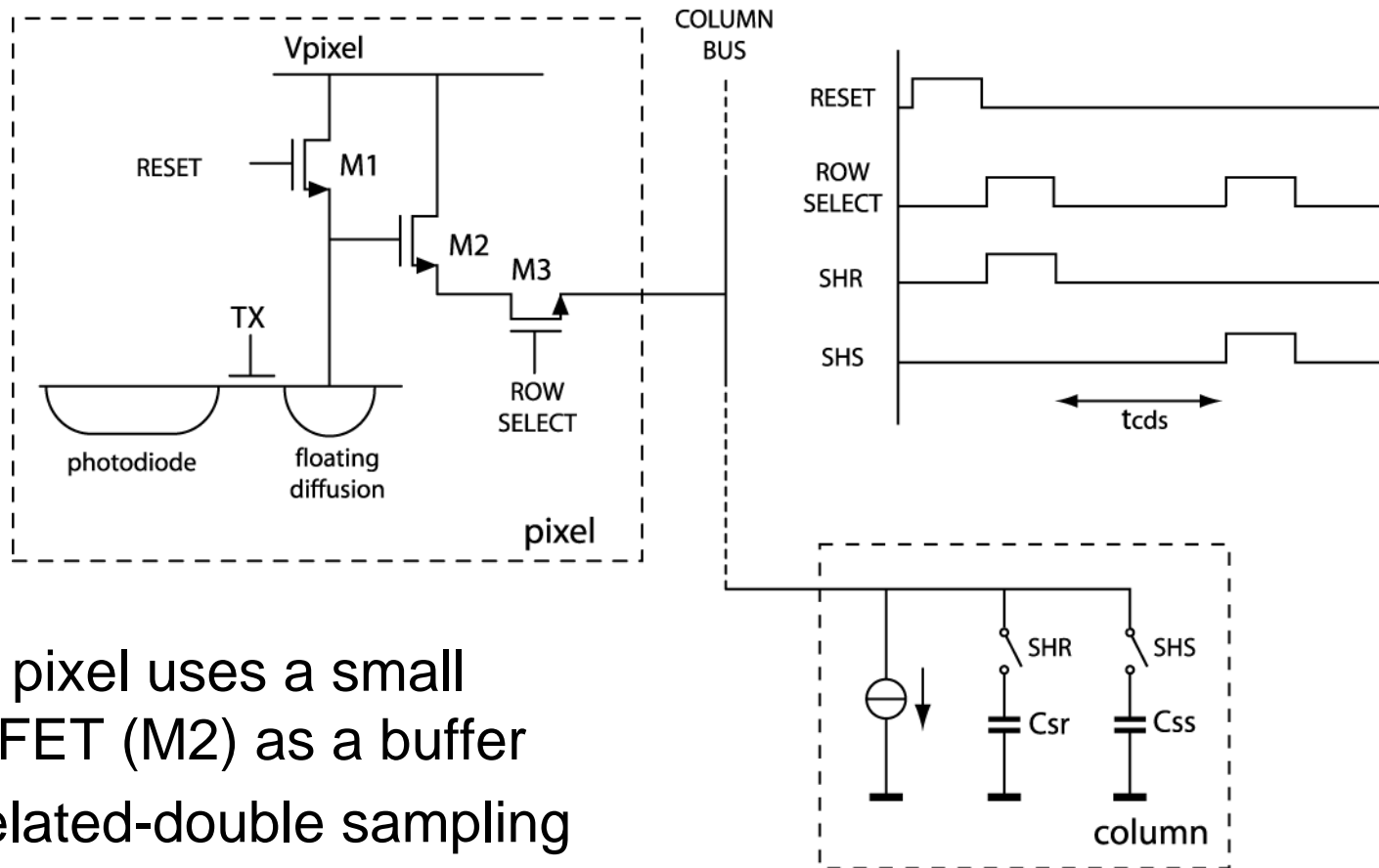


- Each pixel uses a small MOSFET (M2) as a buffer
- Correlated-double sampling removes offset and  $1/f$  noise

# Auto-Zeroing: Summary

- Offsets in the range of 1-10 $\mu$ V can be achieved
- No loss of bandwidth with appropriate amplifier topologies (ping-pong, offset-stabilization)
- Sampled data technique  $\Rightarrow$  kT/C noise is an issue
- Noise aliasing will occur  $\Rightarrow$  increased LF noise
- DOC technique of choice in sampled-data systems e.g. switched-capacitor filters, ADCs etc.


# Chopping Principle

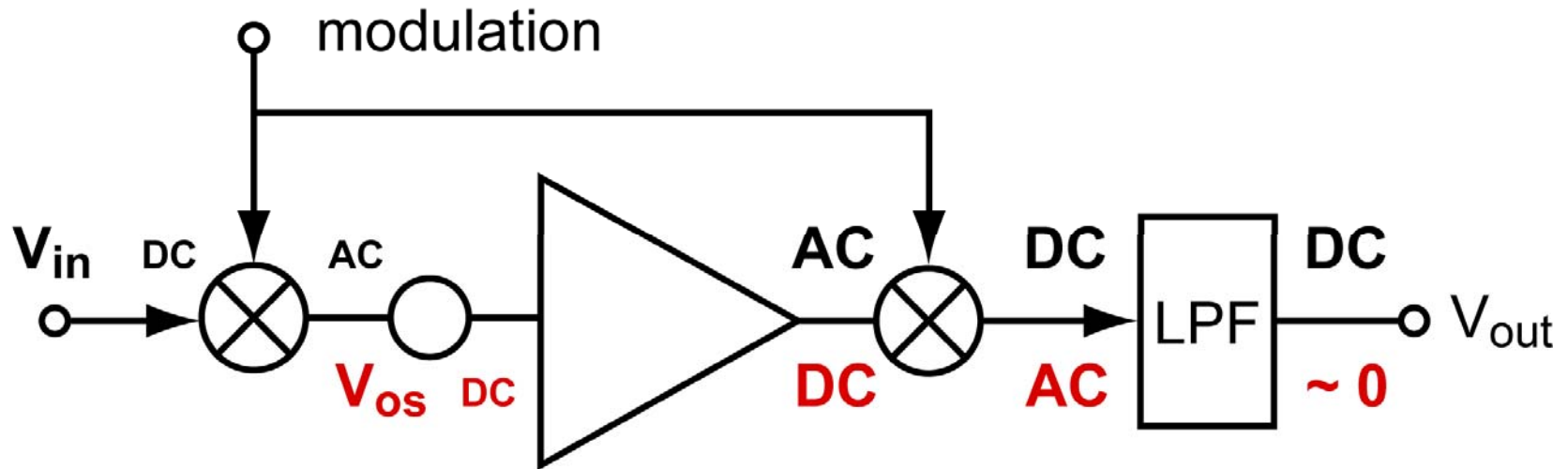

Signal is modulated, amplified and then demodulated<sup>16</sup>


- + Output signal is continuously available
- Low-pass filter required

# Square-wave Modulation

 


- Easily generated modulating signal
- Modulator is a simple polarity-reversing switch
- Switches are easily realized in CMOS

# Chopping in the Time Domain

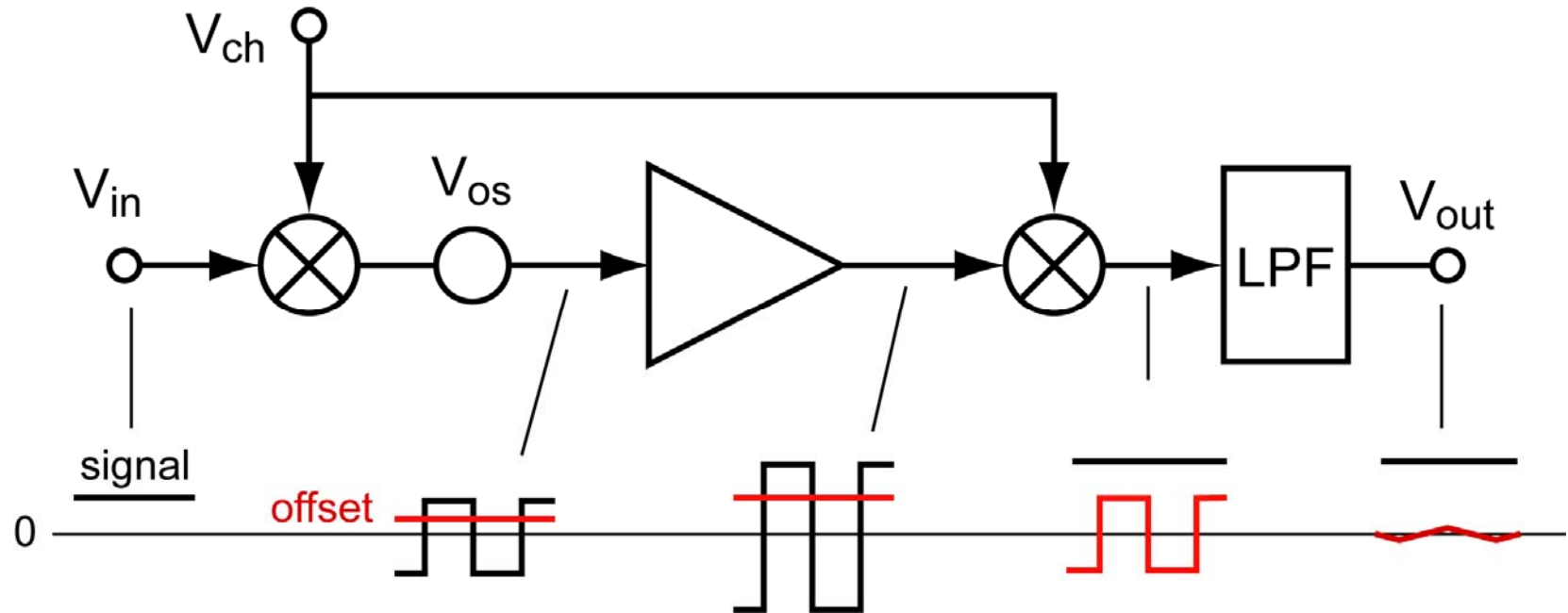


- $V_{res} = 0$  **IF** duty-cycle of  $V_{ch}$  is exactly 50%  $\Rightarrow$  flip-flop
- If  $V_{os} = 10\text{mV}$  &  $f_{ch} = 50\text{kHz}$ , then 1ns skew  $\Rightarrow V_{res} = 1\mu\text{V}$

# Chopping in the Frequency Domain

 


# Residual Noise of Chopping

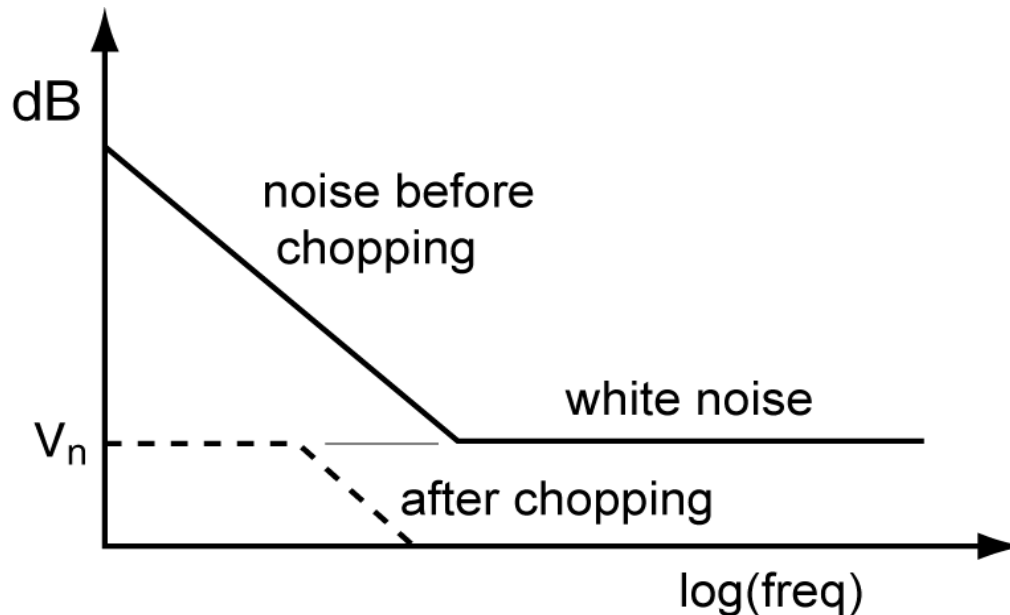

- $1/f$  noise is **completely** removed  
**IF**  $f_{ch} > 1/f$  corner frequency
- Significantly better than auto-zeroing!




# Bandwidth & Gain Accuracy

 



- Limited BW  $\Rightarrow$  lower effective gain  $A_{\text{eff}}$   
**and** chopping artifacts at even harmonics of  $f_{\text{ch}}$
- Gain error  $< 10\% \Rightarrow \text{BW} > 6.4f_{\text{ch}}$

# Chopper Opamp with Feedback

 


- Feedback resistors  $\Rightarrow$  Accurate gain<sup>17,18</sup>
- To suppress  $V_{os2}$ ,  $A_1$  should have high gain
- Miller capacitors  $C_m$  also suppress ripple
- Minimum ripple  $\Rightarrow$  high chopping frequencies

# Residual Offset of Chopping (1)

  

- Due to mismatched charge injection and clock feed-through at the input chopper<sup>19,20</sup>
- Causes a typical offset of 1-10 $\mu$ V
- Input spikes  $\Rightarrow$  bias current (typically 50pA)

# Residual Offset of Chopping (2)

 

- Residual offset<sup>2</sup> =  $2f_{\text{ch}} V_{\text{spike}} \tau$
- Spike shape ( $\tau$ ) depends on source impedance e.g. feedback resistors around an opamp

# Design Considerations

## Input chopper

- Use minimum size switches
- Good layout  $\Rightarrow$  symmetric, balanced clock coupling
- Ensure that switches “see” equal impedances
- Use a flip-flop to ensure an exact 50% duty-cycle


## Chopping frequency $f_{ch}$

- Higher than  $1/f$  noise corner frequency
- Not **too** high, as the residual offset increases with  $f_{ch}$


Amplifier BW  $\gg f_{ch}$  to minimize gain errors
 
# Chopped Transconductor<sup>22</sup>

- Choppers see low & symmetric impedances
- Allows high freq chopping
- PMOS chopper demodulates signal
- NMOS chopper DEMs NMOS current sources




# Lower Residual Offset

 

- Residual offset<sup>2</sup> =  $2f_{\text{ch}} V_{\text{spike}} \tau$
- Low residual offset  $\Rightarrow$  reduce chopping frequency, reduce load impedances OR reduce spike amplitude

# Band-Pass Filtering

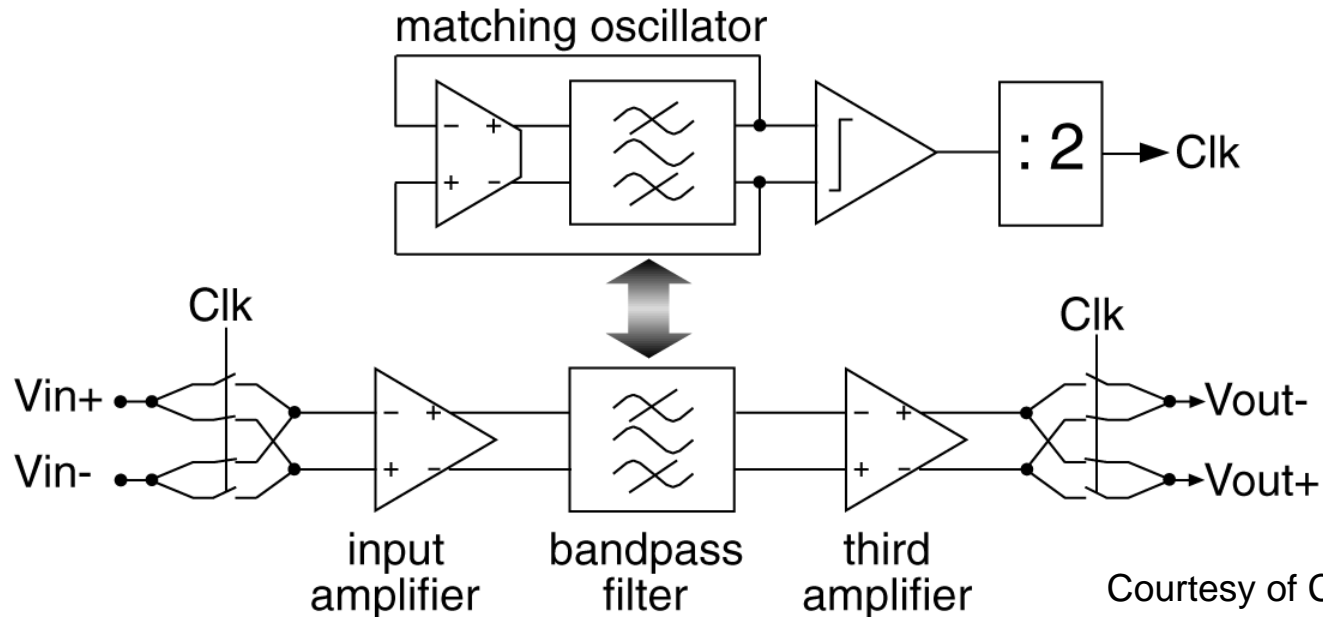


Courtesy of C. Hagleitner, IBM

- Spike spectrum is “whiter” than that of modulated signal  
⇒ BP filter will reduce **relative** spike amplitude<sup>19,23,24</sup>
- Clock frequency tracks BP filter's center frequency  
⇒ low Q filter,  $Q \sim 5$
- Residual offset  $\sim 0.5\mu\text{V}$ !




# Nested Chopping

 

- Inner HF chopper removes  $1/f$  noise
- Outer LF chopper removes residual offset<sup>21</sup>
- Residual offset  $\sim 100\text{nV}$ , but reduced bandwidth
- Note: input choppers should not be merged!

# Dead-Banding

 


- During dead-band amplifiers output is tri-stated<sup>26,27,28</sup>
- Residual offset  $\sim 200\text{nV}$ !
- BUT loss of gain and aliasing due to S&H action  
 $\Rightarrow$  slightly worse noise performance

# Dealing with Spikes: Overview

- BP Filtering:  $\sim 0.5\mu\text{V}$  offset, complex clock timing
- Dead-banding:  $\sim 200\text{nV}$  offset, wide BW
- Nested chopping:  $\sim 100\text{nV}$  offset, but limited BW

Last two techniques represent best compromise between offset magnitude and circuit complexity


# Chopping Artifacts (Ripple)

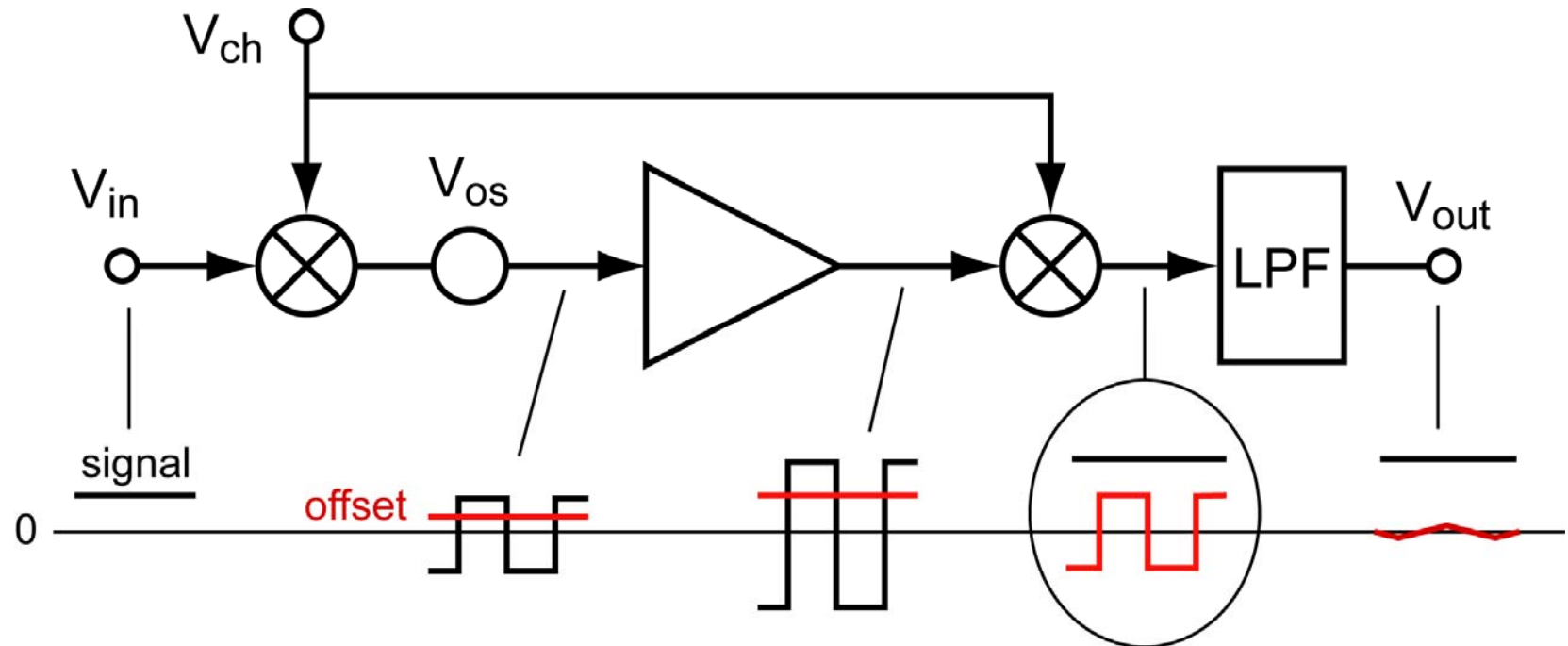

Modulated offset  $\Rightarrow$  chopping artifacts (ripple)


- Can be removed by a low-pass filter
- BUT filter cut-off frequency must be quite low  $\Rightarrow$  difficult to realize on chip

# AC Coupling

 


- AC coupling blocks the amplifier's offset  
⇒ no output ripple!
- But cut-off frequency must again be quite low

# DC Servo Loop

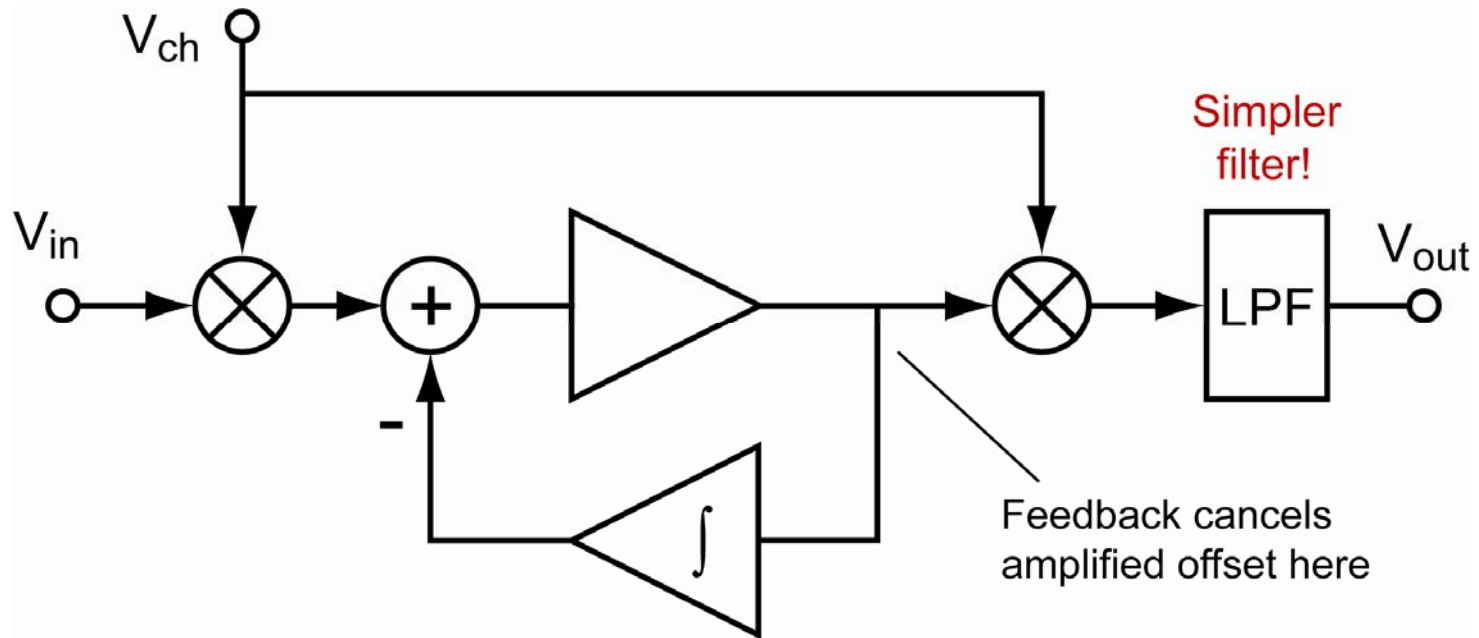


- DC “servo” loop suppress the amplifier’s offset<sup>34,35</sup>
- Integrator is not in the main signal path  
⇒ much easier to realize a low cut-off frequency
- Residual ripple can be removed by a simple LPF

# Auto-zeroing and Chopping

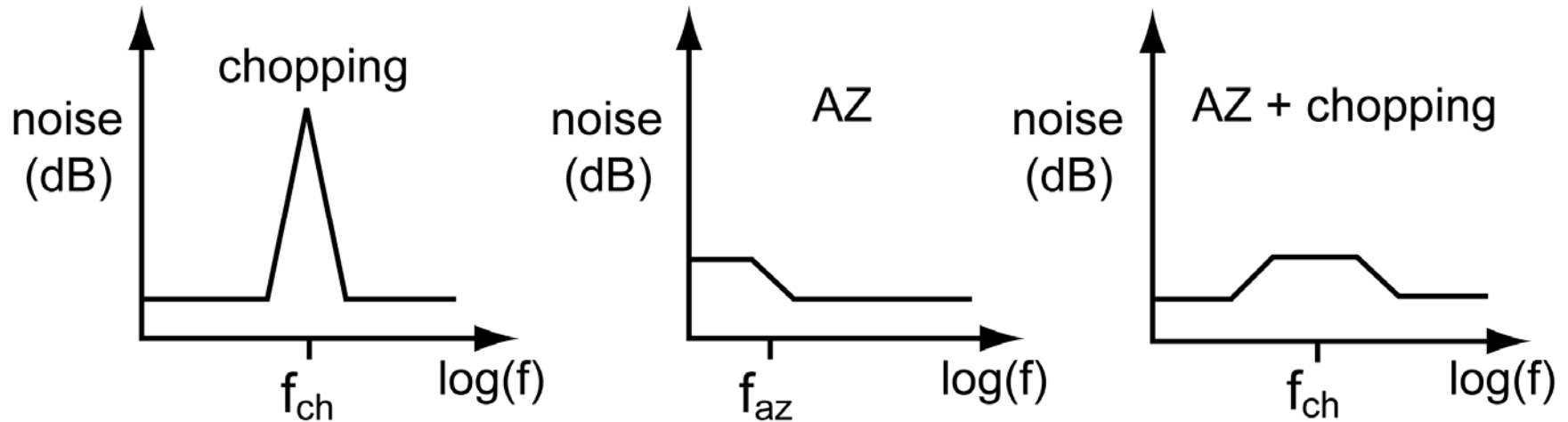

- Compared to standard AZ, significantly improves LF noise performance<sup>30,31,32,33</sup>
- Much less ripple than with chopping alone
- Choosing  $f_{ch} = 2f_{az} \Rightarrow$  residual offset of auto-zeroing is exactly averaged  $\Rightarrow$  aliased noise has notch at DC


# Switched Capacitor Filter

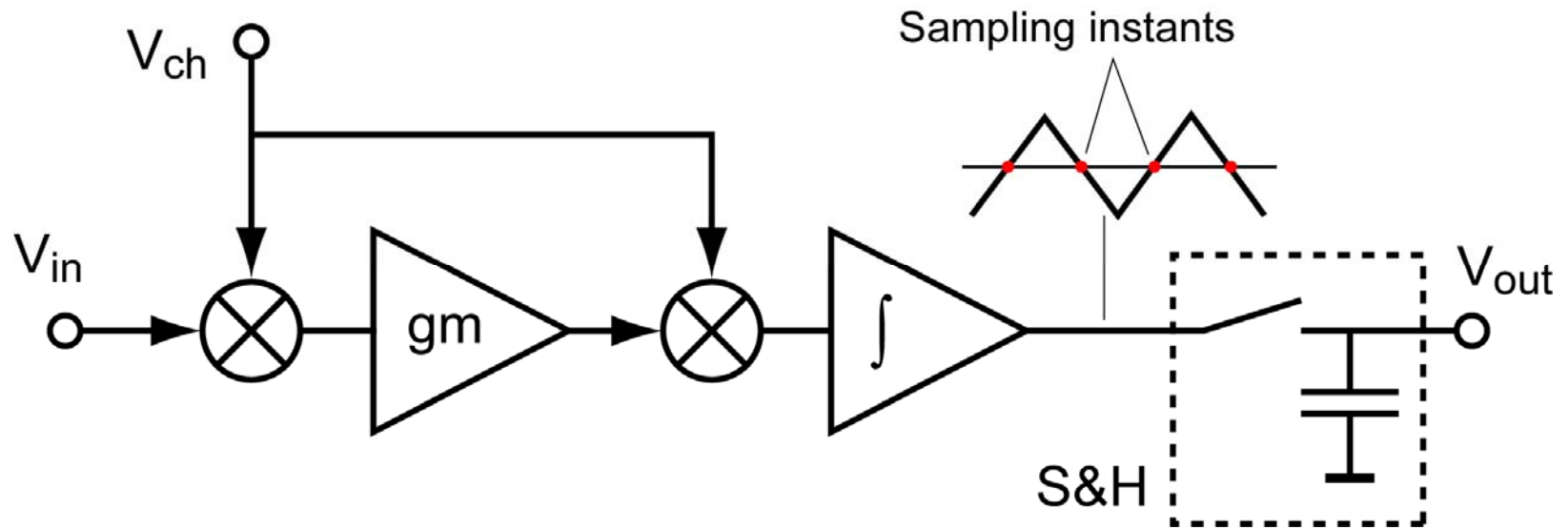

- Chopped offset is integrated & the triangular ripple is then sampled at the zero-crossings<sup>9,37,38</sup>
- SC filter essentially eliminates residual ripple
- Filter introduces delay and a (small) noise penalty



# Digital Filtering

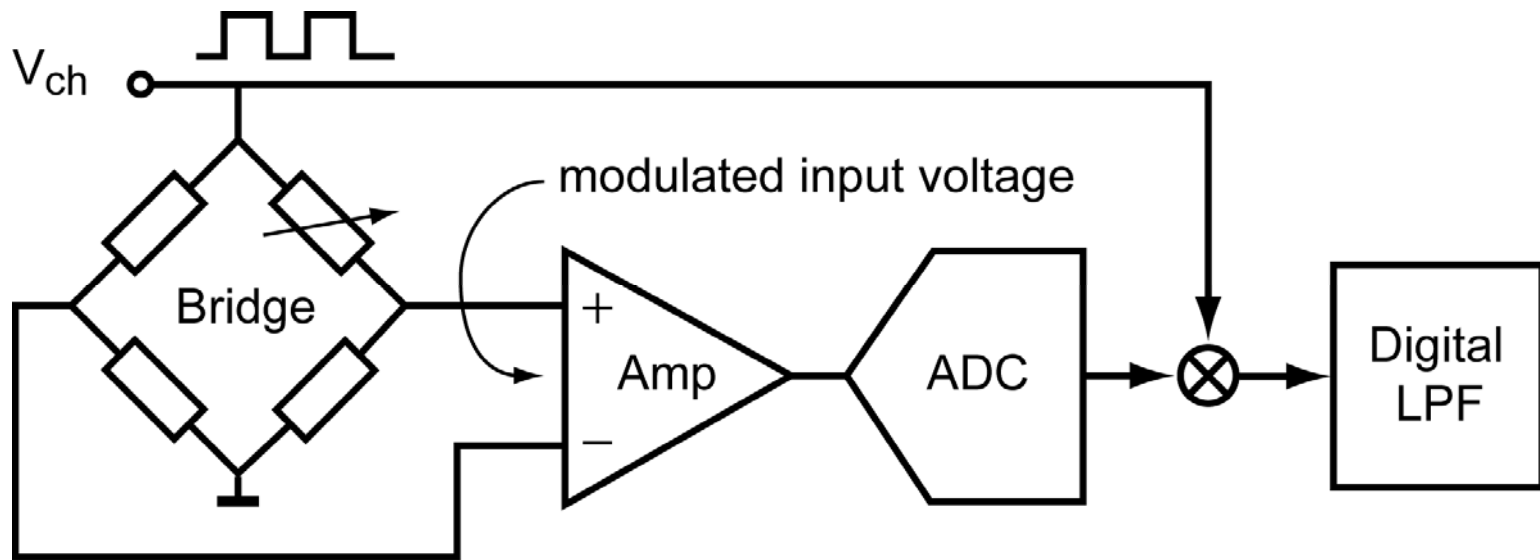

- Chopped signal is digitized
- Demodulation is done digitally<sup>31,39</sup>
- Chopper artifacts are removed by a digital LPF  
e.g. a sinc filter with notches at  $f_{ch}$

# Dealing with Artifacts: Overview

Reduce the amplifier's initial offset

- Auto-zeroing and chopping: increased noise
- DC servo: still requires some analog filtering
- Switched capacitor filtering

Digital Filtering

- Very low cut-off frequencies can be realized
- Decimation filter of a  $\Sigma\Delta$  ADC can be used to remove chopper artifacts  $\Rightarrow$  no extra overhead

# Chopping: Summary

- Offsets in the range of 50nV-10 $\mu$ V can be achieved
- Timing skew limits offset reduction to about 60dB
- Fundamental loss of bandwidth (unless offset-stabilized topologies can be used)
- Eliminates  $1/f$  noise, noise floor set by thermal noise
- DOC technique of choice when noise or offset performance is paramount e.g. in biomedical amplifiers, low-power opamps, smart sensors etc.

# Some Caveats

- Chopping and auto-zeroing rely on amplifier linearity
- Amplifier non-linearity will result in a residual offset!
- Presence of timing jitter  $\Rightarrow$  variable settling (AZ) or non-50% duty-cycles (chopping)  $\Rightarrow$  voltage noise
- Finite switch resistance  $\Rightarrow$  trade-off between CI, thermal noise and BW limitations

# Summary

- Offset and  $1/f$  are part of life!
- Trimming
  - reduces offset but not  $1/f$  noise
  - simple, no loss of bandwidth
- Auto-zeroing
  - eliminates  $1/f$  noise, but noise aliasing  $\Rightarrow$  LF noise
  - Auto-zero period  $\Rightarrow$  Loss of bandwidth
  - CT operation  $\Rightarrow$  OS and Ping-pong topologies
- Chopping
  - eliminates  $1/f$  noise  $\Rightarrow$  best noise efficiency
  - LPF  $\Rightarrow$  loss of bandwidth (unless OS is used)
- Nested DOC techniques  $\Rightarrow$  sub-microvolt offset