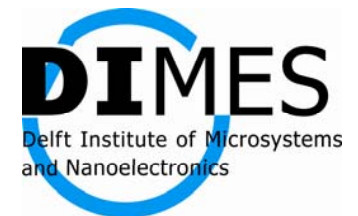


Designing Interface Electronics for Smart Sensors

Kofi Makinwa

Electronic Instrumentation Laboratory / DIMES
Delft University of Technology
Delft, The Netherlands




Sensors are Everywhere!



EE315a



© K.A.A. Makinwa

World Sensor Market

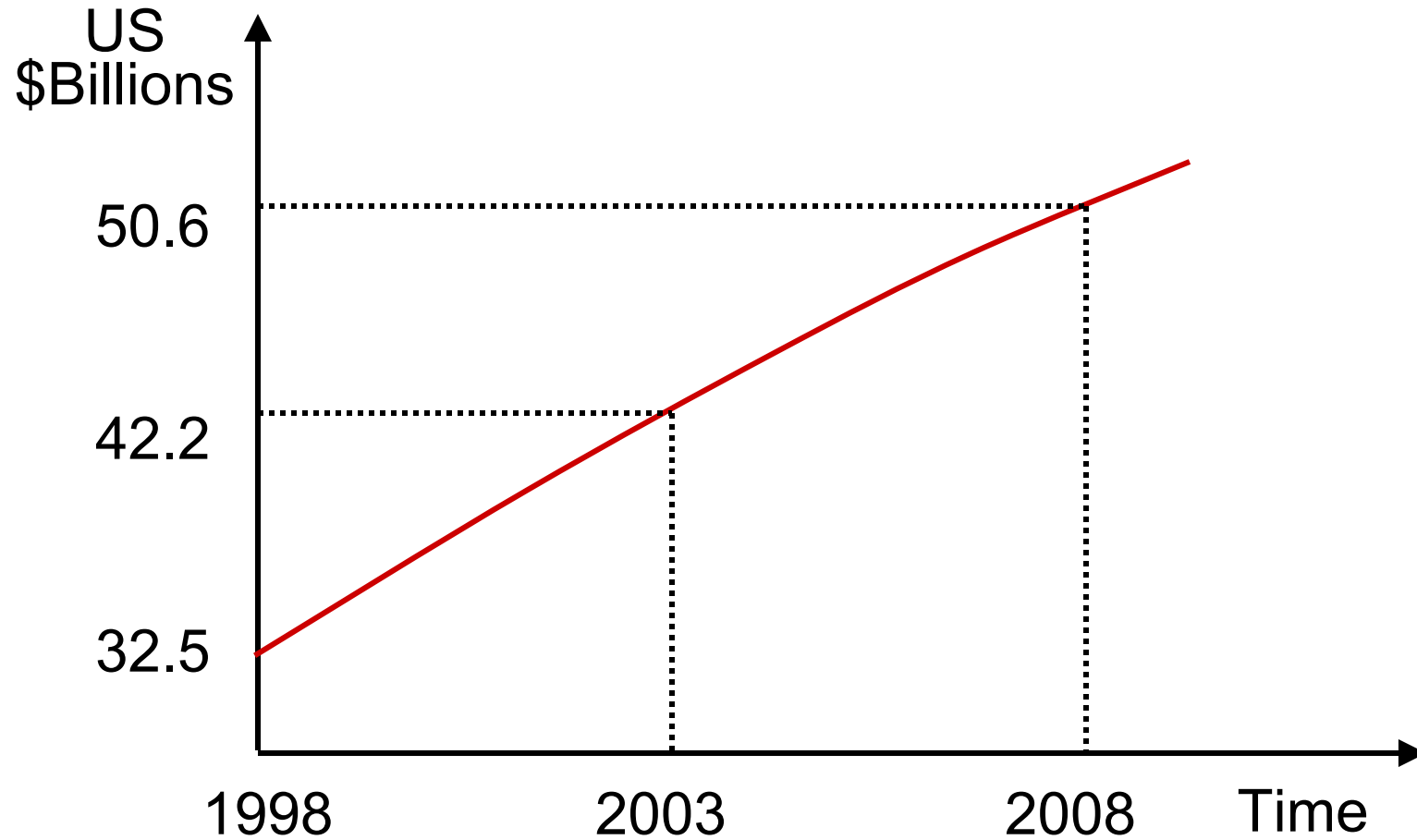


Courtesy of InTechno Consulting

Traditional Sensor Systems

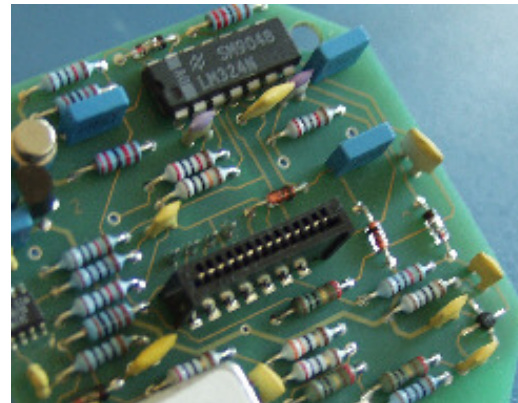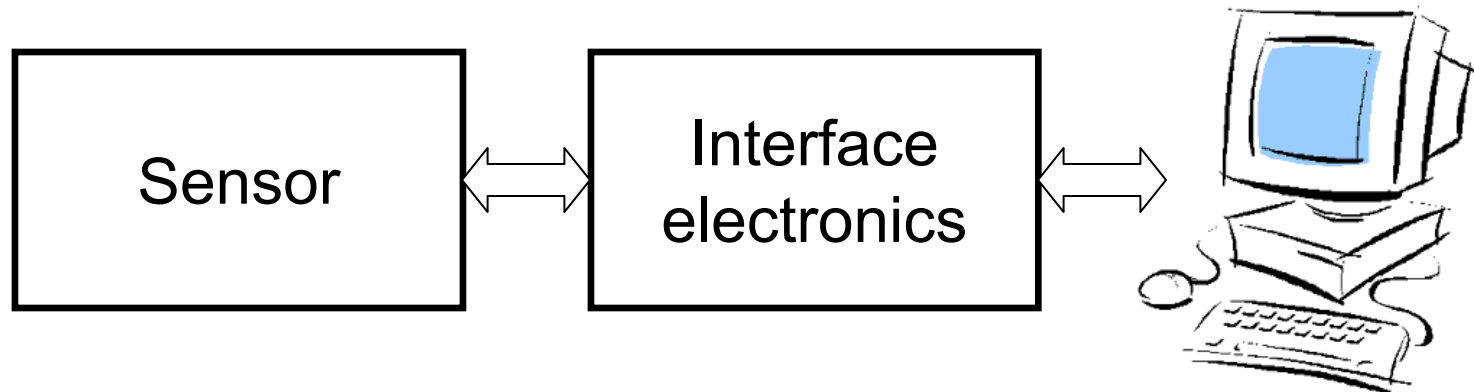

traditional
wind sensor

Smart Sensors

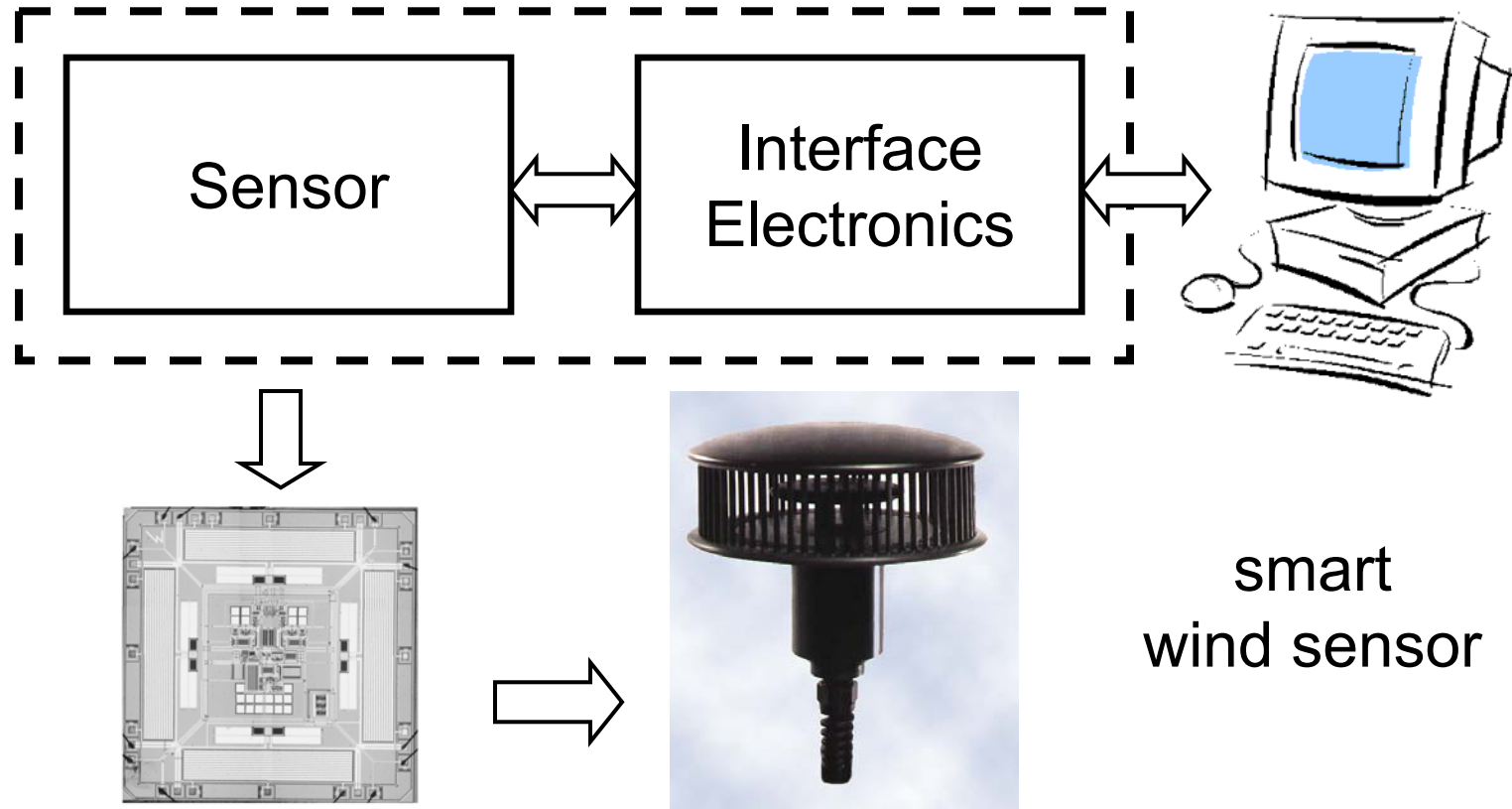

- Sensor + Interface electronics in **one** package
- Robust microprocessor compatible interface

Silicon Sensors

Silicon sensors cover the following domains:

- Thermal \Rightarrow resistors, transistors & thermopiles
- Magnetic \Rightarrow Hall-plates & magFETs
- Optical \Rightarrow photo-diodes
- Chemical \Rightarrow ISFETs
- Electrical \Rightarrow resistors, capacitors & inductors
- Mechanical (requires micro-machining!)
 \Rightarrow moveable proof mass or diaphragm

Silicon is a versatile material!


Interface Electronics?

- Term refers to ***electronic circuits*** that connect ***sensors*** to ***computers***.

Implements the following functions

- sensor excitation\powering
- signal conditioning
- analog-to-digital conversion
- Facilitates calibration and compensation
- (Standard) interfaces to the outside world

Signal Processing Chain

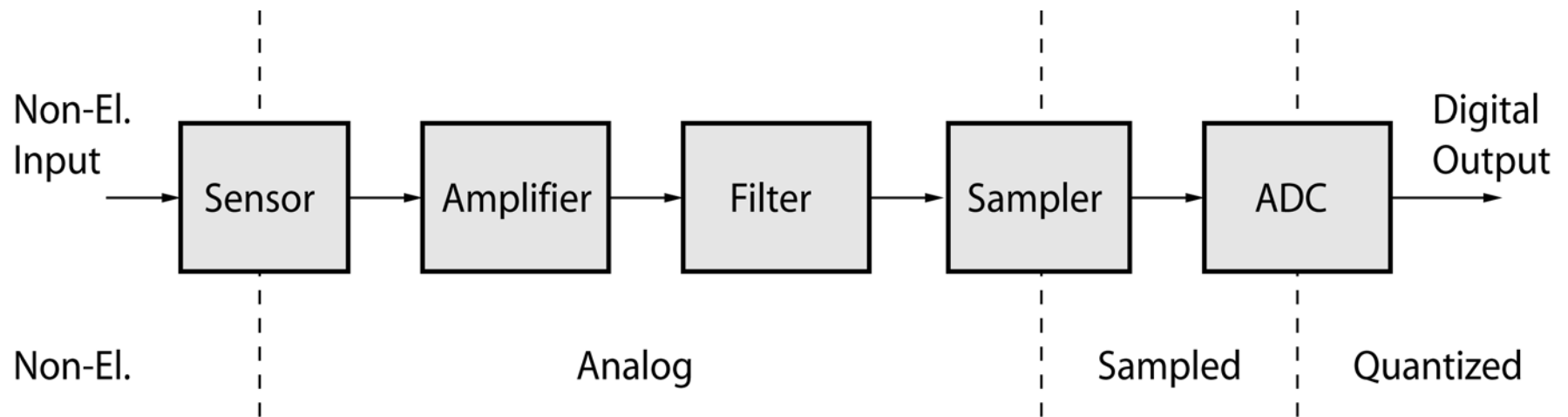

- Amplifier boosts weak sensor signals
- Filter rejects interference, noise and aliases
- ADC converts sensor signal to a digital format
- Tolerances add up \Rightarrow system calibration and trimming

Typical Sensor Characteristics

In general, sensors

- Output a **variety** of **small** analog quantities: microvolts (Hall sensors, thermopiles), microamps (photodiodes), atto-farads (inertial sensors)
- Are relatively **slow** – at least compared to the switching speed of transistors

In addition, silicon sensors

- Are sensitive to **process spread, temperature & (packaging) stress**
- Are rather average as sensors go, so good system performance \Rightarrow good interface electronics

Interface Design Methodology (1)


Do no harm!

- Interface electronics should be transparent
i.e. should not impair **sensor** performance
- An error budget for key specs should be made :
resolution, accuracy, bandwidth, dynamic range etc

Interface Design Methodology (2)

Do system design!

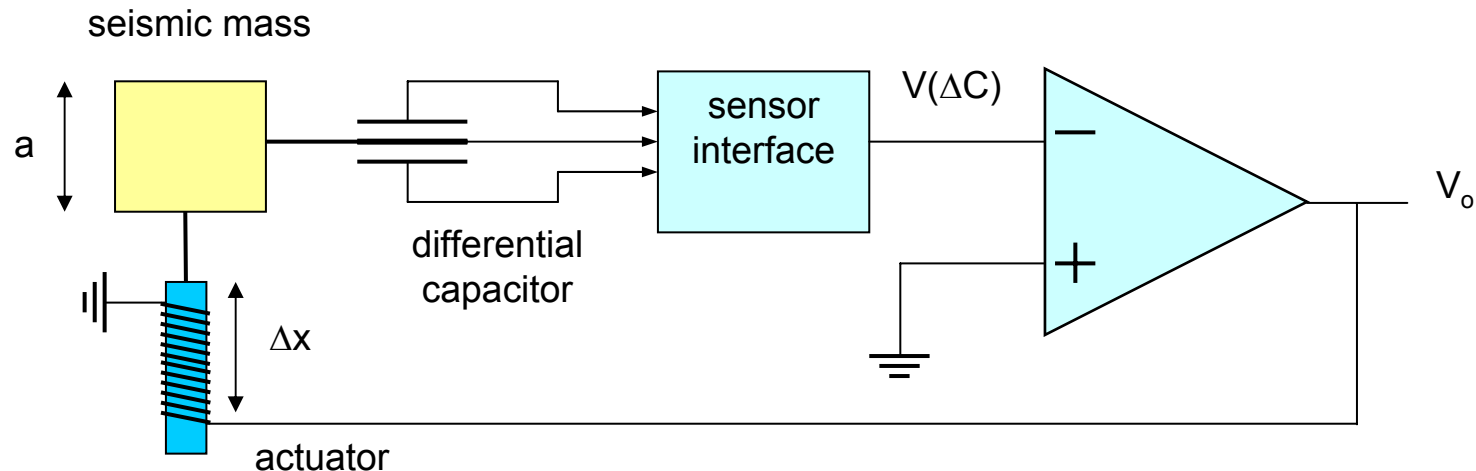
- Regard the combination of sensor and interface electronics as **one** system
- Appropriate biasing may compensate for non-idealities e.g. force feedback improves accelerometer linearity



Interface Design Methodology (3)

Digitize early!

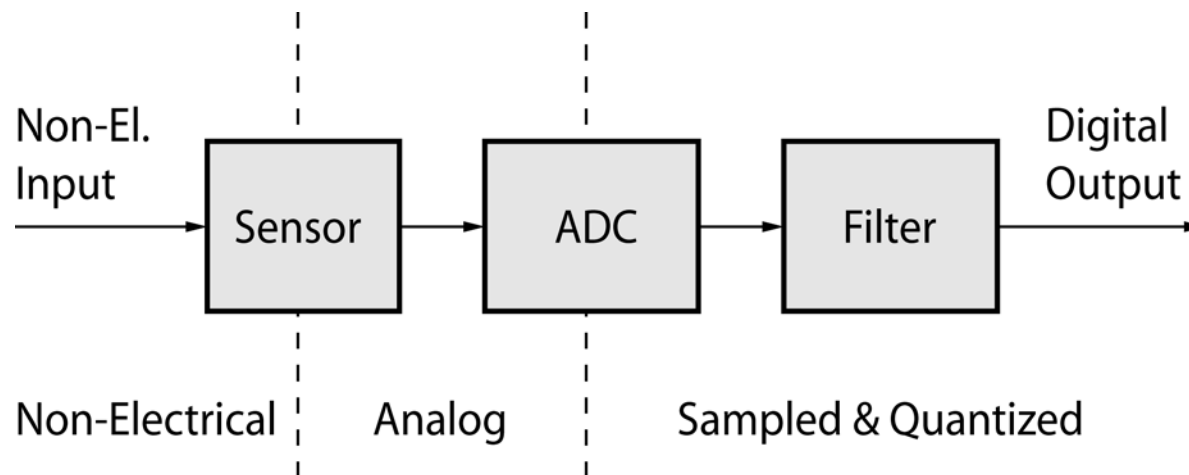
- Analog signal processing is sensitive to process spread (but power efficient at low resolution)
- Digital signal processing is accurate, flexible and increasingly cheap (Moore's Law)
- High resolution $\Sigma\Delta$ ADCs bridge the gap!



Interface Design Methodology (4)

Be dynamic!

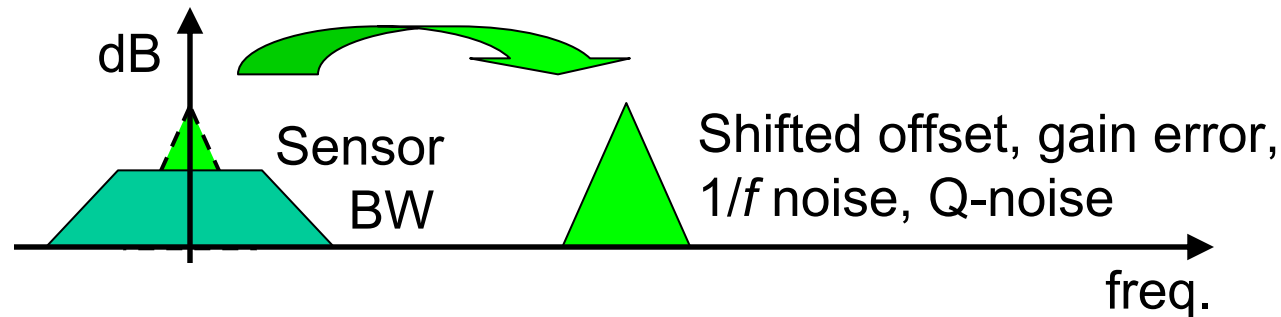- Slow sensors \Rightarrow dynamic techniques can be used to mitigate analog errors
- Gain errors \Rightarrow Dynamic element matching (DEM)
- Offset and $1/f$ noise \Rightarrow auto-zeroing, chopping
- Quantization noise \Rightarrow $\Sigma\Delta$ modulation




Interface Design Methodology

1. Do no harm!
2. Do system design!
3. Digitize early!
4. Be dynamic!


Three case studies: a smart wind sensor, a smart Hall-effect sensor and a smart temperature sensor

A Smart Wind Sensor!

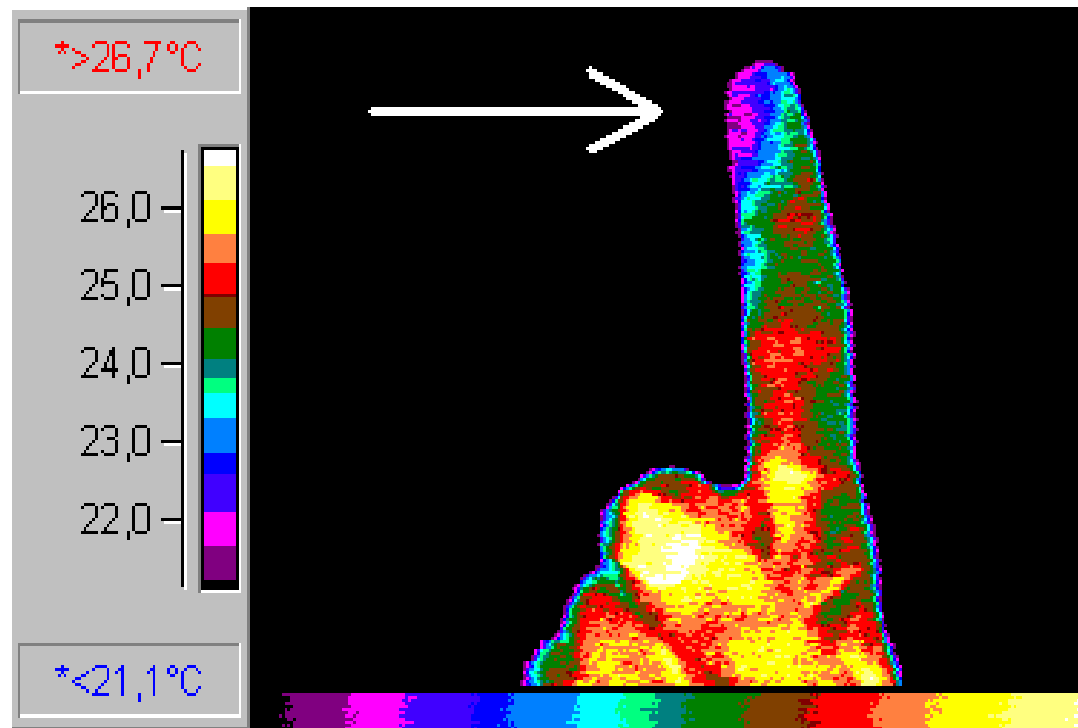


Convective cooling \Rightarrow temperature gradient
 \Rightarrow wind speed and direction

An Electronic Wind Sensor

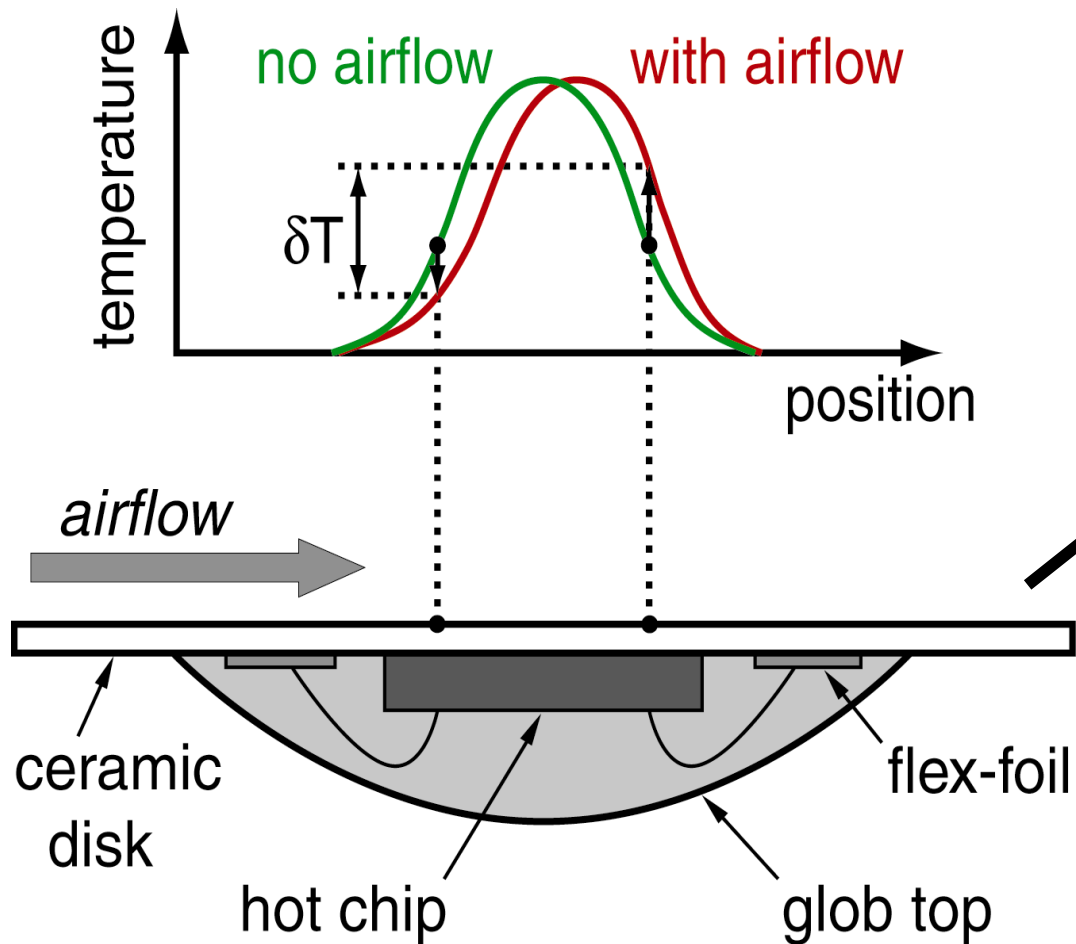

Wind Sensor Chip

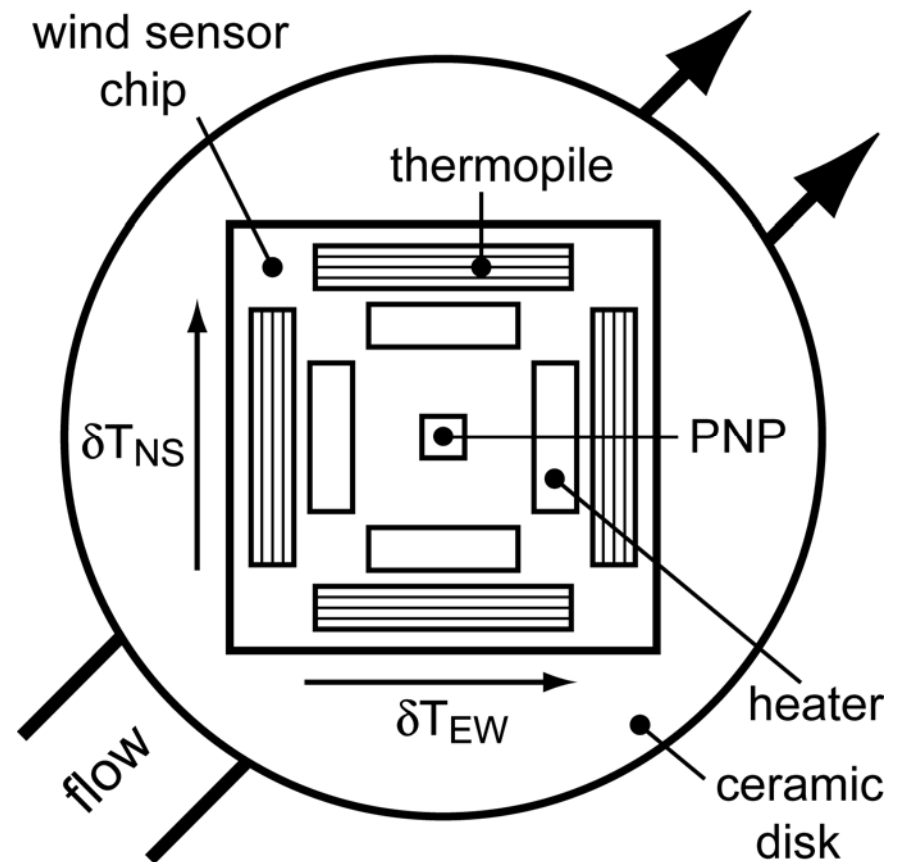- On-chip heaters
 - PNP: measures chip temperature T_{chip}
 - Thermopiles: measure temperature differences δT_{NS} and δT_{EW}
- ⇒ wind speed and direction





Sensor Characteristics

- Slow (~ 1 s time constant)
- Thermopile output is small (microvolts)
- Output is proportional to $\Delta T = T_{\text{chip}} - T_{\text{amb}} \Rightarrow$ regulation
- Sensor suffers from packaging offset (chip is not perfectly centered on disc) \Rightarrow calibration and trimming
- Sensor achieves $\sim 2^\circ$ angle error \Rightarrow thermopile outputs must be digitized with > 8 -bit resolution
- Sensor characteristics depend on chip area \Rightarrow same chip area \Rightarrow simple interface circuitry


Thermal Balancing

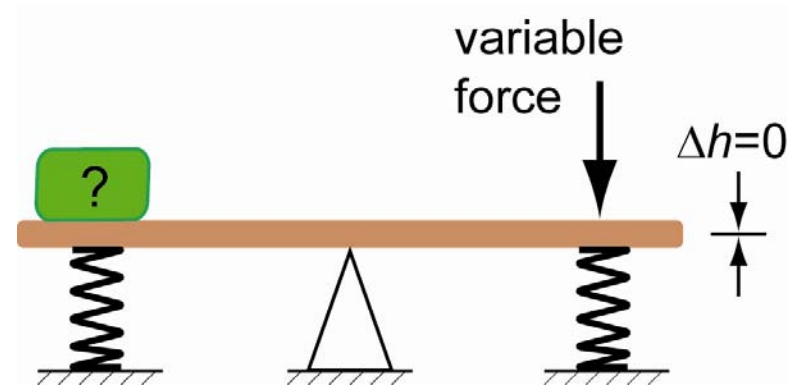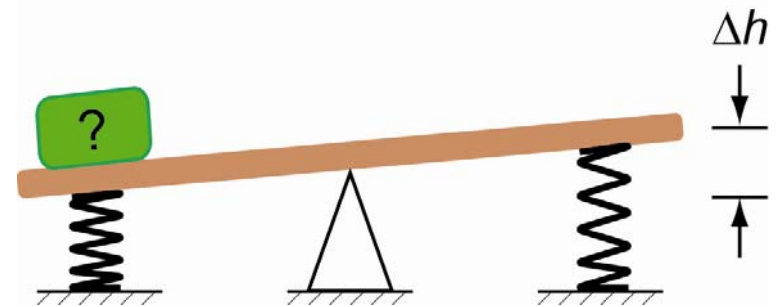- Old principle: **measure** temperature difference δT
- New principle: **cancel** temperature differences
- Measure difference in heater power δP
 \Rightarrow wind speed & direction




Thermal $\Sigma\Delta$ Modulation

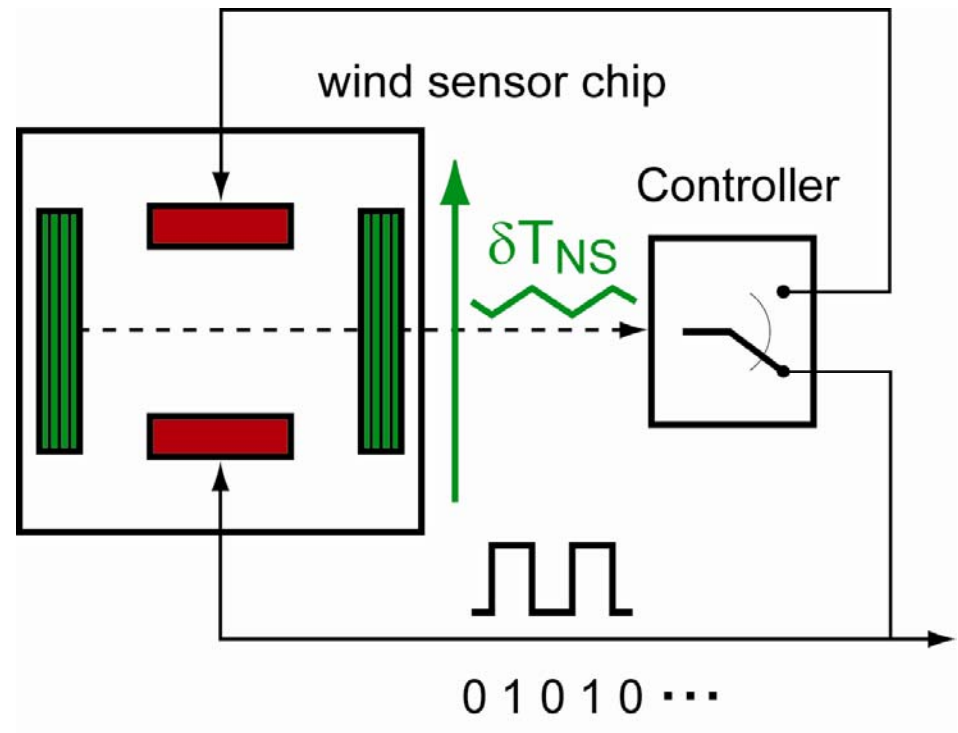- Heaters are pulsed by bitstream
- Pulses are thermally low-pass filtered $\Rightarrow \delta T_{NS} \sim 0$
- Requires only a simple comparator!
- Is a $\Sigma\Delta$ modulator \Rightarrow digital output!




CM Thermal $\Sigma\Delta$ Modulator

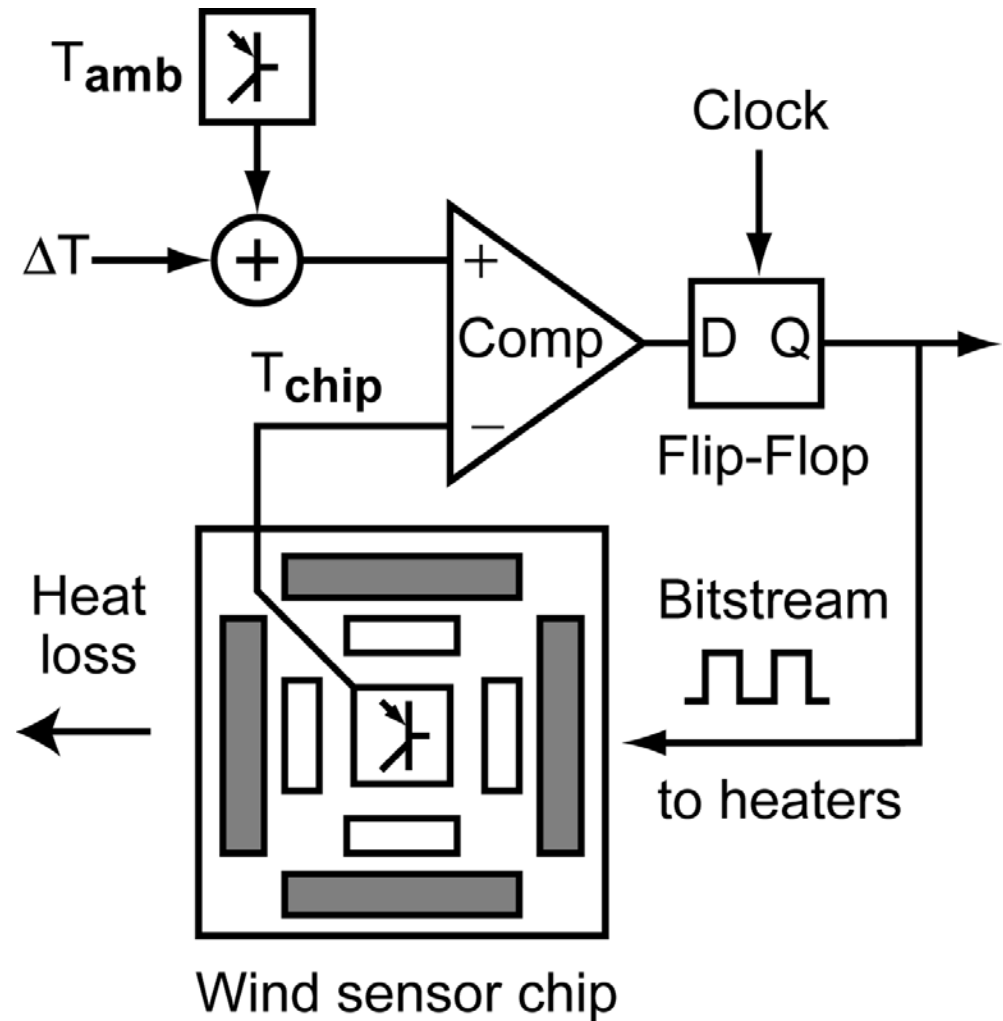- Keeps $T_{\text{chip}} \cong T_{\text{amb}} + 10^\circ\text{C}$
- $T_{\text{chip}} \Rightarrow$ on-chip PNP
- $T_{\text{amb}} \Rightarrow$ external PNP




Smart Wind Sensor

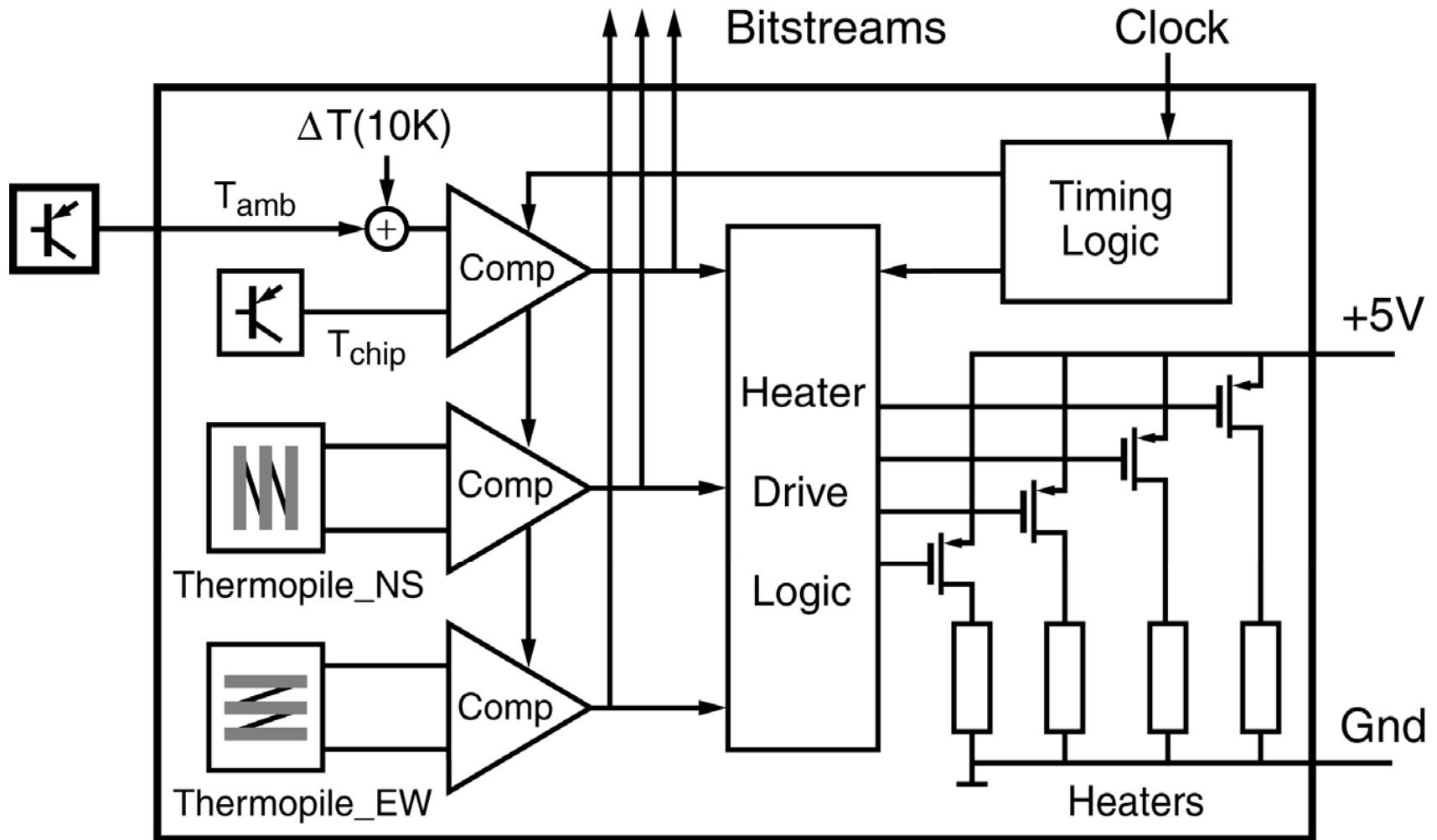


Smart Wind Sensor Chip

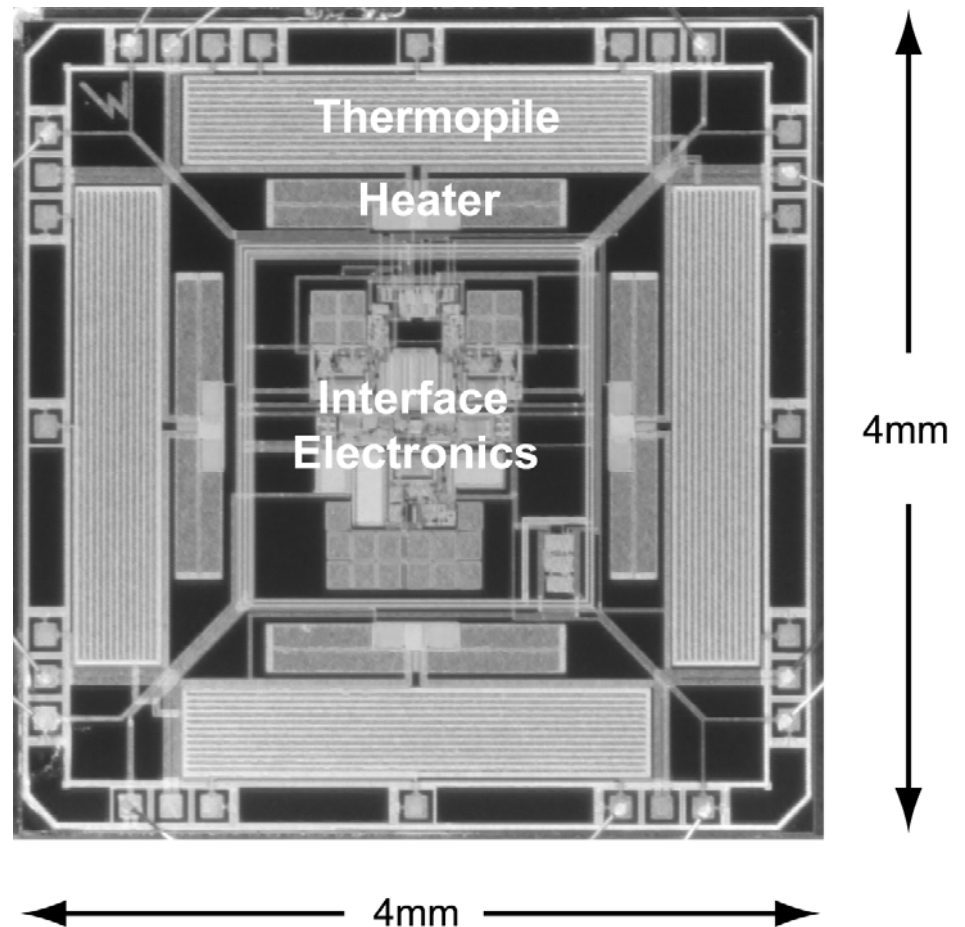- Same area as original sensor
- Even in a $1.6\mu\text{m}$ CMOS process!
- Thermal $\Sigma\Delta$ modulators
⇒ 10-bit resolution
- Bitstream output



Wind Sensor Performance

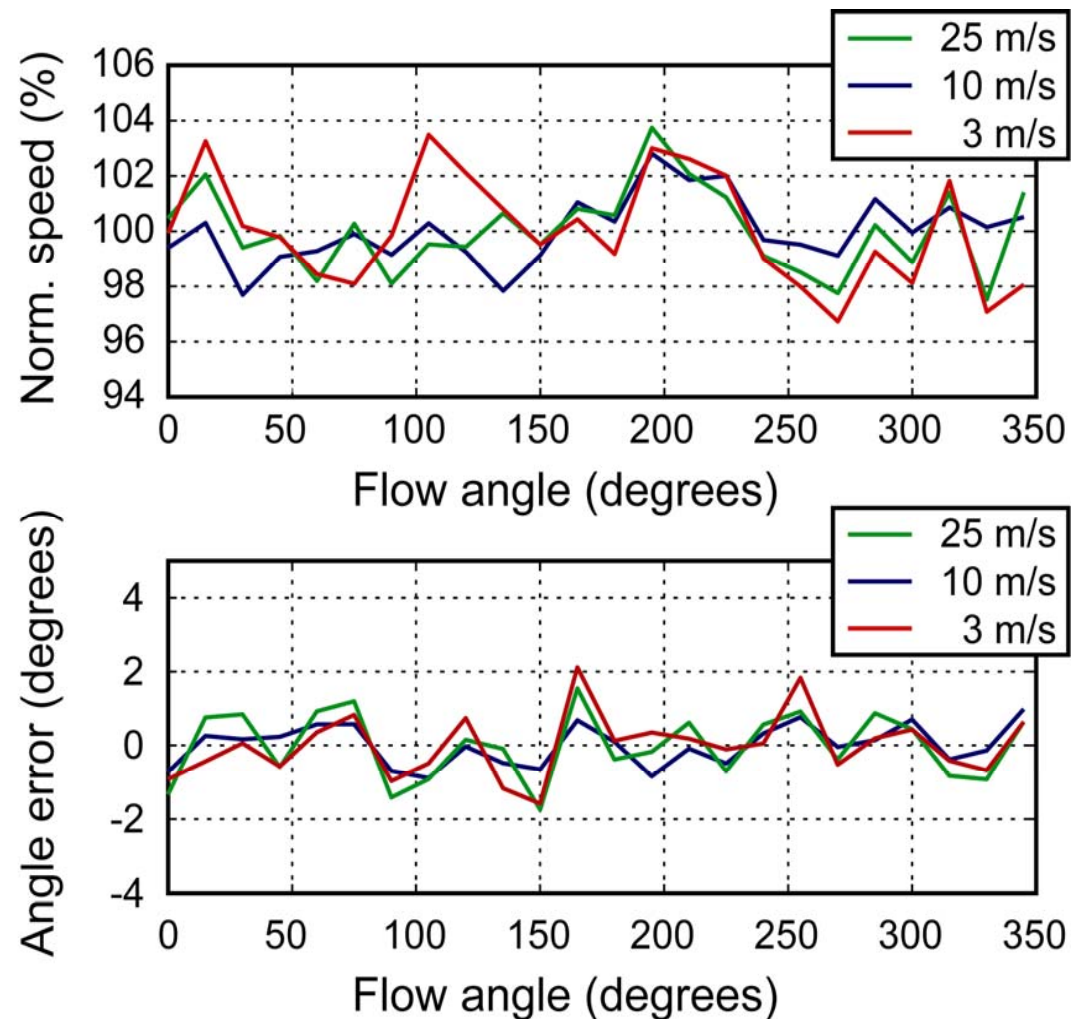- After calibration:
Speed error: $\pm 4\%$
Angle error: $\pm 2^\circ$
- *Same* as for original sensor
- But, with on-chip electronics
- Is being commercialized





Design Summary

1. Do no harm: performance **is** limited by sensor!
2. System design: sensor's thermal inertia is used to realize **simple** thermal balancing control loops
3. Digitize early: sensor is embedded in a $\Sigma\Delta$ modulator
4. Be dynamic: Auto-zeroing cancels offset and $1/f$ noise

A Smart Hall Sensor

Vector plot of Horizontal Field

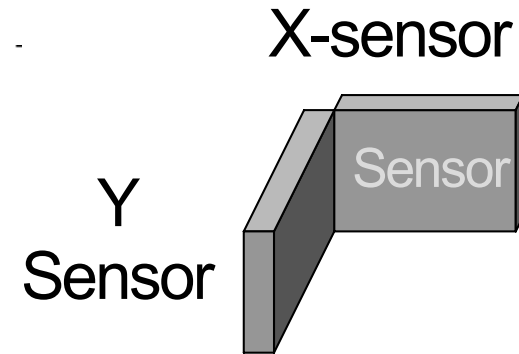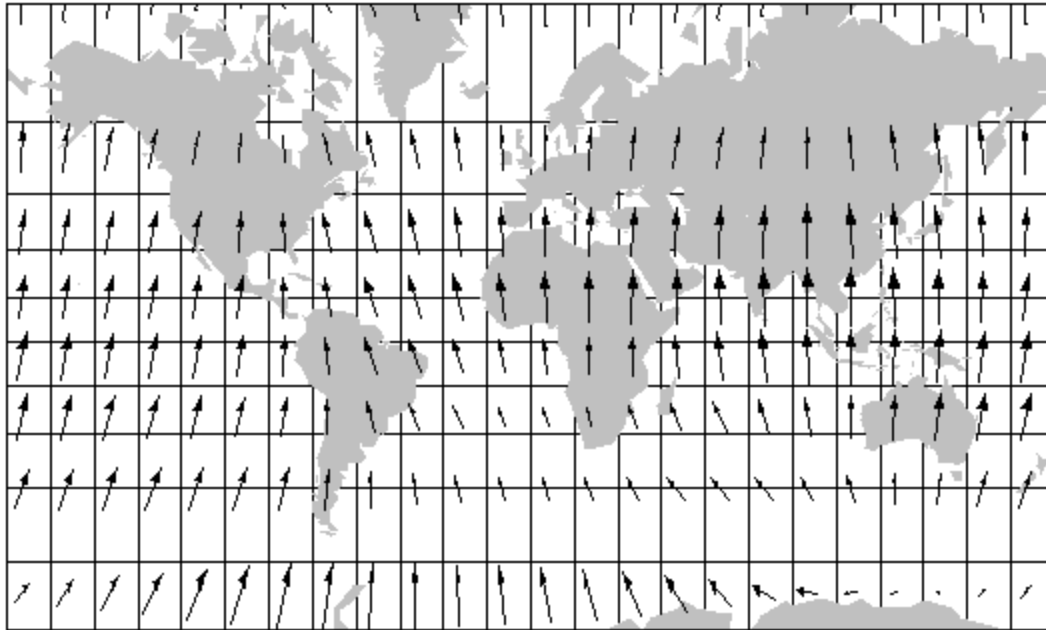


- Compass senses at least two components of earth's field
- Field strength $< 45\mu\text{T}$

Goal: Hall-sensor based compass with 1° angle error


\Rightarrow Hall-sensor precision $< 0.5\mu\text{T}$

\Rightarrow Precision of readout electronics $< 25\text{nV}$!

Hall Effect

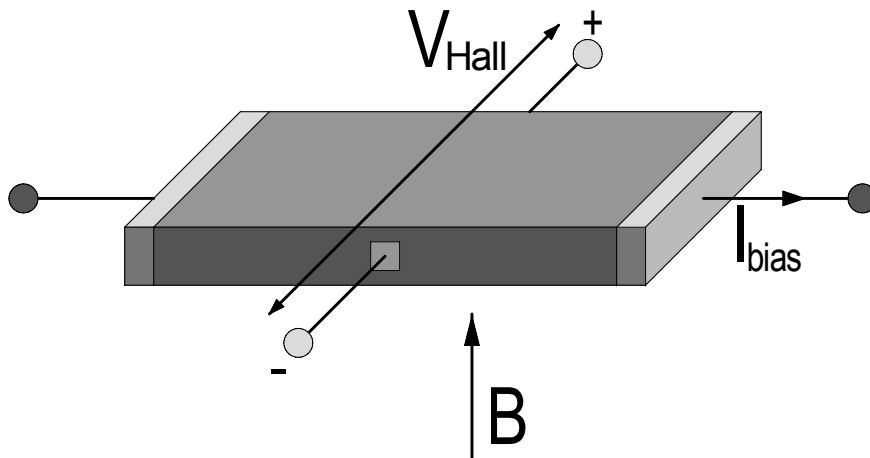
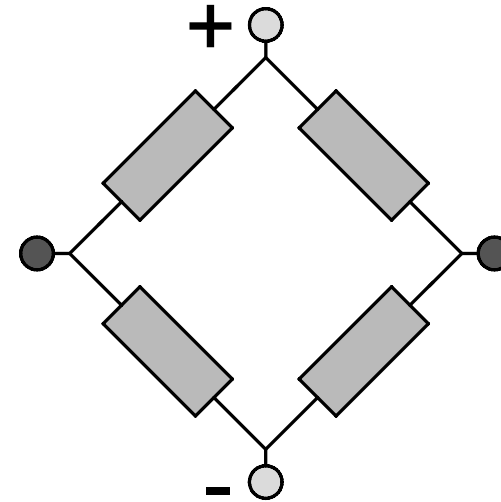
$$V_{\text{Hall}} = S_H I_{\text{Bias}} B$$




Wheatstone bridge model

Resistances in bridge model


- Are mismatched \Rightarrow Offset (10mT typical)
- **Change** due to changes in temperature and packaging stress \Rightarrow Offset drift

Spinning-Current Technique

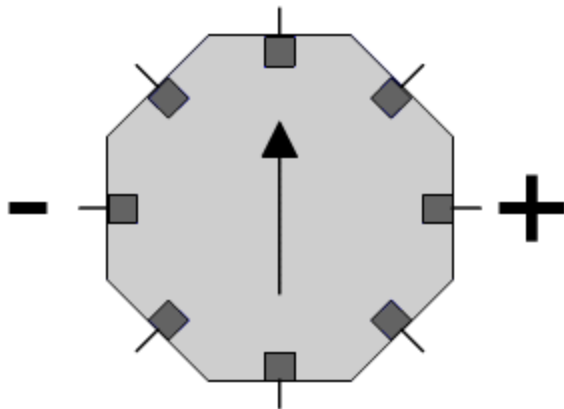


- Bias current rotated, while Hall voltages are summed
 - Cancels offset due to **static** bridge mismatch
- ⇒ 10 - 100 μ T offset
- **But** thermal settling ⇒ tens of milliseconds per spin cycle
- ⇒ Time-varying offset e.g. due to temperature and stress remains a problem

Hall Sensor Offset Reduction

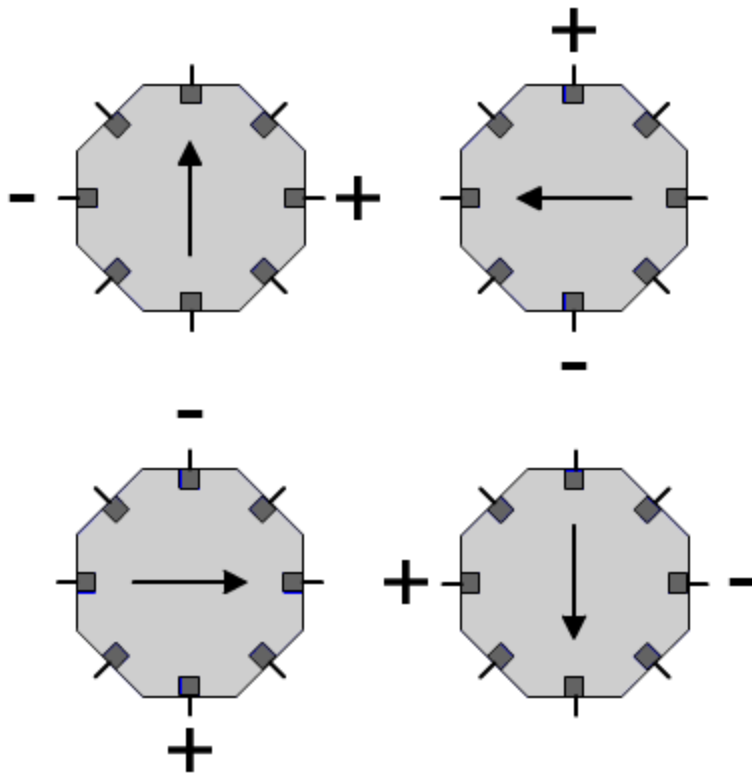


- Orthogonal coupling
 - 4 sensors are biased in 4 different directions
 - Hall voltages are summed
- ⇒ Instantaneous compensation of time-varying offset
- **Stable** offset $< 10\mu\text{T}$
 - ⇒ can be trimmed!
- Also compensates for errors due to nearby metal objects

Spinning-Current Sensor Output

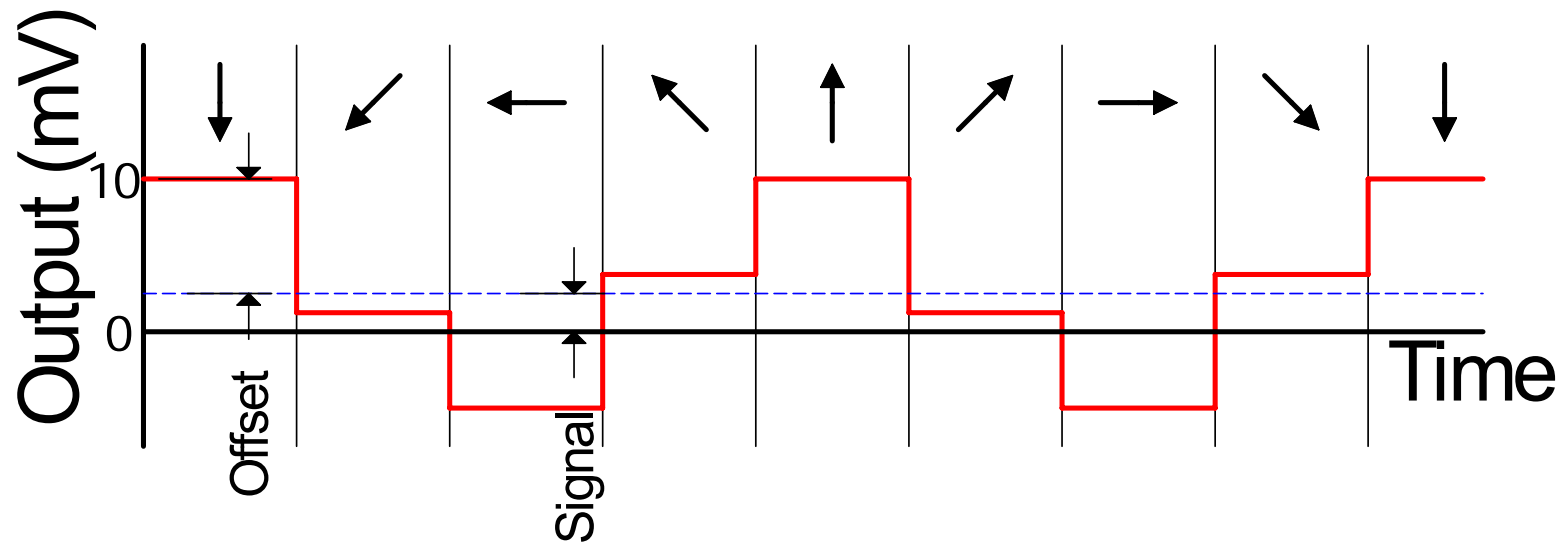

- Typically 10mV worst case offset
- But offset **drift** < 25nV is required after spinning
 - ⇒ Interface electronics with sub-microvolt offset
 - ⇒ Good linearity over an 80 - 100dB dynamic range


System Architecture

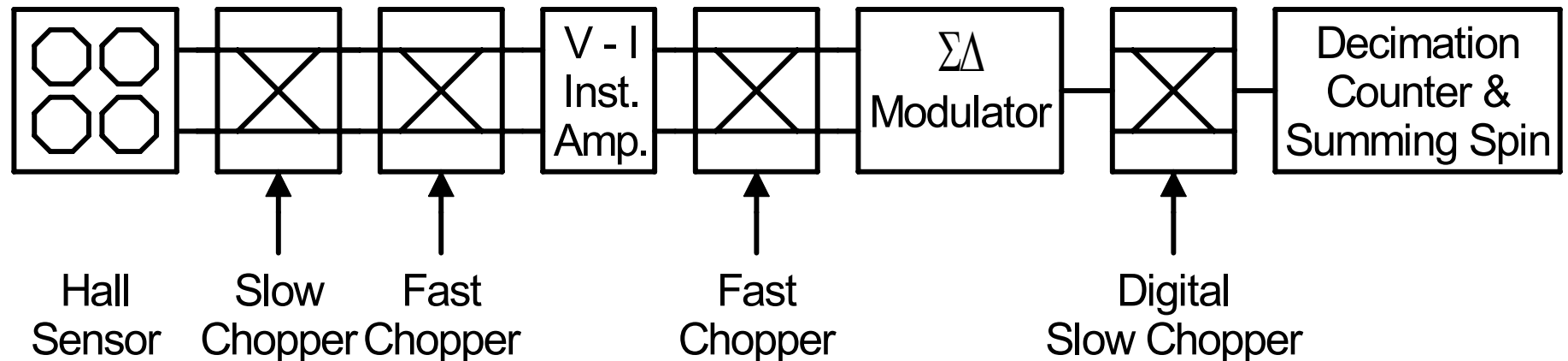

Sub-microvolt offset \Rightarrow nested chopping

- Hall-voltages converted to currents by chopped instrumentation amplifier (fast choppers)
- $\Sigma\Delta$ Modulator digitizes resulting currents
- Entire front-end is again chopped (slow choppers)
- Decimation filter sums and averages Hall-voltages


Precision V-I Converter

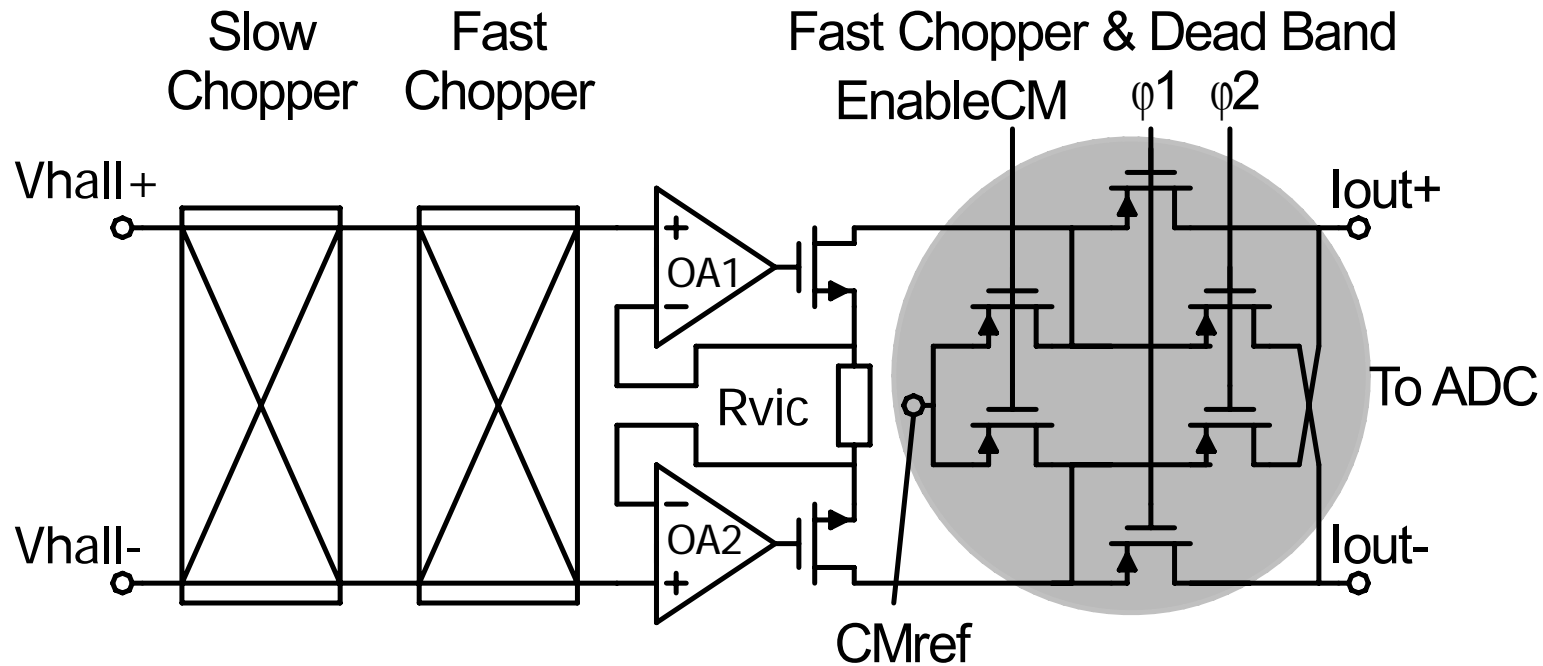

- Fast output chopper implements dead-bands
- During dead-bands, output current flows into a CM node
- Slow output chopper implemented in ADC

Chip Micrograph


Hall Sensor Inst. Amp. ADC

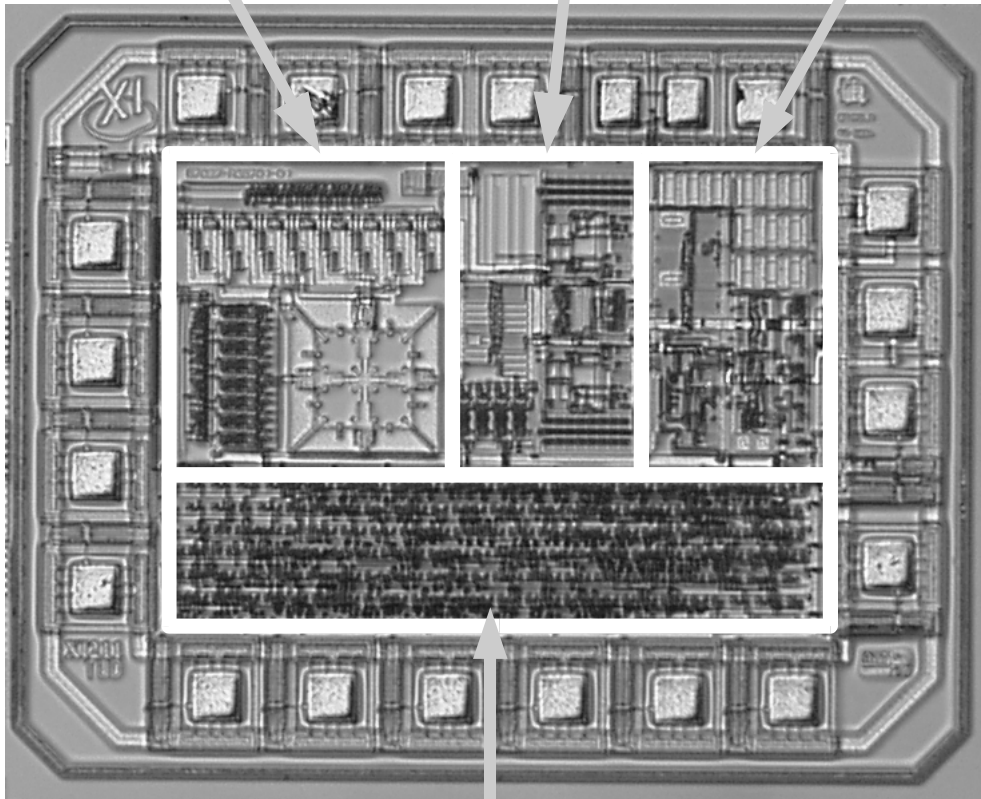

Timing, Control & Interfaces



- 0.5 μ m CMOS
- Area: 2.9 mm²
- Dissipates 21mW (4.2mA @ 5V)
- RS232, SPI/ μ wire and PWM interface
- Commercial product

Sensor Offset Distribution

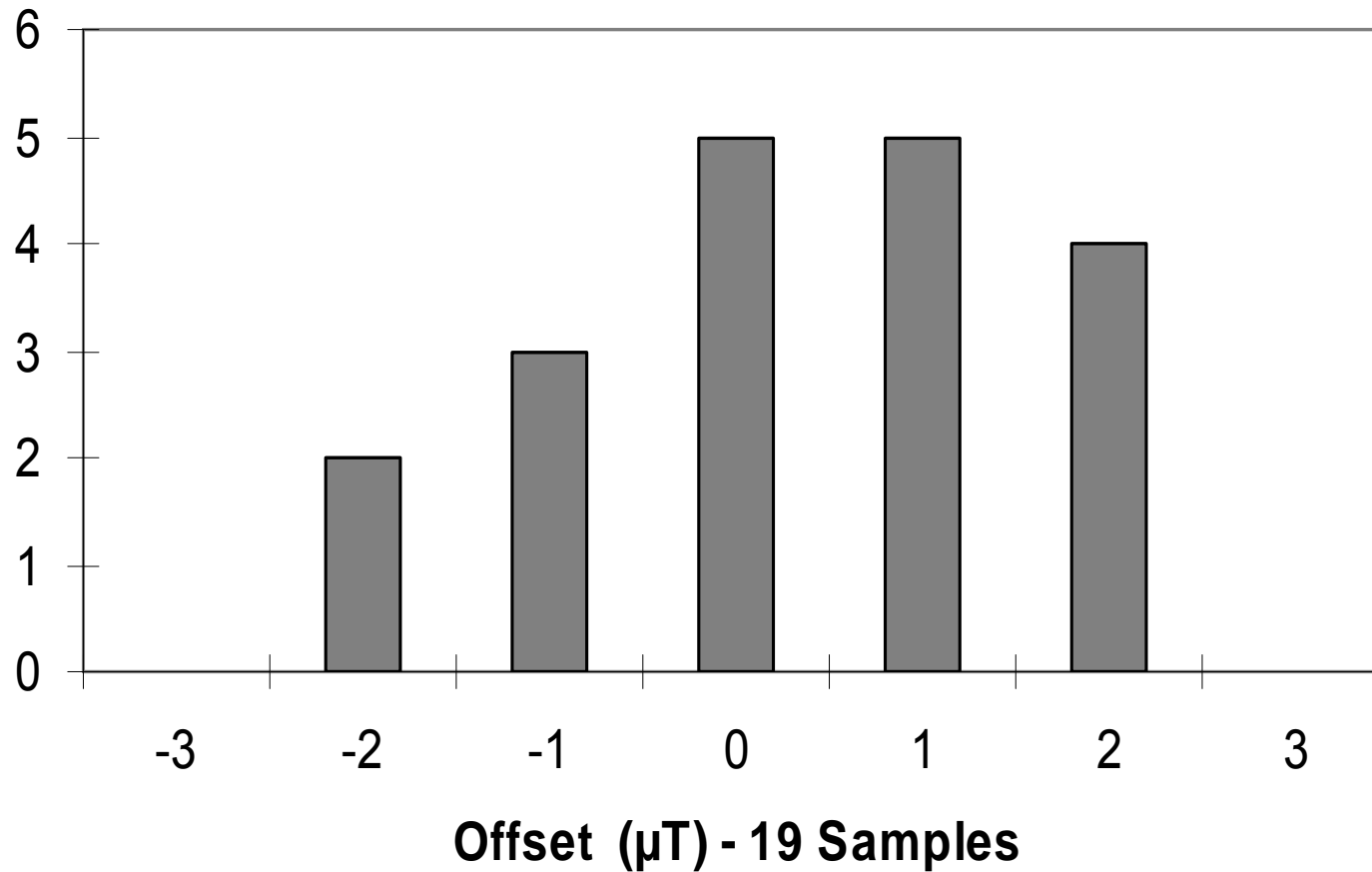

Sensor offset (3σ) $< 4\mu\text{T}$, but offset drift $< 5\text{nT}$ per week!

System Response Measurement

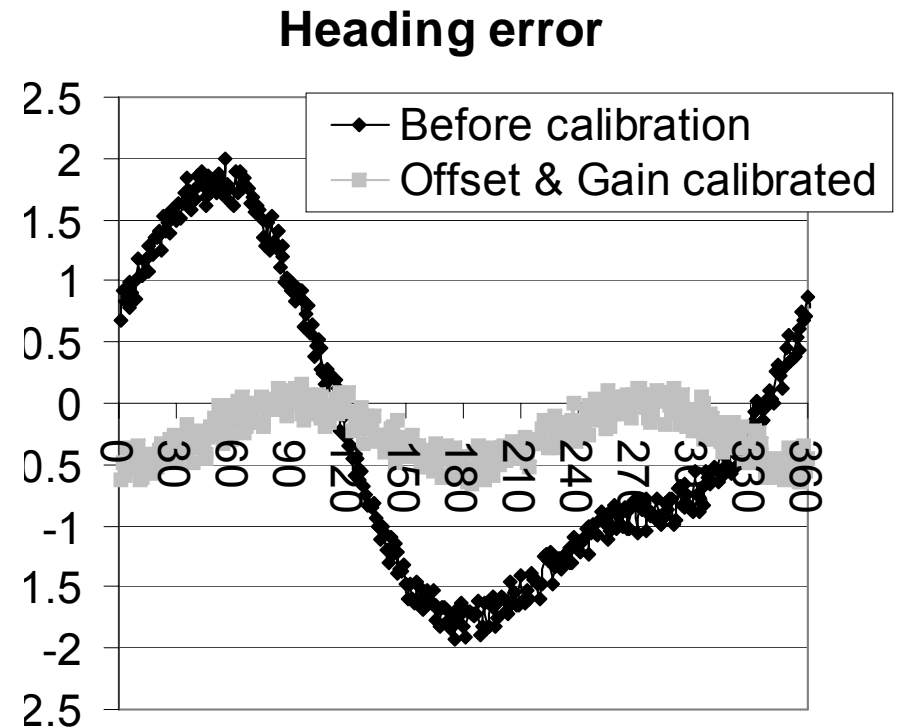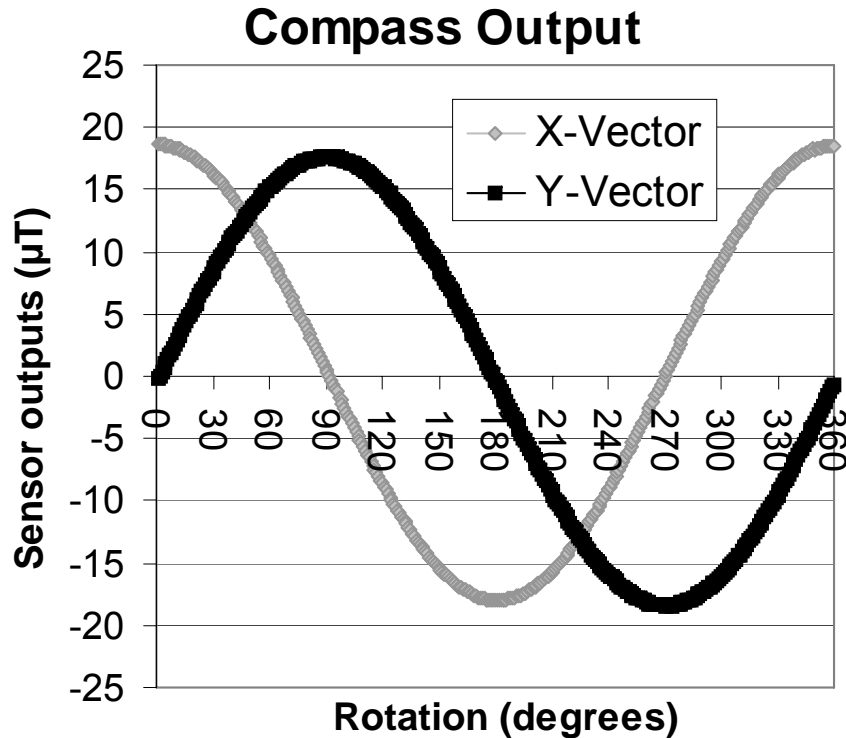


- Angle error $< 1^\circ$ after calibration and trimming!
- State-of-the-art performance!

Design Summary



1. Do no harm: performance **is** limited by Hall sensors!
2. System design: spinning current technique + quad Hall sensor reduces and **stabilizes** sensor offset
3. Digitize early: sensor output is converted to a current and then digitized by a $\Sigma\Delta$ modulator
4. Be dynamic: nested chopping is used to cancel offset and $1/f$ noise

A Smart Temperature Sensor

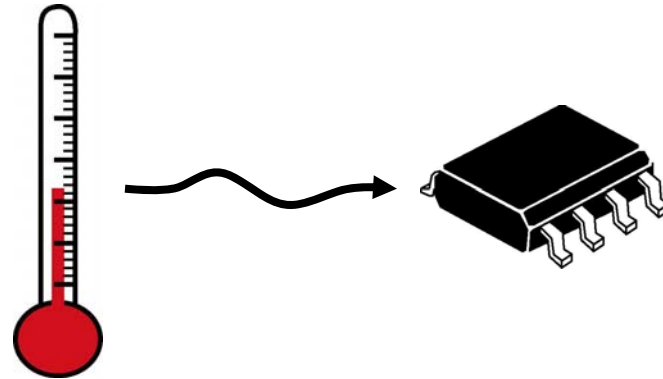


- *Commercial* smart temperature sensors are not very accurate ($\pm 1.0^{\circ}\text{C}$ from -55°C to 125°C)
- By comparison: class-A Pt100 $\pm 0.5^{\circ}\text{C}$
- Our goal: $\pm 0.1^{\circ}\text{C}$ from -55°C to 125°C with only a single-temperature trim

Operating Principle

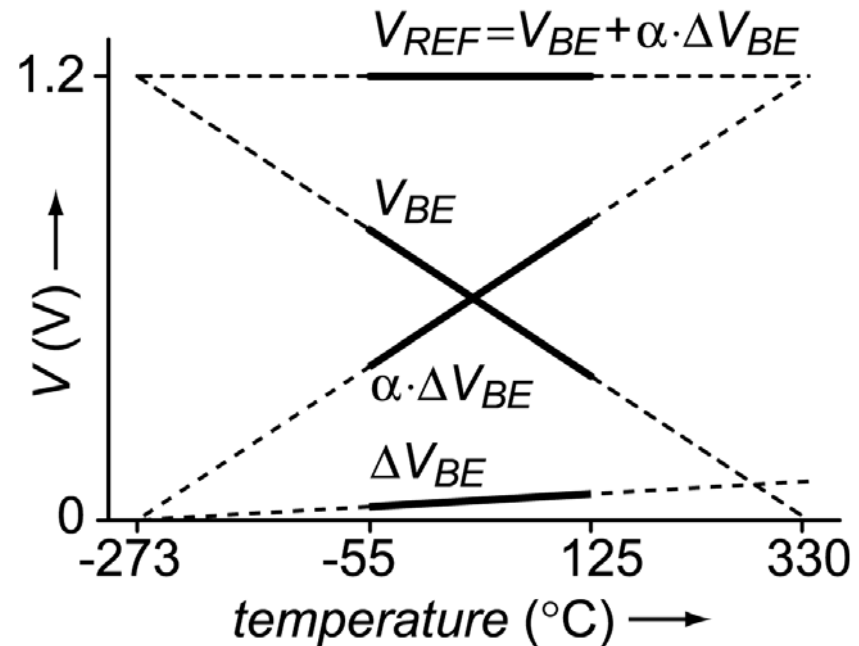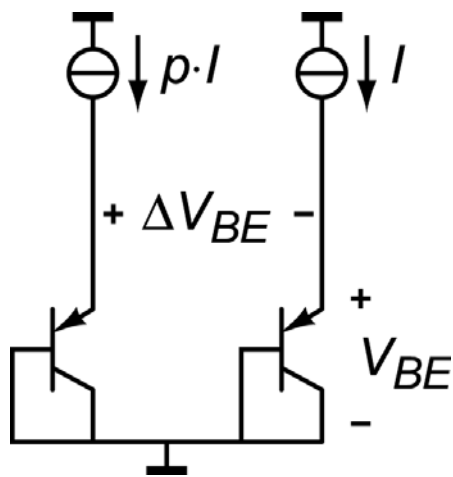

- substrate PNPs generate:
 - ΔV_{BE} proportional to absolute temp. (PTAT)
 - V_{BE} complementary to absolute temp. (CTAT)
- ratiometric measurement:
$$\mu = \frac{V_{TEMP}}{V_{REF}} = \frac{\alpha \cdot \Delta V_{BE}}{V_{BE} + \alpha \cdot \Delta V_{BE}}$$


Dominant Error Sources

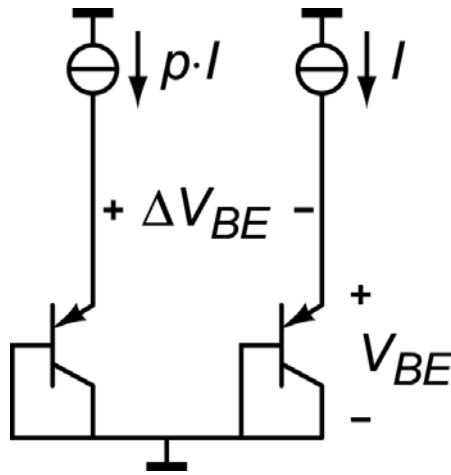

- **process spread** of $V_{BE} \Rightarrow$ errors of $\sim 3^\circ\text{C}$
- **offset** in ΔV_{BE} read-out: $10\mu\text{V} \Rightarrow 0.1^\circ\text{C}$ error
- **mismatch** in 1:p current ratio and gain α : $0.1\% \Rightarrow 0.2^\circ\text{C}$ error

Single-Temperature Calibration

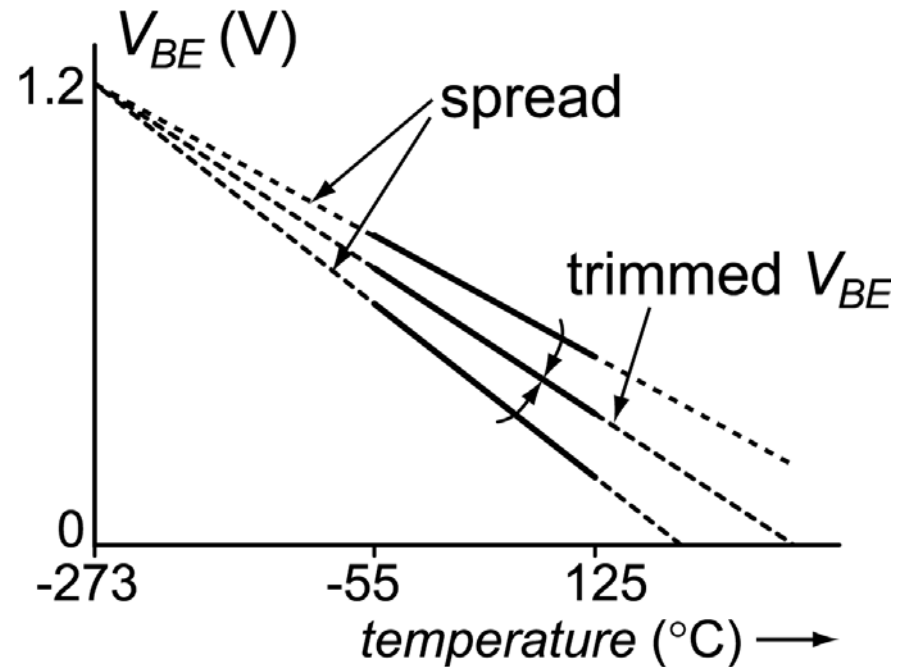
- process spread
⇒ PTAT error in V_{BE}
- So single-temperature trim is sufficient, *provided* all other errors are negligible



Approach:


- reduce all errors except spread to 0.01°C level
- correct spread by trimming the bias current

Block Diagram

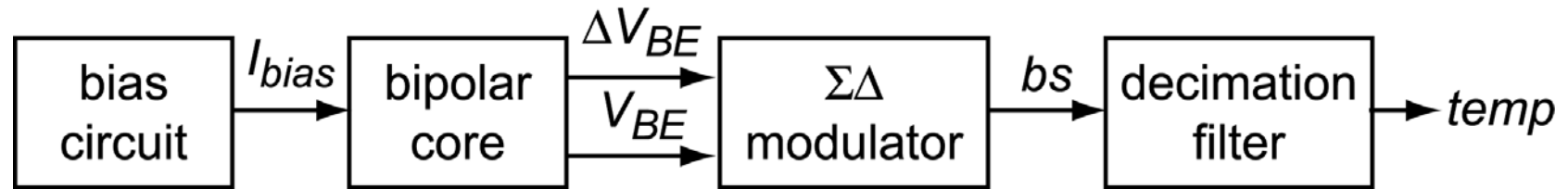


- Bipolar core = two PNPs
- $\Sigma\Delta$ modulator produces bitstream bs that is a digital representation of temperature
- bitstream is filtered and scaled by decimation filter to produce binary reading in $^{\circ}\text{C}$

Dynamic Element Matching

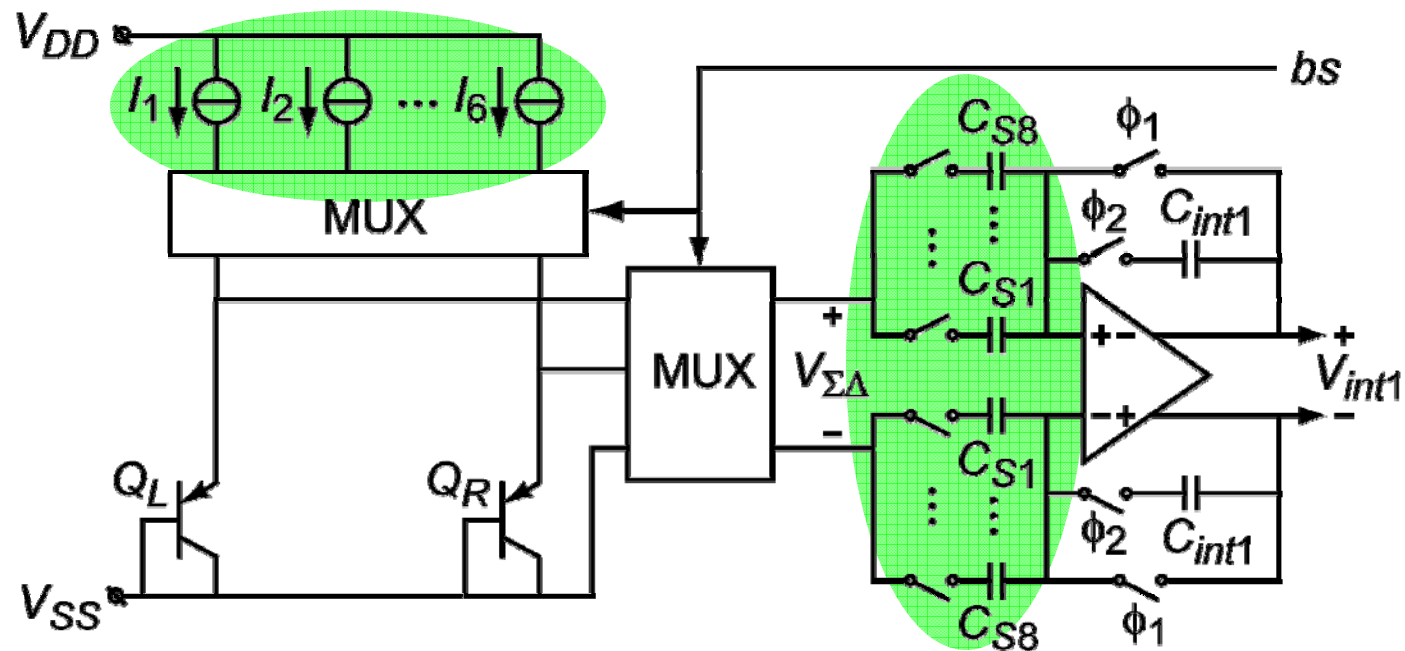


- Accurate 1:5 current ratio for ΔV_{BE}
 \Rightarrow rotate current sources
- Accurate 1:8 sampling capacitor ratio
 \Rightarrow rotate sampling capacitors

Switched-Capacitor Front-End

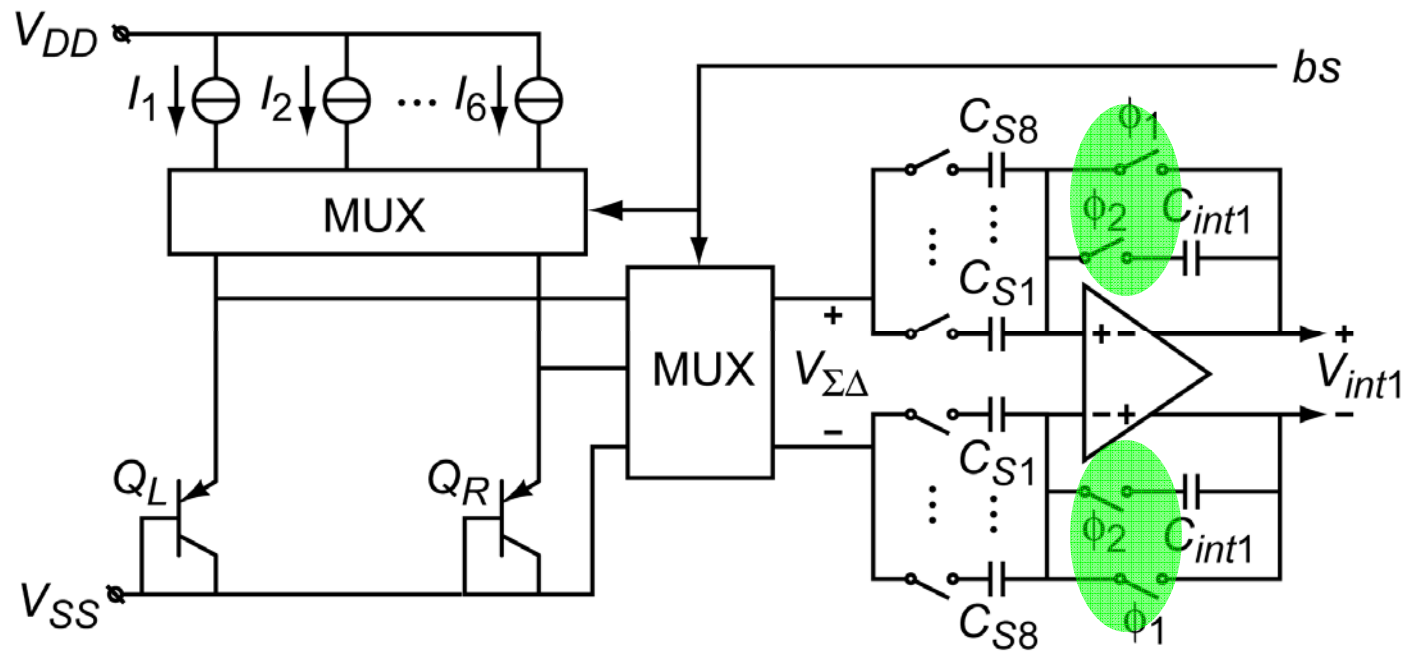


- Correlated double-sampling (CDS) cancels offset and $1/f$ noise of 1st integrator

Chopped $\Sigma\Delta$ Modulator

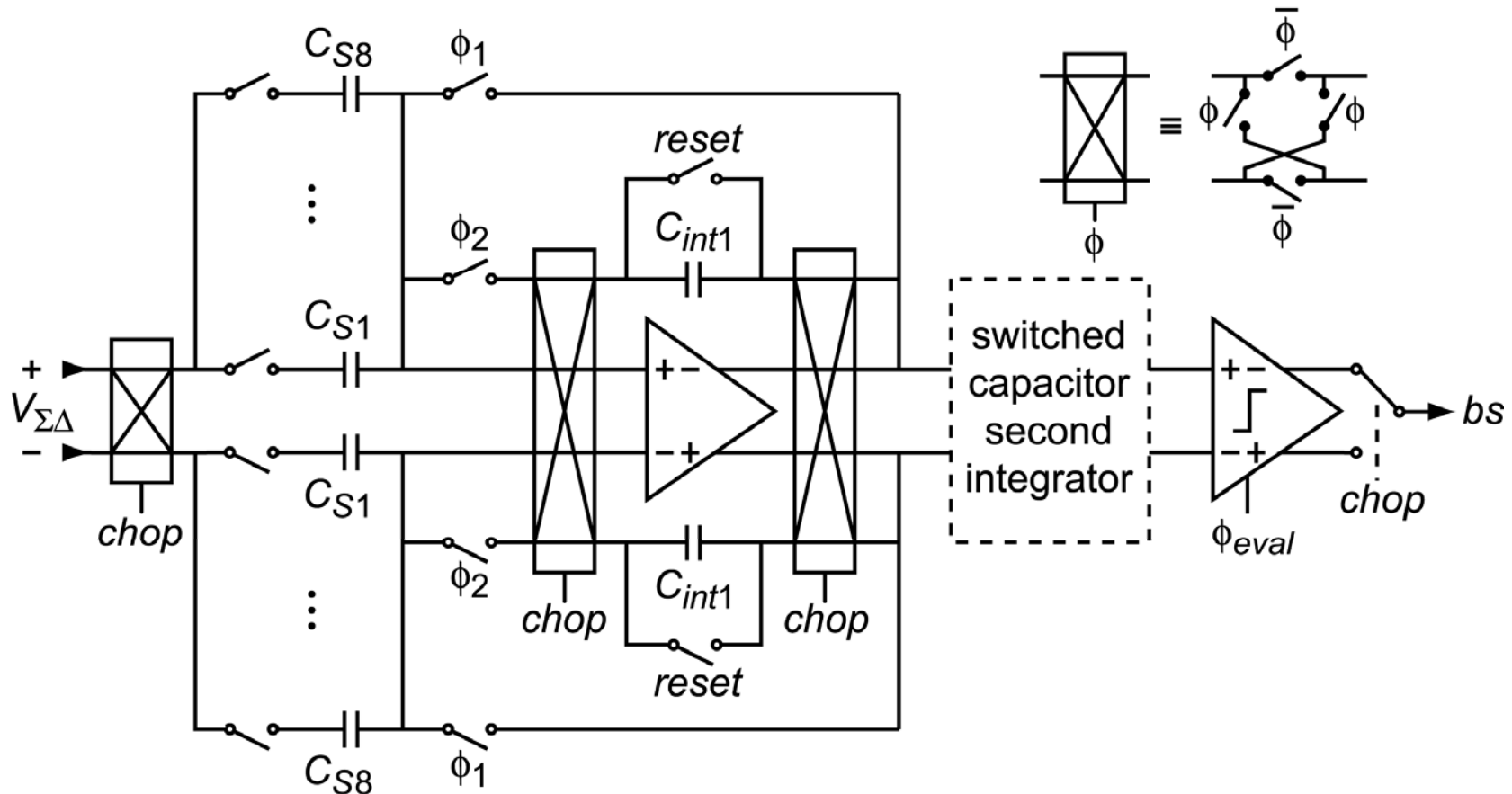


- After CDS, offset of 1st integrator is still $> 10\mu\text{V}$
 \Rightarrow further offset reduction by system-level chopping

Chip Micrograph

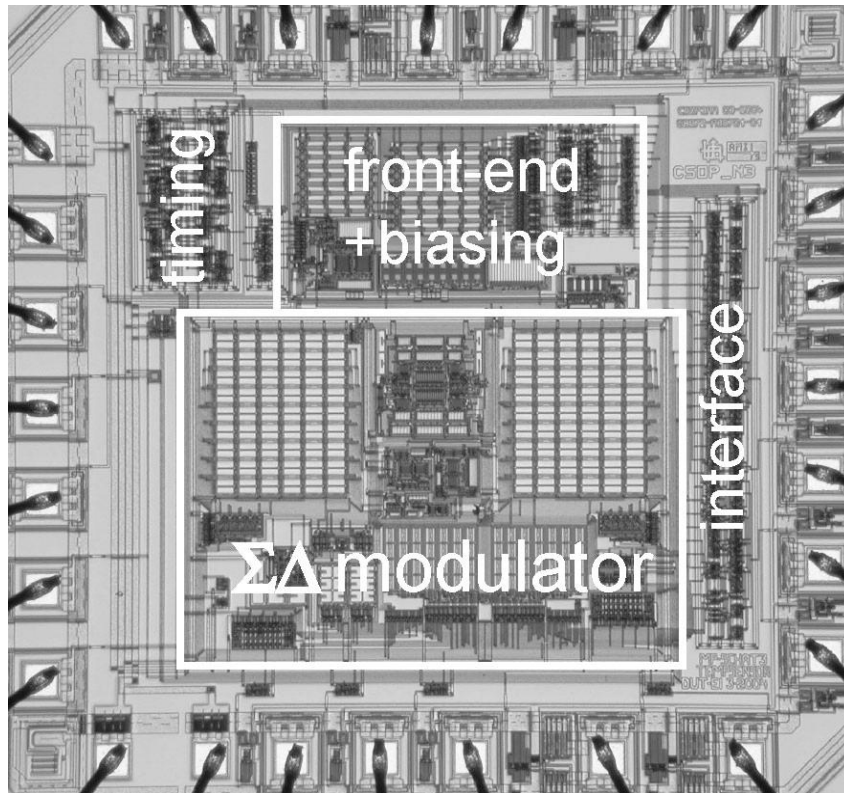

- 0.7 μm CMOS
- Area: 4.5mm²
- supply voltage: 2.5..5.5V
- supply current: 75 μA
- Bitstream output

Measurement Results

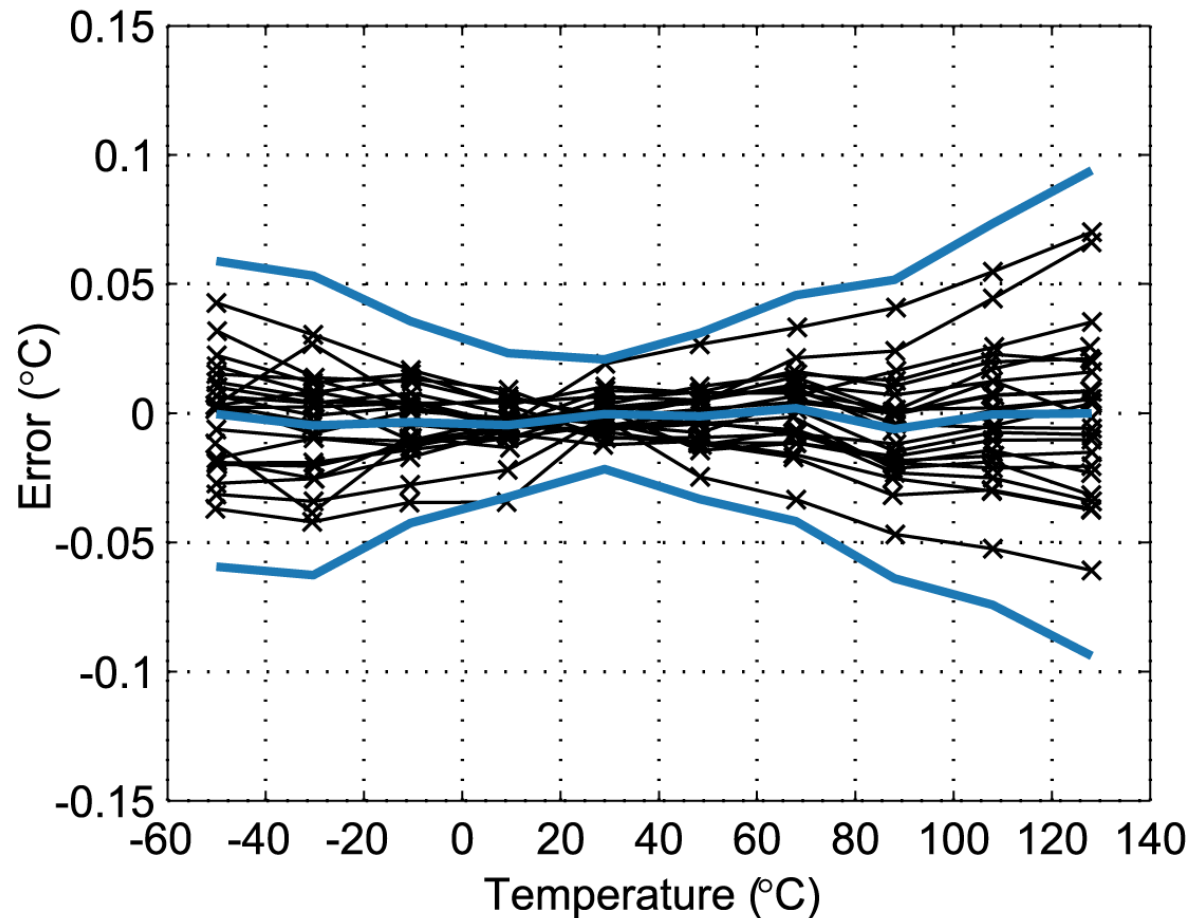


24 samples
from 1 batch

inaccuracy ($\pm 3\sigma$)
after calibration
& trimming at 30°C:

$\pm 0.1^\circ\text{C}$ $-55..125^\circ\text{C}$

State-of-the-art
performance!

Benchmarking

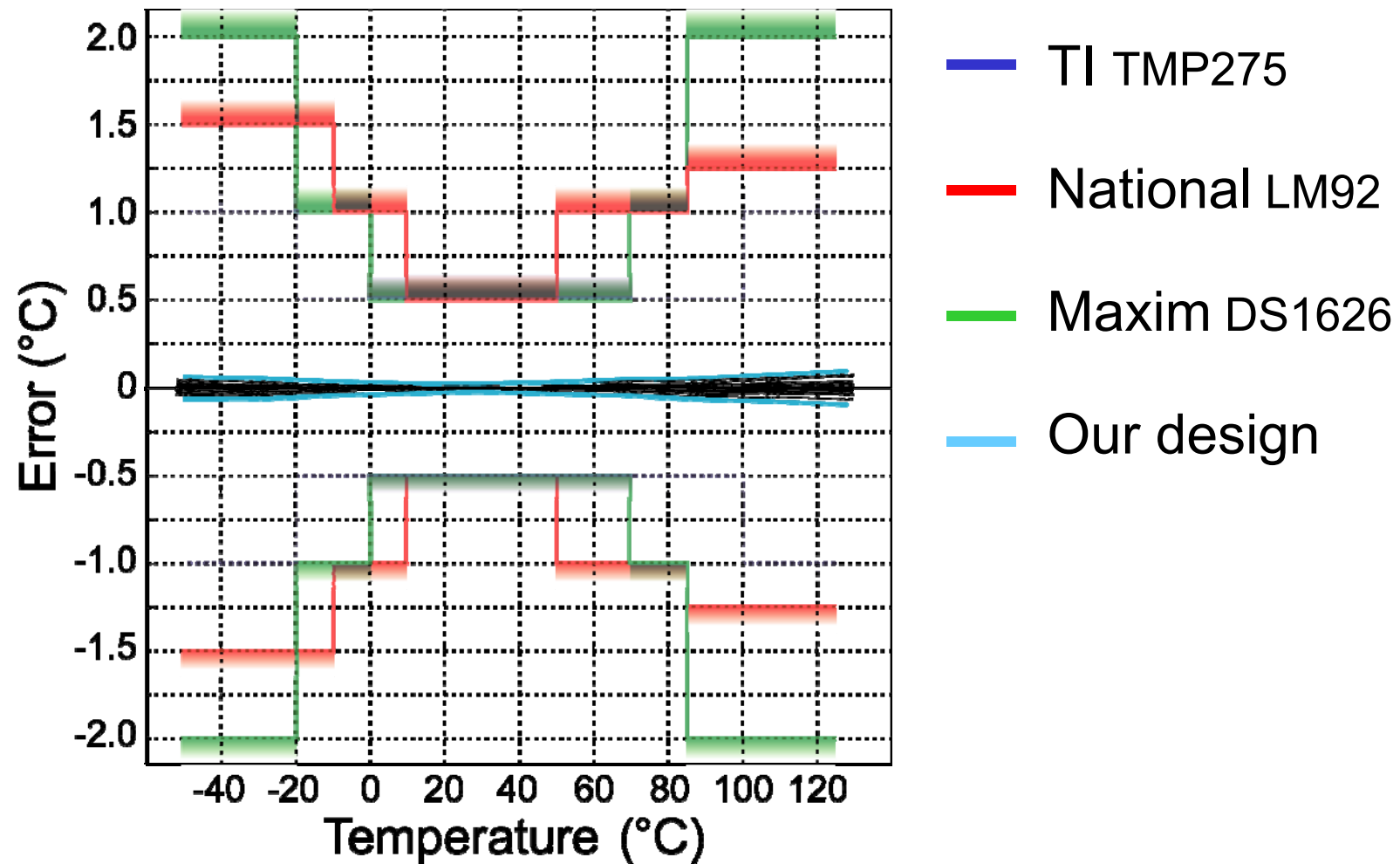

Design Summary

1. Do no harm: accuracy **is** limited by sensor (but resolution is still limited by the ADC)
2. System design: nature of V_{BE} spread is exploited to permit cheap single temperature trimming
3. Digitize early: ΔV_{BE} and V_{BE} are input directly into a charge-balancing $\Sigma\Delta$ modulator
4. Be dynamic: CDS, nested chopping and dynamic element matching are used to cancel offset, $1/f$ noise and gain errors

Summary

- A variety of smart sensors can be made in silicon
- But the resulting sensors are only average
⇒ require good interface electronics!
- The following design methodology helps
 - Do no harm!
 - Do system design!
 - Digitize early!
 - Be dynamic!
- Used to realize a unique wind sensor and state-of-the-art magnetic field and temperature sensors

Acknowledgements

- Mierij Meteo
- Xensor Integration
- NXP Semiconductors
- Dutch Technology Foundation (STW)

- Thank-You for Your Attention!

- Any questions?



Background Reading

1. K.A.A. Makinwa and J.H. Huijsing, “A smart wind sensor using thermal sigma-delta modulation techniques,” *Sensors and Actuators A*, vol. 97-98, pp. 15 – 20, April 2002.
2. K.A.A. Makinwa and J.H. Huijsing, “A smart CMOS wind sensor,” *Digest of Technical Papers ISSCC*, pp. 432 – 479, Feb. 2002.
3. J. van der Meer, F.R. Riedijk, K.A.A. Makinwa and J.H. Huijsing, “A fully-integrated CMOS Hall sensor with a 4.5uT, 3σ offset spread for compass applications,” *Digest of Technical Papers ISSCC*, pp. 246 – 247, Feb. 2005.
4. M. A. P. Pertijs, K. A. A. Makinwa, and J. H. Huijsing, “A CMOS smart temperature sensor with a 3σ inaccuracy of $\pm 0.1^\circ\text{C}$ from -55°C to 125°C ,” *JSSC*, vol. 40, no. 12, pp. 2805 – 2815, Dec. 2005.
5. C.P.L. van Vroonhoven and K.A.A. Makinwa, “A CMOS Temperature-to-Digital Converter with an Inaccuracy of $\pm 0.5^\circ\text{C}$ (3σ) from -55 to 125°C ,” *Digest of Technical Papers ISSCC*, pp. 576 – 577, Feb. 2008.
6. K.A.A. Makinwa and M.F. Snoeij, “A CMOS temperature-to-frequency converter with an inaccuracy of $\pm 0.5^\circ\text{C}$ (3σ) from -40 to 105°C ,” *J. Solid-State Circuits*, vol. 41, is. 12, pp. 2992 – 2997, Dec. 2006.
7. K.A.A. Makinwa, M.A.P. Pertijs, J.C. van der Meer and J.H. Huijsing, “Smart sensor design: The art of compensation and cancellation,” *Proc. ESSCIRC*, pp. 76 – 82, Sept 2007.