

CMOS Sigma-Delta Converters – From Basics to State-of-the-Art

Circuits and Errors

Angel Rodríguez-Vázquez



angel@imse.cnm.es



UNIVERSITAT POLITÈCNICA
DE CATALUNYA
BARCELONATECH

Barcelona, 29-30 / Septiembre / 2010

Materials in this course have been contributed by Fernando Medeiro, José M. de la Rosa, Rocío del Río, Belén Pérez-Verdú and Angel Rodríguez-Vázquez



CT- $\Sigma\Delta$ Non-Idealities

Building-block Errors

- Opamp finite (non-linear) DC gain
- Integrator transient response
- Element tolerances
- Time-constant error
- Non-linearity (Front-end V-I and DAC)
- Noise


Architectural Timing Errors

- Quantizer metastability
- Excess loop delay
- Clock jitter

CT-ΣΔMs : Basic building blocks




Basic building blocks – CT Integrators

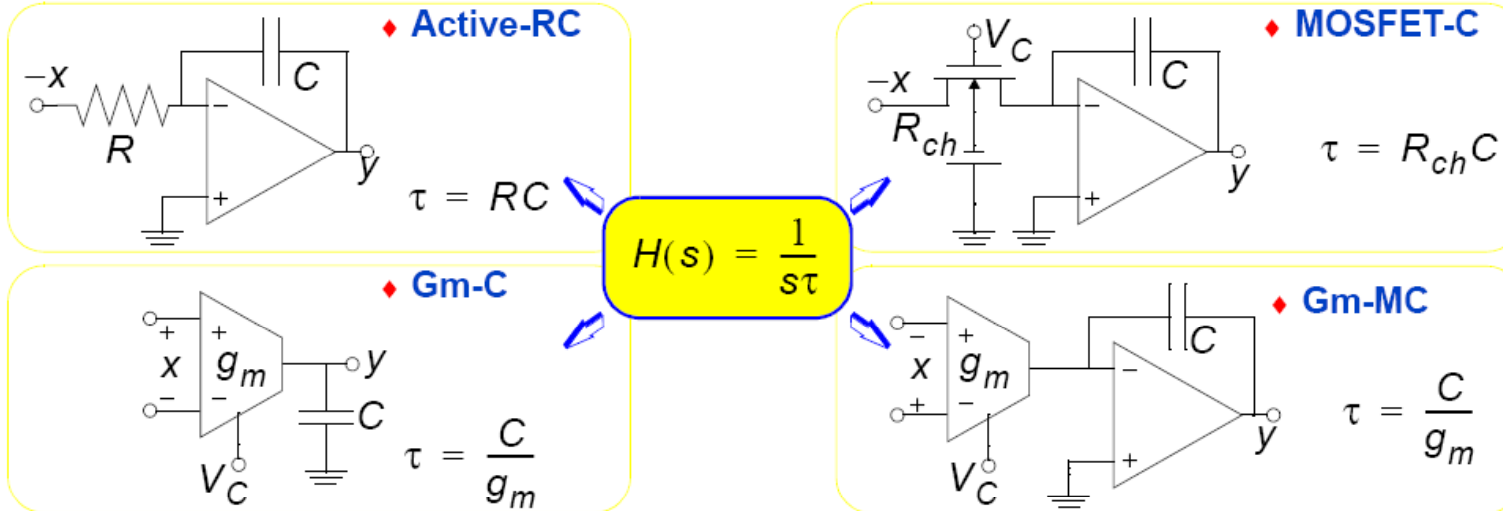

A Gm-MC implementation

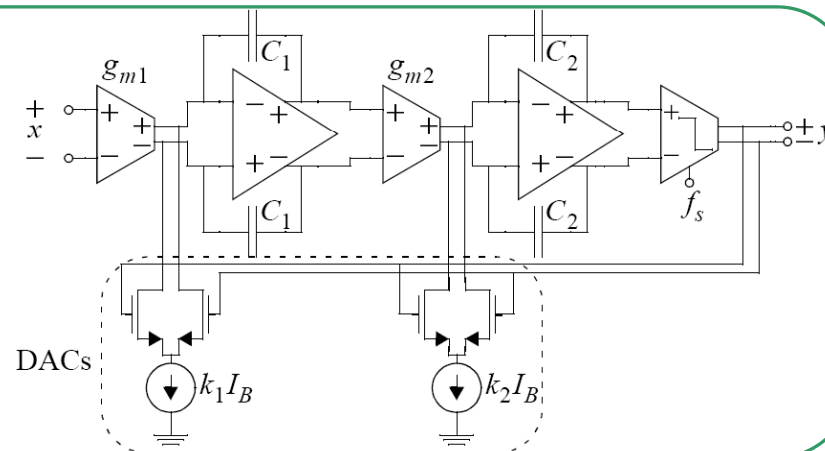- 2nd-order single-loop ΣΔM
- 1-bit switched-current DAC
- 1-bit (latch) comparator



CT-ΣΔMs : Non-ideal integrator transfer function



Integrator Transfer Function (ITF) degraded by circuit non-idealities

$$Y(s) = \frac{1}{\tau \cdot s} X(s)$$

Ideal
Transfer Characteristics

→

$$Y(s) = \left[\frac{1}{\varepsilon_\tau \cdot \tau \cdot s} T_{\varepsilon_H}(s) \right] X(s)$$

First-Order Actual
Transfer Characteristics

$$T_{\varepsilon_H}(s) = \frac{s}{s + \omega_{pl}}$$


$$T_{\varepsilon_H}(s) = \frac{s}{(s + \omega_{pl})(s + \omega_{ph})}$$

$$T_{\varepsilon_H}(s) = \frac{s(s + \omega_z)}{(s + \omega_{pl})(s + \omega_{ph})}$$

.....

First-Order Non-Ideal Integrator Behaviours:

 - ◆ Deviations in the Unity Gain Frequency ε_τ
- ◆ Low-Frequency Pole ω_{pl} . Due to Losses
- ◆ Produce Finite DC Gain
- ◆ Magnitude Errors for $\omega \gg \omega_{pl}$
- ◆ Phase Errors for $\omega \gg \omega_{pl}$
- ◆ High-Frequency Poles and Zeros $T_{\varepsilon_H}(s)$
- ◆ Phase Errors for $\omega \ll \omega_{ph}, \omega_z, \dots$



CT-ΣΔMs : Effect of finite DC gain error



Opamp finite DC gain (I)


RC	MOSFET-C	Gm-C	Gm-MC
$\omega_{pl} < \frac{G}{C \cdot A_0} = \frac{\omega_u}{A_0}$	$\omega_{pl} < \frac{G_{ch}}{C \cdot A_0} = \frac{\omega_u}{A_0}$	$\omega_{pl} = \frac{\omega_u G_{go}}{\epsilon_T G_m}$	$\omega_{pl} < \frac{G_{go}}{C \cdot A_0} = \frac{\omega_u G_{go}}{A_0 G_m}$

RC integrators [Gerf03]

$$ITF(s) = \frac{\alpha/\tau}{s+\gamma} \quad \alpha = \frac{A_0}{1+A_0} \quad \gamma = \frac{1/\tau}{1+A_0}$$

- Same IBN degradation as in SC ΣΔMs ($\tau = 1/f_s$)

 
$$P_{A_0} = \frac{\Delta^2}{12k_1^2 k_q^2} \left[\frac{1}{A_0^{2L} M} + \sum_{m=1}^L \frac{\pi^{2l} L(L-1)\dots(L-m+1)}{(2m+1)M^{2l+1} A_0^{2(L-m)} m!} \right]$$



CT-ΣΔMs : Effect of finite DC gain error



 Opamp finite DC gain (II) – Gm-C integrators




Power Spectral Density of an L th-order ΣΔM

$$S_q(f) = \left| \sum_{i=0}^{L-1} \binom{L}{i} \left(\frac{j\omega}{\omega_{pl}} \right)^i \right|^2 \cdot \frac{\Delta^2}{12 \cdot A_{dc}^{2L} \cdot f_s}$$

Relative increase of P_Q in a 2nd-order ΣΔM

$$\frac{P_q}{P_q|_{A_{dc} \rightarrow \infty}} \approx \frac{5}{\pi^2} \left(\frac{M}{A_{dc}} \right)^4 + \frac{10}{3\pi^2} \left(\frac{M}{A_{dc}} \right)^2 + 1$$

 


CT-ΣΔMs : Integrator transient response



Integrator transient response (I)


- ◆ Less critical than in DT ΣΔMs
- ◆ Need to be taken into account, specially in broadband applications

Influence of GBW [Gerf03]

 

$$P_{GBW} \cong \frac{\Delta^2}{12k_1^2k_q^2} \cdot \left[\frac{\pi^{2L-1}}{(2L+1)M^{2L+1}} \cdot \left(1 + \frac{k_1/\tau}{GBW_1}\right)^2 \prod_{i=2}^L \left(1 + \frac{1}{GBW_i \cdot \tau}\right)^2 \right]$$

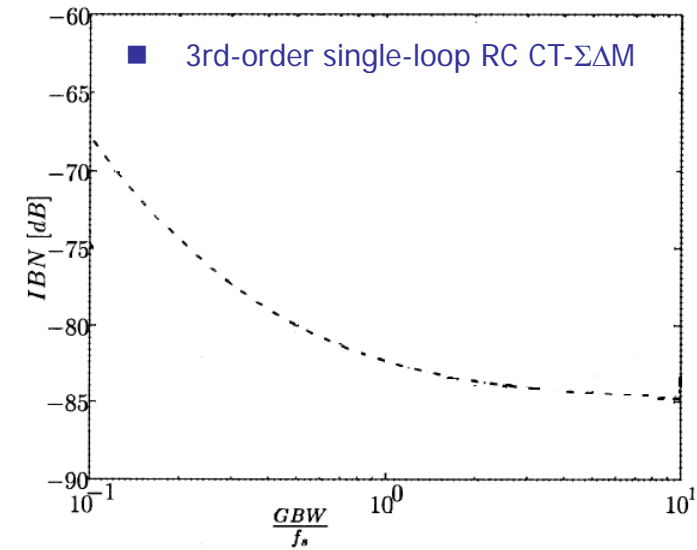$GBW = A_0 \cdot \omega_a$ → $ITF(s) \cong \frac{k_j}{s \cdot \tau} \cdot \frac{\frac{GBW}{GBW + k_j/\tau}}{\frac{s}{GBW + k_j/\tau} + 1}$



Other dynamic effects


- ◆ 2nd-order poles
 - ◆ Slew-rate
- Complex analysis
 - Simulation-based study [Ruiz03]

CT-ΣΔMs : Integrator transient response



Model of GBW for RC-active based CT-ΣΔMs [Ortm04]

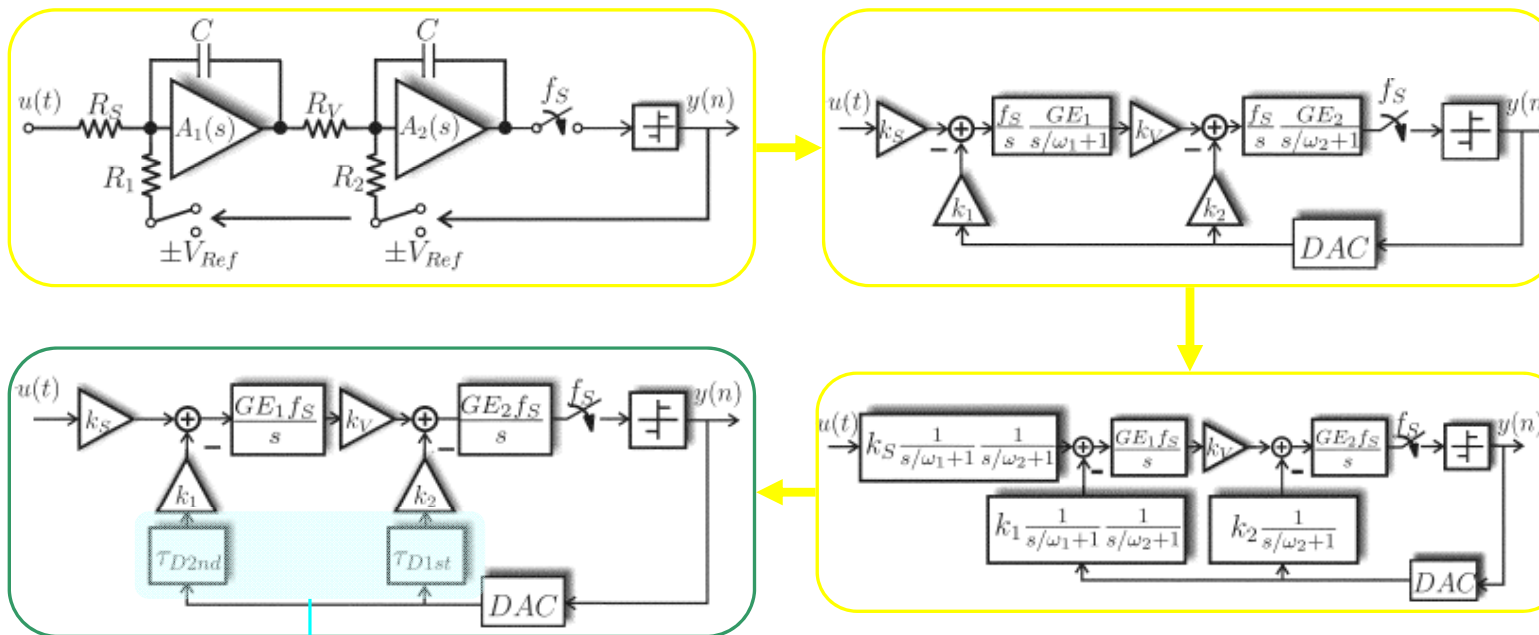- Modeled as a gain error (GE) and extra loop delay
- Each delay is different for each feedback path



$$\tau_{D1st} = \frac{1 - e^{-\omega_2/fs}}{\omega_2} \quad \tau_{D2nd} = \frac{\omega_1^2(1 - e^{-\omega_2/fs}) - \omega_2^2(1 - e^{-\omega_1/fs})}{\omega_1\omega_2(\omega_1 - \omega_2)}$$

CT-ΣΔMs : Circuit element tolerances




Element tolerances

- Scaling coefficients accuracy limited by random errors in resistors/capacitors


$$\frac{\Delta\tau}{\tau} = \frac{\Delta C}{C} - \frac{\Delta g_m}{g_m} \Rightarrow \sigma_\tau = \sqrt{\sigma_C^2 + \sigma_{g_m}^2}$$

- Especially critical in:
 - High-order single-loop architectures (instability)
 - Cascade architectures (analog/digital coefficient ratios)
- Two types of random errors:
 - Absolute tolerances: variations from chip to chip (10-20%)
 - Relative mismatches: variations from device to device on one chip (0.5-1%)

Electrical control of frequency tuning

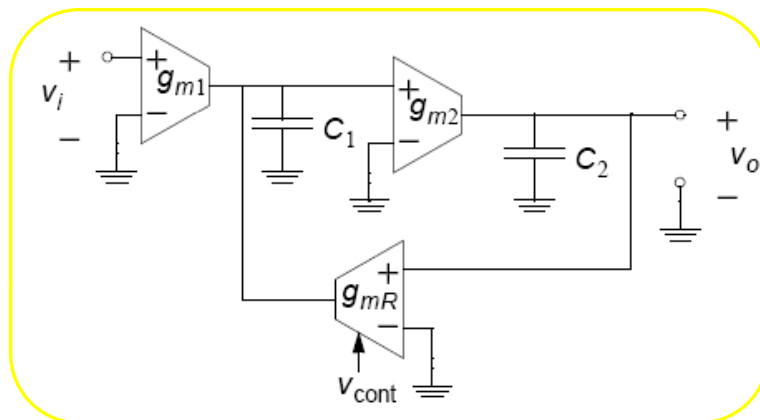

 System-level optimization and synthesis method




CT-ΣΔMs : Circuit element tolerances



Direct synthesis method of CT cascade architectures [Tort06]:

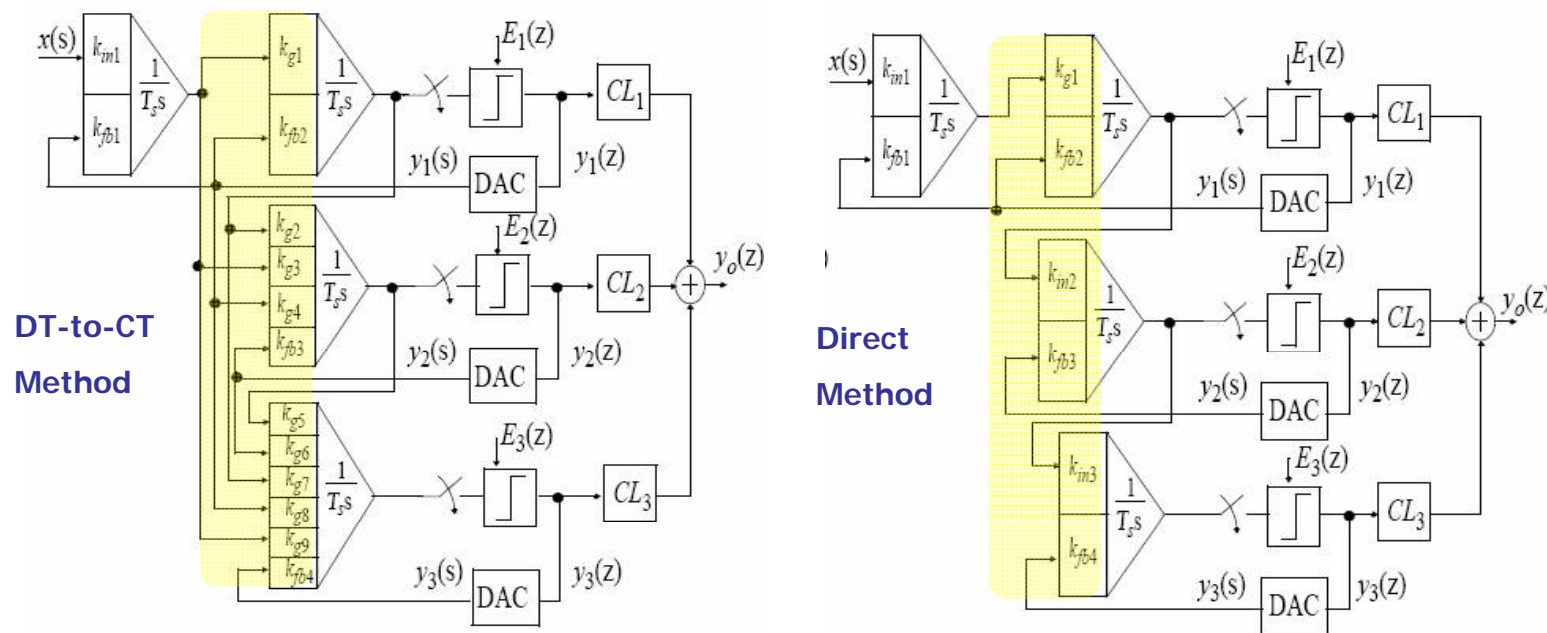- ◆ Optimum placement of poles/zeros of the NTF
- ◆ Synthesis of both analog and digital part of the cascade CT ΣΔ Modulator
- ◆ Reduced number number of analog components
- ◆ Reduced sensitivity to element tolerances




CT-ΣΔMs : Circuit element tolerances




Direct synthesis of cascade architectures (I) [Tort06]

 - ◆ Sensitivity to mismatch (gm,C)
- ◆ A 2-1-1 example



DT-to-CT synthesis method

 


Direct synthesis method

CT-ΣΔMs : Circuit element tolerances



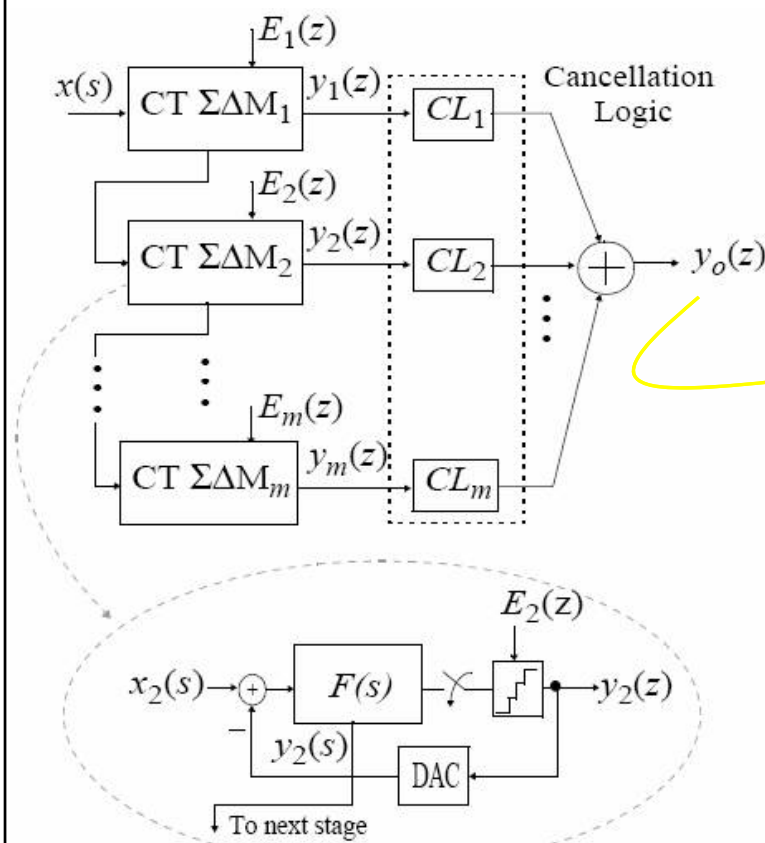Direct synthesis of cascade architectures (II) [Tort06]



$$y_o(z) = \sum_{k=1}^m y_k(z) CL_k(z)$$

$$y_k(z) = \frac{E_k(z) + \sum_{i=1}^{k-1} Z_{ik} y_i(z)}{1 - Z_{kk}}$$


$$CL_k(z) = \frac{-Z_{km} CL_m}{1 - Z_{mm}}$$

$$[Z_{km} \equiv Z(L^{-1}(H_D F_{km})|_{nT_s})]$$

CT- $\Sigma\Delta$ Ms : Circuit element tolerances



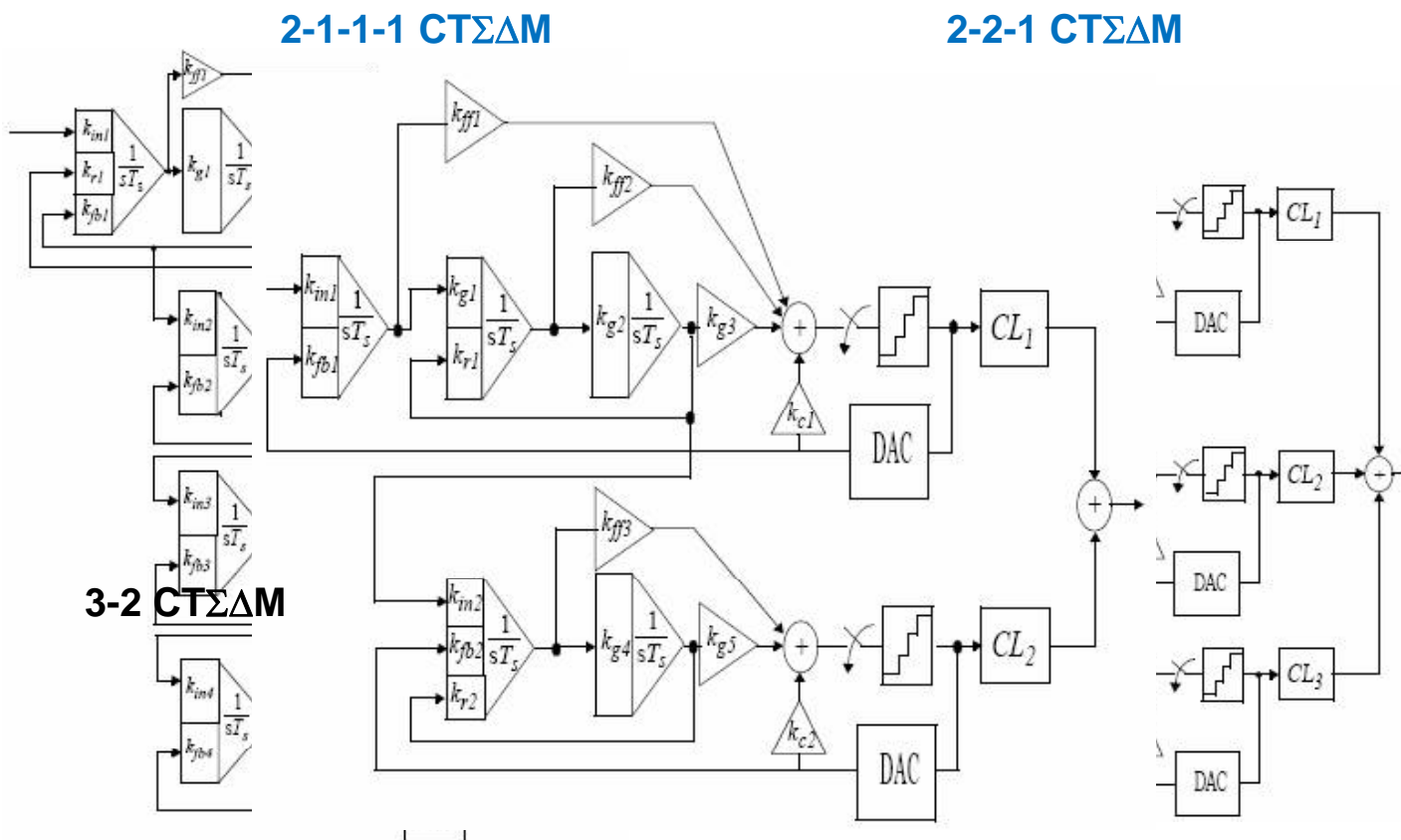
- Synthesized cascaded CT SDMs to cope with 12-bit@20-MHz




CT- $\Sigma\Delta$ Ms : Synthesis methods



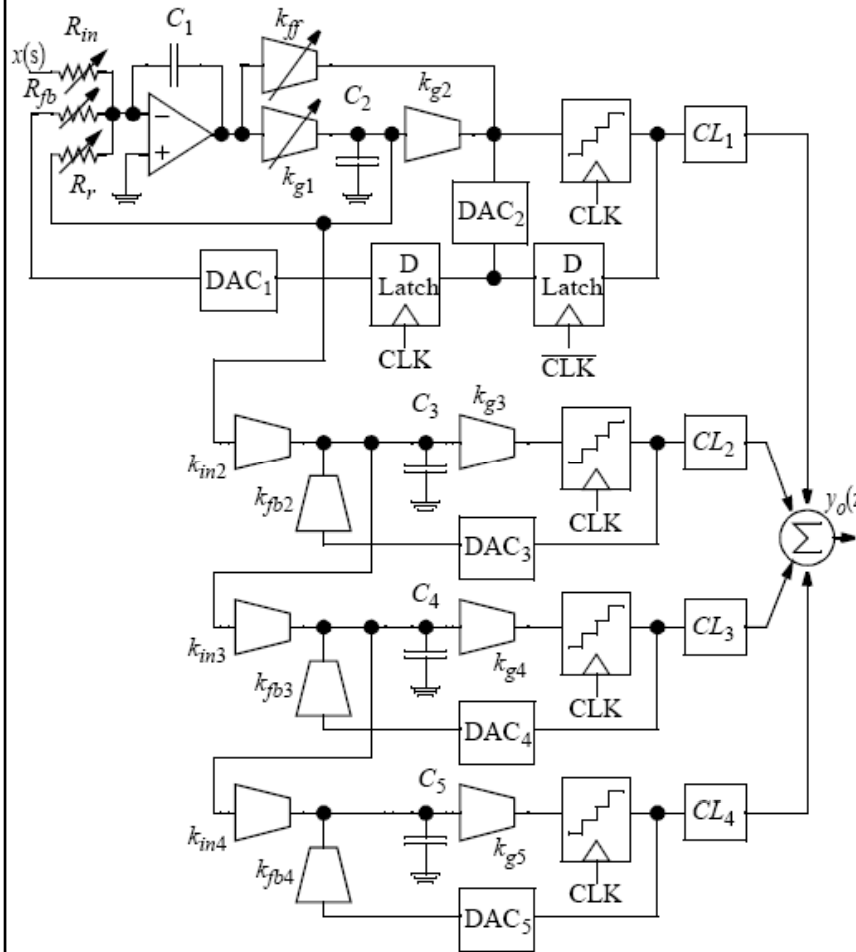■ A case study: A 12-bit@20MHz, 4-b, 2-1-1 CT $\Sigma\Delta$ M (RC/Gm Integrators)



Parameter	Value
R_{in}, R_{fb}	1k Ω
R_r	2.9k Ω
$k_{g2} \dots k_{g5}$	50 μ A/V
k_{g1}	500 μ A/V
k_{ff}	120 μ A/V
$k_{in2} \dots k_{in4}, -k_{fb2} \dots -k_{fb4}$	450 μ A/V
C_1	7.5pF
$C_2 \dots C_5$	1.875pF

 


CT-ΣΔMs : Integrator time-constant error



Integrator time-constant error (I)

$$ITF(s) = \frac{A_0}{1 + sC(1 + \epsilon_\tau)/g_0}$$

$$\epsilon_\tau = C_p/C$$

 

- ◆ Capacitor plate parasitic capacitances
- ◆ Parasitic capacitances of the inter-connection lines
- ◆ Parasitic input capacitances of the circuits connected to the node
- ◆ Parasitic output capacitances of the circuits connected to the node

RC ϵ_τ	MOSFET-C ϵ_τ	Gm-C ϵ_τ	Gm-MC ϵ_τ
$1 + \frac{G}{C \cdot A_0 \cdot \omega_a} + \frac{C + C_T}{C \cdot A_0}$	$1 + \frac{G_{ch}}{C \cdot A_0 \cdot \omega_a} + \frac{C + C_T}{C \cdot A_0}$	$1 + \frac{C_T}{C}$	$1 + \frac{G_{go}}{C \cdot A_0 \cdot \omega_a} + \frac{C + C_T}{C \cdot A_0}$

CT- $\Sigma\Delta$ Ms : Integrator time-constant error




Integrator time-constant error (II)

$$\Delta P_{Q_{A_o \epsilon_\tau}}|_{\text{dB}} \cong \begin{cases} \frac{3M^2}{\pi^2} \cdot \frac{1}{A_o^2} + (1 + \epsilon_\tau)^2 & \text{(1st-order modulator)} \\ (1 + \epsilon_\tau)^4 + \frac{10}{3\pi^2} \cdot \frac{(1 + \epsilon_\tau)^2}{A_o^2} M^2 + \frac{5}{\pi^4 A_o^4} M^4 & \text{(2nd-order modulator)} \end{cases}$$

Optimum SNR for:

$$\tau = 1/f_s$$

 



CT-ΣΔMs : Non-linear errors



Causes of Non-linearity

- ◆ Intrinsic non-linearity of the resistor material
- ◆ Modulation of thickness of the conductive layer with resistor voltage


V-I transformation in RC integrators

  

➡ **Ideally** $i = R_0^{-1} \cdot v$

$$g_{NL}(v) = R_0^{-1} \cdot \{ a_2 \cdot v^2 + a_3 \cdot v^3 + o(v) \}$$

V-I transformation in Gm-C integrators

 

Normalized Large Signal Characteristic

$$i(v) = \begin{cases} -1 & v \leq -\sqrt{2} \\ v\sqrt{1 - (v/2)^2} & |v| \leq \sqrt{2} \\ 1 & v \geq \sqrt{2} \end{cases} \quad i = \frac{I_0}{2I_B} \quad v = V_{in} \left(\frac{G_{m0}}{2I_B} \right)$$

$$G_{m0} = 2\sqrt{\frac{2\beta_1 I_B}{n}}$$

CT-ΣΔMs : Non-linear errors




Effect on Non-linearity in Gm-C CT-ΣΔMs [Bree01]

$$i(v) = \beta v \sqrt{2I_B/\beta - v} \cong \sum_{k=1}^{\infty} g_{m_k} v^k$$


$$i(v) \cong g_{m_1} v + g_{m_3} v^3$$
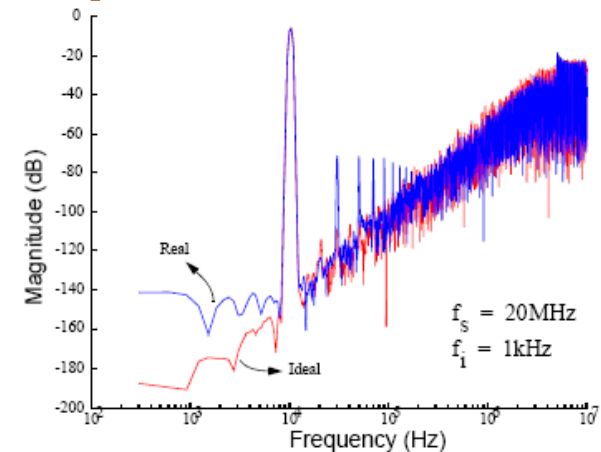
$$THD \cong HD_3 \cong \frac{g_{m_3} V_i^2}{g_{m_1}}$$




Linearization strategies

 Source Degeneration of Basic Differential Pairs




Exploiting the Ohmic Region of MOSTs

 

$$I_d = 2\beta(V_1 - V_2) \left[(V_i - V_{T0}) - \frac{n}{2}(V_1 + V_2) \right]$$

MOST Saturated Transconductors

 - Functional cancellation
- Square-law functions combination




CT-ΣΔMs : Nonlinearities and noise



Typical Nonlinear-Tolerant Architecture

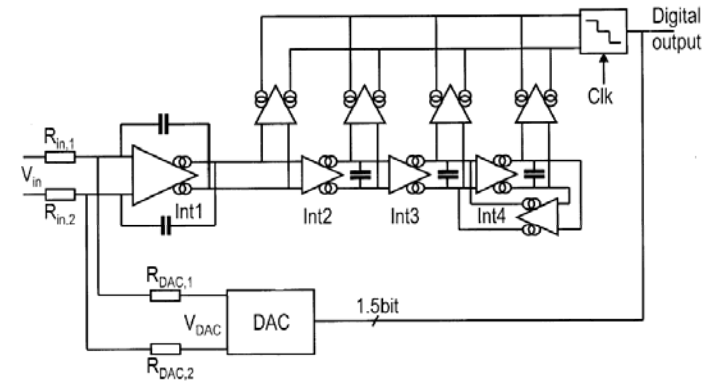- ◆ RC-active front-end integrator
- ◆ Gm-C subsequent integrators




Other sources of non-linearity

- ◆ Multi-bit DACs
- ◆ Linearity must be the same or lower than the required resolution
- ◆ Corrected by same techniques as those employed in SC ΣΔMs
 - DEM
 - Calibration



Circuit noise

- ◆ Dominated by noise sources from the front-end integrator and DAC
- ◆ Flicker noise reduced by proper sizing and/or chopper techniques
- ◆ Unsampled noise – effect of sampling reduced by the loop gain

 
$$P_{Th} \cong \frac{KT}{4C} \frac{\pi^{2L}}{(2L+1)M^{2L+1}}$$




CT-ΣΔMs : Comparator metastability

 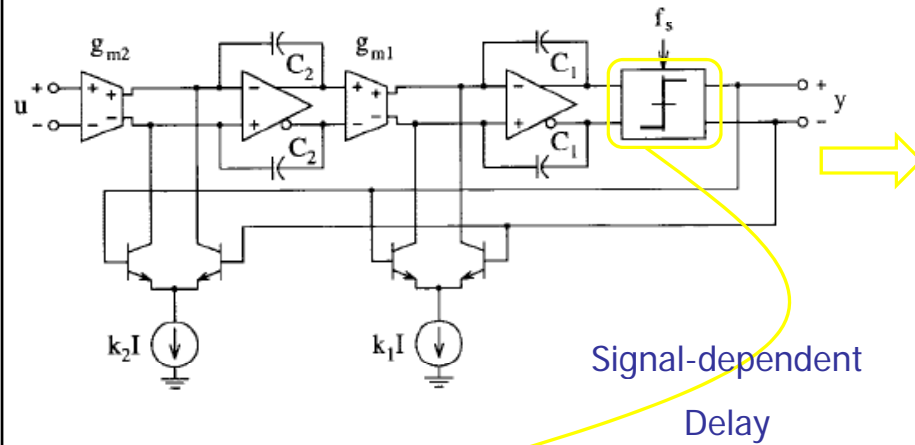

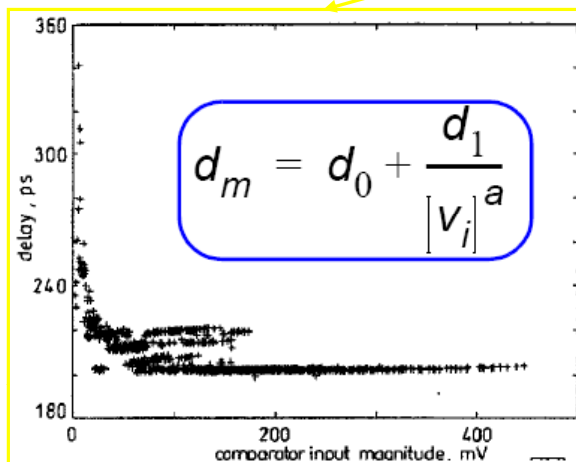
- Can be cancelled by using additional latches [Dagh04]




- Modeled as a jitter noise [Cher00]

 

CT-ΣΔMs : Excess loop delay

 


DAC transient response delay

 




$$Y(f) = \frac{g_q g_1 g_2}{(st)^2 + g_q g_1' g_2 \cdot e^{-\tau_d s} + g_q g_2' \cdot (st) e^{-\tau_d s}} X(f) + \frac{(st)^2}{(st)^2 + g_q g_1' g_2 \cdot e^{-\tau_d s} + g_q g_2' \cdot (st) e^{-\tau_d s}} E(f)$$

- ◆ Adds additional poles to STF/NTF
- ◆ Causes instability
- ◆ Stability condition:

 - 2nd-order $\rho_d \leq \frac{g_2'}{2g_1'g_2}$
- *L*th-order $\rho_d \propto \frac{1}{[H(f)]_{\text{outband}}}$




 
 
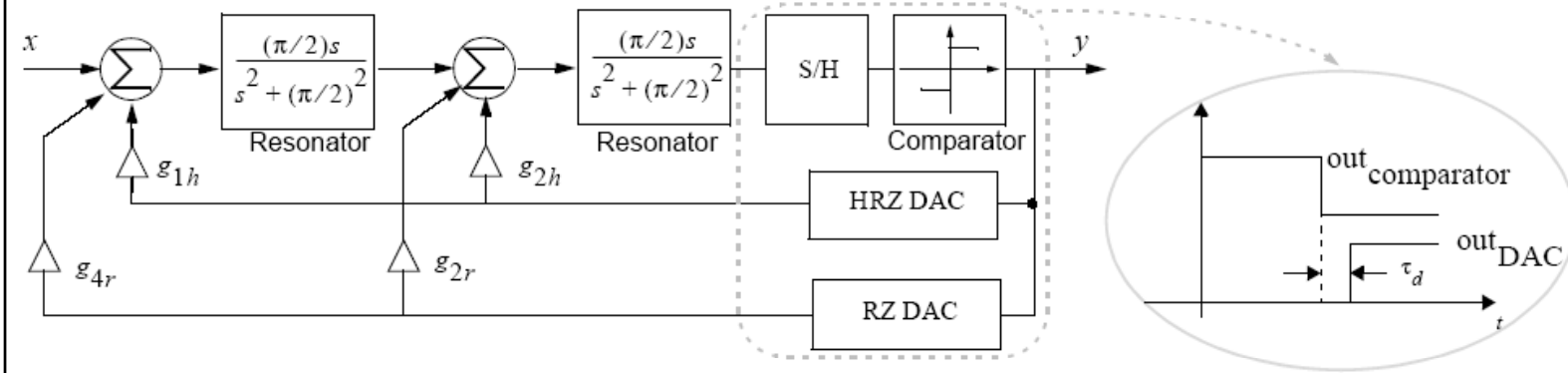
CT- $\Sigma\Delta$ Ms : Excess loop delay – Raising Instability



CT- $\Sigma\Delta$ Ms : Excess loop delay – Cancellation



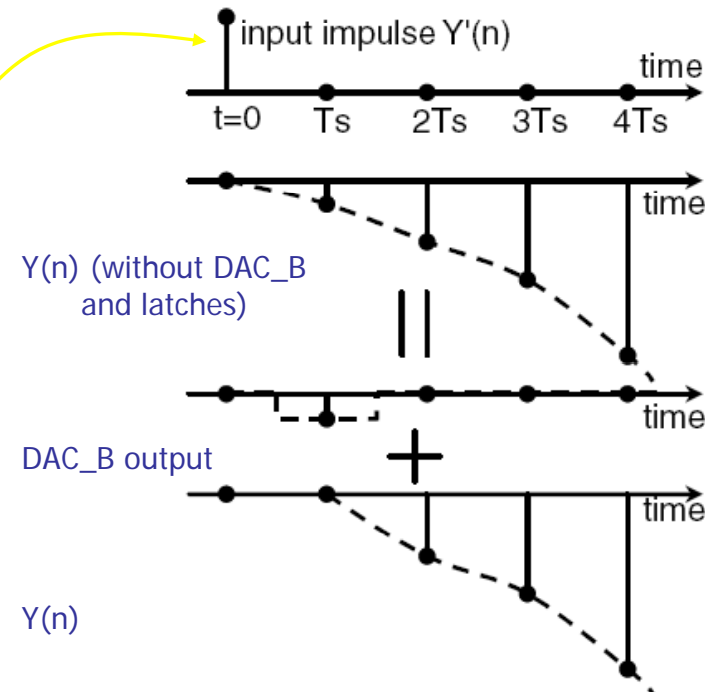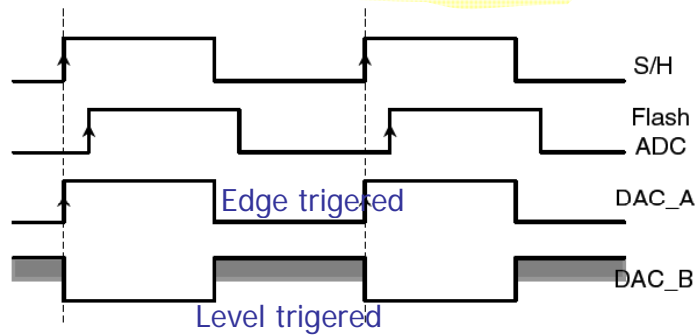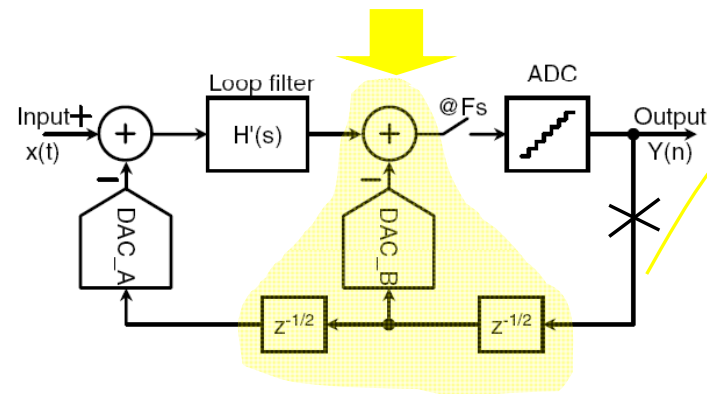 - ◆ Extra feedback paths (DACs) with tunable gains [Cher00]
- ◆ Using only one additional DAC and two latches [Yan04]




CT- $\Sigma\Delta$ Ms : Excess loop delay – Compensation



□ Digital compensation [Font05]

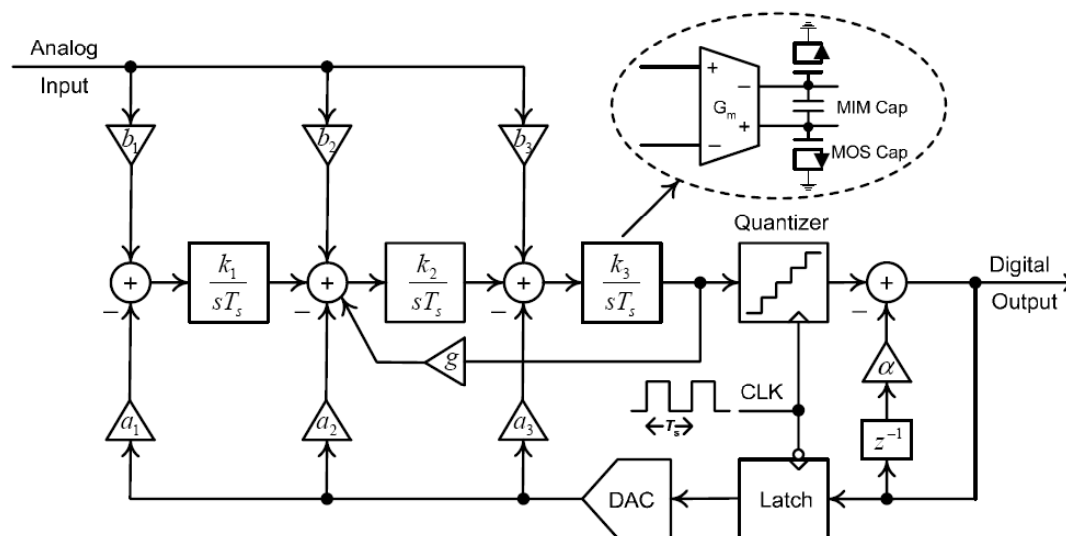- ◆ Implemented in a 3rd-order single loop architecture with 5-level quantizer
 - 90nm CMOS
 - 74-dB SNDR-peak, 600kHz bandwidth
 - 6.0mW, 1.5V
- ◆ Excess loop delay compensated in the digital domain
- ◆ Half-a-clock-cycle delay
 - Relax comparators speed
 - Provide maximum isolation between quantizer and DAC switch events




CT-ΣΔMs : Clock jitter error




□ Clock jitter (I)

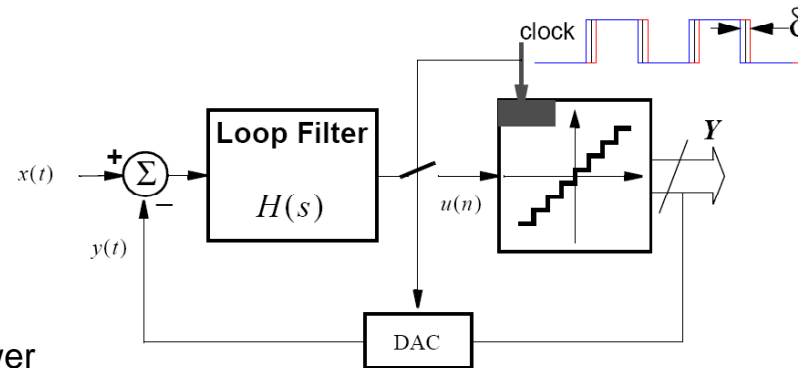- ◆ S/H
 - Shaped by the modulator NTF
 - Can be neglected
- ◆ DAC
 - Directly adds with the input
 - Increases the in-band noise power



 CT ΣΔMs are more sensitive to clock jitter than DT ΣΔMs



□ White noise model approximation (NRZ DAC) [Cher00][Zwan96]

- ◆ Standard deviation of jitter error: $\sigma_q^2 \cong \sigma_j^2 I_{DAC}^2$


- ◆ SNR degradation: $SNR_J = 10 \log \left(\frac{1}{16MB_w^2 \sigma_j^2} \right)$

$$\frac{\sigma_{jCT}}{\sigma_{jDT}} = \left(\frac{\pi}{2M} \right)^2$$

CT-ΣΔMs : Clock jitter error



 □ Clock Jitter (II) – White noise model approximation (NRZ/RZ DAC) [Tao99a]




■ Lowpass CT-ΣΔMs

$$P_{jitter}|_{RZ} \cong \left(\frac{T_s}{T_0}\right)^2 P_{jitter}|_{NRZ}$$

■ Bandpass CT-ΣΔMs

$$SNR_J \cong \begin{cases} 10\log \left[\frac{\text{sinc}(\pi f_n T_s)}{64 \sigma_j^2 B_w^2 M} \right] & \text{NRZ} \\ 10\log \left[\frac{\text{sinc}(\pi f_n T_s)}{64 \left(\frac{T_s}{T_0}\right)^2 \sigma_j^2 B_w^2 M} \right] & \text{RZ} \end{cases}$$

$\frac{\sigma_j^2|_{CT}}{\sigma_j^2|_{DT}} \cong 0,14$

 

CT-ΣΔMs : Clock jitter error



□ Clock Jitter (III) – lingering effect [Olia03a]


- ◆ Jitter-induced noise includes both **white** and **shaped** components
- ◆ State-space analysis of CT-ΣΔMs with RZ DAC shows that:

$$S_{\varepsilon}(z) = (\sigma_s^2 T) \sum_{m_2=1}^N \sum_{j_2=1}^{m_2-1} \sum_{m_1=1}^N \sum_{j_1=1}^{m_1-1} a_{m_1} a_{m_2} z^{j_1-j_2} \times \mathbf{C} \mathbf{A}^{m_1-j_1-1} \mathbf{\Lambda} \mathbf{A}_T^{m_2-j_2-1} \mathbf{C}_T$$

□ Multi-bit NRZ DACs


- ◆ Commonly used in CT-ΣΔMs for broadband telecom applications
- ◆ Less sensitive to clock jitter

■ RZ DAC

 

$$\Delta Q(n) \cong \Delta I_{\text{DAC}}(n) \cdot \Delta T(n)$$


■ NRZ DAC

 

CT-ΣΔMs : Clock jitter error



 □ Clock Jitter (IV) – Multi-bit NRZ DACs [Tort05]




$$\varepsilon(n) = (y(n) - y(n-1)) \frac{\Delta T(n)}{T_s} \quad [\text{Ris94}]$$

$$P_\varepsilon = E\{\varepsilon(n)^2\} = \frac{\sigma_{\Delta T}^2}{T_s^2} E\{[y(n) - y(n-1)]^2\}$$

- Using state-space formulation of NTF:

$$P_\varepsilon = \frac{\sigma_{\Delta T}^2}{T_s^2} \cdot \left(\frac{T_s^2 A^2 \omega_{in}^2}{2} + \frac{X_{FS}^2}{6(2^B - 1)^2} \cdot \psi(\bar{g}, \bar{p}, \bar{\lambda}, L) \right)$$
 
$$\psi(\bar{g}, \bar{p}, \bar{\lambda}, L) = 1 - \bar{g}^T \cdot \bar{p} + \sum_{k=1}^L \sum_{j=1}^L g_k p_k g_j p_j \frac{\lambda_k^{-1} - \lambda_k^{-1} \lambda_j^{-1}}{1 - \lambda_k^{-1} \lambda_j^{-1}}$$



$$SNR_{\text{jitter}} \equiv \frac{A^2}{2 \cdot P_{\varepsilon_band}} = \frac{A^2}{2 \cdot B_w \cdot (\sigma_{\Delta T})^2 \cdot \left[\frac{A^2 \omega_i^2}{f_s} + \frac{X_{FS}^2 \cdot f_s}{3(2^B - 1)^2} \psi(\bar{g}, \bar{p}, \bar{\lambda}, L) \right]}$$


CT- $\Sigma\Delta$ Ms : Clock jitter error



□ Clock Jitter (V): Comparison of [Tort05] with previous approaches

Assuming


2nd-order single-bit
If the inc

 

CT- $\Sigma\Delta$ Ms : Clock jitter error





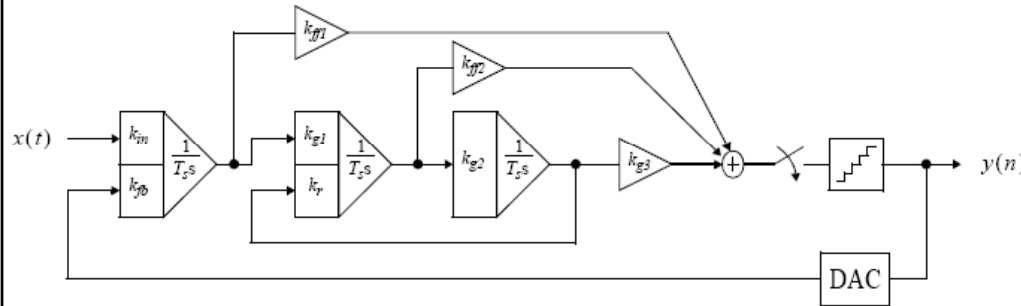
□ Clock Jitter (V) – Multi-bit NRZ DACs [Tort05]



Two cases:

- CT $\Sigma\Delta$ M1: $B=2$ bit, $f_s=400$ MHz

   - CT $\Sigma\Delta$ M2: $B=5$ bit, $f_s=160$ MHz






CT- $\Sigma\Delta$ Ms : Clock jitter error



□ Clock Jitter (VI) – Compensation techniques

  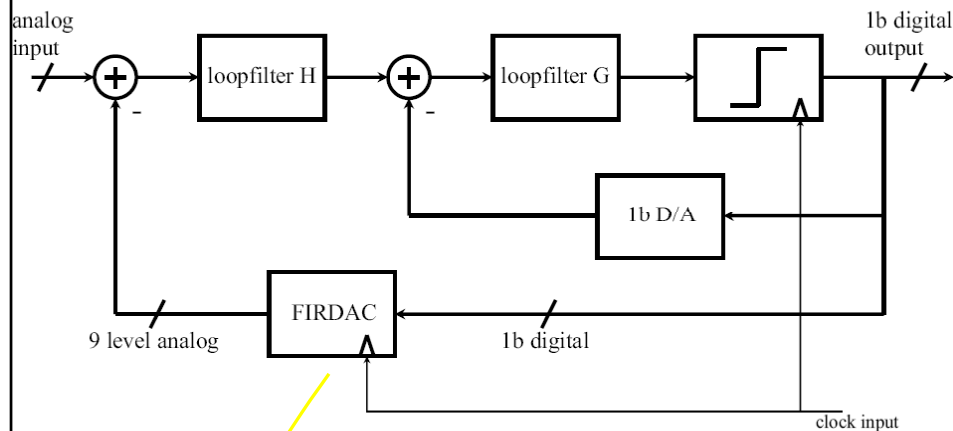- ◆ Multi-bit quantization (non-linear DAC)
- ◆ Switched-capacitor DAC [Veld03]
 - Voltage-mode operation (proper for active RC integrators)
 - Slower than switched-current (current steering) DAC
- ◆ FIRDAC to generate a multilevel signal [Putt04]



CT-ΣΔMs : Case studies




A case study: A Gm-C 12-bit@20MHz, 4-b, 3-2 CT ΣΔM

- ◆ 130nm mixed-signal CMOS, 1P8M
- ◆ Cascade 3-2 multi-bit (4b) CT ΣΔM
- ◆ Gm-C loop-filter implementation
- ◆ Current-steering feedback DACs + DEM
- ◆ 12-bit effective resolution
- ◆ 40MS/s output rate (20MHz bandwidth)
- ◆ 240MHz clock frequency
- ◆ 1.2V ± 10% analog/digital power supply
- ◆ On-chip tuning of analog components
- ◆ Estimated power consumption is 45mW


Loop-filter coefficients

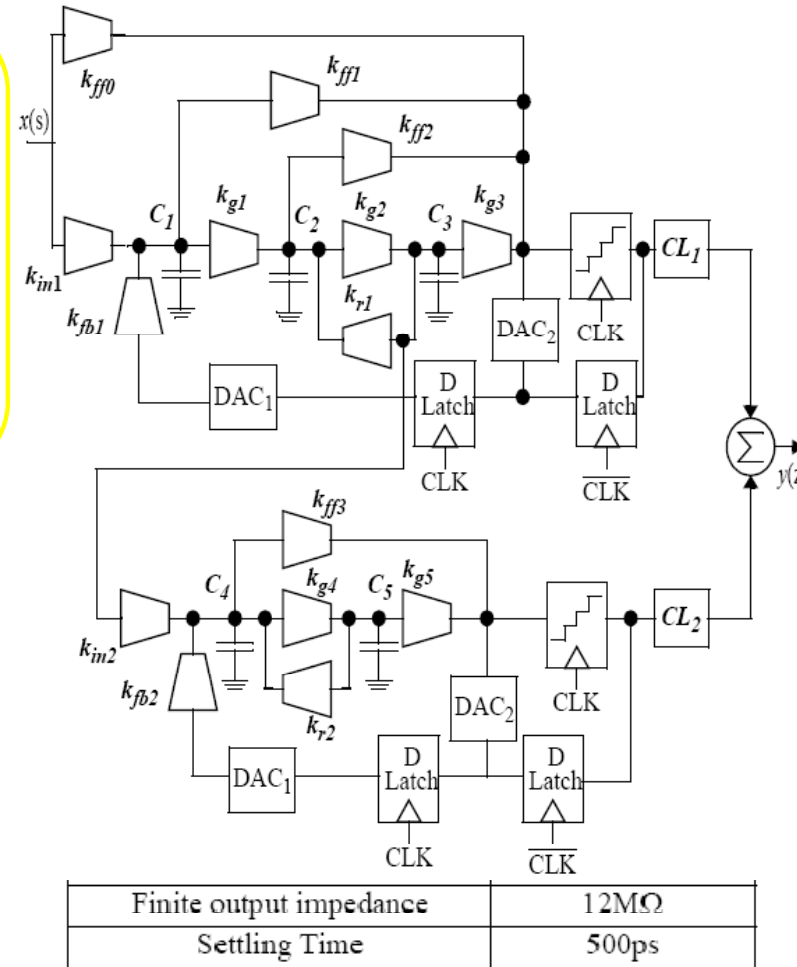$C_u = 3.65 \text{ pF} ; k_u = 190 \mu\text{A/V}$
$C_1 = C_2 = C_3 = C_u ; C_4 = C_5 = 2C_u$
$k_{in1} = 852 \mu\text{A/V} ; k_{fb1} = 730 \mu\text{A/V}$
$k_{ff0} = 2k_u ; k_{ff1} = 4k_u ; k_{ff2} = 2k_u ; k_{ff3} = 5k_u$
$k_{g1} = k_{g5} = 3k_u ; k_{g2} = 5k_u ; k_{g3} = k_u ;$ $k_{g4} = 7k_u$
$k_{in2} = 5k_u ; k_{fb2} = 6k_u$
$k_{r1} = k_{r2} = k_u$




Transconductors

 - ◆ Resistive source degenerated front-end transconductor
- ◆ Loop-filter transconductors based on quadratic term cancellation



Transistor-level performance


DC Gain	78.3 dB
Diff. Input Amplitude	0.3V
Diff. Output Amplitude	0.3V
HD3	-89dB
Power consumption	8.8mW

 

DC Gain	52dB
Diff. Input Amplitude	0.3V
Diff. Output Amplitude	0.3V
HD3	-60dB
Power consumption	622μW

Current-steering DACs

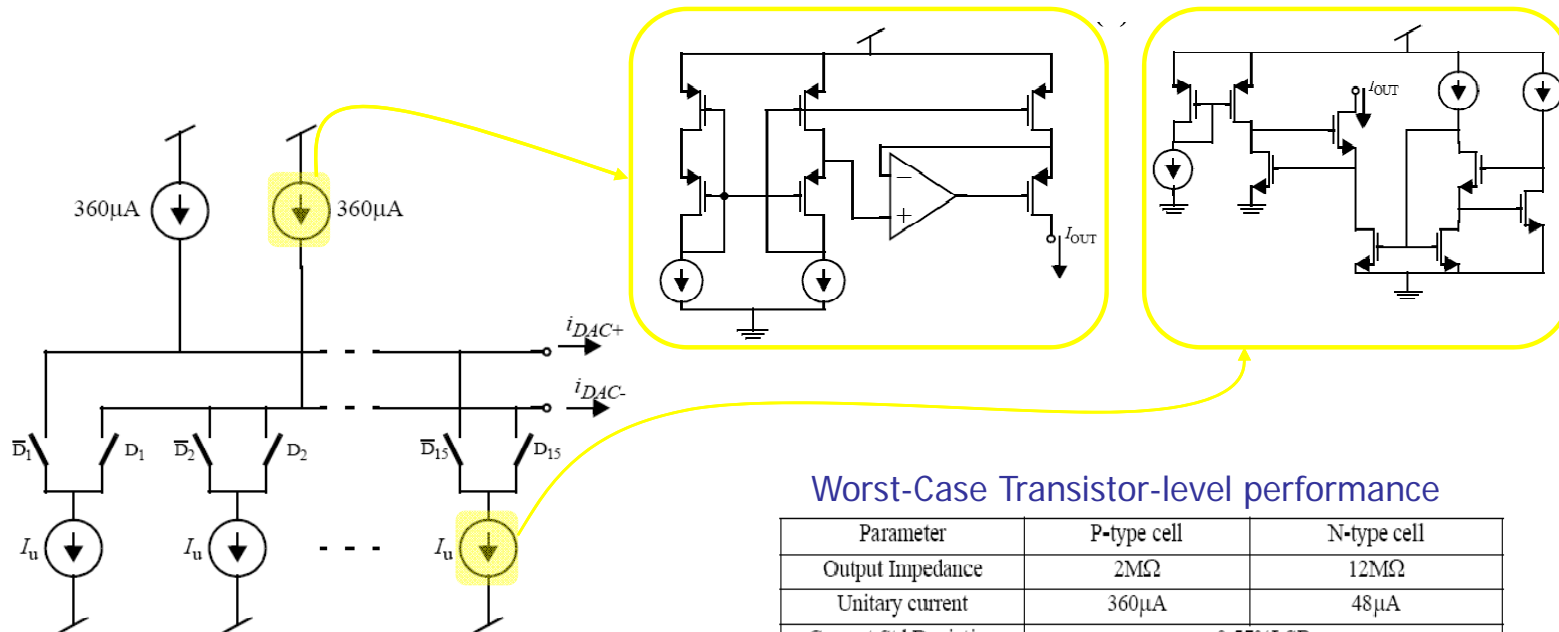- ◆ 2 360- μ A P-type gain-boosted current sources
- ◆ 15 N-type regulated-cascode current cells





Worst-Case Transistor-level performance

Parameter	P-type cell	N-type cell
Output Impedance	2M Ω	12M Ω
Unitary current	360 μ A	48 μ A
Current Std Deviation	0.57%LSB	
Settling Time	--	430ps
Power Cons. (mW)	0.49mW	0.1mW


CT- $\Sigma\Delta$ Ms : Case studies



Chip implementation

 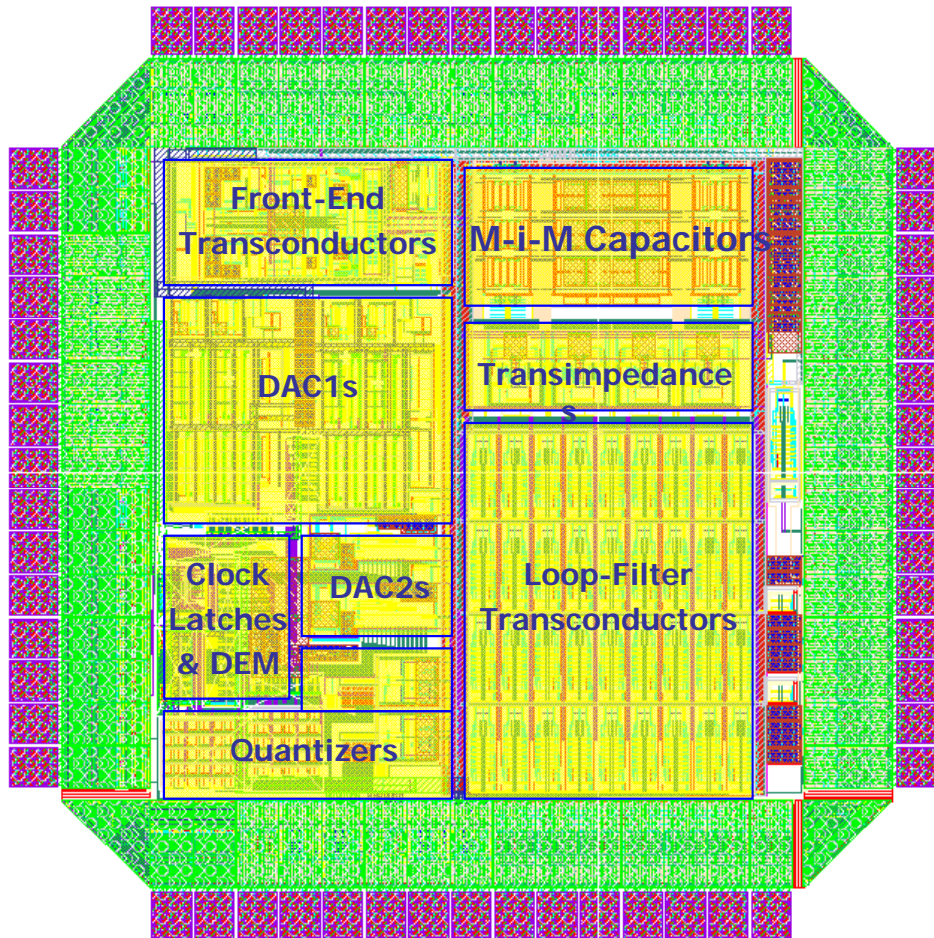


Transistor-level simulation results

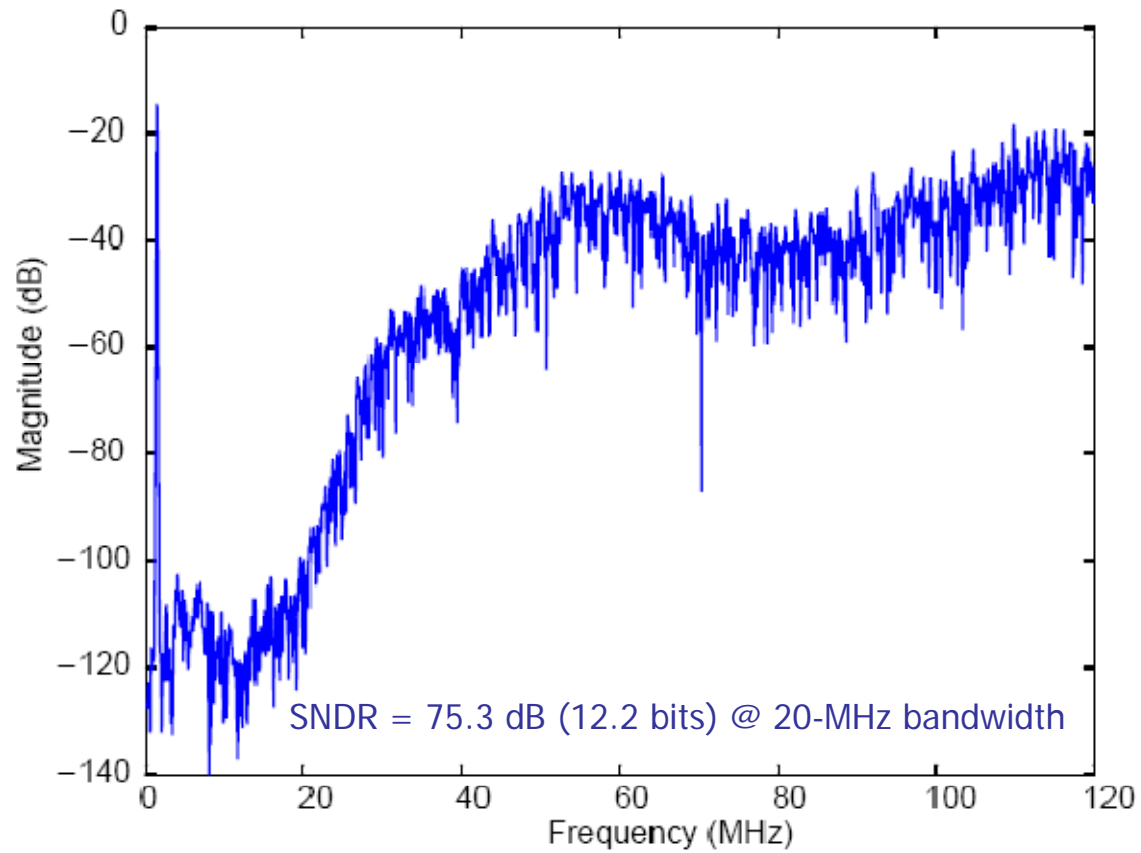

CT-ΣΔMs : Case studies





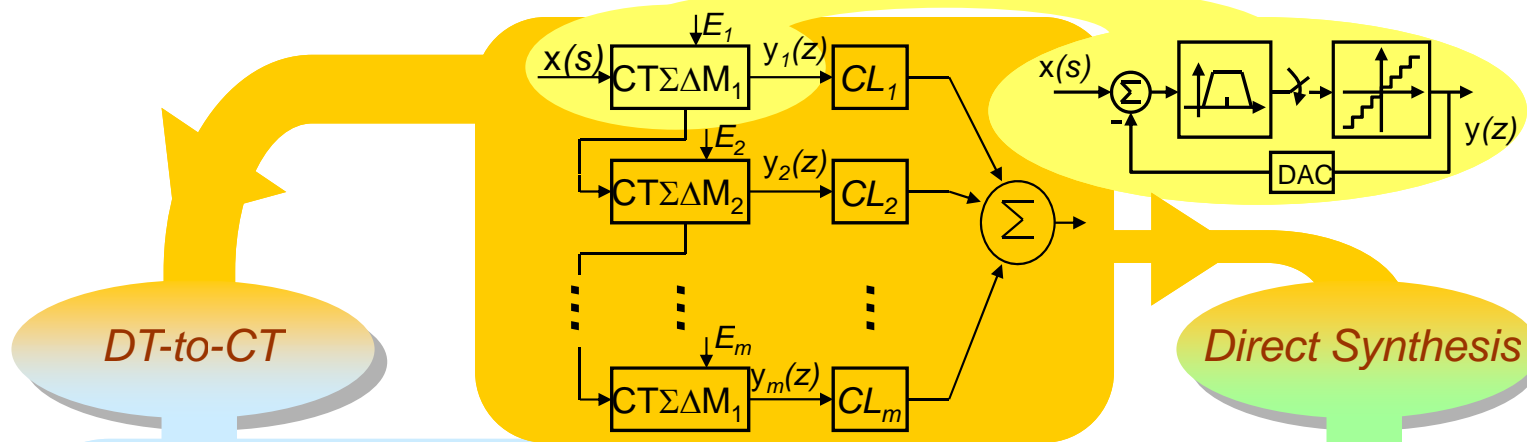□ A case study: A 1.2-V 13-bit@20MHz, 4-b, 2-2-1 CT ΣΔM



DT-to-CT

Direct Synthesis

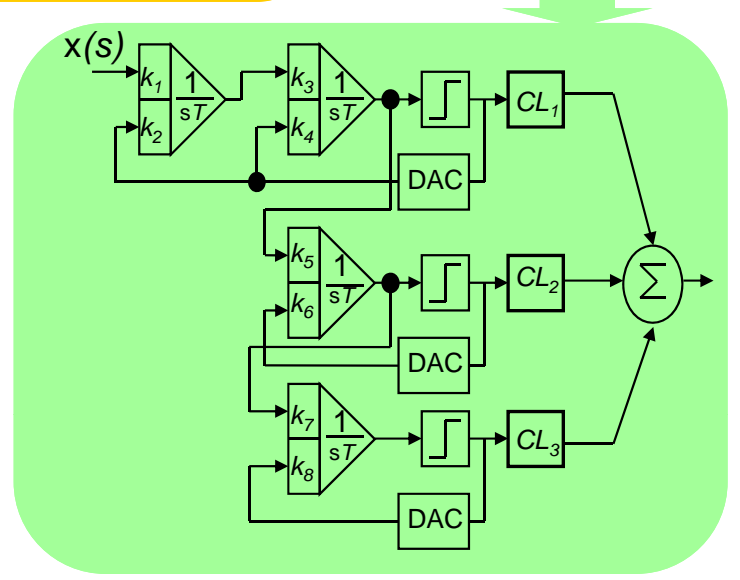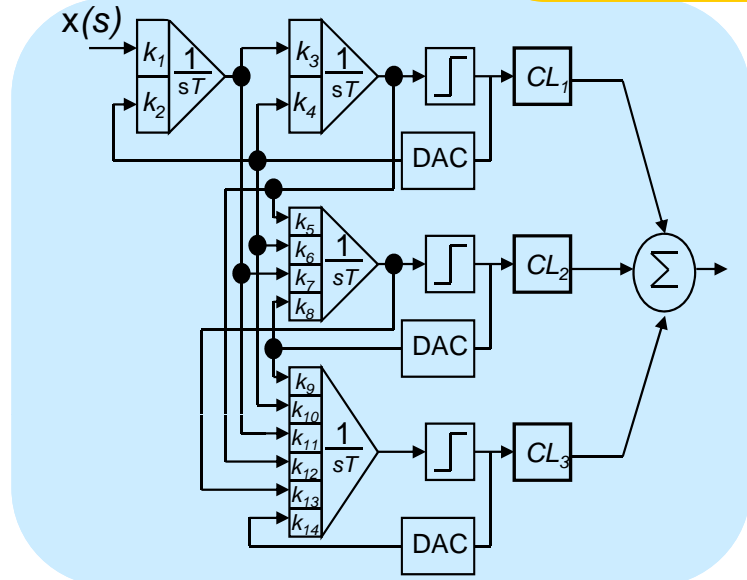



Jitter optimization

Input-dependent Term


$$SDT = \frac{A^L \omega_i^L}{f_s}$$

$$MDT = \frac{A_{FS}^L}{3(2^B - 1)^2} \psi(\bar{g}, \bar{p}, \bar{\lambda}, L)$$

$$SNR_{\text{jitter}} = 10 \log \frac{A^2}{2B_w(\sigma_{\Delta T})^2 \left[\frac{A^2 \omega_i^2}{f_s} + \frac{X_{FS}^2 \cdot f_s}{3(2^B - 1)^2} \psi(\bar{g}, \bar{p}, \bar{\lambda}, L) \right]}$$

$$\psi(\bar{g}, \bar{p}, \bar{\lambda}, L) = 1 - \bar{g}^{-T} \cdot \bar{p} + \sum_{k=1}^{L-1} \sum_{j=1}^L g_k p_k g_j p_j \frac{\lambda_k^{-1} - \lambda_k^{-1} \lambda_j^{-1}}{1 - \lambda_k^{-1} \lambda_j^{-1}}$$


Filter-dependent Term

 

CT-ΣΔMs : Case studies



2-2-1 Modulator

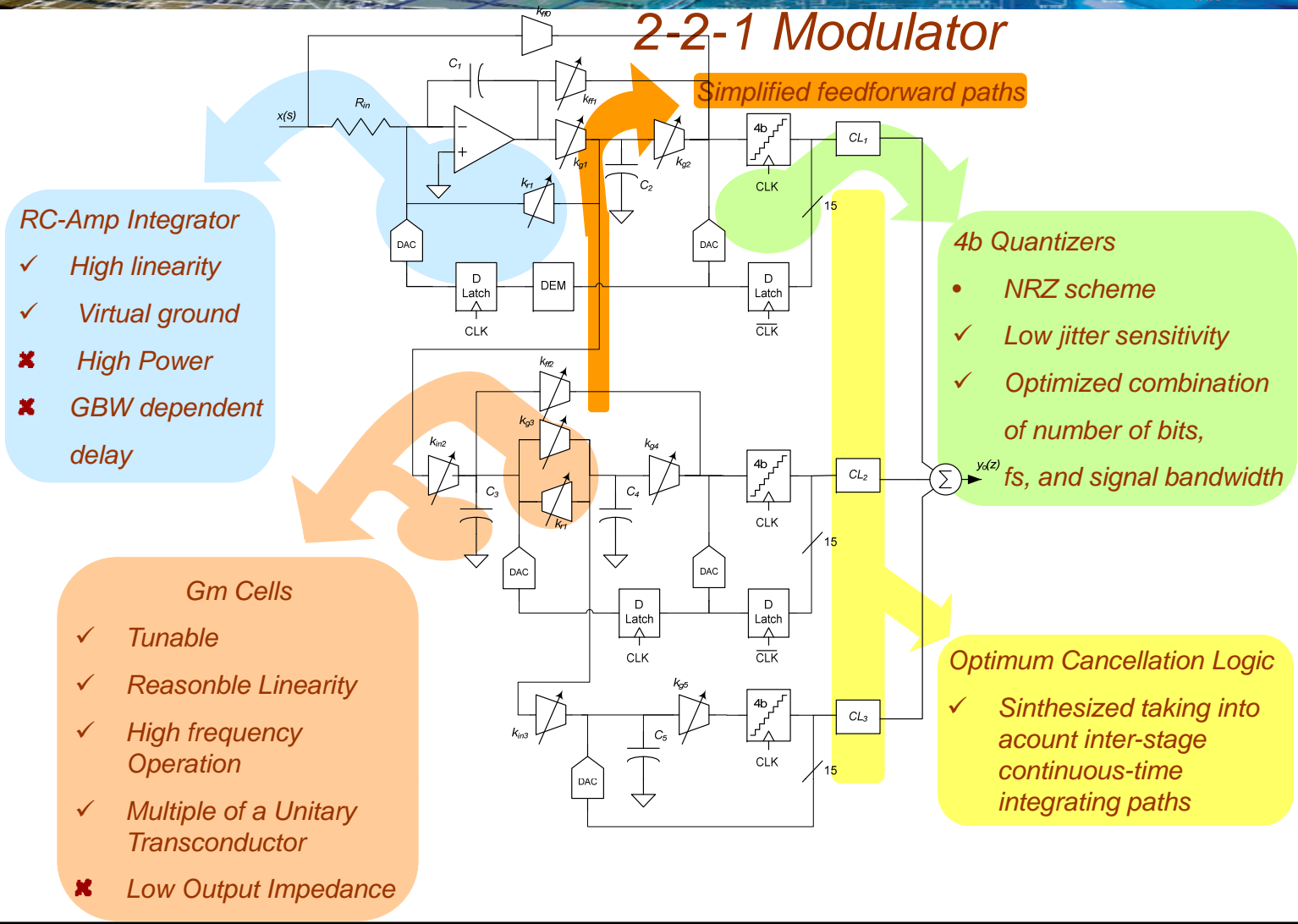

RC-Amp Integrator

- ✓ High linearity
- ✓ Virtual ground
- ✗ High Power
- ✗ GBW dependent delay

Gm Cells

- ✓ Tunable
- ✓ Reasonable Linearity
- ✓ High frequency Operation
- ✓ Multiple of a Unitary Transconductor
- ✗ Low Output Impedance

Simplified feedforward paths


4b Quantizers

- NRZ scheme
- ✓ Low jitter sensitivity
- ✓ Optimized combination of number of bits, fs, and signal bandwidth

Optimum Cancellation Logic



- ✓ Synthesized taking into account inter-stage continuous-time integrating paths

Input OpAmp

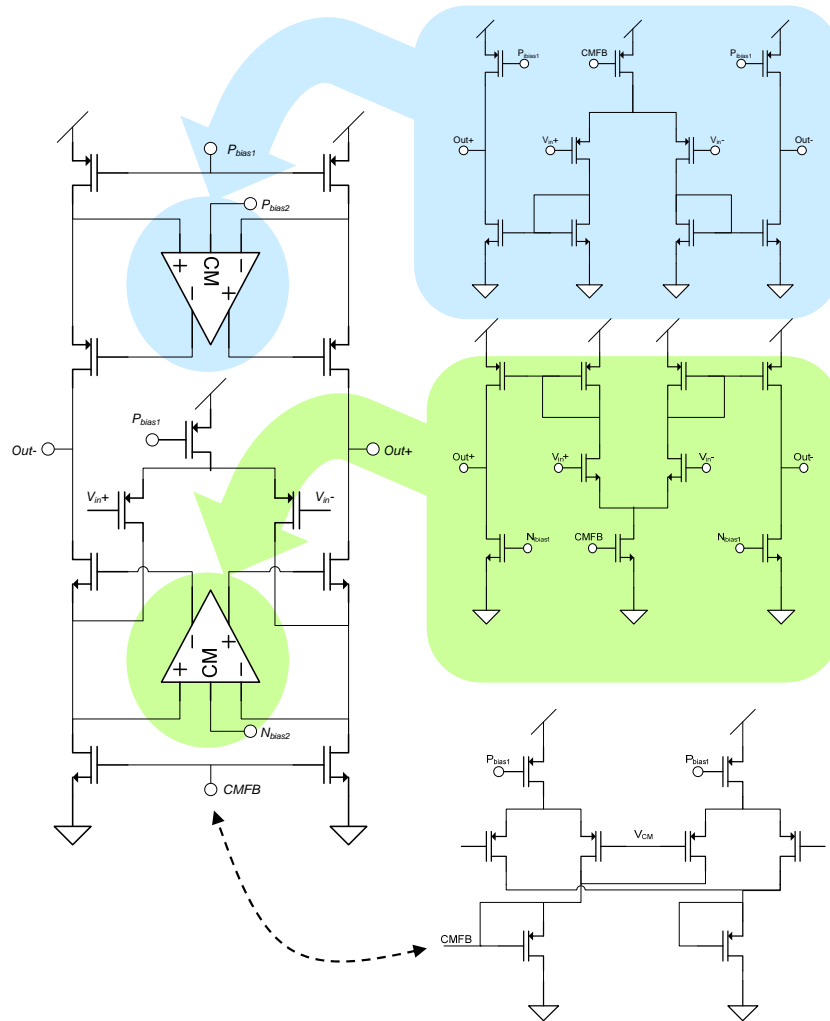


Amplifier Characteristics	
GB	600MHz
DC Gain	71dB
Phase Margin	80°
Parasitic Input Capacitance	0.36pF
Parasitic Output Capacitance	0.4pF
Differential Output Swing	0.7V
Power Consumption	20mW

Unitary Transconductor

 
 


Transconductor Characteristics	
DC Gain	58dB
Diff. Input Amp.	0.3V
Diff. Output Amp.	0.3V
HD3	-57dB
σ_{gm}/g_m	<1.5%
Power	350 μ W

 

Simulation Results

SNDR	80dB
Power	65mW
Minimum SNDR due to mismatch	77dB
Signa Bandwidth	20MHz
Jitter requirements	<5ps
Sampling Frequency	240MHz

  

CT- $\Sigma\Delta$ Ms : References



- [Bree00] L.J. Breems, E.J. Van der Zwan and J. Huijsing, "A 1.8-mW CMOS SD Modulator with Integrated Mixer for A/D Conversion of IF Signals". *IEEE Journal of Solid-State Circuits*, Vol. 35, pp. 468-475, April 2000.
- [Bree01] L. Breems and J.H. Huijsing, *Continuous-Time Sigma-Delta Modulation for A/D Conversion in Radio Receivers*. Kluwer Academic Publishers, 2001.
- [Cher00] J.A. Cherry and W.M. Snelgrove, *Continuous-Time Delta-Sigma Modulators for High-Speed A/D Conversion*. Kluwer Academic Publishers, 2000.
- [Font05] P. Fontaine, A. N. Mohieldin and A. Bellaourar, "A Low-Noise Low-Voltage CT DS Modulator with Digital Compensation of Excess Loop Delay". *Proc. of the 2005 IEEE Int. Solid-State Circuits Conf.*, pp. 498-499, 2005.
- [Gerf03] F. Gerfers, M. Ortmanns and Y. Manoli, "A 1.5-V 12-bit Power-Efficient Continuous-Time Third-Order SD Modulator". *IEEE Journal of Solid-State Circuits*, Vol. 38, pp. 1343-1352, August 2003.
- [Olia03a] O. Olieai, "State-Space Analysis of Clock Jitter in Continuous-Time Oversampling Data Converters". *IEEE Transactions on Circuits and Systems I*, Vol. 50, pp. 31-37, January 2003.
- [Olia03b] O. Olieai, "Design of Continuous-Time Sigma-Delta Modulators With Arbitrary Feedback Waveform". *IEEE Transactions on Circuits and Systems II*, Vol. 50, pp. 437-444, August 2003.
- [Ortm01] M. Ortmanns, F. Gerfers, and Y. Manoli, "On the synthesis of cascaded continuous-time Sigma-Delta modulators". *Proc. of the 2001 IEEE Int. Symp. on Circuits and Systems*, Vol. 5, pp. 419-422, May 2001.
- [Ortm04] M. Ortmanns, F. Gerfers and Y. Manoli, "Compensation of Finite Gain-Bandwidth Induced Errors in Continuous-Time Sigma-Delta Modulators". *IEEE Transactions on Circuits and Systems I*, Vol. 51, pp. 1088-1099, June 2004.
- [Ortm05] M. Ortmanns, F. Gerfers and Y. Manoli, "A Case Study on 2-1-1 Cascaded Continuous-Time Sigma-Delta Modulators". *IEEE Transactions on Circuits and Systems I*, Vol. 52, pp. 1515-1525, August 2005.

CT- $\Sigma\Delta$ Ms : References



- [Tao99a] H. Tao, L. Toth and M. Khoury, "Analysis of Timing Jitter in Bandpass Sigma-Delta Modulators". *IEEE Transactions on Circuits and Systems I*, Vol. 46, pp. 991-1001, August 1999.
- [Tao99b] H. Tao and J.M. Khoury, "A 400MS/s Frequency Translating BandPass Delta-Sigma Modulator". *IEEE Journal of Solid-State Circuits*, Vol. 34, pp. 1741-1752, December 1999.
- [Tort05] R. Tortosa, J.M. de la Rosa, A. Rodríguez-Vázquez and F.V. Fernández, "Analysis of Clock Jitter Error in Multibit Continuous-Time SD Modulators with NRZ Feedback Waveform". *Proc. Of the 2005 Int. Symposium on Circuits and Systems (ISCAS)*, May 2005.
- [Tort06] R. Tortosa, J.M. de la Rosa, F.V. Fernández and A. Rodríguez-Vázquez: "A New High-Level Synthesis Methodology of Cascaded Continuous-Time Sigma-Delta modulators". *IEEE Trans. On Circuits and Systems – II: Express Briefs*, pp. 739-743, August 2006.
- [Tort07] R. Tortosa, A. Aceituno, J.M. de la Rosa, F.V. Fernández and A. Rodríguez-Vázquez: "A 12-bit@40Ms/s Gm-C Cascade 3-2 Continuous-Time Sigma-Delta Modulator". *Proc. Of the 2007 Int. Symposium on Circuits and Systems (ISCAS)*, May 2007.
- [Yan04] S. Yan and E. Sánchez-Sinencio, "A Continuous-Time SD Modulator With 88-dB Dynamic Range and 1.1-MHz Signal Bandwidth". *IEEE Journal of Solid-State Circuits*, pp. 75-86, January 2004.