

CMOS Sigma-Delta Converters – From Basics to State-of-the-Art

Circuits and Errors

Angel Rodríguez-Vázquez



angel@imse.cnm.es




UNIVERSITAT
POLITÈCNICA
DE CATALUNYA
BARCELONATECH

Barcelona, 29-30 / Septiembre / 2010

Materials in this course have been contributed by Fernando Medeiro, José M. de la Rosa, Rocío del Río, Belén Pérez-Verdú and Angel Rodríguez-Vázquez

 DT- $\Sigma\Delta$ M's: Overview of non-idealities




- Ideal In-Band Error Power:

$$P_Q = \frac{1}{12} \left(\frac{\Delta}{2^B - 1} \right)^2 \frac{\pi^{2L}}{(2L+1)OSR^{2L+1}}$$


- Actual In-Band Error Power:

$$P_T = P_Q + \Delta P_Q + P_{TH} + P_J + P_{HD} + \dots$$


Finite Amplifier Gain

 


Non-Linearities

 


Thermal Noise

 


Comparitor Hysteresis

 


Capacitor Mismatch

 


Settling Errors

 

Clock Jitter

 

DAC Non-linearity

 


... among others ...


DT- $\Sigma\Delta$ M's: Overview of non-idealities



- Depending on the building-block:

 

 Fully-diff SC schematic
of a 2nd-order $\Sigma\Delta$



Clock:
- Jitter

Amplifiers:

- Output swing
- DC gain
- Dynamic limitations (GB, SR)
- Thermal and 1/f noise
- Gain non-linearity

Switches:

- Finite on-resistance
- Thermal noise
- Charge injection
- Clock feedthrough
- Non-linearity

References:

- Thermal and 1/f noise
- Output impedance

Capacitors:

- Mismatch
- Non-linearity

Comparators:

- Hysteresis
- Offset

Multi-bit ADCs & DACs:

- Gain error
- Offset error
- Non-linearity

DT- $\Sigma\Delta$ M_s: Overview of non-idealities



- Depending on their effect:

ERRORS DEGRADING NTF

- AMPLIFIER DC GAIN
- CAPACITOR MISMATCH
- INTEGRATOR SETTLING
 - Amplifier GB
 - Amplifier SR
 - Switch R_{on}

**Impact depends
on topology**



😊 SINGLE-LOOP $\Sigma\Delta$ M_s

→ Low sensitivity

😢 CASCADE $\Sigma\Delta$ M_s

→ Noise leakages

  Imperfect cancellation of
low-order quantization errors



DT- $\Sigma\Delta$ M_s: Overview of non-idealities



Depending on their effect:

ERRORS DEGRADING NTF

- AMPLIFIER DC GAIN
- CAPACITOR MISMATCH
- INTEGRATOR SETTLING
 - ▼ Amplifier GB
 - ▼ Amplifier SR
 - ▼ Switch R_{on}

Impact depends
on topology



SINGLE-LOOP $\Sigma\Delta$ M_s

→ Low sensitivity



CASCADE $\Sigma\Delta$ M_s

→ Noise leakages

Imperfect cancellation of
low-order quantization errors

MODELED AS ADDITIVE ERRORS

- CIRCUIT NOISE
 - ▼ Thermal noise (switches, opamps, refs)
 - ▼ 1/f noise (opamps, refs)
- CLOCK JITTER
- DISTORTION
 - ▼ Non-linear amplifier gain
 - ▼ Non-linear capacitors
 - ▼ Non-linear settling
 - ▼ Non-linear switches

Front-end
dominates


Similar impact on
different topologies

DT-ΣΔMs: Integrator leakage




- Effect of amplifier gain on the integrator transfer function:

Ideal SC integrator

 

 SC integrator considering amplifier finite gain



$$v_{o,n} = v_{o,n-1} + g \cdot v_{i,n-1} \rightarrow v_{o,n} = \frac{1}{1 + \frac{(1+g)}{A_{DC}}} \left[\left(1 + \frac{1}{A_{DC}} \right) \cdot v_{o,n-1} + g \cdot v_{i,n-1} \right]$$

$$H(z) = g \frac{z^{-1}}{1 - z^{-1}}$$


$$H(z) \approx g \frac{z^{-1}}{1 - z^{-1} \left(1 - \frac{g}{A_{DC}} \right)} = g \frac{z^{-1}}{1 - z^{-1} (1 - g\mu)}$$

Shift of the pole
from DC ($z = 1$)


DT- $\Sigma\Delta$ M: Integrator leakage



 - Effect on single-loop $\Sigma\Delta$ M:



2nd-order $\Sigma\Delta$ M

 

- Ideally: $H(z) = \frac{z^{-1}}{1-z^{-1}}$

$$Y(z) = z^{-2}X(z) + (1-z^{-1})^2E(z)$$

- In practice: $H(z) = \frac{z^{-1}}{1-z^{-1}(1-\mu)}$

$$\begin{aligned} NTF(z) &= [1-z^{-1}(1-\mu)]^2 \\ &= (1-z^{-1})^2 + 2\mu z^{-1}(1-z^{-1}) + \mu^2 z^{-2} \end{aligned}$$

$\xrightarrow{\hspace{1cm}}$ $\xrightarrow{\hspace{1cm}}$ $\xrightarrow{\hspace{1cm}}$

$$P_Q(\mu) \approx \frac{\Delta^2}{12} \left(\frac{\pi^4}{5OSR^5} + \frac{2\mu^2}{3OSR^3} + \frac{\mu^4}{OSR} \right)$$

L th-order $\Sigma\Delta$ M:

$$\Delta P_Q \approx \frac{\Delta^2}{12} \frac{L\mu^2\pi^{2L-2}}{(2L-1)OSR^{(2L-1)}}$$

Quite insensitive to
leakages (μ^2 , $L-1$ shaping)




DT- $\Sigma\Delta$ M: Integrator leakage



Effect on cascade $\Sigma\Delta$ M:

2-1-1 $\Sigma\Delta$ M

 

Analog	Digital	
$g_2' = 2g_1'g_2$	$d_0 = \frac{g_3'}{g_1'g_2g_3} - 1$	$H_1(z) = z^{-1}$
$g_4' = g_3''g_4$	$d_1 = \frac{g_3''}{g_1'g_2g_3}$	$H_2(z) = (1-z^{-1})^2$
	$d_2 = 0$	$H_3(z) = z^{-1}$
	$d_3 = \frac{g_4''}{g_1'g_2g_3g_4}$	$H_4(z) = (1-z^{-1})^3$

Mismatch between
analog and digital
filtering

- Ideally:

$$Y(z) = STF(z)X(z) + NTF_1(z)E_1(z) + NTF_2(z)E_2(z) + NTF_3(z)E_3(z)$$

$$\Rightarrow \begin{cases} STF(z) = z^{-4} \\ NTF_1(z) = 0 \\ NTF_2(z) = 0 \\ NTF_3(z) = d_2(1-z^{-1})^4 \end{cases}$$

- In practice: $H(z) = \frac{z^{-1}}{1-z^{-1}(1-\mu)}$


$$P_Q(\mu) \approx \frac{\Delta_1^2}{12} \left(\frac{4\mu^2\pi^2}{3OSR^3} \right) + \frac{\Delta_2^2}{12} d_1^2 \left(\frac{\mu^2\pi^4}{5OSR^5} \right) + \frac{\Delta_3^2}{12} d_3^2 \left(\frac{\mu^2\pi^6}{7OSR^7} + \frac{\pi^8}{9OSR^9} \right)$$

low-order leakages
(L_1-1, L_2-1, \dots)

DT- $\Sigma\Delta$ Ms: Integrator leakage



 Comparison of integrator leakage effect on 4th-order $\Sigma\Delta$ Ms



- Sensitivity to int. leakages of cascades increases with OSR and L
- 1st-stage leakages dominate (L_1 -1 shaping)









DT- $\Sigma\Delta$ M_s: Capacitor mismatch



- Circuit primitive:



- Physical implementations:

        

DT-ΣΔMs: Capacitor mismatch




$$C = C_{oxc}^* \cdot (W \cdot L)$$

Actual \neq Ideal


Local and global errors in:

- ▶ Area
- ▶ Capacitance per Unit Area


▶ Edge Errors

 

 ▶ Errors in thickness and dielectric constant gradient




SC integrator

 

$$g = \frac{C_1}{C_2} = \frac{nC_u}{mC_u}$$

$$\frac{\sigma_g}{g} = \sqrt{\frac{1}{n} + \frac{1}{m}} \cdot \frac{\sigma_{Cu}}{C_u}$$

 
$\sigma_c \sim 0.05\% - 0.1\%$
using good quality
caps and adequate
layout strategies



DT- $\Sigma\Delta$ Ms: Capacitor mismatch



 - Effect on single-loop $\Sigma\Delta$ s:



2nd-order $\Sigma\Delta$ M

- Ideally: $g_1 = g_1'$
 $g_2' = 2g_1'g_2$

$$Y(z) = z^{-2}X(z) + (1 - z^{-1})^2E(z)$$

- In practice: $g_i^* = g_i(1 \pm \varepsilon_{g_i})$


$$\varepsilon_{g_i} = 3 \frac{\sigma_{g_i}}{g_i} = 3 \sqrt{\frac{1}{m_i} + \frac{1}{n_i}} \sigma_C$$

$$STF(z) \cong (1 - |\varepsilon_{g_1} - \varepsilon_{g_1}|)z^{-2} \cong z^{-2}$$

$$NTF(z) \cong (1 + \varepsilon_g)(1 - z^{-1})^2, \quad \varepsilon_g = \varepsilon_{g_2} + \varepsilon_{g_1}$$

Slight increase of error,
but shaping is preserved

 
$$P_Q(\varepsilon_g) \cong \frac{\Delta^2}{12} \left[\frac{(1 + \varepsilon_g)^2 \pi^4}{5OSR^5} \right]$$



DT- $\Sigma\Delta$ Ms: Capacitor mismatch



Effect on cascade $\Sigma\Delta$ Ms:

 

- Ideally:

$$Y(z) = STF(z)X(z) + NTF_1(z)E_1(z) + \\ + NTF_2(z)E_2(z) + NTF_3(z)E_3(z)$$

$$\Rightarrow \begin{cases} STF(z) = z^{-4} \\ NTF_1(z) = 0 \\ NTF_2(z) = 0 \\ NTF_3(z) = d_2(1-z^{-1})^4 \end{cases}$$

- In practice: $g_i^* = g_i(1 \pm \varepsilon_{g_i})$

$$\Rightarrow \begin{cases} STF(z) \approx z^{-4} \\ NTF_1(z) \approx \varepsilon_1 z^{-2} (1-z^{-1})^2 \\ NTF_2(z) \approx d_1 \varepsilon_2 z^{-1} (1-z^{-1})^3 \\ NTF_3(z) \approx d_2 (1+\varepsilon_3) (1-z^{-1})^4 \end{cases}$$





low-order leakages

(L_1, L_2, \dots)

DT- $\Sigma\Delta$ M_s: Capacitor mismatch




- Effect on cascade $\Sigma\Delta$ M_s:

  

DT- $\Sigma\Delta$ M_s: Capacitor mismatch



- Effect on cascade $\Sigma\Delta$ M_s:

 

Sensitivity to mismatch rapidly increases with:


- Oversampling ratio (OSR)
- Cascade order (L)

1st-stage leakages dominate (L_1 shaping)


DT- $\Sigma\Delta$ Ms: Integrator incomplete settling



 - ⇒ The relationship between opamp input and output is non-linear and dynamic



 - Integrator temporal evolution
 - ◆ error due to amplifier finite bandwidth
 - ◆ slew-rate limitation
- Modulator output spectrum
 - ◆ increase on the noise floor
 - ◆ harmonic distortion due to slewing
- SNDR degradation




DT- $\Sigma\Delta$ Ms: Integrator incomplete settling



Integrator temporal evolution: [Rio00]

 
- Both integration and sampling dynamics considered
- 1 pole model + SR limitation in amplifiers
- All parasitic caps taken into account



DT-ΣΔMs: Integrator incomplete settling



Integrator temporal evolution: [Rio00]

 


• **Integration-Phase:**

- finite opamp dynamic
- linear operation or slew

$$C_{eqi} = C_1 + C_p + C_i \left(1 + \frac{C_1 + C_p}{C_o} \right)$$

$$v_a\left(\frac{T_s}{2}\right) = \begin{cases} v_{aH} \exp\left(-\frac{g_m T_s}{C_{eqi}}\right) & \text{Linear} \\ \frac{i_o}{g_m} \operatorname{sgn}(v_{aH}) \exp\left[-\frac{g_m}{C_{eqi}}\left(\frac{T_s}{2} - t_{oi}\right)\right] & \text{Partial Slew} \\ v_{aH} \frac{i_o}{C_{eqi}} \operatorname{sgn}(v_{aH}) \frac{T_s}{2} & \text{Slew} \end{cases}$$

 
$$v_o\left(\frac{T_s}{2}\right) = v_{o,n} + \frac{C_1}{C_o} (v \neq V_{ref}) + \left(1 + \frac{C_p + C_1}{C_o}\right) v_a\left(\frac{T_s}{2}\right)$$



DT-ΣΔMs: Integrator incomplete settling



Integrator temporal evolution: [Rio00]

 

• **Integration-Phase:**

- finite opamp dynamic
- linear operation or slew

$$C_{eqi} = C_1 + C_p + C_o \left(1 + \frac{C_p}{C_o} \right)$$

$v_{a/i} \exp\left(\frac{g_m T_s}{C_{eqi}}\right)$	Linear
$\frac{i_o}{g_m} \operatorname{sgn}(v_{a/i}) \exp\left[\frac{g_m}{C_{eqi}} \left(\frac{T_s}{2} - t_{oi}\right)\right]$	Partial Slew
$v_{a/i} - \frac{i_o}{C_{eqi}} \operatorname{sgn}(v_{a/i}) \frac{T_s}{2}$	Slew
$v_o\left(\frac{T_s}{2}\right) = v_{o,n} + \frac{C_1}{C_o} (v_i \neq V_{ref}) + \left(1 + \frac{C_p + C_1}{C_o}\right) v_a\left(\frac{T_s}{2}\right)$	SR_i

• **Sampling-Phase:**

- finite opamp dynamic
- linear operation or slew

$$C_{eqs} = C_p + (C_1 + C_{n1} + C_{n2}) \left(1 + \frac{C_p}{C_o} \right)$$

$v_{a/s} \exp\left(\frac{g_m T_s}{C_{eqs}}\right)$	Linear
$\frac{i_o}{g_m} \operatorname{sgn}(v_{a/s}) \exp\left[\frac{g_m}{C_{eqs}} \left(\frac{T_s}{2} - t_{os}\right)\right]$	Partial Slew
$v_{a/s} - \frac{i_o}{C_{eqs}} \operatorname{sgn}(v_{a/s}) \frac{T_s}{2}$	Slew
$v_o(T_s) = v_o\left(\frac{T_s}{2}\right) + \left(1 + \frac{C_p}{C_o}\right) [v_a(T_s) - v_a\left(\frac{T_s}{2}\right)]$	SR_s

DT-ΣΔMs: Integrator incomplete settling






Integrator temporal evolution: [Rio00]

	INTEGRATION	SAMPLING
1	LINEAR	LINEAR
2	PARTIAL SLEW	LINEAR
3	SLEW	LINEAR
4	LINEAR	PARTIAL SLEW
5	PARTIAL SLEW	PARTIAL SLEW
6	SLEW	PARTIAL SLEW
7	LINEAR	SLEW
8	PARTIAL SLEW	SLEW
9	SLEW	SLEW

GB AND SR LIMITATIONS
DURING BOTH CLOCK-PHASES

$$v_{o,n} \approx v_{o,n-1} - \frac{C_1}{C_o}(V_{12} - V_{11}) - \dots - \frac{C_i}{C_o}(V_{i2} - V_{i1}) + \\ + \Theta(\tau_i) + \Theta(\tau_s)$$


Traditionally not taken into account

   

DT-ΣΔMs: Integrator incomplete settling



Effect of the amplifier GB:

 


→ If only amplifier GB is considered
(assuming no SR limitation)

$$GB_i = \frac{g_m}{C_{eq,i}}$$

$$GB_s = \frac{g_m}{C_{eq,s}}$$

$$v_o(z) = \frac{C_S}{C_I} (1 - \varepsilon_{st}) \frac{z^{-1} v_m(z) - z^{-1/2} v_{fb}(z)}{1 - z^{-1}}$$
 
$$\varepsilon_{st} \sim \theta_i \left[\exp\left(-GB_i \frac{T_s}{2}\right) \right] + \theta_s \left[\exp\left(-GB_s \frac{T_s}{2}\right) \right] + \theta_i \cdot \theta_s$$




- Can be viewed as a **systematic error in the integrator weight**
- Effect on ΣΔMs similar to a mismatch between analog and digital coeffs
- It causes low-order **noise leakages** in cascade ΣΔMs

DT- $\Sigma\Delta$ M_s: Integrator incomplete settling

- Additional effect of the amplifier SR (+ GB):

 - "Dominant" linear dynamics are not mandatory in order to fulfill specs
- SR can be traded for GB
- It can be used to optimize the power consumption of amplifiers





Non-linear dynamics cause distortion!
SR at the front-end integ must be carefully tackled

DT-ΣΔMs: Integrator incomplete settling



  - Additional effect of the switches Ron (+ GB + SR):



→ Input is sampled with an error

$$① \quad \epsilon_{on,s} = \exp\left(-\frac{1}{2R_{on}C_S}\frac{T_s}{2}\right)$$

→ Linear dynamics are slowed down

$$② \quad GB_{i,on} = \frac{GB_i}{1 + GB_i \cdot 2R_{on}C_S}$$

$$③ \quad GB_{s,on} = \frac{GB_s}{1 + GB_s \cdot 2R_{on}C_{ns}}$$




→ Slew time shortens

DT-ΣΔMs: Circuit noise



Main noise sources in SC integrators:

   - Switches → Thermal noise
- Amplifiers → Thermal and flicker noise
- References → Thermal and flicker noise



■ Noise contribution of the switches (input-referred):

Switches for sampling


$$S_S = 2kT \cdot 2R_{on}$$

$$H_{S\phi_1}(s) = \frac{1}{1 + s \cdot 2R_{on}C_S}$$

$$BW_{n, S\phi_1} = \int_0^{+\infty} |H_{S\phi_1}(f)|^2 df = \frac{1}{4 \cdot 2R_{on}C_S}$$

$$S_{in, S\phi_1}(f) \cong \frac{2BW_{n, S\phi_1}}{f_s} \cdot S_S \cong \frac{kT}{C_S f_s}$$

← Aliased component [Fisc82]

 


DT-ΣΔMs: Circuit noise




Main noise sources in SC integrators:

- Switches → Thermal noise
- Amplifiers → Thermal and flicker noise
- References → Thermal and flicker noise

Sampling:

 

Integration:

 

■ Noise contribution of the switches (input-referred):

Switches for sampling

$$S_S = 2kT \cdot 2R_{on}$$

$$H_{S\phi_1}(s) = \frac{1}{1 + s \cdot 2R_{on}C_S}$$

$$BW_{n, S\phi_1} = \int_0^{+\infty} |H_{S\phi_1}(f)|^2 df = \frac{1}{4 \cdot 2R_{on}C_S}$$

$$S_{in, S\phi_1}(f) \approx \frac{2BW_{n, S\phi_1}}{f_s} \cdot S_S \approx \frac{kT}{C_S f_s}$$

Switches for integration

$$H_{S\phi_2}(s) = \frac{1 + s/z_1}{(1 + s/p_1)(1 + s/p_2)} \quad z_1 = \frac{g_m}{C} \quad p_1 \equiv \frac{g_m}{C_{eq, i}} \quad p_2 \equiv \frac{C_{eq, i}}{C} \cdot \frac{1}{2R_{on}C_S}$$


$$BW_{n, S\phi_2} = \int_0^{+\infty} |H_{S\phi_2}(f)|^2 df \approx \frac{p_2}{4} \approx \frac{1}{4 \cdot 2R_{on}C_S}$$

$$S_{in, S\phi_2}(f) \approx \frac{2BW_{n, S\phi_2}}{f_s} \cdot S_S \approx \frac{kT}{C_S f_s}$$

DT-ΣΔMs: Circuit noise



 - Noise contribution of the amplifier (input-referred):




Thermal component

$$H_{op}(s) = \frac{1}{(1+s/p_1)(1+s/p_2)} \quad p_1 \equiv \frac{g_m}{C_{eq,i}} \quad p_2 \equiv \frac{C_{eq,i}}{C} \cdot \frac{1}{2R_{on}C_S}$$

$$BW_{n, op} = \int_0^{+\infty} |H_{op}(f)|^2 df \approx \frac{p_1}{4} \approx \frac{g_m}{4C_{eq,i}}$$

$$S_{in, op}^t(f) \approx \frac{2BW_{n, op}}{f_s} \cdot S_{op}^t \approx \frac{GB_i}{2f_s} \cdot S_{op}^t$$

← Aliased component

 

Flicker component

- Low-pass filtered version at the integ input:
$$S_{op}^f(f) |H_{op}(f)|^2 \approx S_{op}^t f_{cr, op} / |f|$$
- Folded tails are “submerged” into the aliased thermal noise

$$S_{in, op}^f(f) \approx S_{op}^t \frac{f_{cr, op}}{|f|}$$

Similar treatment for the references

Total noise PSD for the front-end integ:

$$S_{eq, in}(f) \approx \underbrace{\frac{2kT}{C_S f_s}}_{\text{switches}} + S_{op}^t \left(\frac{GB_i}{2f_s} + \frac{f_{cr, op}}{|f|} \right) + S_{ref}^t \left(\frac{GB_{ref}}{2f_s} + \frac{f_{cr, ref}}{|f|} \right)$$

Switches:

- kT/C is the ultimate limitation on the converter resolution
- It can only be decreased by increasing C_s and/or f_s (it does not depend on R_{on} !)
- $\times 2$ in fully-diff implementations (3-dB increase, but signal power is 6dB larger!)


Amplifiers & References:

- GBs should be as low as settling errors allow (reduces folding!)
- $1/f$ contributions decrease with the corner frequency
- Adequate techniques can be applied in low-freq apps: CDS, chopper, ... [Enz96]

$$P_{CN, in} \approx \left[\frac{2kT}{C_S} + S_{op}^t \frac{GB_i}{2} + S_{ref}^t \frac{GB_{ref}}{2} \right] \frac{1}{OSR} + 2 \ln\left(\frac{f_b}{f_o}\right) (S_{op}^t f_{cr, op} + S_{ref}^t f_{cr, ref})$$

In-band error power due to circuit noise in the ΣΔM

 
Effect of noise leakages and thermal noise on a 2-1 cascade



DT- $\Sigma\Delta$ M: Circuit noise



 Effect of 1/f and thermal noise on the spectra of a 4th-order $\Sigma\Delta$ M
(silicon results for several fs)




Be careful with Flicker models for transistors!
Front-end amplifier needed redesign!


DT-ΣΔMs: Clock jitter



- Sampling time uncertainty [Boser88]:

 



→ If jitter is modeled as random:

 

$$S_J = \frac{A_x^2 (2\pi f_x \sigma_J)^2}{2 f_s}$$

$$P_J = \frac{A_x^2 (2\pi f_x \sigma_J)^2}{2 OSR}$$

  Error is larger, the larger input freq (wideband apps!)




DT-ΣΔMs: Non-linearity of capacitors



- In an ideal capacitor: $dq = Cdv$
- In practice: $dq = C(v)dv$, with C being voltage-dependent
 
$$C(v) = C(1 + a_1 v + a_2 v^2 + \dots)$$




- Considering the effect of the sampling cap only [Bran97]:

$$v_{o,n} \approx v_{o,n-1} + g_1 v_{in,n-1} \left(1 + \frac{a_1}{2} v_{in,n-1} + \frac{a_2}{3} v_{in,n-1}^2 \right)$$

$$A_2 \approx \frac{1}{2} \left(\frac{a_1}{2} A_x^2 \right) \Rightarrow HD_2 \approx 20 \log_{10} \left(\frac{a_1}{4} A_x \right)$$

$$A_3 \approx \frac{1}{4} \left(\frac{a_2}{3} A_x^3 \right) \Rightarrow HD_3 \approx 20 \log_{10} \left(\frac{a_2}{12} A_x^2 \right)$$
 
$$a_1 = 500 \text{ppm/V}, a_2 = 500 \text{ppm/V}^2$$





- Even-order distortion cancels w/ fully-diff
- Non-linearity of sampling cap dominates
- Valid for weak non-linearities (MOS caps are very non-linear!)


DT- $\Sigma\Delta$ M: Non-linear Amplifier Gain



  → Actual amplifier gain depends on output voltage:


 
$$A_{DC} = 500, \gamma_1 = 10\%/\text{V} \text{ (single-ended } \Sigma\Delta\text{M)}$$



$$A_{DC}(v_o) = A_{DC}(1 + \gamma_1 v_o + \gamma_2 v_o^2 + \dots)$$

$$HD_2 \cong 20 \log_{10} \left(\frac{\gamma_1 (1+g)}{2} g A_x \right)$$





$$HD_3 \cong 20 \log_{10} \left(\frac{\gamma_2 (1+g)}{4} g^2 A_x^2 \right) \quad [\text{Yin94}]$$

- Increasing A_{DC} helps a lot!
- A_{DC} at the front-end larger than noise leakages require

DT- $\Sigma\Delta$ Ms: Non-linear settling



    - SR can trade for GB in the integrator settling, but non-linear dynamics cause distortion:





SR at the front-end larger than settling requires

DT-ΣΔMs: Non-linear switch resistance



  - Switches exhibit a finite R_{ON} which is also non-linear:




$$R_{ON,n} = \frac{1}{k'_n \left(\frac{W}{L} \right)_n (V_{DD} - v_I - V_{Tn})}$$


$$R_{ON,p} = \frac{1}{k'_p \left(\frac{W}{L} \right)_p (v_I - |V_{Tp}|)}$$

$$R_{ON,eq} = R_{ON,n} // R_{ON,p}$$

■ Non-linear sampling [Geer02]:

 

 - Distortion is dynamic (increases with input freq!)
- Front-end switch dominates
- R_{ON} at the front-end smaller than settling requires
- Very important in low-voltage!




Most suited sizing depends on parasitics, Vref/Vsupply, ...


DT- $\Sigma\Delta$ Ms: Comparators and multi-bit quantizers



■ Single-bit $\Sigma\Delta$ Ms:

 

Comparator:

 


1-bit DAC \rightarrow Inherently linear

- ◆ **Offset** \rightarrow Attenuated by the integrator DC gain
- ◆ **Hysteresis** \rightarrow Shaped similarly to quantization error [Boser88]

$$P_h = 4h^2 \frac{\pi^{2L}}{(2L+1)OSR^{2L+1}}$$

■ Multi-bit $\Sigma\Delta$ Ms:

 


Multi-bit ADC \rightarrow Errors attenuated/shaped

Multi-bit DAC \rightarrow Non-linearity directly added to the input!

$$[\text{Mede99}]: \sigma_D^2 = \frac{1}{2} \left(\frac{\Delta}{2^B - 1} \right)^2 \text{INL}_{\text{LSB}}^2$$

 Effect of DAC errors on a 2nd-order 3-bit $\Sigma\Delta$ M




DEM techniques
Dual quantization

A 2.5-V Cascade SDM in CMOS 0.25μm for ADSL/ADSL+

2-1-1 w/ dual quantization

- Two different amplifiers: 2-stage OA in the 1st stage, and 1-stage OA in 2nd and 3rd stages.
- Standard CMOS switches (no clock-boosting).
- Only 2-branch integrators and 2x16 unit capacitors (MiM).
- Comparators: regenerative latch + preamplification stage.
- 3-bit quantizer in the last stage:
 - ◆ Resistive-ladder DAC (no calibration).
 - ◆ Flash ADC: Static differential input stage + latched comparators.
- Power-down control.

 

DT-ΣΔMs: Case study - Blocks Specs



Blocks Specs

EQUATION DATABASE

	Typical	Worst Case
Quantization noise	-88.1dB	-86.2dB
Ideal Corner analysis:	-90.3dB	
DC gain leakage	Fast and slow devices models	
Cap. mismatch leakage	Temperature range: [-40°C, +110°C] ($\sigma_C = 0.05\% \text{ to } 0.1\%$)	-95.4dB -89.4dB
DAC error	-96.4dB	
Thermal noise	-84.8dB	-82.2dB
kT/C noise	-88.1dB	-86.0dB
Amplifier noise	-87.5dB	-84.5dB
Clock jitter	-90.1dB	
In-band error power	-82.3dB	-80.3dB
Dynamic range	82.8dB (13.5bit)	80.8dB (13.1bit)

MODULATOR	Topology	2-1-1(3b)
	Oversampling ratio	16
	Reference voltage	1.5V
	Clock frequency	70.4MHz
	Clock jitter	15ps (0.1%)
FRONT-END INTEGRATOR	Sampling capacitor	0.66pF
	Cap. sigma (MiM, 1pF)	0.05%
	Cap. tolerance	±20%
	Bottom parasitic cap.	1%
	Switch on-resistance	150Ω
AMPLIFIER	DC gain	3000 (70dB)
	GB (1.5pF)	265MHz
	Slew rate (1.5pF)	800V/μs
	Output swing	±1.8V
	Input equivalent noise	6nV/sqrt(Hz)
COMPARATORS	Hysteresis	20mV
	Offset	±10mV
	Resolution time	3ns
3-bit QUANTIZER	DAC /NL	0.5%FS

DT- $\Sigma\Delta$ Ms: Case study



$$P_{CN} = P_{kT/C} + P_{op} = \frac{4kT}{C_S} \cdot \frac{1}{OSR} + \frac{2\pi \cdot GB_{eff} S'_{op}}{2OSR}$$

$$GB_{eff} \cong \frac{GB}{1 + GB/f_{on}} = \frac{GB}{1 + GB \cdot 2\pi \cdot 2R_{on}C_S}$$

	Typical	Worst Case
Quantization noise	-88.1dB	-86.2dB
Ideal	-90.3dB	
DC gain leakage	-99.8dB	
Cap. mismatch leakage ($\sigma_C = 0.05\% \mid 0.1\%$)	-95.4dB	-89.4dB
DAC error	-96.4dB	
Thermal noise	-84.8dB	-82.2dB
kT/C noise	-88.1dB	-86.0dB
Amplifier noise	-87.5dB	-84.5dB
Clock jitter	-90.1dB	
In-band error power	-82.3dB	-80.3dB
Dynamic range	82.8dB (13.5bit)	80.8dB (13.1bit)

MODULATOR	Topology	2-1-1(3b)
	Oversampling ratio	16
	Reference voltage	1.5V
	Clock frequency	70.4MHz
	Clock jitter	15ps (0.1%)
FRONT-END INTEGRATOR	Sampling capacitor	0.66pF
	Cap. sigma (MiM, 1pF)	0.05%
	Cap. tolerance	±20%
	Bottom parasitic cap.	1%
	Switch on-resistance	150Ω
AMPLIFIER	DC gain	3000 (70dB)
	GB (1.5pF)	265MHz
	Slew rate (1.5pF)	800V/μs
	Output swing	±1.8V
	Input equivalent noise	6nV/sqrt(Hz)
COMPARATORS	Hysteresis	20mV
	Offset	±10mV
	Resolution time	3ns
3-bit QUANTIZER	DAC /NL	0.5%FS

DT-ΣΔMs: Case study - Integrator Dynamics



Integrator Dynamics

- $GB > 2.5f_s$ is ideally enough to limit settling errors (this architecture w/ $OSR = 16$).
 - Switch on-resistance slows down the effective amplifier response:

$$GB_{eff} \cong \frac{GB}{1 + GB/f_{on}} = \frac{GB}{1 + GB \cdot 2\pi \cdot 2R_{on}C_S}$$


$R_{on} \sim 150\Omega$ requires just $GB > 3.2f_s$

Standard switches (no clock-boosting)

GB = 265MHz

(no clock-boosting) (assuming that 85% of
the clock cycle is useful)

 - Slew rate must be large enough to let the linear dynamic to correctly settle.
$$SR/(V_{ref} \cdot f_s) = 6.5 \rightarrow SR = 800V/\mu s$$
 - Partially slew-rate limited operation of the front-end integrator introduces distortion.



DT- $\Sigma\Delta$ M_s: Case study - Amplifiers



	INTEG G1	INTEG. 2	INTEG. 3	INTEG. 4
Unit capacitor	0.66pF	0.45pF	0.45pF	
DC gain		3000 (70dB)	600 (56dB)	
GB (1.5pF)		265MHz	210MHz	
Slew rate (1.5pF)		800V/ μ s	350V/ μ s	
Output swing		$\pm 1.80V$	$\pm 1.60V$	
Input equivalent noise	6nV/sqrt(Hz)		50nV/sqrt(Hz)	

↓ ↓

OPA

OPB


- SC CMFB nets
- pMOS input scheme
 - Cancelled body effect
(substrate noise coupling)
 - Smaller 1/f noise

DT- $\Sigma\Delta$ Ms: Case study - Amplifiers



	INTEG. 1	INTEG. 2	INTEG. 3	INTEG. 4
Unit capacitor	0.66pF	0.45pF	0.45pF	
DC gain		3000 (70dB)	600 (56dB)	
GB (1.5pF)		265MHz	210MHz	
Slew rate (1.5pF)		800V/ μ s	350V/ μ s	
Output swing		$\pm 1.80V$	$\pm 1.60V$	
Input equivalent noise	6nV/sqrt(Hz)		50nV/sqrt(Hz)	

- SC CMFB nets
- pMOS input scheme
- Cancelled body effect
(substrate noise coupling)
- Smaller 1/f noise

 

OPA 2-stage amplifier

Telescopic 1st stage
2-path compensation

Typical	Worst Case
DC gain	78.6dB
GB (1.5pF)	446.8MHz
PM (1.5pF)	64.0°
SR (1.5pF)	1059V/ μ s
Output swing	$\pm 2.09V$
Input eq. noise	5.1nV/sqrt(Hz)
Input capacitance	126fF
Power consumption	17.2mW
	5.5nV/sqrt(Hz)
	129fF
	19.4mW

DT- $\Sigma\Delta$ M_s: Case study - Amplifiers




	INTEG. 1	INTEG. 2	INTEG. 3	INTEG. 4
Unit capacitor	0.66pF	0.45pF	0.45pF	
DC gain	3000 (70dB)		600 (56dB)	
GB (1.5pF)	265MHz		210MHz	
Slew rate (1.5pF)	800V/ μ s		350V/ μ s	
Output swing	\pm 1.80V		\pm 1.60V	
Input equivalent noise	6nV/sqrt(Hz)		50nV/sqrt(Hz)	

- SC CMFB nets
- pMOS input scheme
- Cancelled body effect
(substrate noise coupling)
- Smaller 1/f noise

OPB folded-cascode amplifier

	Typical	Worst Case
DC gain	58.0dB	56.8dB
GB (1.5pF)	393.5MHz	331.7MHz
PM (1.5pF)	70.3°	67.7°
SR (1.5pF)	377V/ μ s	373V/ μ s
Output swing	\pm 1.97V	\pm 1.72V
Input eq. noise	4.1nV/sqrt(Hz)	5.1nV/sqrt(Hz)
Input capacitance	300fF	343fF
Power consumption	6.6mW	6.9mW


 


DT- $\Sigma\Delta$ M_s: Case study - Switch ON-Resistance



- Slow-down of the integrators dynamics
 - Incomplete sampling (RC time constant)
 - Dynamic distortion (front-end integrator)
- $R_{on} \sim 150\Omega$

Standard CMOS switches

  

DT- $\Sigma\Delta$ M_s: Case study - Switch ON-Resistance




Dynamic distortion

evaluated through
electrical simulation


- Sinewave input

THD < -96dB

 

- DMT input

MTPR < -81dB

 


DT- $\Sigma\Delta$ M_s: Case study - MiM Capacitors



CMOS tech with
mixed-signal facilities

Thin oxide between
metal 4 and metal 5

 

Cap. matching	0.05% (1pF)
Bottom plate parasitic	1%
Cap. spread	$\pm 20\%$


- Very good matching (0.1% assumed for 6- σ design)
- Helps to limit the capacitive load to integrators

→ Integrators weights:

- Front-end integ, 0.66pF: 27 μ m x 27 μ m
- Remaining integs, 0.45pF: 22 μ m x 22 μ m

→ Also MiM caps in OPA, in the SC CMFB nets, and in the anti-aliasing filter

 DT- $\Sigma\Delta$ M: Case study - Quantizers



Comparator

Pre-amp + Regenerative latch + SR latch

(Different supplies)

Hysteresis	127.5 μ V	Offset	6.3mV
Resolution time, LH	3.9ns	Resolution time, HL	2.8ns
Input capacitance	100fF	Power consumption	0.3mW


3-bit Quantizer

Resistive-ladder DAC

- 700- Ω ladder between references +2V/+0.5V (14x50 Ω , 3.21mW)
- Unsalicided $n+$ poly used in resistors
- References obtained from the on-chip analog supply

Flash ADC

 - Static input scheme (no caps)
 - ◆ Reduces capacitive load to 4th integrator
 - ◆ Saves silicon area
- Extra differential pair in comparators




DT- $\Sigma\Delta$ M: Case study - Layout & Prototyping



CMOS 0.25μm

2.78mm² w/o pads

44-pin plastic QFP



 


4-layer PCB



- Dedicated analog, mixed, and digital supplies
- Guard rings with dedicated pad/pin
- Increased distance among analog and digital blocks
- Layout symmetry and common-centroid techniques
- Shielded bus for distributing the clock signals
- Extensive on-chip decoupling
- Pad ring divided blocking cells
- Multiple bonding techniques

   DT- $\Sigma\Delta$ M's: Case study - Experimental results



Part of a commercial modem



In mass production
(STMicroelectronics)

DT- $\Sigma\Delta$ Ms: References



- [Boser88] B.E. Boser and B.A. Wooley, "The Design of Sigma-Delta Modulation Analog-to-Digital Converters". *IEEE Journal of Solid-State Circuits*, vol. 23, pp. 1298-1308, December 1988.
- [Bran97] B. Brandt, P.F. Ferguson, and M. Rebeschini, "Analog Circuit Design of $\Sigma\Delta$ ADCs", Chapter 11 in *Delta-Sigma Data Converters: Theory, Design and Simulation* (S.R. Norsworthy, R. Schreier, and G.C. Temes, Editors). IEEE Press, 1997.
- [Enz96] C.C. Enz and G.C. Temes, "Circuit Techniques for Reducing the Effects of Op-Amp Imperfections: Autozeroing, Correlated Double Sampling, and Chopper Stabilization". *Proceedings of the IEEE*, vol. 84, no. 11, pp. 1584-1614, November 1996.
- [Fisc82] J.H. Fischer, "Noise Sources and Calculation Techniques for Switched Capacitor Filters". *IEEE Journal of Solid-State Circuits*, vol. 17, no. 4, pp. 742-752, August 1982.
- [Geer02] Y. Geerts, M. Steyaert, and W. Sansen, *Design of Multi-Bit Delta-Sigma A/D Converters*. Kluwer Academic Publishers, 2002.
- [Mede99] F. Medeiro, B. Pérez-Verdú, and A. Rodríguez-Vázquez, *Top-Down Design of High-Performance Modulators*. Kluwer Academic Publishers, 1999.
- [Rio00] R. del Río, F. Medeiro, B. Pérez-Verdú, and A. Rodríguez-Vázquez, "Reliable Analysis of Settling Errors in SC Integrators: Application to $\Sigma\Delta$ Modulators". *IEE Electronics Letters*, vol. 36, no. 6, pp. 503-504, March 2000.
- [Yin94] G. Yin and W. Sansen, "A High-Frequency and High-Resolution Fourth-Order $\Sigma\Delta$ A/D Converter in BiCMOS Technology". *IEEE Journal of Solid-State Circuits*, vol. 29, pp. 857-865, August 1994.

More details on errors and case study ...

- [Rio06] R. del Río, F. Medeiro, B. Pérez-Verdú, J.M. de la Rosa, and A. Rodríguez-Vázquez, *CMOS Cascade Sigma-Delta Modulators for Sensors and Telecom: Error Analysis and Practical Design*. Springer, 2006.