

June 5, 2012



Variation-Tolerant Design of Analog CMOS Circuits – Lecture 1

Marvin Onabajo

Assistant Professor

**Dept. of Electrical & Computer Eng.
Northeastern University, Boston, USA**

monabajo@ece.neu.edu

<http://www.ece.neu.edu/~monabajo>

Short Course held at:



**Universitat Politècnica de Catalunya
Barcelona, Spain**


Outline – Lecture 1

- Introduction
 - Course overview
 - Greetings from Northeastern University
- CMOS process variation
 - Trends
 - Impacts
- System-level calibration trends
 - Systems-on-a-chip examples (receivers, transceivers)
- Production test simplification and cost reduction
 - Example: loopback testing
- Built-in testing of analog circuits
 - Introduction
 - On-chip power detection
 - RF LNA built-in testing example

Course Overview

- Lecture 1 – June 5, 2012
 - CMOS process variation challenges
 - System-level calibration trends (transceiver systems-on-a-chip examples)
 - Production test simplification and cost reduction (example: loopback testing)
 - Built-in testing of analog circuits
- Lecture 2 – June 6, 2012
 - Digitally-assisted analog circuit design and performance tuning
 - Case study: digitally-assisted linearization of operational transconductance amplifiers
 - Case study: variation-aware continuous-time $\Delta\Sigma$ analog-to-digital converter design
- Lecture 3 – June 7, 2012
 - On-chip DC and RF power measurements with differential temperature sensors
 - Case study: differential temperature sensor design
 - Temperature sensors as variation monitors
 - Mismatch reduction for transistors in high-frequency differential analog signal paths
 - Example: mixer design with analog tuning for transistors biased in weak inversion

Reference Book

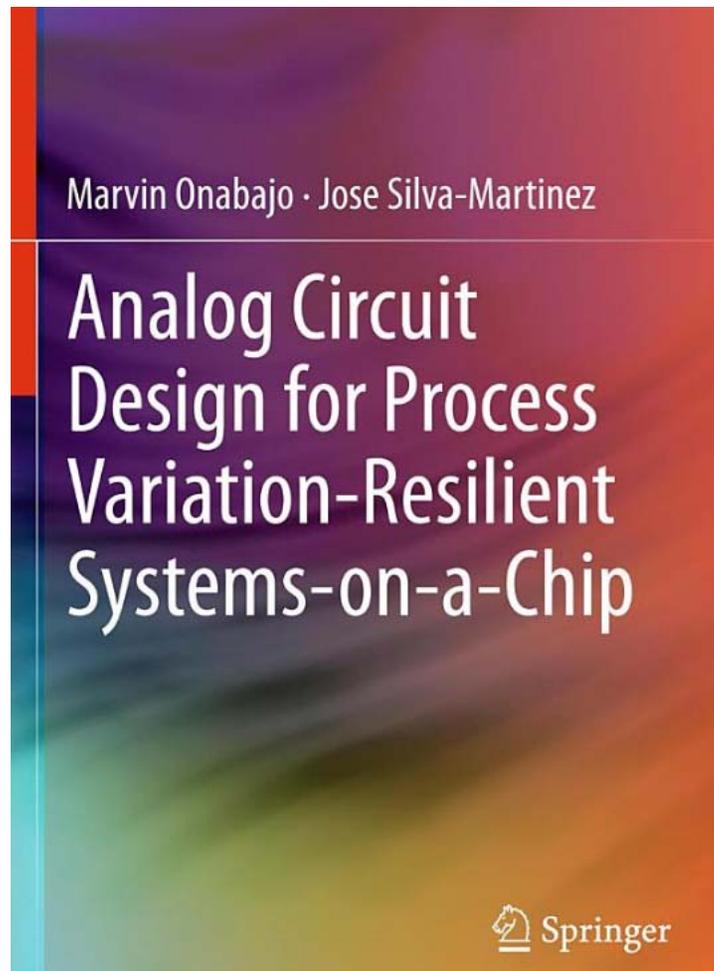

- M. Onabajo and J. Silva-Martinez, Analog Circuit Design for Process Variation-Resilient Systems-on-a-Chip, Springer (**ISBN: 978-1-4614-2295-2**).
- Includes descriptions of many concepts and projects discussed in this course

Greetings from Northeastern University




- Location: Boston, Massachusetts, USA
- Web: www.northeastern.edu
- Student population
 - Undergraduate: ~16,000
 - Graduate: ~5000
 - International: 15% (125 countries)
- Colleges and schools
 - College of Arts, Media, and Design
 - College of Business Administration
 - **College of Computer and Information Science!!!**
 - **College of Engineering!!!**
 - Bouvé College of Health Sciences
 - College of Professional Studies
 - College of Science
 - College of Social Sciences and Humanities
 - School of Law

Electrical & Computer Eng. Graduate Program

- Programs Offered (full time & part time):
 - M.S. in ECE
 - Ph.D. in EE and CE
- Faculty:
 - 48 regular faculty members
 - 11 IEEE Fellows (including 2 Life Fellows)
 - 1 member of NAE
 - 7 recipients of NSF/CAREER awards
 - 1 recipient of Presidential Early Career Award for Scientists and Engineers
- Looking for motivated, hard-working, and well-prepared graduate students → www.ece.neu.edu

Concentrations and Research Programs

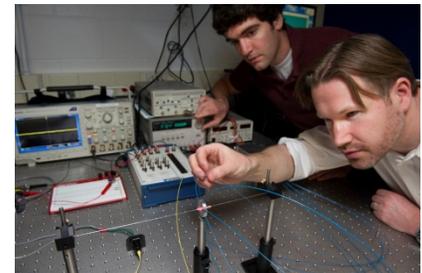- Communication and Signal Processing
- Computer Engineering
- Control and Signal Processing
- Electromagnetics, Plasma, and Optics
- Electronic Circuits, Semiconductor Devices, and Micro-fabrication
- Power Systems, Power Electronics, and Motion Control



Research Centers and Institutes

- Bernard M. Gordon Center for Subsurface Sensing & Imaging Systems (CenSSIS)
- Center for Awareness and Localization of Explosive-Related Threats (ALERT)
- Center for Communication and Digital Signal Processing (CDSP)
- Northeastern University Center for Electrical Energy Research (NUCEER)
- Center for High-Rate Nanomanufacturing (CHN)
- Center for Microwave Magnetic Materials and Integrated Circuits (CM³IC)
- Institute for Information Assurance (IIA)
- Institute for Complex Scientific Software (ICSS)
- Center for Ultra-wide-area Resilient Electric Energy Transmission Network (CURENT)

Outline – Lecture 1

- Introduction
 - Course overview
 - Greetings from Northeastern University
- CMOS process variation
 - Trends
 - Impacts
- System-level calibration trends
 - Systems-on-a-chip examples (receivers, transceivers)
- Production test simplification and cost reduction
 - Example: loopback testing
- Built-in testing of analog circuits
 - Introduction
 - On-chip power detection
 - RF LNA built-in testing example

Wireless Product Trends

- Support of multiple communication standards and more features
- Increasing circuit integration and system complexity per chip
- Technology optimizations for digital circuits
 - Create analog design challenges
- Increasing process-voltage-temperature (PVT) variations
 - Lower manufacturing yield and reduced reliability




Design Objectives

- Development of analog & mixed-signal circuits with extra features for integration into reliable single-chip systems
 - Digitally assisted analog design
 - On-chip calibration to improve performance and yield
- New built-in test capabilities with on-chip measurement circuits
- “Self-healing” integrated systems
 - On-chip adjustment of parameters to maintain high performance despite of environmental changes and aging effects
 - For future medical and military devices that require high reliability

The Single-Chip Transceiver as Paradigm

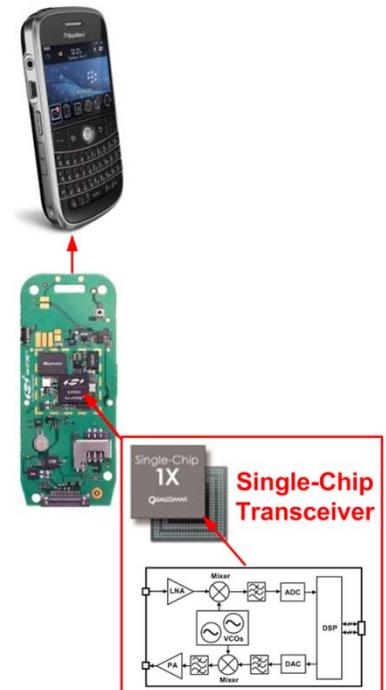- “Digital intensive” System-on-Chip (SoC)
 - Shrinking of transistor dimensions in complementary metal-oxide-semiconductor (CMOS) technologies
 - Process variations and interferences have more impact on analog circuits
 - Reduced access to internal blocks for testing
 - Increased test cost




Process Variation Problems

Example: Intra-die threshold voltage variability vs. technology node

CMOS Techn.	250nm	180nm	130nm	90nm	65nm	45nm
$\sigma\{V_{th}\} / V_{th}$	4.7%	5.8%	8.2%	9.3%	10.7%	16%

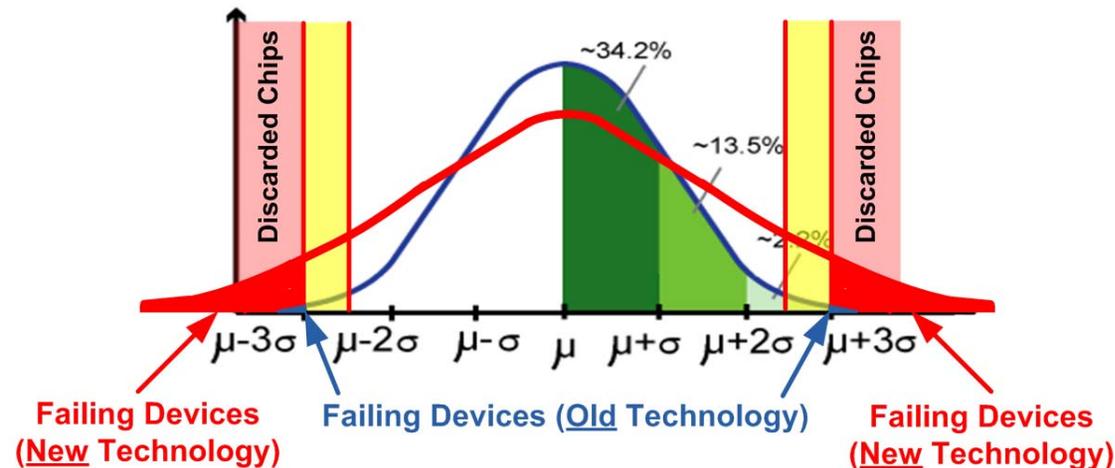
- Defect densities are higher in newer technologies → lower yield
- Increased intra-die variability from device scaling & dopant fluctuations
 - Yield impact on analog specifications:



M. Onabajo, D. Gómez, E. Aldrete-Vidrio, J. Altet, D. Mateo, and J. Silva-Martinez, "Survey of robustness enhancement techniques for wireless systems-on-a-chip and study of temperature as observable for process variations," *Springer J. Electronic Testing: Theory and Applications*, vol. 27, no. 3, pp. 225-240, June 2011.

Variation-Aware Design Approaches



- Based on device corner models
 - Allows for analog parameter variations
 - Leads to overdesign [1]
- Statistical design
 - Yield estimation based on Monte Carlo simulations
 - Long simulation times
- Less reliance on device matching
 - Random dopant fluctuations cause threshold voltage mismatch in neighboring devices, especially below the 65nm node [2]
 - On-chip variation sensing becomes more important

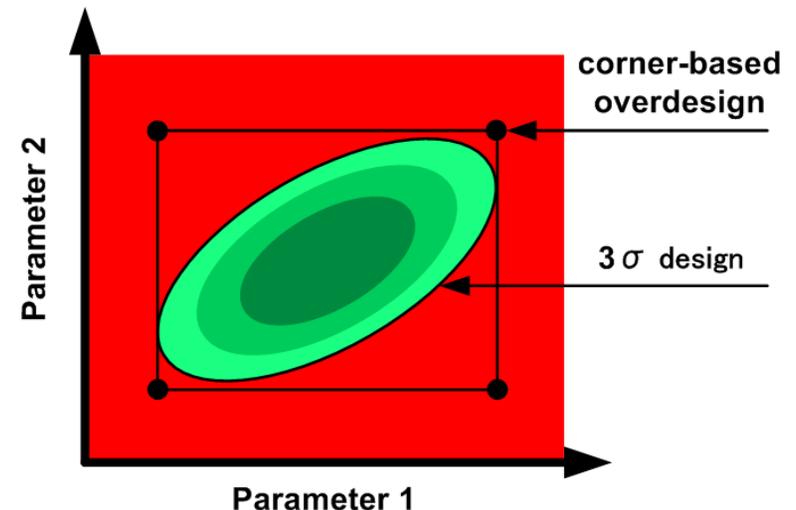

- [1] G. G. E. Gielen, "Design methodologies and tools for circuit design in CMOS nanometer technologies," in *Proc. 36th European Solid-State Device Research Conference (ESSDERC)*, pp. 21-32, Sept. 2006.
- [2] K. Agarwal, J. Hayes, and S. Nassif, "Fast characterization of threshold voltage fluctuation in MOS devices," *IEEE Trans. Semiconductor Manufacturing*, vol. 21, no. 4, pp. 526-533, Nov. 2008.

Larger SoC Sizes → Lower Yields

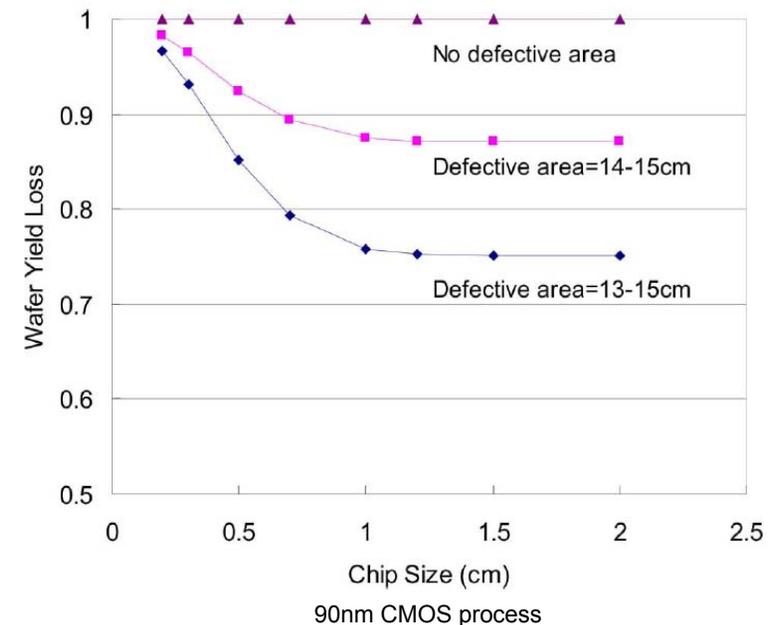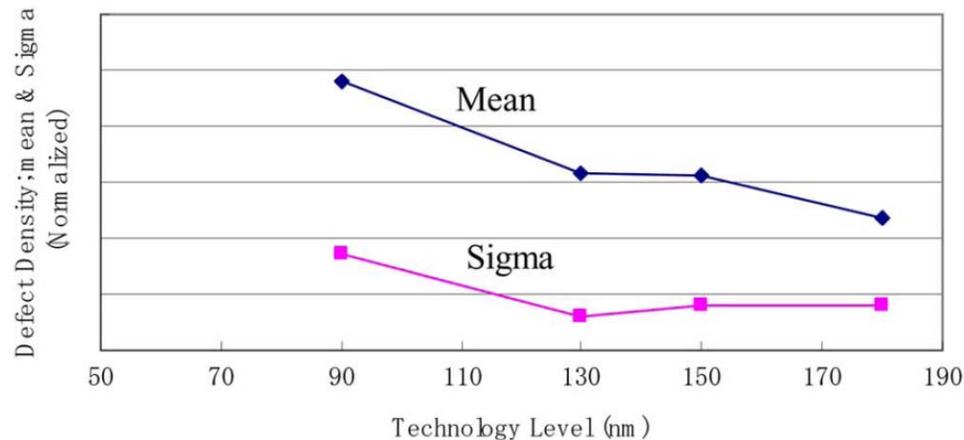- Yields decrease as SoC integration levels increase
- Defect densities become worse with technology nodes and larger chip sizes:





Figures from:

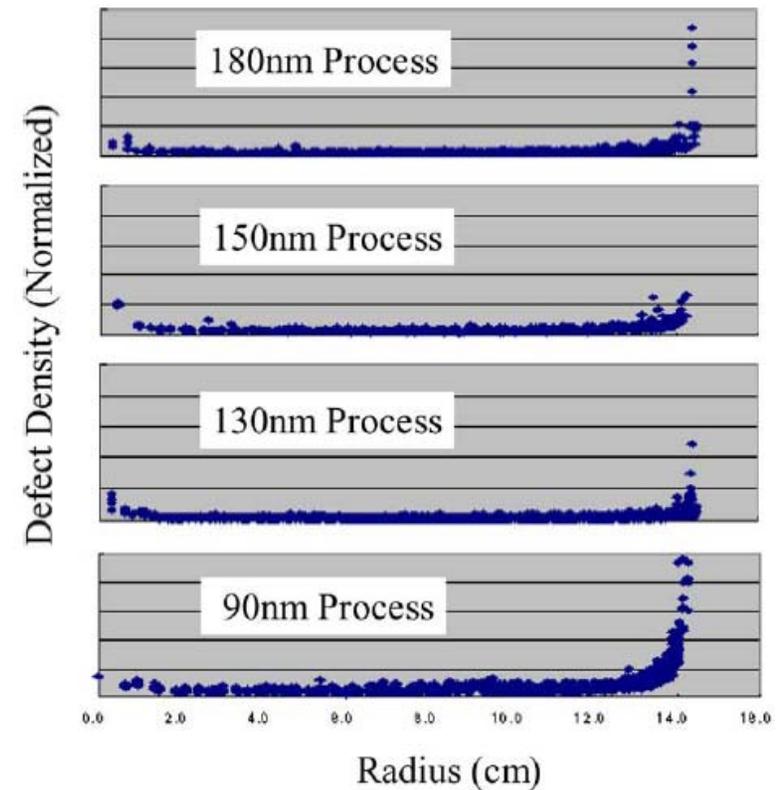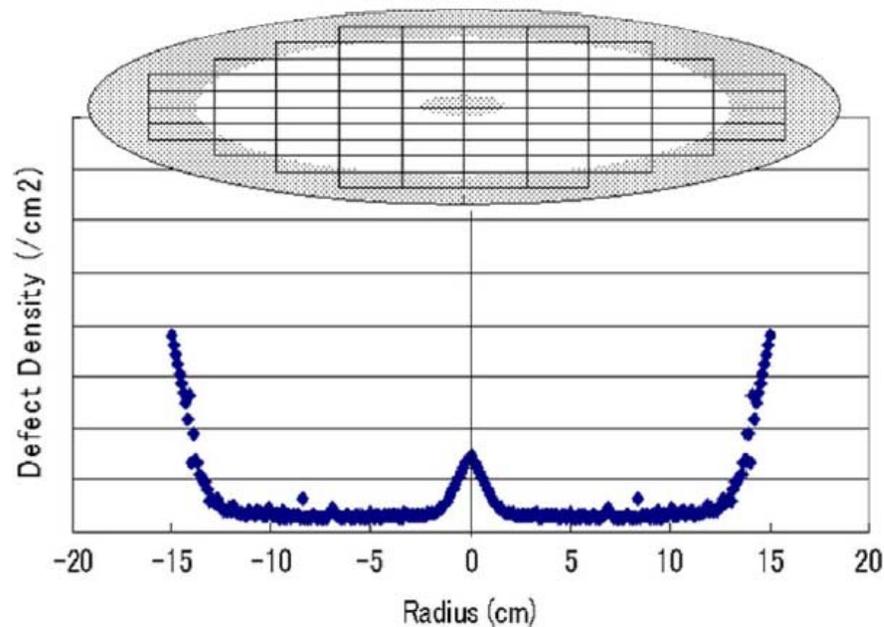H. Masuda, M. Tsunozaki, T. Tsutsui, H. Nunogami, A. Uchida, and K. Tsunokuni, "A Novel Wafer-Yield PDF Model and Verification With 90-180nm SOC Chips," *IEEE Trans. Semiconductor Manuf.*, vol. 21, no. 4, pp. 585-591, Nov. 2008.

Larger SoC Sizes → Lower Yields

- Manufacturing defects are more concentrated at the wafer edge




Figures from:

H. Masuda, M. Tsunozaki, T. Tsutsui, H. Nunogami, A. Uchida, and K. Tsunokuni, "A Novel Wafer-Yield PDF Model and Verification With 90-180nm SOC Chips," *IEEE Trans. Semiconductor Manuf.*, vol. 21, no. 4, pp. 585-591, Nov. 2008.

Outline – Lecture 1

- Introduction
 - Course overview
 - Greetings from Northeastern University
- CMOS process variation
 - Trends
 - Impacts
- **System-level calibration trends**
 - **Systems-on-a-chip examples (receivers, transceivers)**
- Production test simplification and cost reduction
 - Example: loopback testing
- Built-in testing of analog circuits
 - Introduction
 - On-chip power detection
 - RF LNA built-in testing example

Image-Rejection Receivers

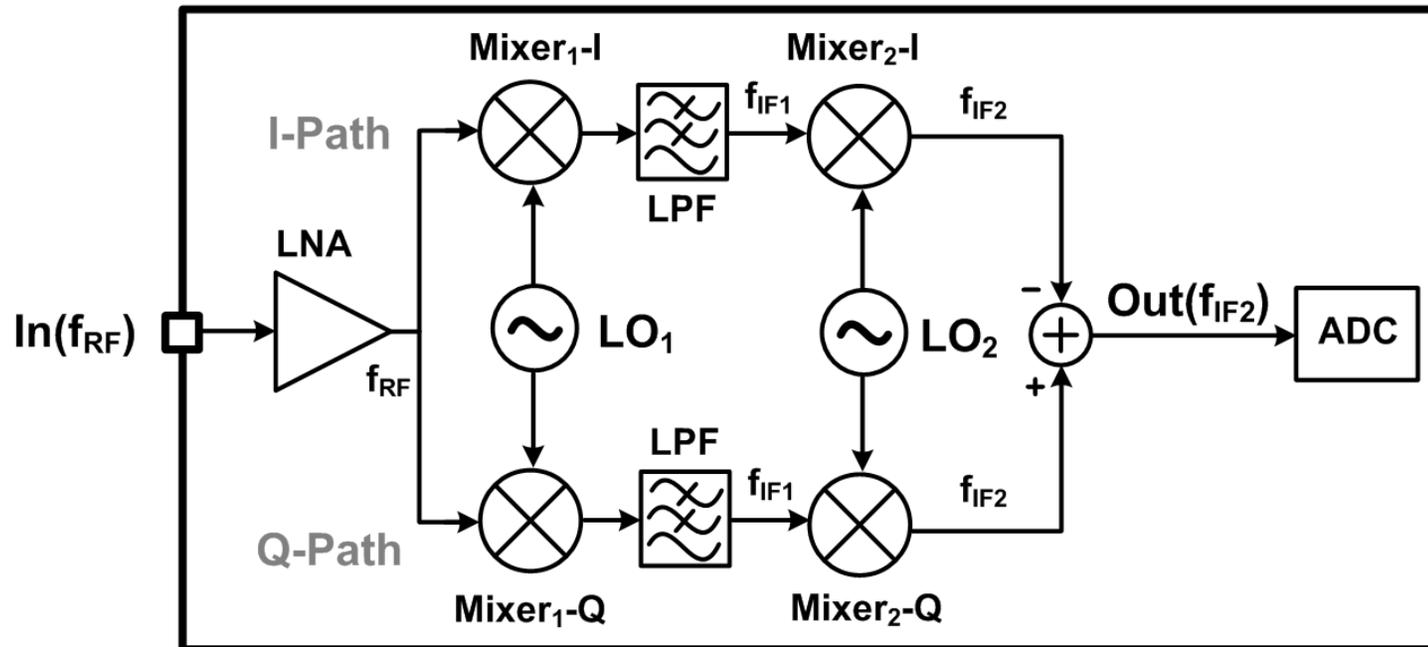

- Image-rejection ratio (IRR) depends on:

- I/Q amplitude mismatch (ΔA)
- Phase mismatch ($\Delta\theta$)


$$IRR_{(dB)} \approx 10 \cdot \log \left(\frac{4}{(\Delta\theta)^2 + (\Delta A)^2} \right)$$

- Typical IRR performance

- Almost 60dB are required for acceptable BER performance
- Often limited to 25dB-40dB due to mismatches

Analog I/Q Calibration for Image-Rejection Receivers

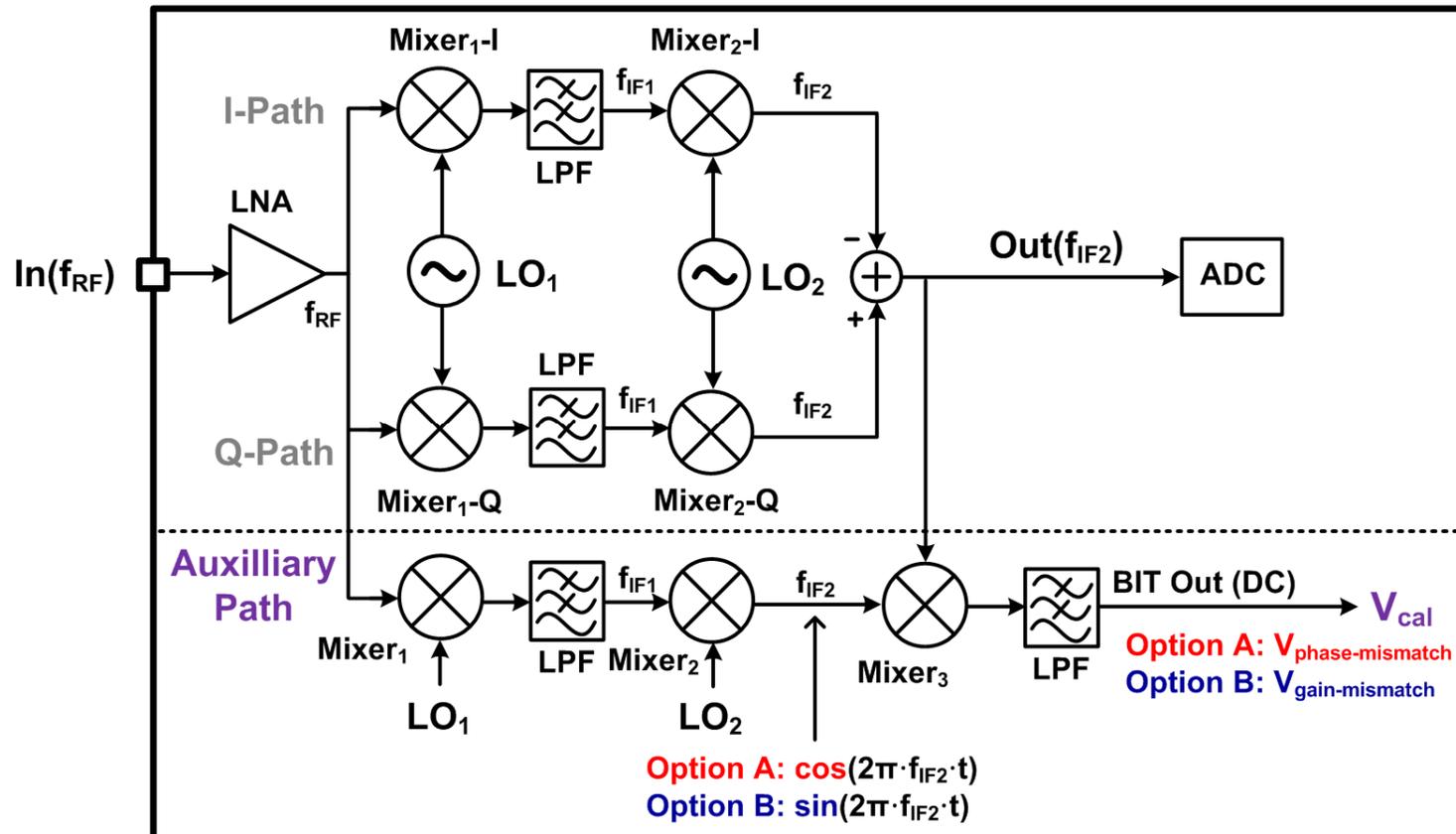
- [1] R. Montemayor and B. Razavi, "A self-calibrating 900-MHz CMOS image-reject receiver," in *Proc. Eur. Solid-State Circuits Conf. (ESSCIRC)*, Sept. 2000, pp. 320-323.



- Analog DC voltage (V_{cal}) can be directly used to tune the bias voltages of analog circuits for mismatch compensation, resulting in high IRR (e.g. 57dB in [1])

Digital I/Q Correction Example

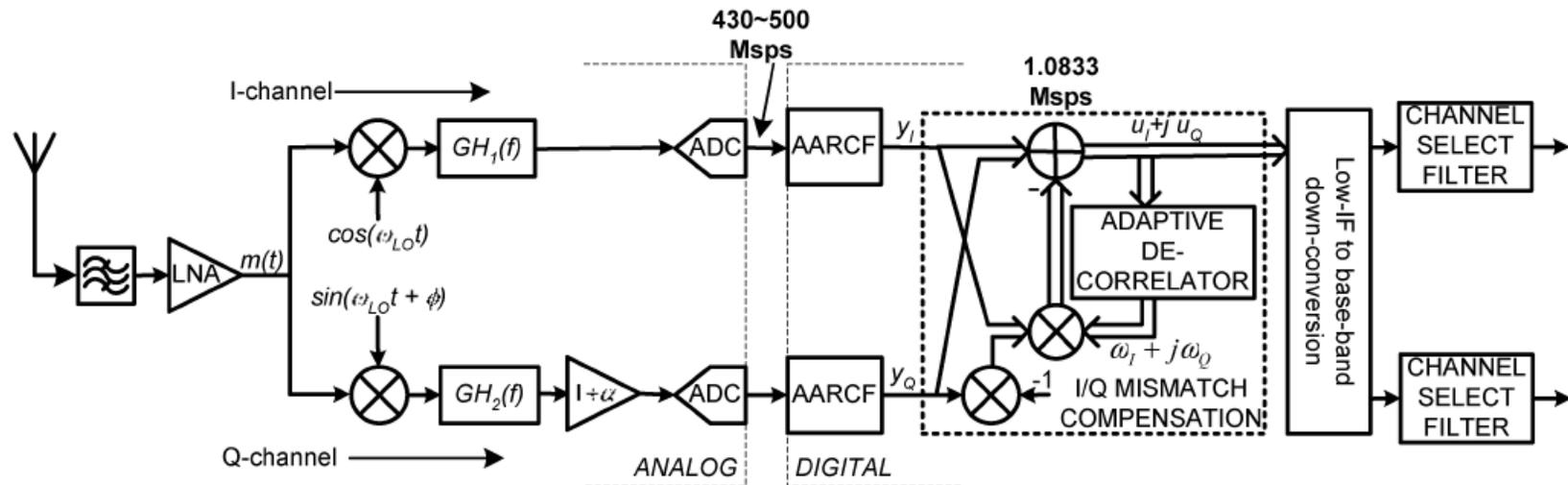I. Elahi, K. Muhammad, and P. T. Balsara, "I/Q mismatch compensation using adaptive decorrelation in a low-IF receiver in 90-nm CMOS process," *IEEE J. Solid-State Circuits*, vol. 41, no. 2, pp. 395-404, Feb. 2006.



- I/Q mismatch compensation follows anti-aliasing rate change filter (AARCF) in this low-IF receiver example
 - **Gain mismatch** appears as **difference in auto-correlation** between I and Q
 - **Phase mismatch** appears as **nonzero cross-correlation** between I and Q
 - **Adaptive decorrelator** drives auto-correlation and cross-correlation between I and Q outputs towards zero by adjusting the correction coefficients:

$$\omega_{I(n+1)} = \omega_{I(n)} + \mu \cdot [u_{I(n)} u_{I(n)} - u_{Q(n)} u_{Q(n)}]$$


$$\omega_{Q(n+1)} = \omega_{Q(n)} + 2 \mu \cdot u_{I(n)} u_{Q(n)}$$

- * μ is the adaptation step size, which is inversely proportional to the signal energy
 → periodic training sequences (preambles) are required

Digital I/Q Correction Example (cont.)

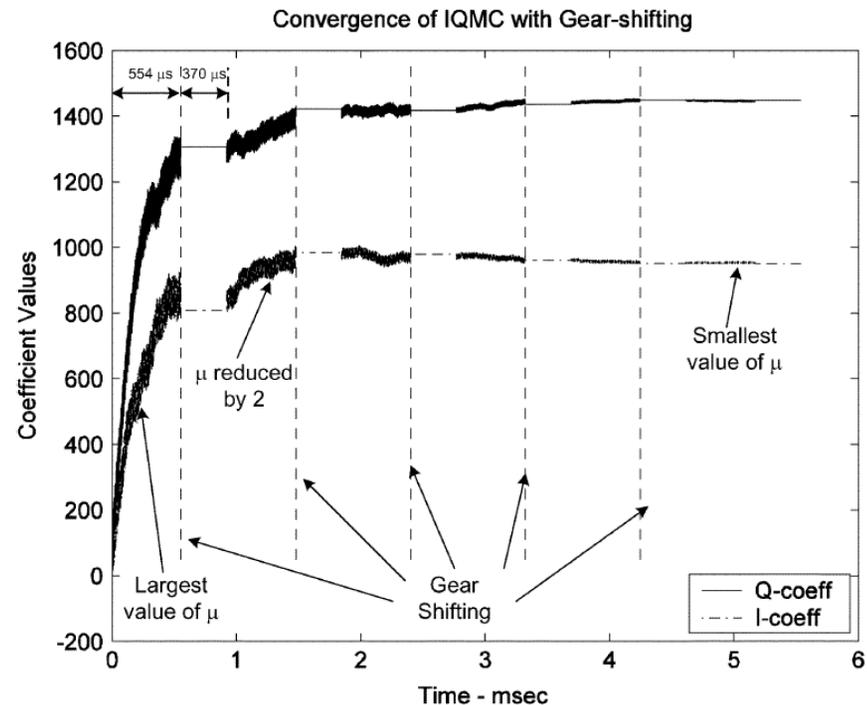I. Elahi, K. Muhammad, and P. T. Balsara, "I/Q mismatch compensation using adaptive decorrelation in a low-IF receiver in 90-nm CMOS process," *IEEE J. Solid-State Circuits*, vol. 41, no. 2, pp. 395-404, Feb. 2006.

- 15-20dB IRR improvement
- Convergence times in the milliseconds range




Temperature °C	Phase Mismatch degrees	Gain Mismatch (Percentage)	Raw IRR (dB)	IRR after IQMC with fixed coefficients (dB)
-40	0.458	-7.83	27.76	42.3
-20	0.247	-8.2	27.37	40.3
25	1.037	-7.24	28.26	55.0
85	0.257	-7.6	28.05	41.7


Another Digital Receiver Calibration Example

- General calibration effectiveness
 - Typical I/Q mismatch accuracy **after calibration**: $\Delta\text{gain} < 0.1\text{dB}$, $\Delta\text{phase} < 1^\circ$
 - Received constellation improvement to guarantee the specified bit error rate
- Reference:
 - K.-H. Lin, H.-L. Lin, S.-M. Wang, R. C. Chang, "Implementation of digital IQ imbalance compensation in OFDM WLAN receivers," in *Proc. IEEE Intl. Symp. on Circuits and Systems*, pp. 3534-3537, 2006.

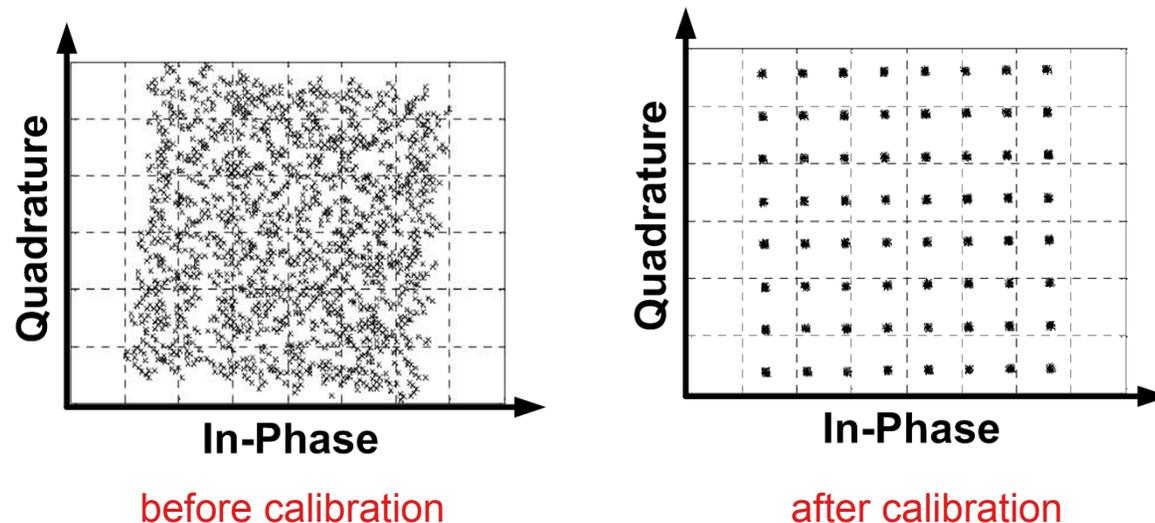64-QAM constellations with I/Q imbalance
($\Delta\text{phase} = 10^\circ$, $\Delta\text{gain} = 20\%$)




Loopback

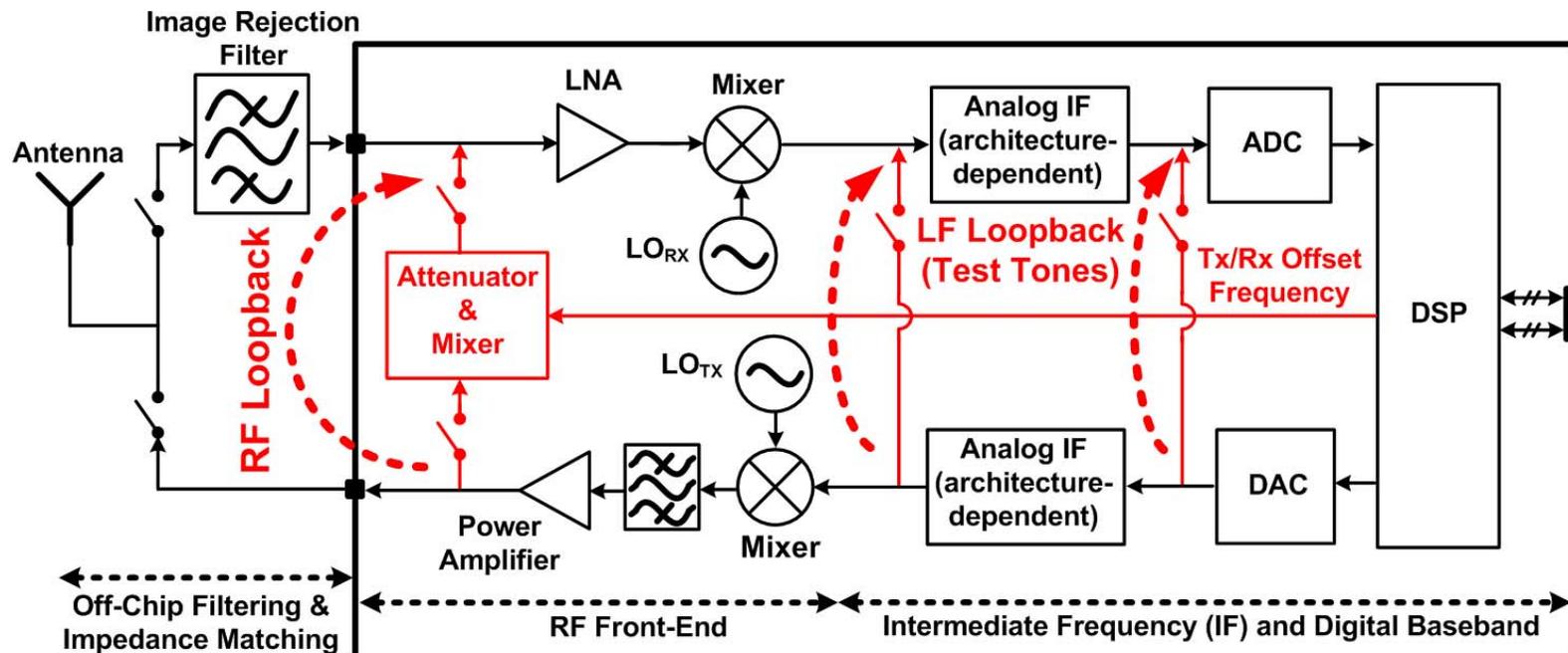


- Dedicated test signal generation and true self-test
- System-level BER/EVM testing or local loopback
- Cannot be executed on-line
- Limited information regarding failure causes and fault locations

Digitally Assisted Receiver Calibration

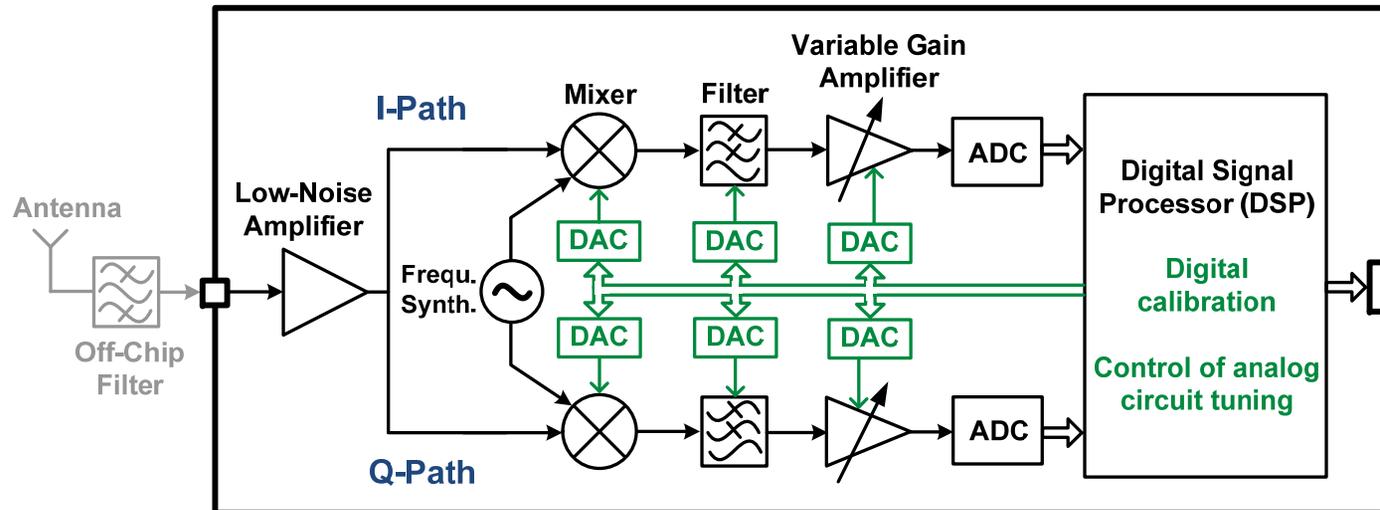

- Emerging system-level approach
 - Analog tuning with digital-to-analog converters (DACs) → wide range, coarse
 - Digital correction → accurate
 - Focus of the presented research efforts:
 - Performance adjustment features for analog circuits
 - Enable system-level calibration (self-healing) during testing and/or normal operation
- } higher yield & reliability

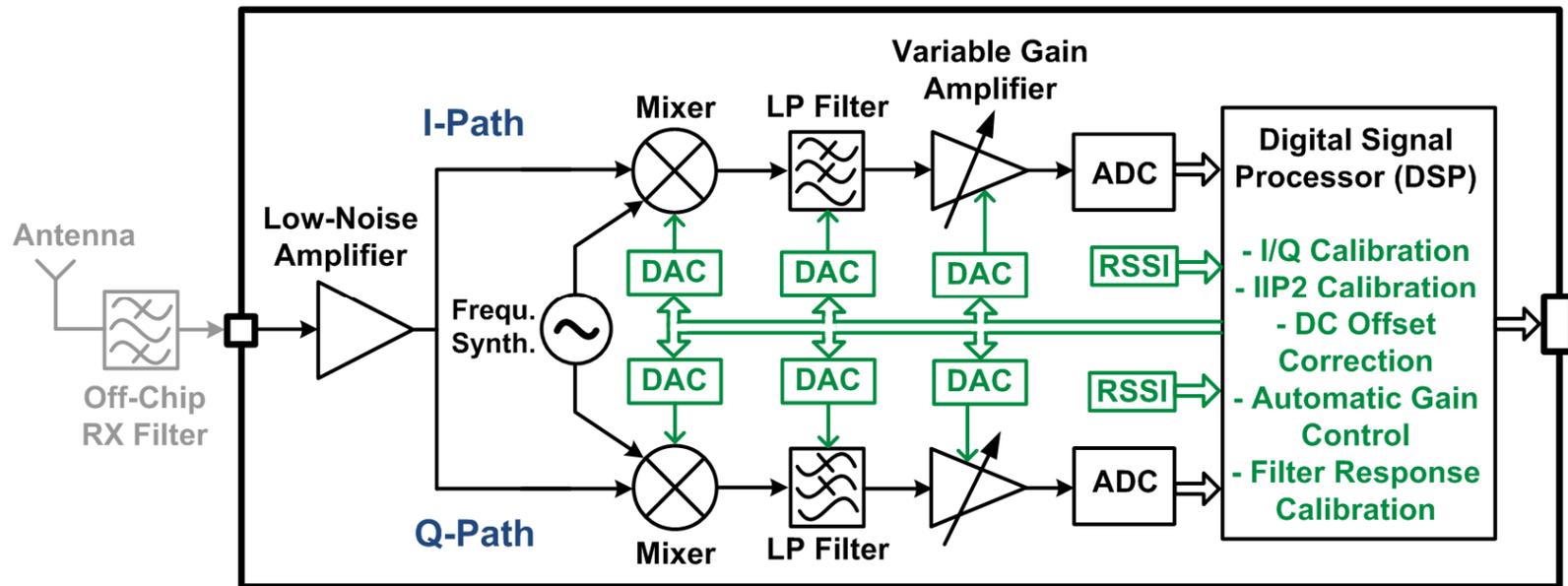More Considerations: Digitally Assisted Calibration



- Calibration optimization
 - System-level metrics: bit error rate (BER), error vector magnitude (EVM)
 - On-chip DSP: Fast Fourier Transform (FFT)
 - enables determination of non-linearities
 - Typical limitation: no observability for individual blocks
 - unknown fault causes/locations

Transceiver Calibration: Industry Examples

- **5.2-5.8GHz 802.11a WLAN transceiver** (0.18 μ m CMOS) – **Athena Semiconductor**
 - Digital I/Q mismatch correction
 - Multiple internal loopback switches for self-calibration in test mode
 - 8-bit DACs for DC offset minimization after mixers and filters


I. Vassiliou, et. al., "A single-chip digitally calibrated 5.15-5.825-GHz 0.18- μ m CMOS transceiver for 802.11a wireless LAN," *IEEE J. Solid-State Circuits*, vol. 38, no. 12, pp. 2221-2231, Dec. 2003.
- **2.4GHz Bluetooth radio** (0.35 μ m CMOS) – **Broadcom**
 - Bias networks with digital settings for LNA, mixer, filter
 - Direct tuning patent (US 7,149,488 B2) with 2 RSSIs and digital block-level bias trimming

H. Darabi, et. al., "A dual-mode 802.11b/bluetooth radio in 0.35- μ m CMOS," *Solid-State Circuits, IEEE J. Solid-State Circuits*, vol. 40, no. 3, pp. 698-706, March 2005.
- **2.4GHz 802.11g WLAN transceiver** (0.25 μ m CMOS) – **MuChip**
 - Baseband I/Q gain and phase calibration
 - Extra analog mixer & peak detector

Y.-H. Hsieh, et. al., "An auto-I/Q calibrated CMOS transceiver for 802.11g," *IEEE J. Solid-State Circuits*, vol. 40, no. 11, pp. 2187-2192, Nov. 2005.
- **Single-chip GSM/WCDMA transceiver** (90nm CMOS) – **Freescale Semiconductor**
 - DC offset, I/Q gain & phase, IIP2 calibration in the digital signal processor
 - 6-bit DACs for analog compensation

D. Kaczman, et. al., "A Single-Chip 10-Band WCDMA/HSDPA 4-Band GSM/EDGE SAW-less CMOS Receiver With DigRF 3G Interface and +90 dBm IIP2," *IEEE J. Solid-State Circuits*, vol. 44, no. 3, pp. 718-739, March 2009.

Calibration with Enhanced Fault Coverage

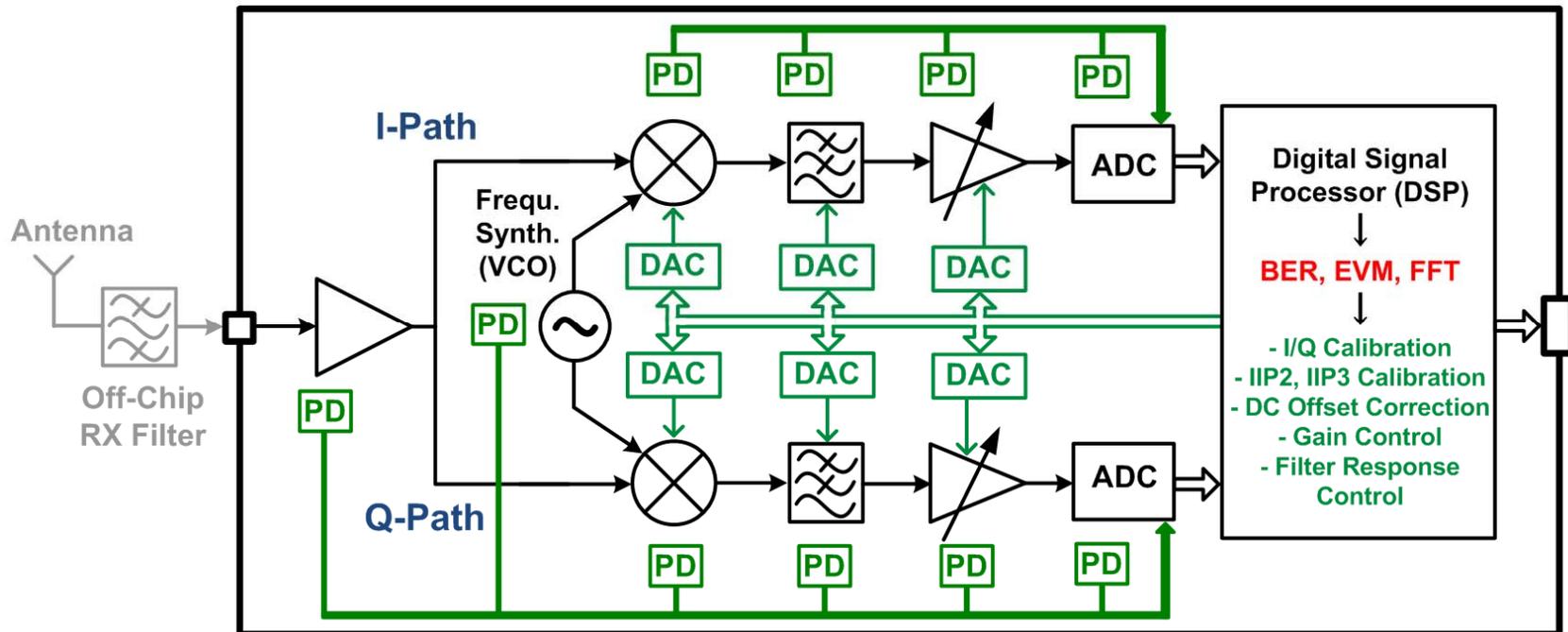


- Power detectors (PDs) for built-in testing
 - Block-level fault and performance identification
 - Localized analog tuning (coarse but fast)

Outline – Lecture 1

- Introduction
 - Course overview
 - Greetings from Northeastern University
- CMOS process variation
 - Trends
 - Impacts
- System-level calibration trends
 - Systems-on-a-chip examples (receivers, transceivers)
- **Production test simplification and cost reduction**
 - **Example: loopback testing**
- Built-in testing of analog circuits
 - Introduction
 - On-chip power detection
 - RF LNA built-in testing example


Conceptual Test Economics

- Characterization phase
 - Design debug → comprehensive testing to obtain product specifications
- Production testing
 - Screening out of faulty devices based on specified limits (pass/fail)
 - Quick functionality checks with sufficient accuracy
- The commonly mentioned “Rule of Ten” for testing
 - Defect detection cost increases ~10 times at each stage of the chip assembly
 - Common practice: selective (sampled) verification at each stage
 - ♦ More economical
 - ♦ General need: improve test coverage at wafer test or enable recovery from faults/variations with calibration

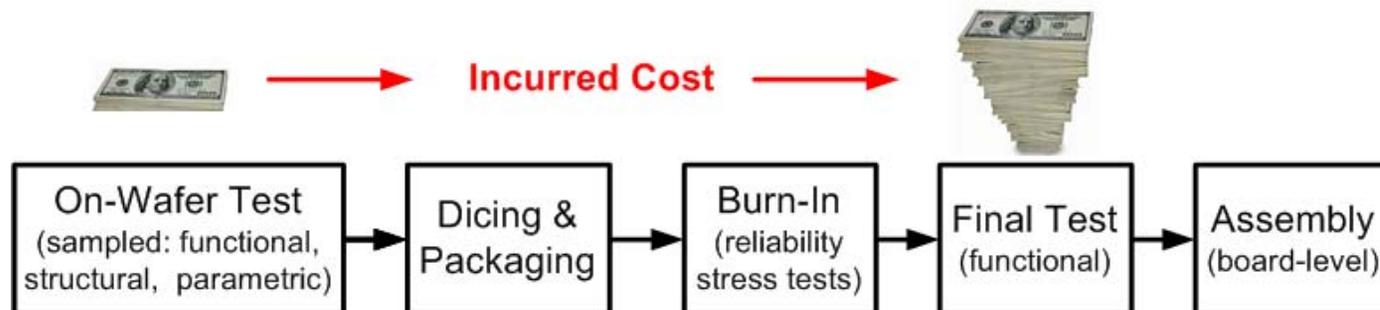

Conceptual Test Economics (cont.)

- Relative test cost increase
 - Up to 40-50% of total cost for complex mixed-signal chips
- Cost reduction efforts
 - Earlier fault detection
 - Test time reduction
 - Sampled testing (high-yield products)
- Potential savings with built-in testing
 - Less inputs/outputs → lower pin count
 - ♦ ATE pin cost: \$200/pin - \$10,000/pin
 - Minimization of wafer test time cost
 - ♦ Range: 0.03¢/sec. (digital) - 0.07¢/sec. (analog)
 - Elimination of external RF measurement equipment → multi-site testing
 - ♦ Parallel testing of multiple dies on wafer with digital resources

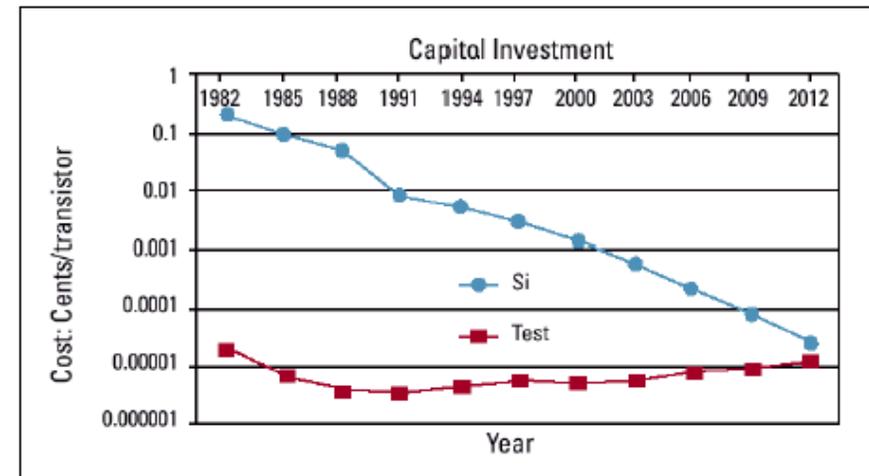

Silicon Cost vs. Test Cost


(source: National Instruments Corp.,
<http://zone.ni.com/devzone/cda/tut/p/id/2869>)

Technical Manufacturing Test Issues

- System-on-chip complexity
 - Verification of all functions is impractical in production testing
 - Coupling and interference effects → block-level tests less reliable
- Limited access to internal nodes
 - Solutions: on-chip power detectors, multiplexed outputs (low-frequency)
- Process variations
 - Necessitates tuning or calibration
 - Requires: measurement/estimation of critical parameters
→ analog/digital compensation
- RF test interfaces
 - Sensitive to impedance matching → costly interface hardware
 - Avoid RF signal capture → dedicated equipment and/or long processing times

Conventional RF Transceiver Testing

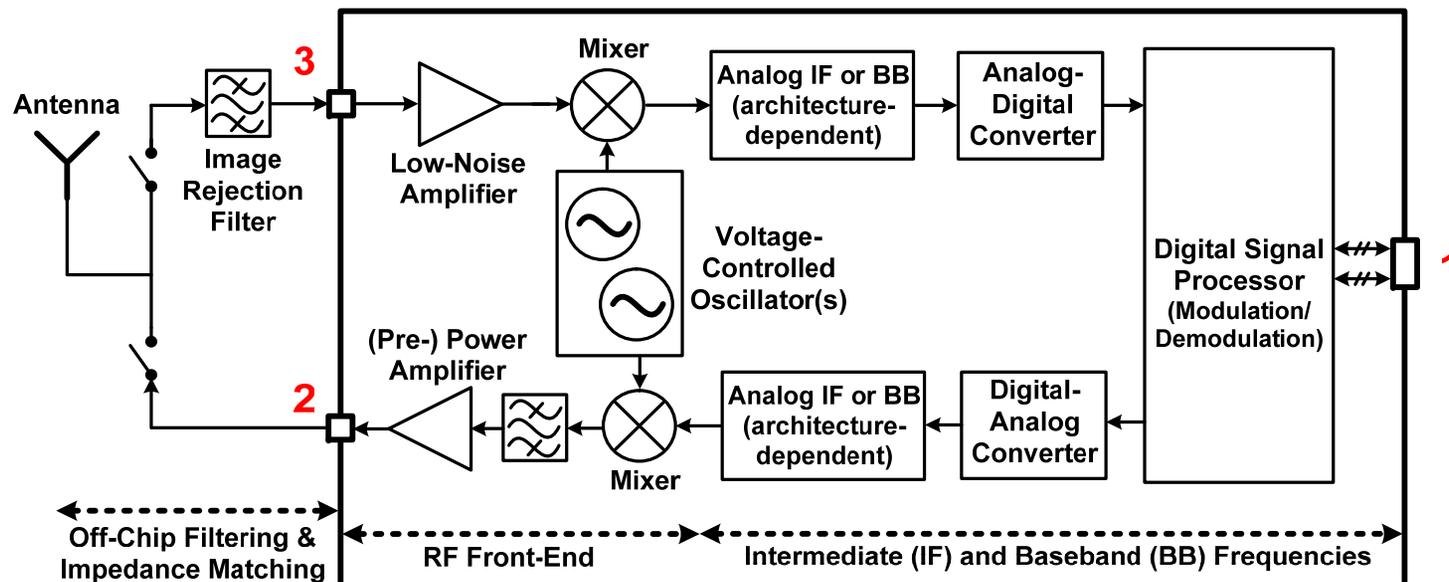- Block-level characterization
 - Design debug & characterization test phases
- System-level verification in production
 - Transmitter (TX): digital baseband input (1) → RF output capture (2)
 - ♦ Basic measures: Output power (spectrum), TX gain
 - Receiver (RX): RF source (3) → digital baseband output (1)
 - ♦ Basic measures: bit error rate (BER), error vector magnitude (EVM)



Conventional RF Transceiver Testing (cont.)

- Common performance tests [1]
 - Test selection during production testing depends on:
product / manufacturer / application
 - TX/RX gain, RX noise figure, RX dynamic range, TX adjacent channel power ratio (ACPR), RX I/Q amplitude/phase mismatch, local oscillator rejection,...
- Higher-level tests (BER, EVM) reduce test time & cost [2], [3]
 - A system-level functional test can replace:
 - ♦ several lower-level tests
 - ♦ block-level characterization
 - BER/EVM are affected by noise figure, I/Q mismatch, etc.
- RF ATE cost
 - RF measurements raise equipment and test development cost
 - In terms of dollars [4]:
 - ♦ Range: \$100K/tester (low-speed digital) - \$2M/tester (RF)
 - ♦ High-volume products can require up to 20 ATE platforms

RF Transceiver Testing References

- Cited on the previous slide:

- [1] K. B. Schaub, J. Kelly, *Production Testing of RF and System-on-a-Chip Devices for Wireless Communications*, Boston, MA: Artech House, 2004.
- [2] E. Lowery, "Integrated Cellular Transceivers: Challenging Traditional Test Philosophies," *Proc. of the 28th Annual IEEE/SEMI International Electronics Manufacturing Tech. Symposium*, pp. 427-436, July 2003.
- [3] A. Halder and A. Chatterjee, "Low-Cost Alternate EVM Test for Wireless Receiver Systems," *Proc. of the 23rd VLSI Test Symposium*, pp. 255-260, May 2005.
- [4] J. Ferrario, R. Wolf, S. Moss, "Architecting Millisecond Test Solutions for Wireless Phone RFIC's," *Proc. of the International Test Conference*, vol. 1, pp. 1325-1332, October 2003.


- Other useful sources:

- [5] M. Burns, G. W. Roberts, *An Introduction to Mixed-Signal IC Test and Measurement*, New York, NY: Oxford University Press, 2001.
- [6] M. Jarwala, D. Le, M. S. Heutmaker, "End-to-End Test Strategy for Wireless Systems", *Proc. of the International Test Conference*, pp. 940-946, October 1995.
- [7] M. Onabajo, F. Fernandez, J. Silva-Martinez, and E. Sánchez-Sinencio, "Strategic test cost reduction with on-chip measurement circuitry for RF transceiver front-ends – an overview," in *Proc. 49th IEEE Intl. Midwest Symp. on Circuits and Systems*, vol. 2, pp. 643-647, Aug. 2006.
- [8] O. Eliezer, R. B. Staszewski, and D. Mannath, "A statistical approach for design and testing of analog circuitry in low-cost SoCs." in *Proc. IEEE Intl. Midwest Symposium on Circuits and Systems (MWSCAS)*, Aug. 2010, pp. 461-464.

The Loopback Method

- System-level approach

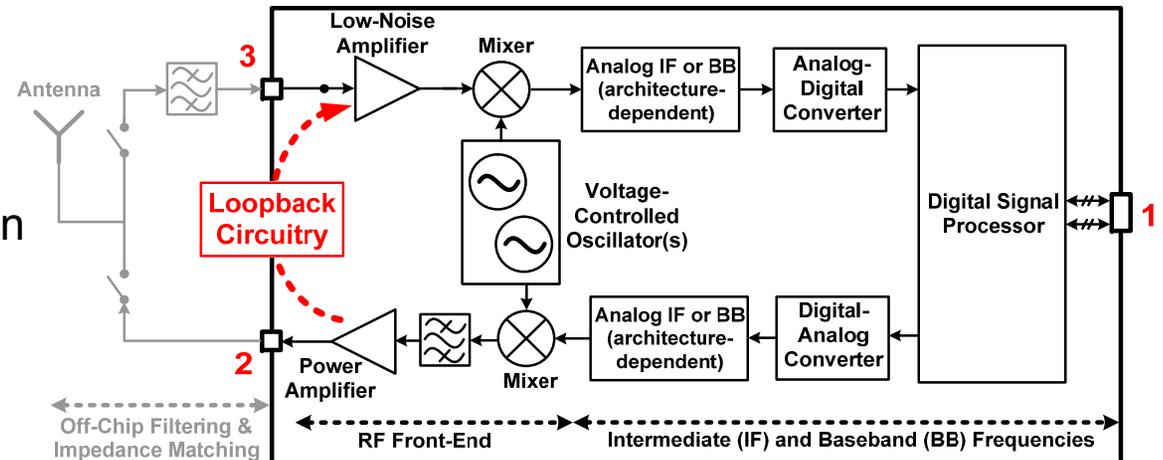- Only low-frequency inputs/outputs at point 1
- Transceiver resources used for RF signal generation & modulation operations
- ATE calculations reduced to digital comparisons



- Loopback circuitry

- Required to match the conditions of transmitter output and receiver input


- Testing algorithms

- Propositions based on BER calculations and spectral analysis (ref.: [A]-[G])
- Verified with simulations or discrete components (off-chip loopback)

- On-chip loopback has further benefits

- No high-frequency signals routed off-chip
- Potential for transceiver self-test & calibration in the field

On-Chip Loopback Implementation

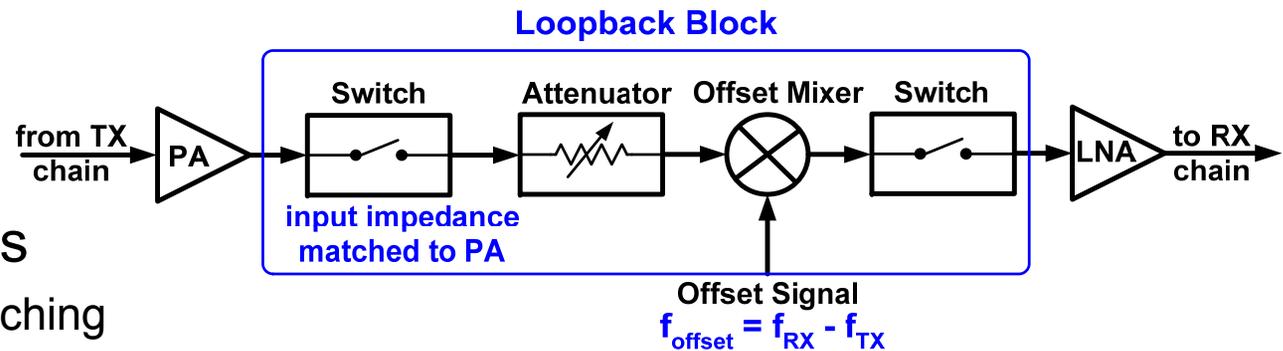

- Basic requirements

- Input impedance matching
- Attenuation
- Frequency translation (if $f_{\text{RX}} \neq f_{\text{TX}}$)
- Switches with high isolation

- First switch/attenuator for loopback application [H]

- Switches optimized for compactness and insertion loss
- Fixed resistive attenuator (no tuning)

- First offset mixer [I]

- Optimized for suppression of unwanted RF mixing by-products
- Quadrature mixing → single-ended PA cannot be included in test loop
- Passive topology → max. output power -20dBm


Loopback References

- Cited on the previous slides:

- [A] M. Jarwala, D. Le, M. S. Heutmaker, "End-to-End Test Strategy for Wireless Systems", *Proc. of the International Test Conference*, pp. 940-946, October 1995.
- [B] B. R. Veillette, G. W. Roberts, "A built-in self-test strategy for wireless communication systems", *Proc. of the International Test Conference*, pp. 930-939, October 1995.
- [C] J. Dabrowski, "Loopback BIST for RF front-ends in digital transceivers", *Proc. of the Intl. Symposium for System-on-Chip*, pp. 143-146, November 2003.
- [D] D. Lupea, U. Pursche, and H.-J. Jentschel, "RF-BIST: Loopback Spectral Signature Analysis," *Proc. of the Design, Automation, and Test in Europe Conference and Exhibition*, pp. 478-483, 2003.
- [E] A. Haider, S. Bhattacharya, G. Srinivasan, and A. Chatterjee, "A system-level alternate test approach for specification test of RF transceivers in loopback mode," *Proc. of the 18th International Conference on VLSI Design*, pp. 289-294, January 2005.
- [F] M. Negreiros, L. Carro, A. A. Susin, "An Improved RF Loopback for Test Time Reduction", *Proc. of the Design, Automation, and Test in Europe Conference and Exhibition*, March 2006.
- [G] G. Srinivasan, A. Chatterjee, F. Taenzler, "Alternate loop-back diagnostic tests for wafer-level diagnosis of modern wireless transceivers using spectral signatures", *Proc. of the 24th VLSI Test Symposium*, May 2006.
- [H] J.-S. Yoon and W. R. Eisenstadt, "Embedded loopback test for RF ICs," *IEEE Transactions on Instrumentation and Measurement*, pp. 1715-1720, Oct. 2005.
- [I] S. Bota, E. Garcia-Moreno, E. Isern, R. Picos, M. Roca, K. Suenaga, "Compact Frequency Offset Circuit for Testing IC RF Transceivers," *Proc. of the 8th International Conference on Solid-State and Integrated Circuit Technology (ICSICT)*, pp. 2125-2128, October 2006.

- Other useful sources:

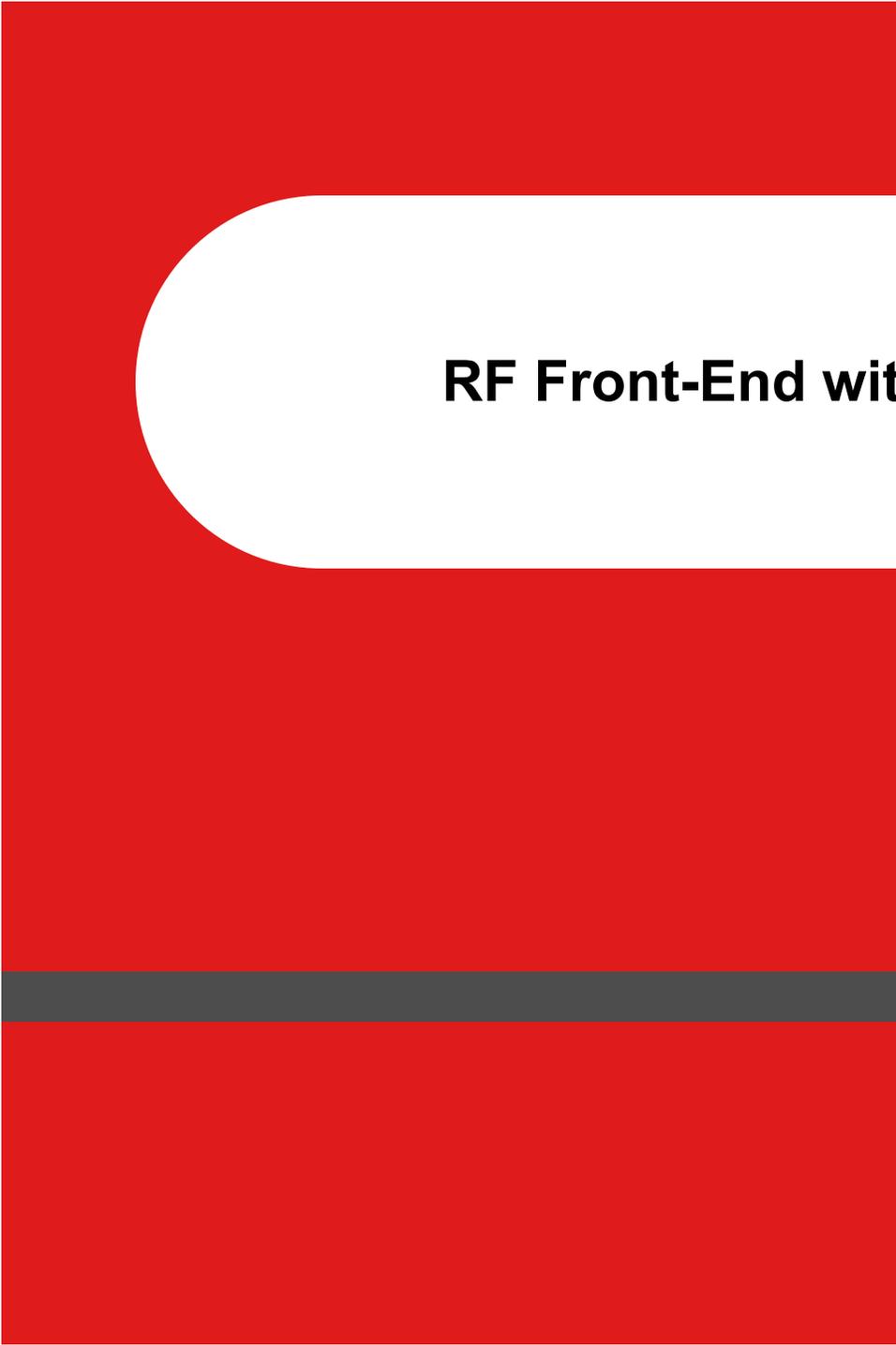- [J] J. J. Dabrowski and R. M. Ramzan, "Built-in loopback test for IC RF transceivers," *IEEE. Trans. Very Large Scale Integration (VLSI) Systems*, vol. 18, no. 6, pp. 933-946, June 2010.
- [K] H. Shin, J. Park, J. A. Abraham, "Spectral prediction for specification-based loopback test of embedded mixed-signal circuits," *Springer J. Electronic Testing*, vol. 26, no. 1, pp. 73-86, Jan. 2010.



RF Front-End with On-Chip Loopback

Team at Texas A&M University:

Marvin Onabajo

Felix Fernandez

Edgar Sánchez-Sinencio


Jose Silva-Martinez



Loopback Project Overview


- Proof-of-concept RF front-end

Parameter	Value
Tx frequency	2GHz
PA output power	0dBm
Rx frequency	2.1GHz
LNA gain	21dB
Mixer gain	6.9dB

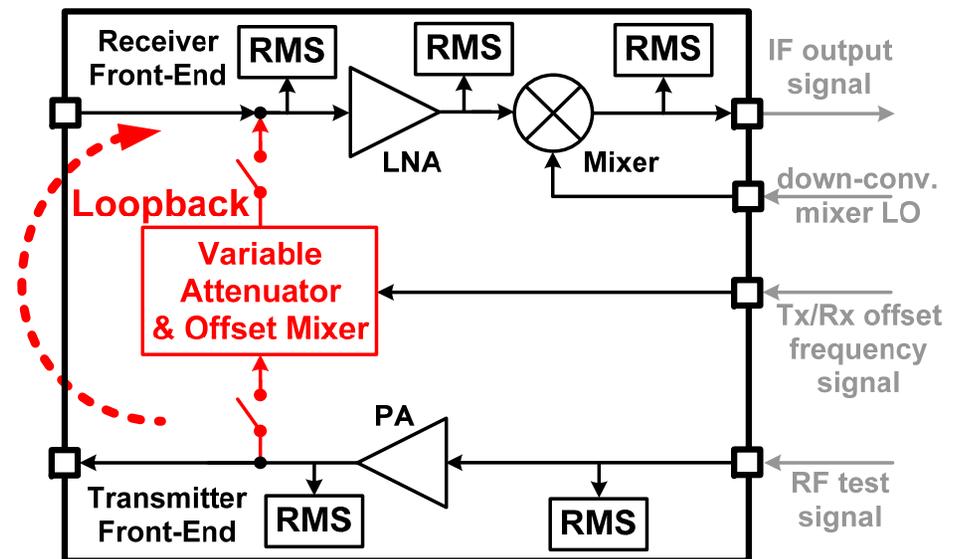

- Root-mean-square (RMS) power detectors
 - To measure gains and 1-dB compression points of the RF blocks
 - To improve the test coverage and identification of fault locations
- Test coverage
 - Project focus: front-end circuits
 - In case of a fully integrated transceiver: system-level BER

Proposed Loopback Block: Overview

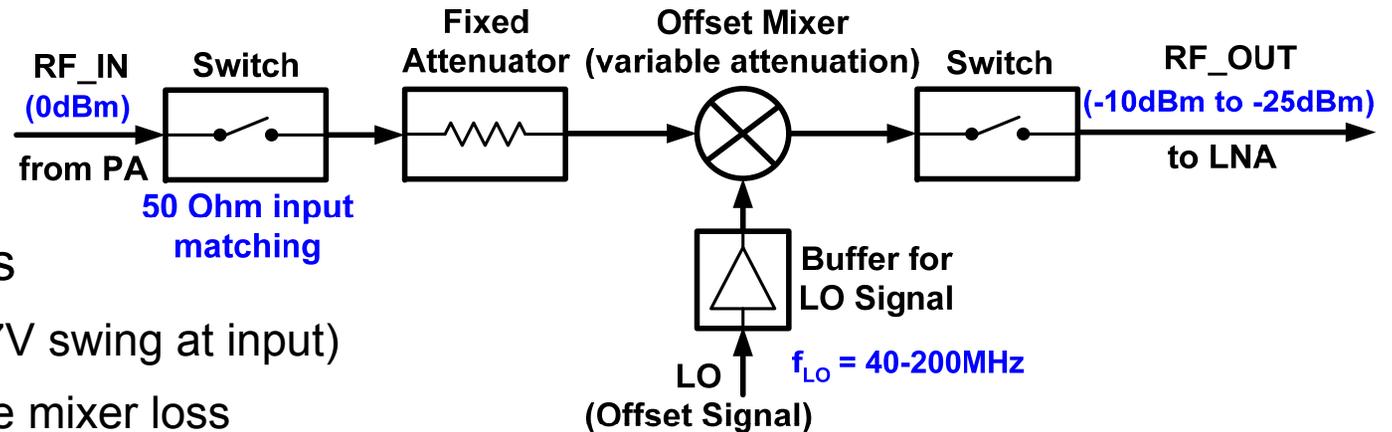


- Design challenges
 - Linearity (up to 0.7V swing at input)
 - Avoiding excessive mixer loss
 - Low impedance at the LNA gate node
 - ◆ This case: $\sim 150\Omega$
 - ◆ High load-driving capability needed
 - Minimum die area/complexity
- Reconfigurability
 - Specs ensure compatibility with multiple standards (1.9-2.4GHz)
 - Offset mixing required if $f_{RX} \neq f_{TX}$ (ex.: W-CDMA, CDMA2000)

Target Specifications:

Parameter	Value
Input impedance	50 Ω (matched to PA)
Tx/Rx offset frequency range	40-200MHz
Attenuation range (continuous)	10-25dB
Operating frequency	< 2.5GHz
Tx/Rx isolation (loopback deactivated)	> 80dB
Output noise: depends on communication standard and power level	


Input Stage: Switch/Fixed Attenuator

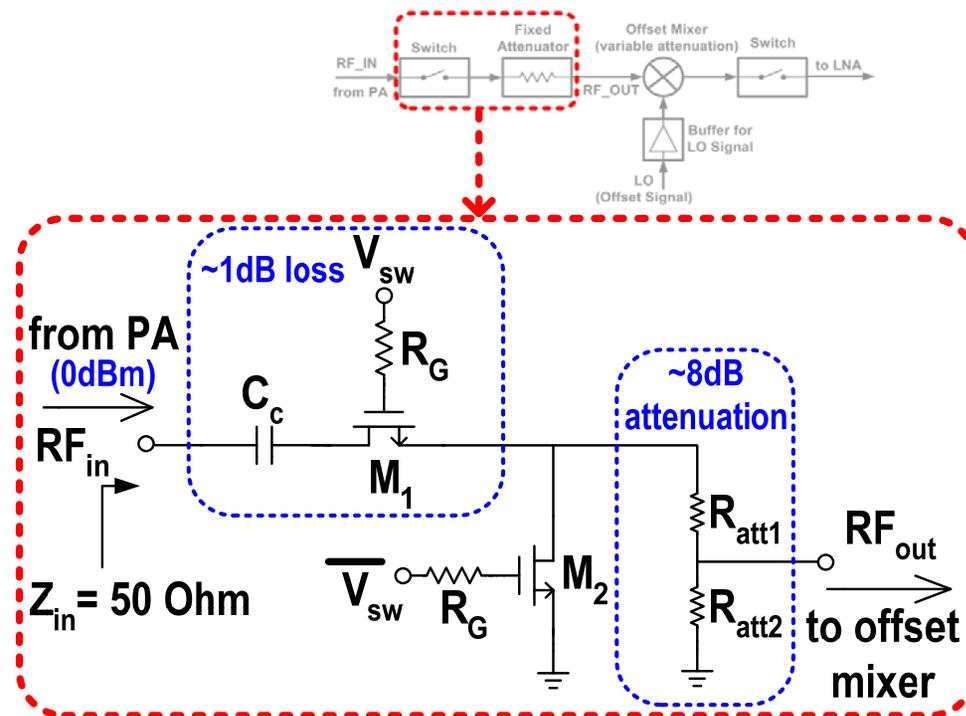- Switch
 - M_1 : low insertion loss/high linearity (large W/L) vs. high isolation (small W/L)
 - R_G : improves linearity (1-dB comp. pt. increase: ~ 4 dB) & high-frequency performance
 - M_2 : ~ 10 dB more isolation in off-state
- Fixed attenuator (R_{att1} , R_{att2})
 - Decreases signal level at mixer input \rightarrow relaxed mixer linearity



Offset Mixing with a Switching Mixer

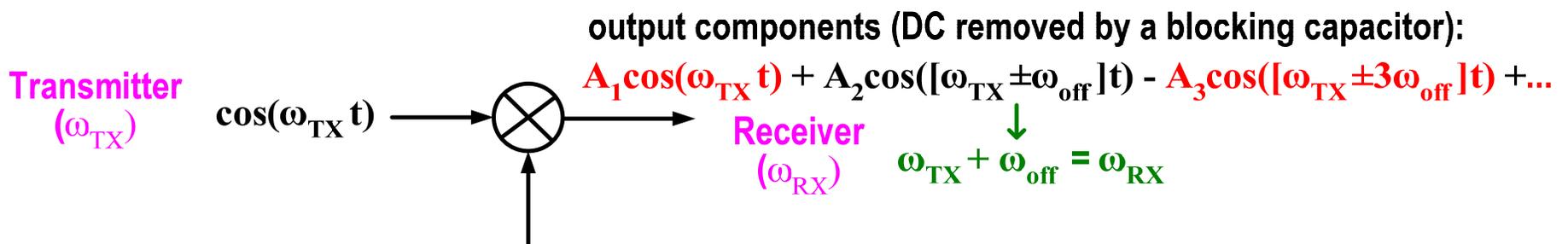- Goals
 - Allow single-ended input from transmitter → inclusion of PA in the loop
 - Digital rail-to-rail signal can be used to provide the offset signal (simple to generate with low-cost ATE)
 - Avoid complexity → more robust
- Mixing scheme:




on/off switching represented with Fourier series:


$$\frac{1}{2} + (2/\pi)\cos(\omega_{off} t) - (2/3\pi)\cos(3\omega_{off} t) + (2/5\pi)\cos(5\omega_{off} t) - \dots$$

Suppression of Undesired Spectral Components

- RF feedthrough at $f_{\text{RFin}} = f_{\text{TX}}$
 - Appears as common-mode signal
 - Attenuated by the common-mode rejection property of the differential output stage in the mixer
 - Unwanted components at the receiver input
 - ◆ Located $\geq 2 \times f_{\text{offset}}$ (80-400MHz) away from desired signal
 - ◆ Equal or lower power than the desired signal
 - ◆ Must be suppressed according to communication standards

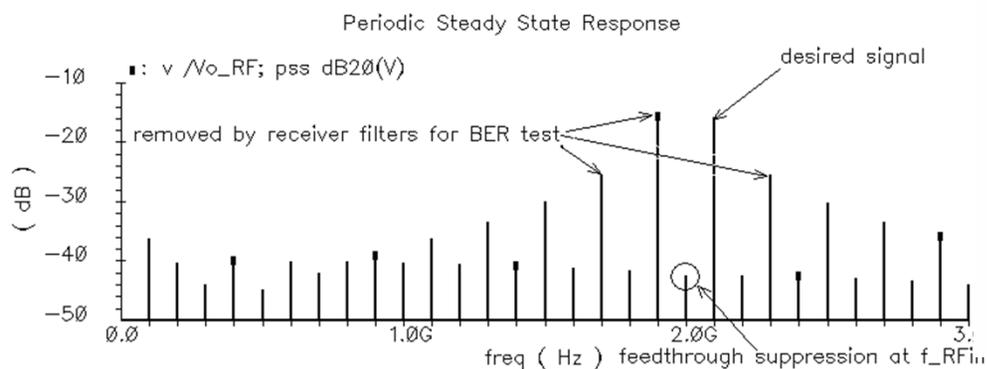



Output spectrum of second mixer stage

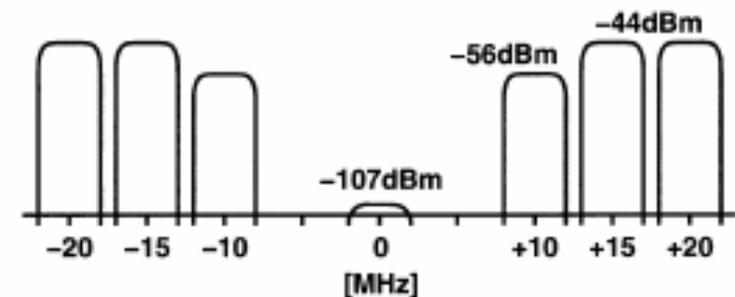

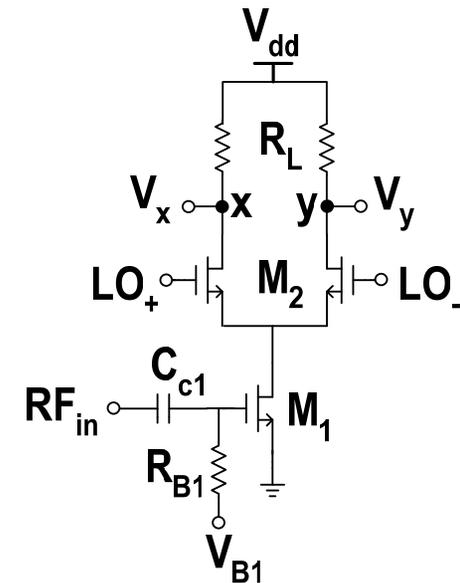
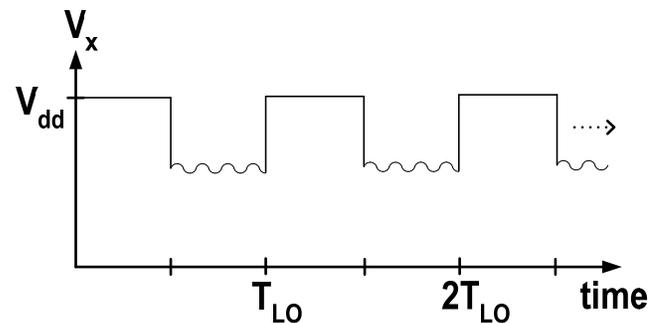
Example: W-CDMA blocker template
(tolerable interference at 10MHz offset is
>50dB above the desired signal)

Offset Mixer Topology Development

- Simple single-balanced mixer \Rightarrow
 - Differential offset signal ($LO_{+/-}$)
 - Problem: voltage fluctuation from switching (at nodes x and y)




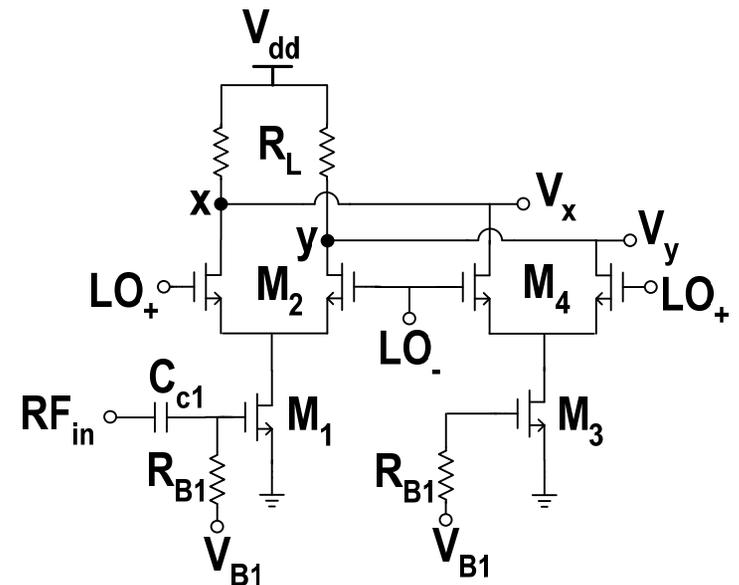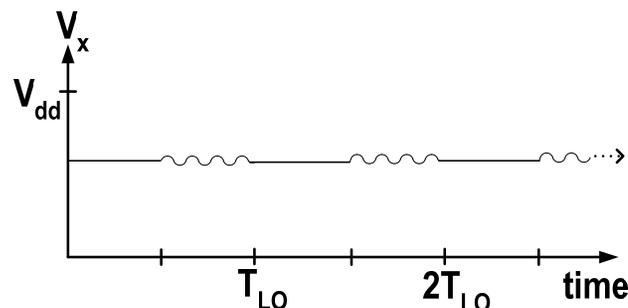- Modified mixer core \Rightarrow
 - Auxiliary branch for DC stabilization
 - $M_3=M_1$, $M_4=M_2$
 - Reversed $LO_{+/-}$ phase in aux. branch




Proposed Offset Mixer Topology

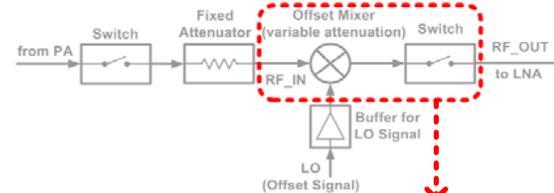- 2 gain settings in the mixer core
 - R_{L2}/R_{L3} activated to reduce gain
 - Range: ~14dB



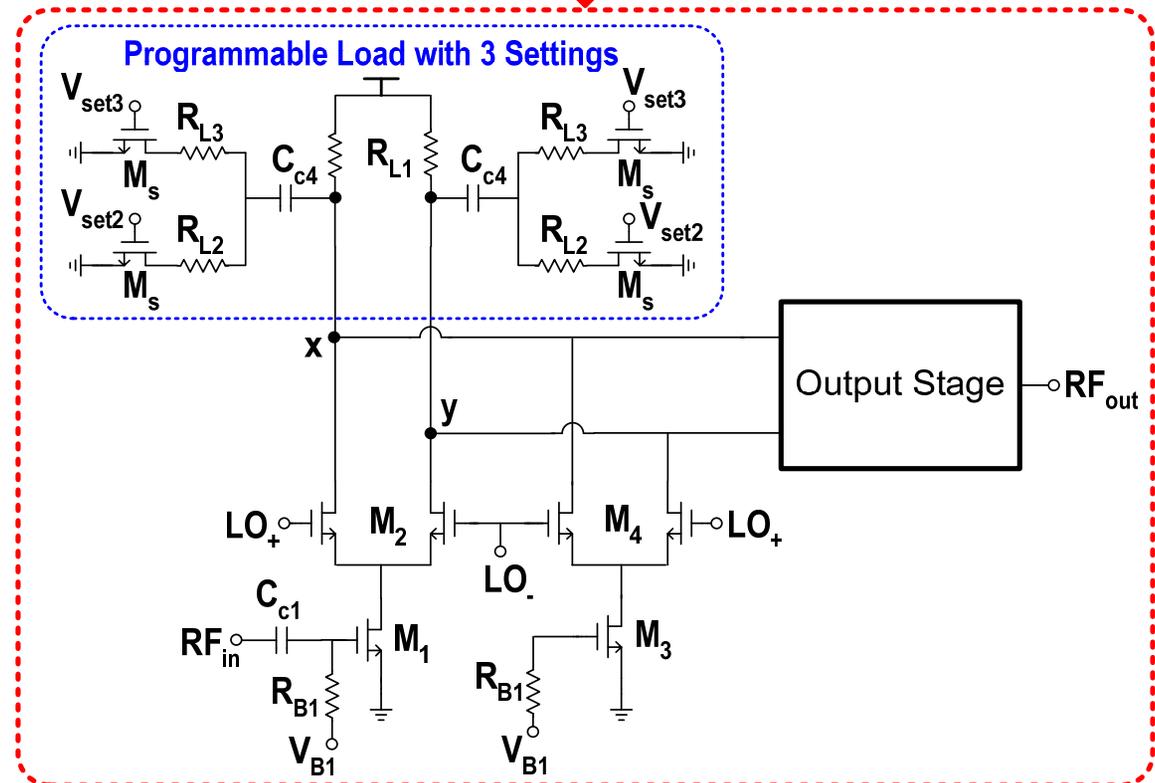- Coupling capacitor C_{c4}
 - Prevents DC operating point changes at nodes x/y
 - Allows use of NMOS switch instead of PMOS (lower on-resistance for same size/parasitics)



- Conversion gain

$$G_{mix_diff} = \frac{2g_{m1}R_{L[setting]}}{\pi}$$

Offset Mixer Output Stage

- Continuous gain tuning
 - Load transistor (M_L) is biased in triode region
 - Range with V_{att_ctrl} : $\sim 6\text{dB}$

- Load-driving improvement


$$G_{out} = \frac{g_{m6} R_{ON}(M_L)}{2}$$

- Output switch

- To disconnect loopback:
 V_{att_ctrl} high, V_{B3}/V_{B2} low



- Common-mode attenuation of RF feedthrough
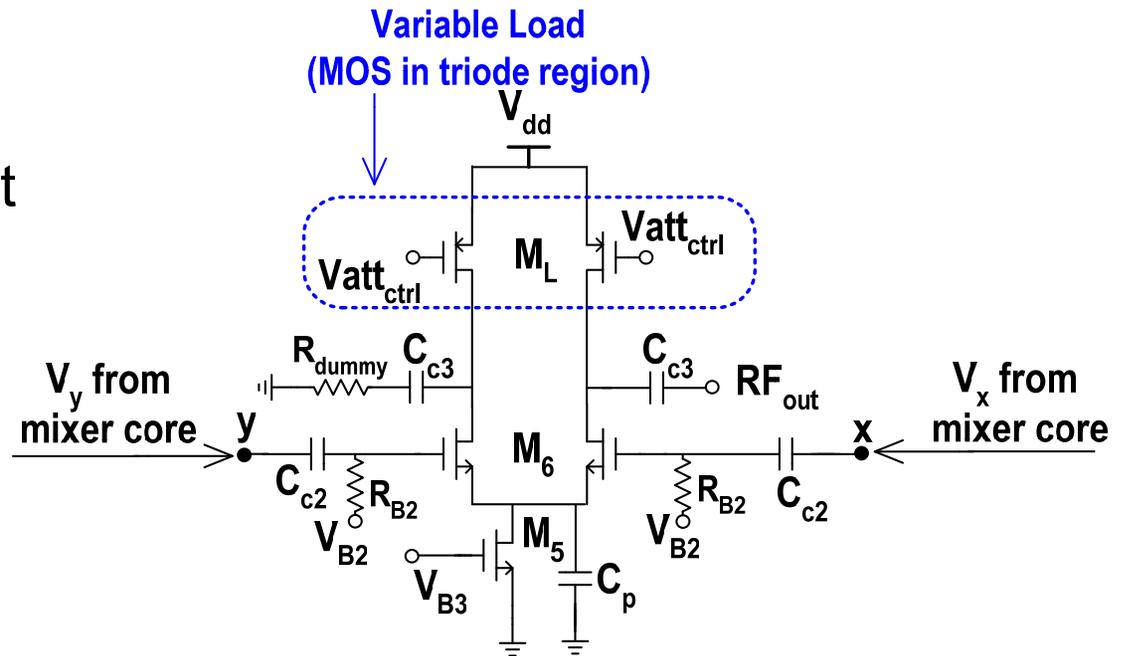
$$A_{v(\omega_{RFin})} = A_{v_cm} = \frac{g_{m6} R_{ON}(M_L)}{1 + 2g_{m6} (r_{ds5} \parallel \frac{1}{j\omega C_p})}$$



Testchip with the Prototype Front-End

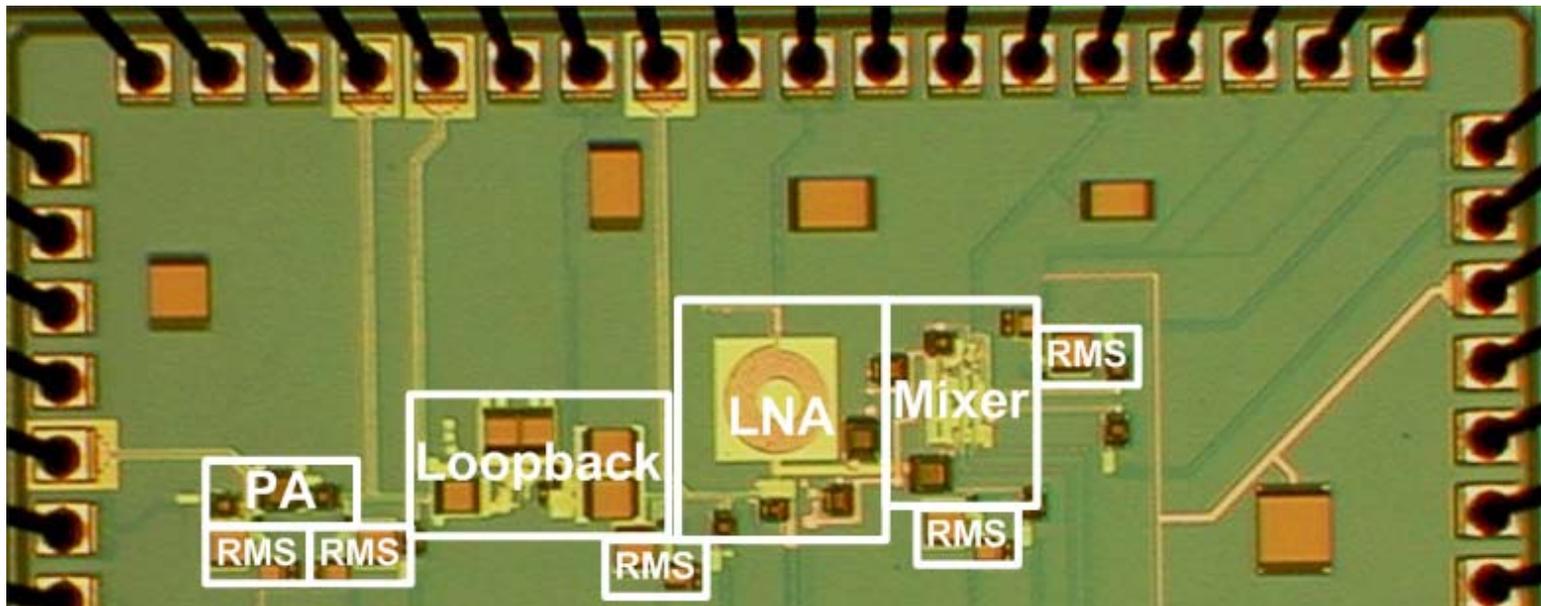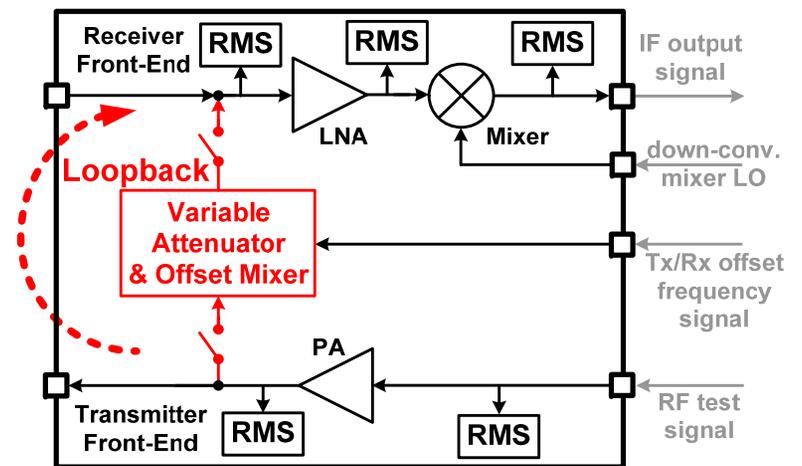- UMC 0.13 μm CMOS technology
- Loopback block die area
 - 0.052mm²
 - 40% of the combined PA, LNA, and down-conversion mixer area
 - Roughly 1-4% overhead for a transceiver



Measurement Results

Parameter	Target	Simulation	Measurement
Input impedance	50Ω	50Ω	50Ω*
Tx/Rx offset frequency range	40-200MHz	40-200MHz	40-200MHz
Attenuation range**	10-25dB	10.9-27.3dB	25.8-41.5dB
Operating frequency	< 2.4GHz	< 2.4GHz	< 2.4GHz
Tx/Rx isolation (deactivated)	> 80dB	> 89dB**	> 27.4dB***


- * On-chip resistor (subject to PVT variations)
- ** Not accounting for RF feedthrough via substrate, mutual inductance between bonding wires, and PCB.
- *** Measurement setup does not permit verification of isolation with more certainty. (Coupling between nearby traces on the PCB: measured isolation between pins ranged from 30dB to 50dB)

Measurement Results (cont.)

- Fabrication-specific comments
 - Strong PVT variations
 - ◆ Gain degradation up to 10dB implied from reductions of:
 - 20% for effective RF transconductances
 - 10% for polysilicon resistors(in each of the two offset mixer stages)
 - Coupling losses
 - ◆ At the input attenuator
 - ◆ Capacitors in the offset mixer
- General suggestions
 - Avoid MOS capacitors
(signal leakage to ground through parasitic capacitances)
 - Design with ~10dB more gain in the loopback
 - ◆ To provide sufficient margin for worst-case PVT conditions
 - ◆ To allow 1-dB compression point testing for the LNA


Measured Loopback Output Spectrum

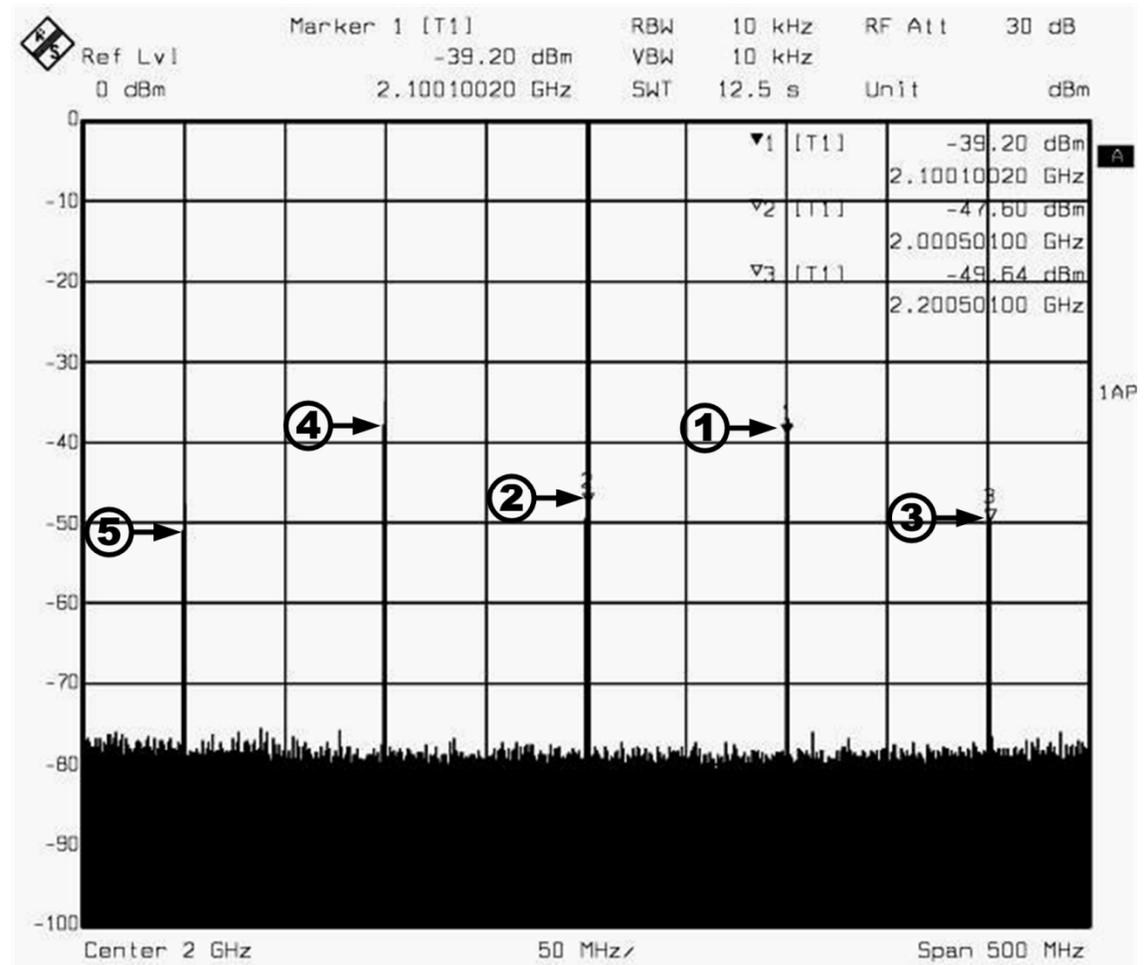- $P_{in} = -3.5\text{dBm}$ at 2GHz
- $f_{offset} = 100\text{MHz}$
→ $f_{out} = 2.1\text{GHz}$
- 25.8dB attenuation setting
- -9.9dB from buffer/cable losses
- $P_{out} = -39.2\text{dBm}$




Tuning and Frequency-Dependence

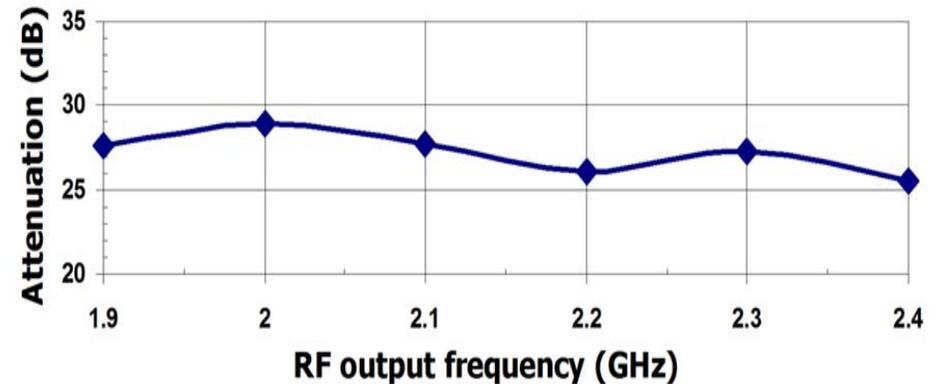- Attenuation vs. RF frequency →
 - Δ attenuation \approx 4dB (1.9- 2.4GHz)



- Tuning range

Control Mechanism	Attenuation
Discrete setting 1 (switched resistance value)	25.8dB
Discrete setting 2 (switched resistance value)	28.6dB
Discrete setting 3 (switched resistance value)	30.2dB
Control voltage (load transistor in triode region)	+ (0dB-11.3dB)
Combined	25.8dB-41.5dB

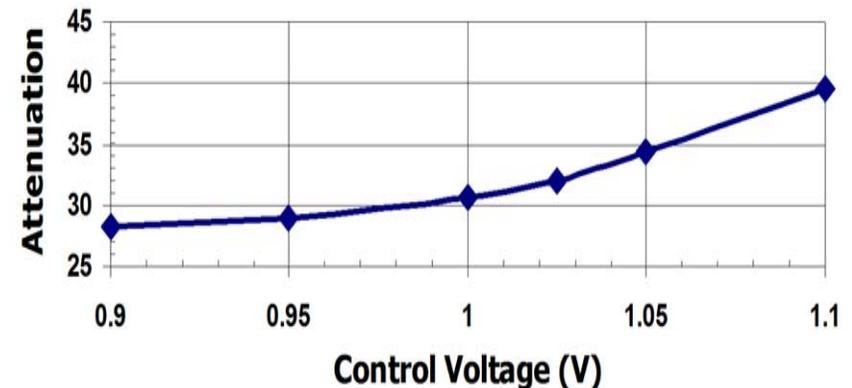

Continuous attenuation vs. control voltage
 ($P_{in} = -12.5$ dBm, $f_{RFout} = 2.1$ GHz)

Summary: On-Chip Loopback Method


- Application-specific design constraints for the offset mixer
 - Location between PA and LNA
 - Low-frequency digital offset signal
 - Minimal complexity→ Influenced the construction of the topology
- The proposed loopback topology provides continuous attenuation control and offset mixing for transceivers in the 1.9-2.4GHz range
- Design margin for gain discrepancies due to PVT variations is critical

Outline – Lecture 1

- Introduction
 - Course overview
 - Greetings from Northeastern University
- CMOS process variation
 - Trends
 - Impacts
- System-level calibration trends
 - Systems-on-a-chip examples (receivers, transceivers)
- Production test simplification and cost reduction
 - Example: loopback testing
- **Built-in testing of analog circuits**
 - **Introduction**
 - **On-chip power detection**
 - **RF LNA built-in testing example**

Analog Built-In Testing

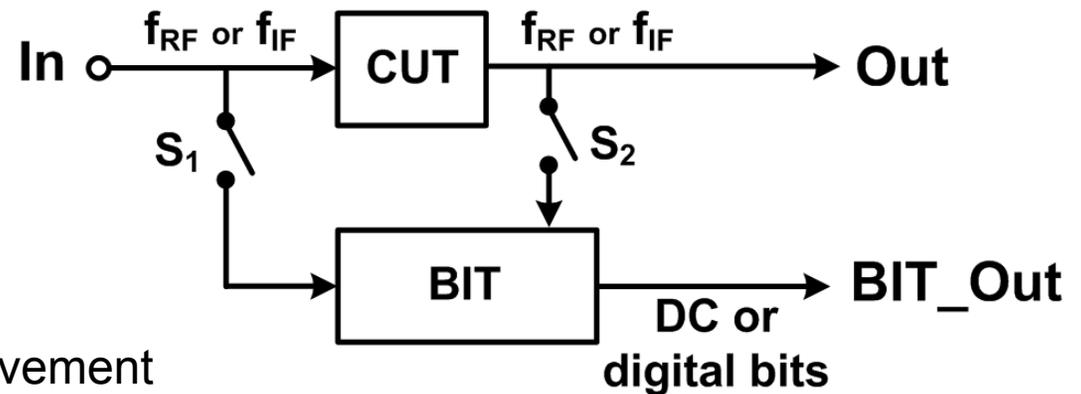- Goal: on-chip extraction of performance parameters
 - Improved fault coverage
 - Enables tuning






- Benefits
 - Performance and yield improvement
 - Manufacturing test time and cost reduction
- Trade-offs
 - Possible loading effects on circuit under test (CUT)
 - Die area requirement
 - Power dissipation (particularly critical in online testing)


Built-In Test (BIT) Approaches

- Supply current sensing
 - Oscillation-based testing
 - Use of on-chip peak/power/RMS detectors
 - Spectral analysis (on-chip FFT in DSP)
 - Analog instrumentation (e.g., on-chip analog spectrum analyzer)
 - ...
- Commonality: BIT results must be correlated with specifications!

Envisioned On-Chip Calibration Example

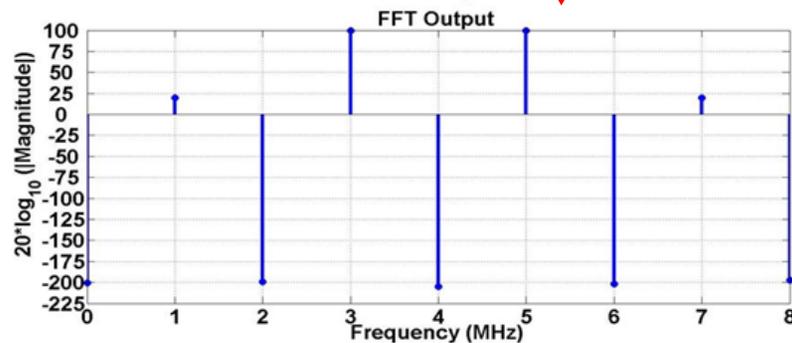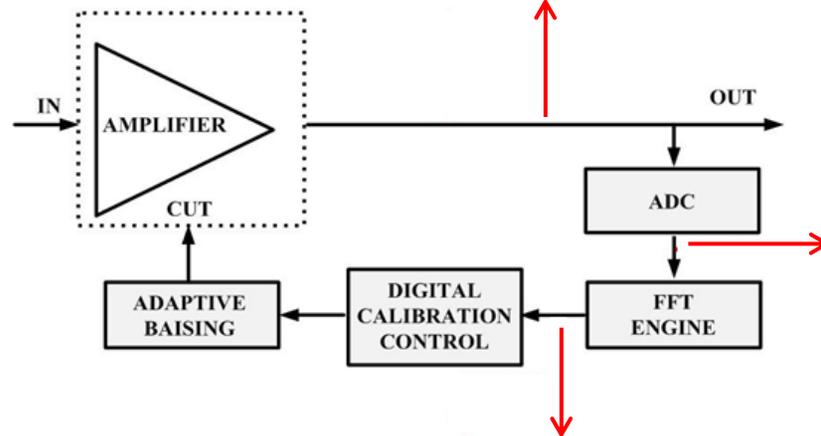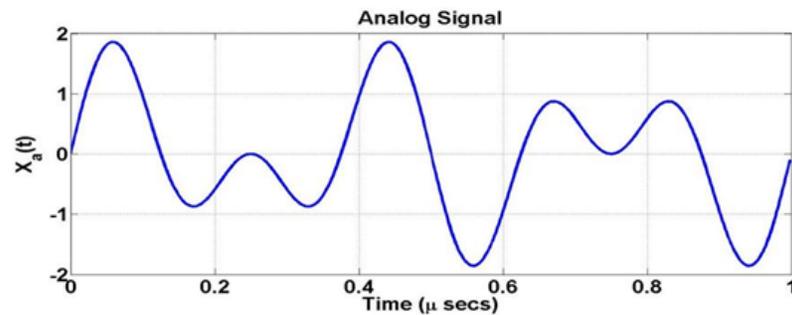


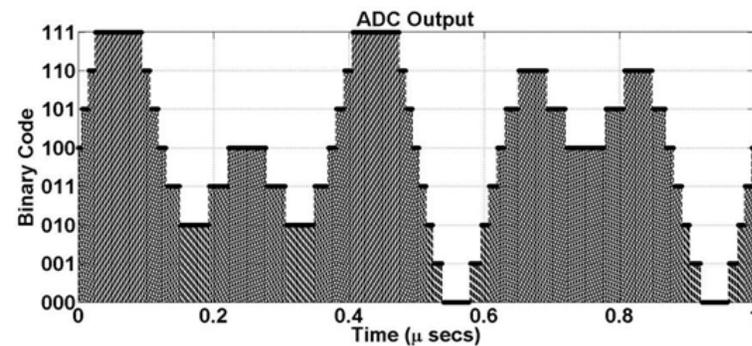- Based on on-chip FFT engine and digitally tunable analog blocks
- Project started at Northeastern University




- For low-frequency (<50MHz) appl.
- Focus: FFT area and power minimization

On-Chip Peak/Power/RMS Detectors

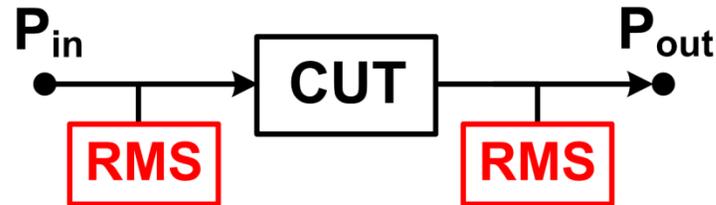


- Applications
 - Built-in testing
 - Received signal strength indicators (RSSIs)
- Design consideration
 - Gain
 - Linearity (1dB compression)
 - Input impedance matching
- Often used at RF frequencies when direct digitization of the signals is not feasible

Power Detectors for RF Built-In Testing

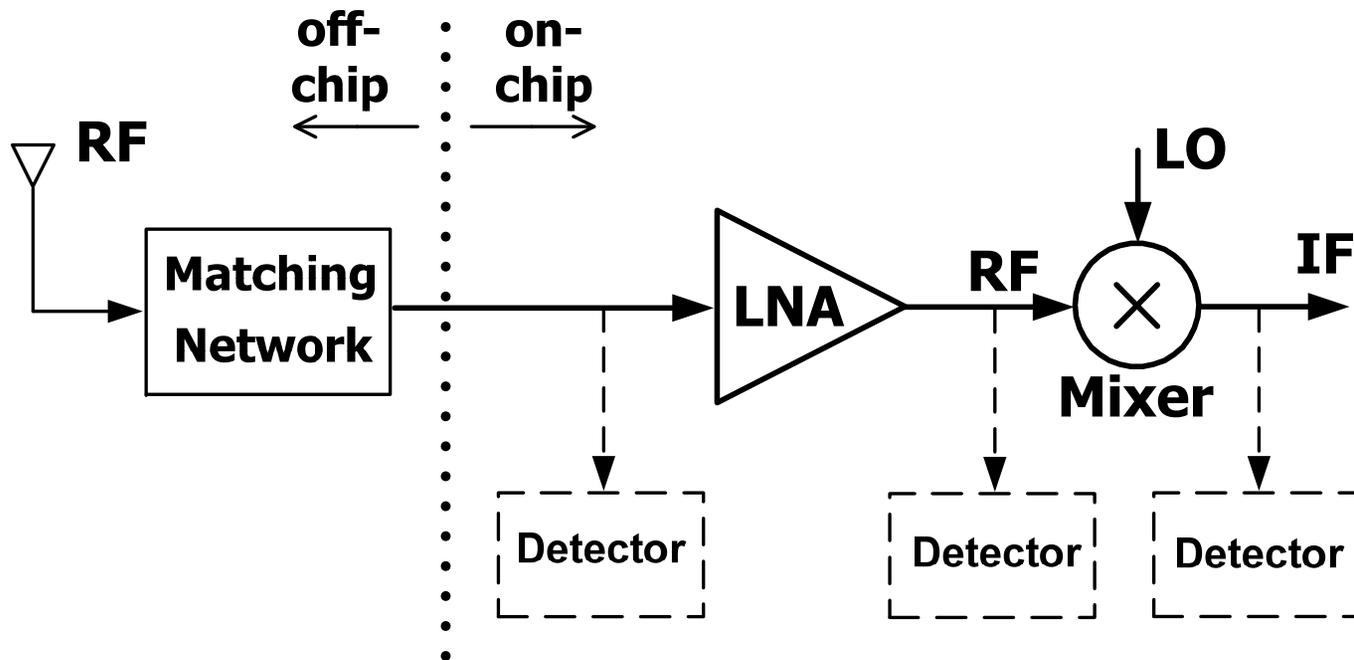


- Benefits
 - On-chip block-level characterization information
 - Analog local tuning loops for fast coarse calibration
 - Direct RF signal measurements without DSP (avoiding difficult high-speed digitization)

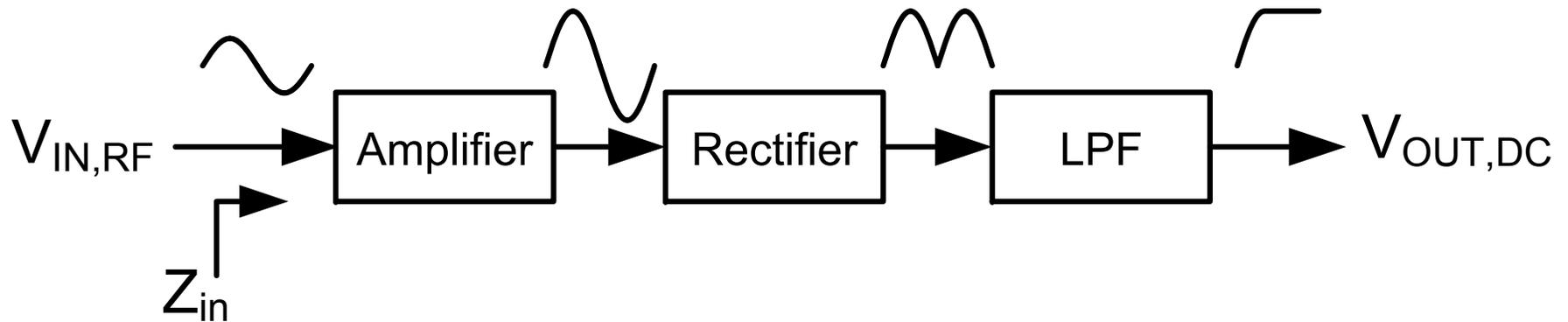Basic Root-Mean-Square (RMS) Detection Concept



- Desired power detector characteristics:
 - High input impedance
 - Small die area
 - Large dynamic range
 - Wide input frequency range

Input Impedance Considerations

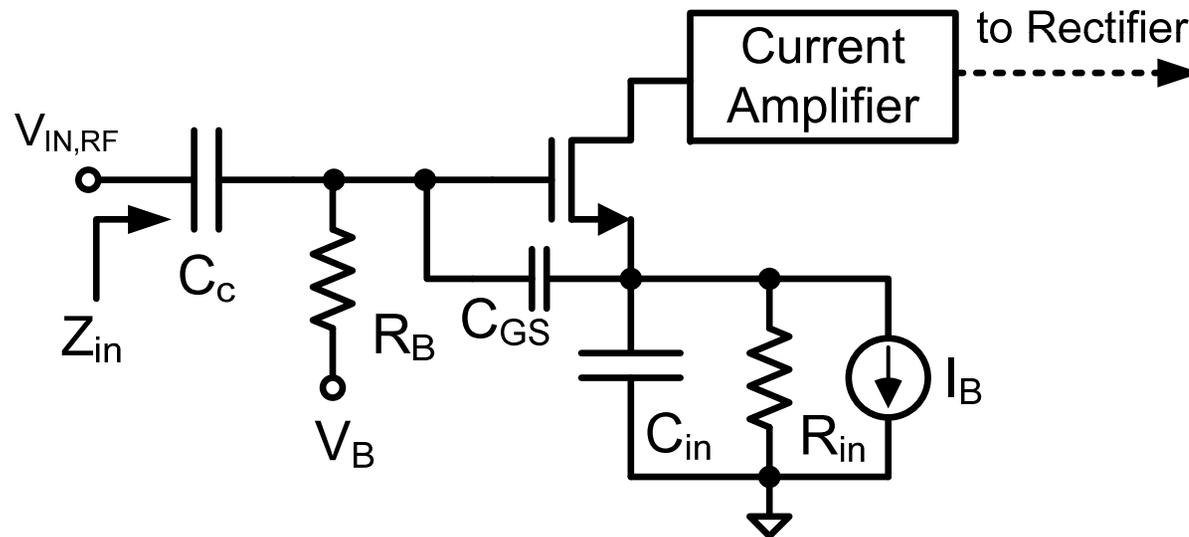

$$Z_{in} = \frac{1}{sC_c} + R_B \parallel \left[\frac{1}{sC_{gs}} + \frac{R_{in}}{1 + sR_{in}C_{in}} \left(1 + \frac{g_m}{sC_{gs}} \right) \right]$$

- Z_{in} reduction at RF frequencies
 - Due to input device capacitances
- Input transistor dimensions should be minimized

RMS Detector Example Circuit


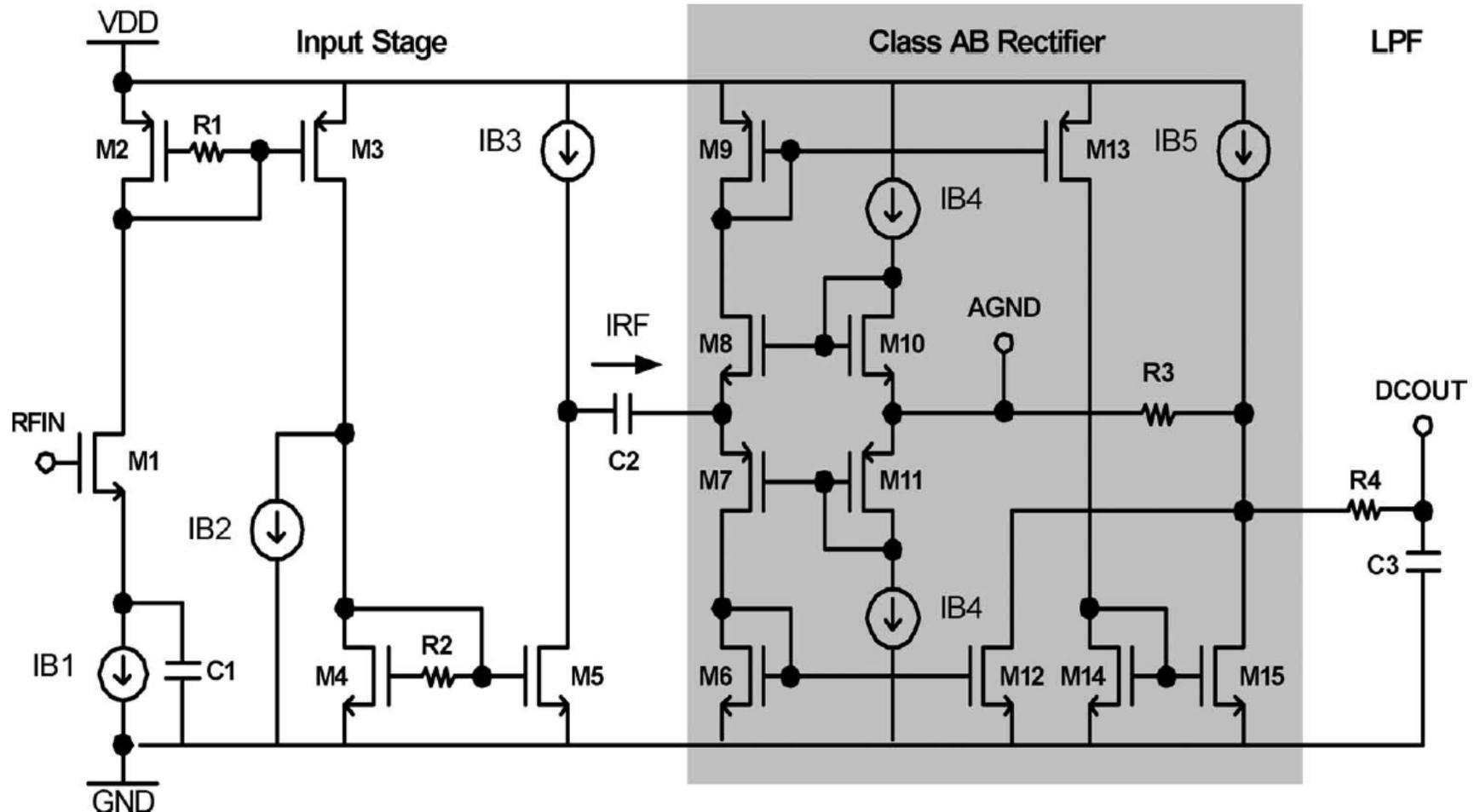


Figure from:

A. Valdes-Garcia, R. Venkatasubramanian, J. Silva-Martinez, and E. Sánchez-Sinencio, "A broadband CMOS amplitude detector for on-chip RF measurements," *IEEE Trans. Instrum. Meas.*, vol. 57, no. 7, pp. 1470–1477, Jul. 2008.


Example RMS Detector Characteristics

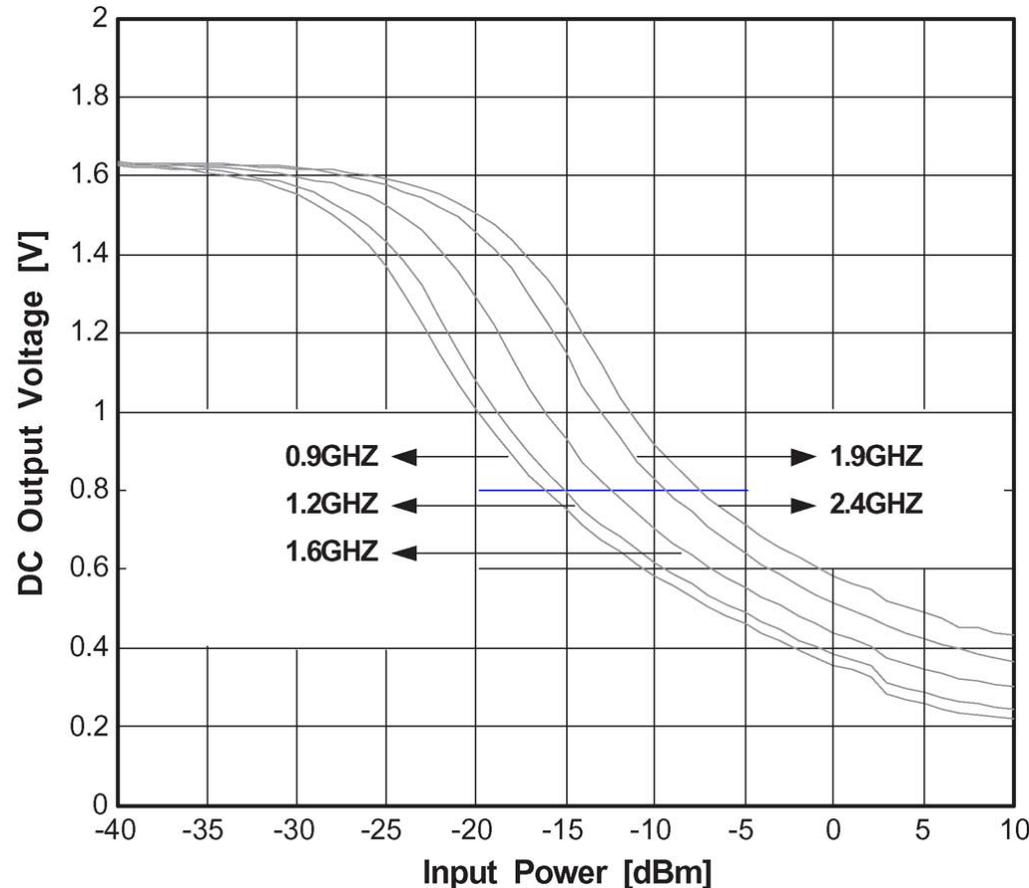


Measured DC output voltage vs. RF input power at several frequencies

- Conversion gain:
50mV/dBm
- Settling time:
40ns
- Dynamic range:
30dB

Gain & 1dB-Compression Measurements

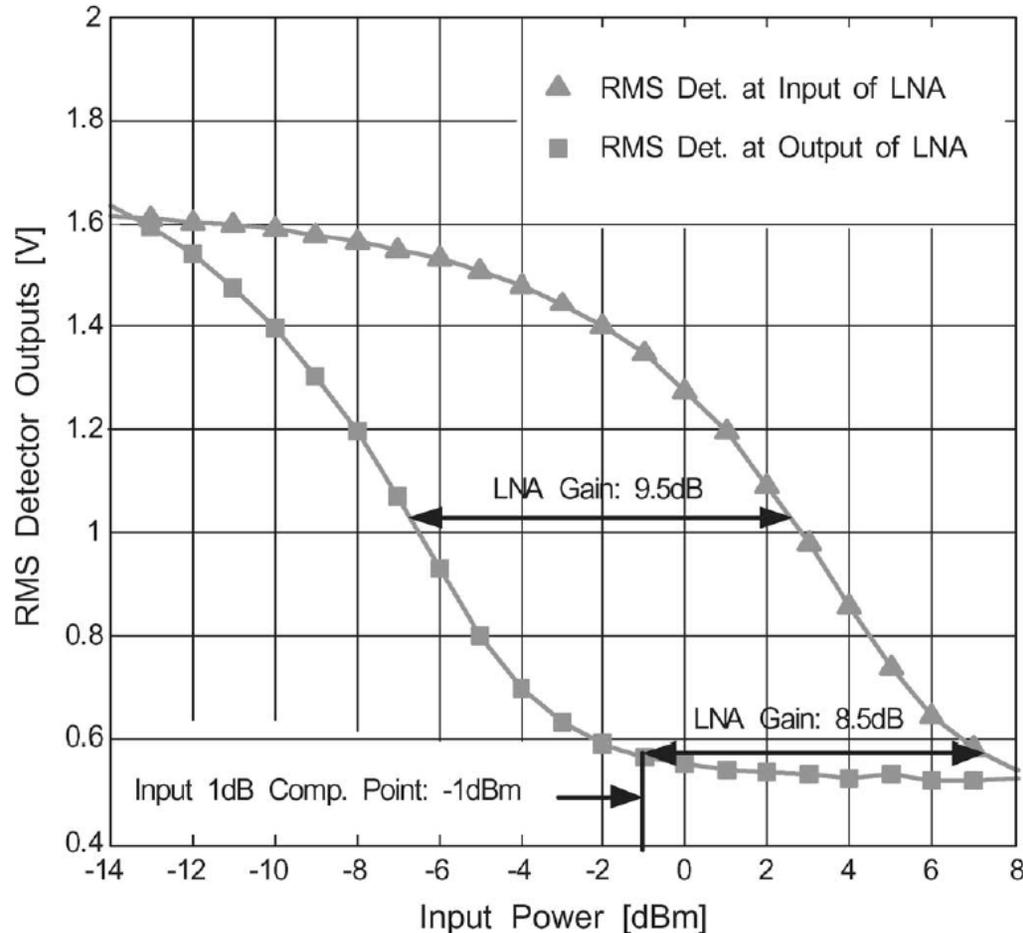

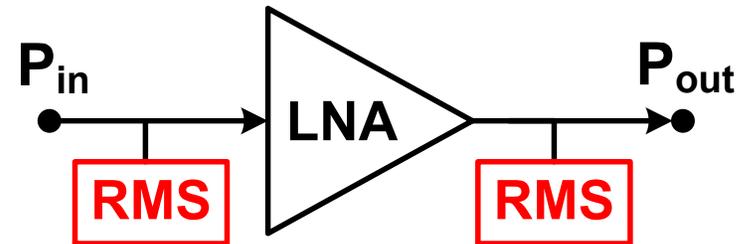Measured response of the RF detectors at the input and output of the LNA



Accuracy: ~1dB

Detector Performance Examples

Reported Measurement Results:

Reference	[1]	[2]	[3]	[4]
Technology	0.25 μ m BiCMOS	0.35 μ m CMOS	0.18 μ m CMOS	0.18 μ m CMOS
Area	-	0.031mm ²	0.06mm ²	-
Dynamic Range	40dB	> 30dB	> 25dB	~10dB
Min. Detectable Signal	~ -40dBm	-25dBm	-15dBm	50mV
Operating Frequency	1.3GHz	0.9 – 2.4GHz	5.2GHz	2.5GHz
Power	< 1mW	8.6mW	3.5mW	-

- [1] Q.Yin, W. R. Eisenstadt, R. M. Fox, and T. Zhang, "A translinear RMS detector for embedded test of RF ICs," *IEEE Trans. Instrum. Meas.*, vol. 54, no. 5, pp. 1708–1714, Oct. 2005.
- [2] A. Valdes-Garcia, R. Venkatasubramanian, J. Silva-Martinez, and E. Sánchez-Sinencio, "A broadband CMOS amplitude detector for on-chip RF measurements," *IEEE Trans. Instrum. Meas.*, vol. 57, no. 7, pp. 1470–1477, July 2008.
- [3] H.-H. Hsieh and L.-H. Lu, "Integrated CMOS power sensors for RF BIST applications," in *Proc. IEEE VLSI Test Symp.*, May 2006, pp. 229-233.
- [4] F. Jonsson and H. Olson, "RF detector for on-chip amplitude measurements," *Electron. Letters*, vol. 40, no. 20, pp. 1239-1240, June 2004.



RF Built-In Testing with Current Injection

Team at Texas A&M University:

Xiaohua Fan

Marvin Onabajo


Edgar Sánchez-Sinencio

Jose Silva-Martinez



RF LNA Built-In Testing Example

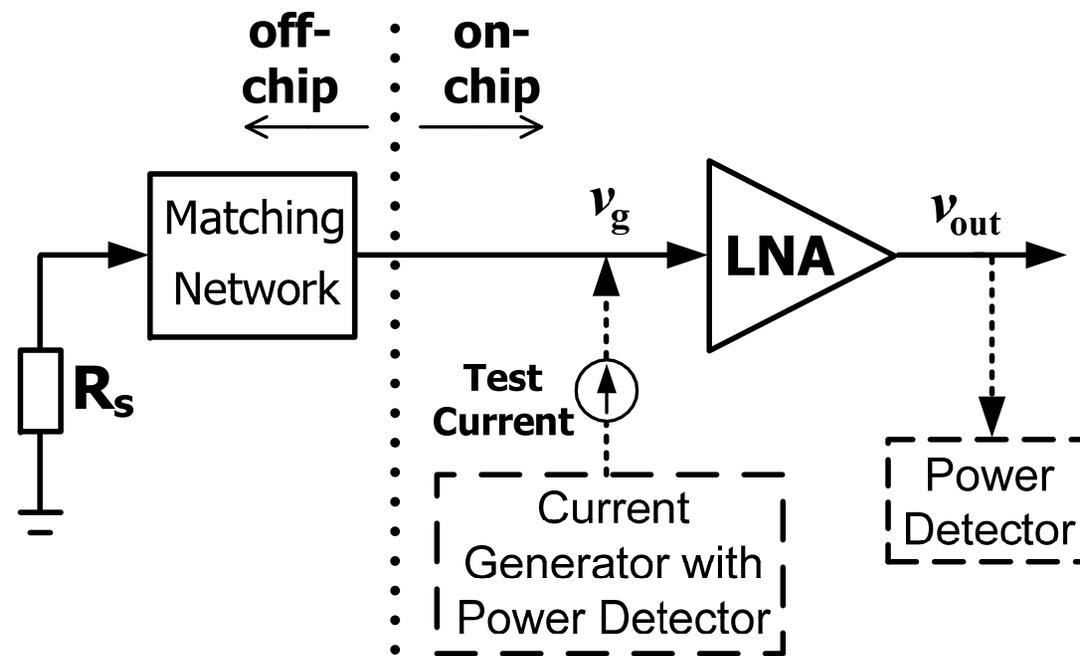
- Input impedance measurements with on-chip power detectors
 - Detection of faults in the off-chip matching network
 - Suitable for final in-package/board-level test stages



X. Fan, M. Onabajo, F. O. Fernández-Rodríguez, J. Silva-Martinez, and E. Sánchez-Sinencio, "A current injection built-in test technique for RF low-noise amplifiers," *IEEE Trans. Circuits and Systems I: Regular Papers*, vol. 55, no. 7, pp. 1794-1804, Aug. 2008.

Current Injection Testing Theory

Thévenin-Norton transformation:

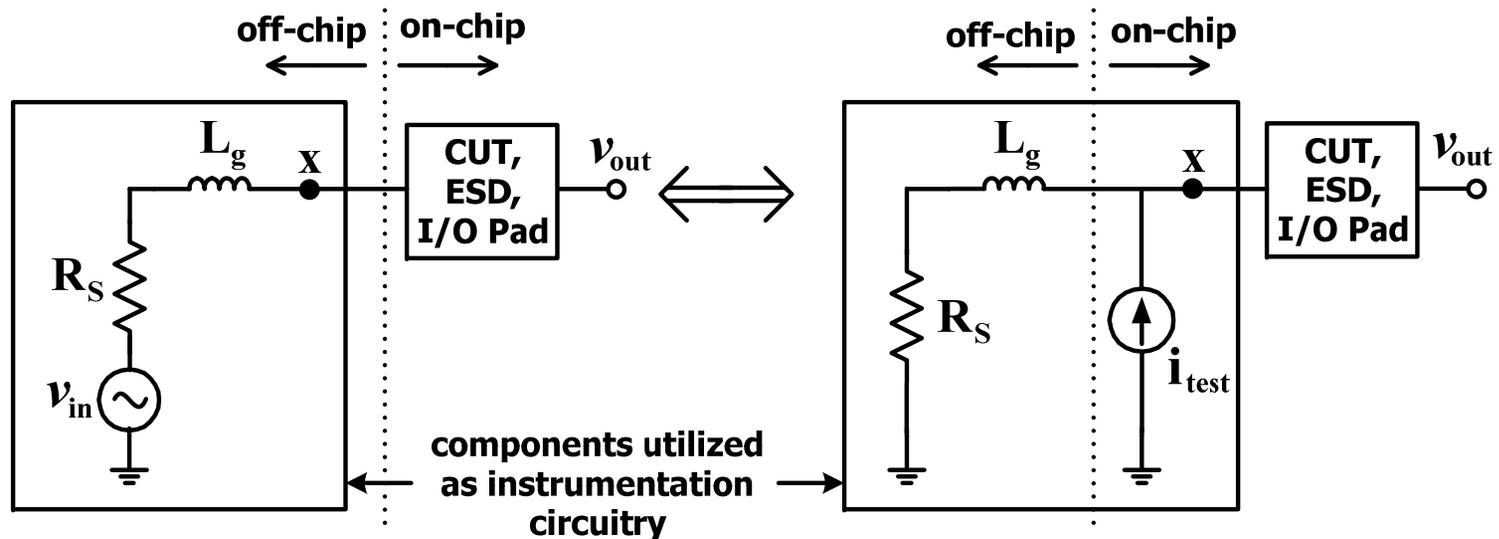

- Voltage gain determination with sensitivity to R_s/L_g


- part of the test interface hardware
→ well-controlled variation, or:

- under test (external matching network)
→ sensitivity allows fault detection

$$v_{in} = i_{test} \times (R_s + j\omega L_g)$$

$$G = \frac{v_{out}}{v_{in}} = \left(\frac{1}{R_s + j\omega L_g} \right) \left(\frac{v_{out}}{i_{test}} \right)$$

Current Injection Test Example

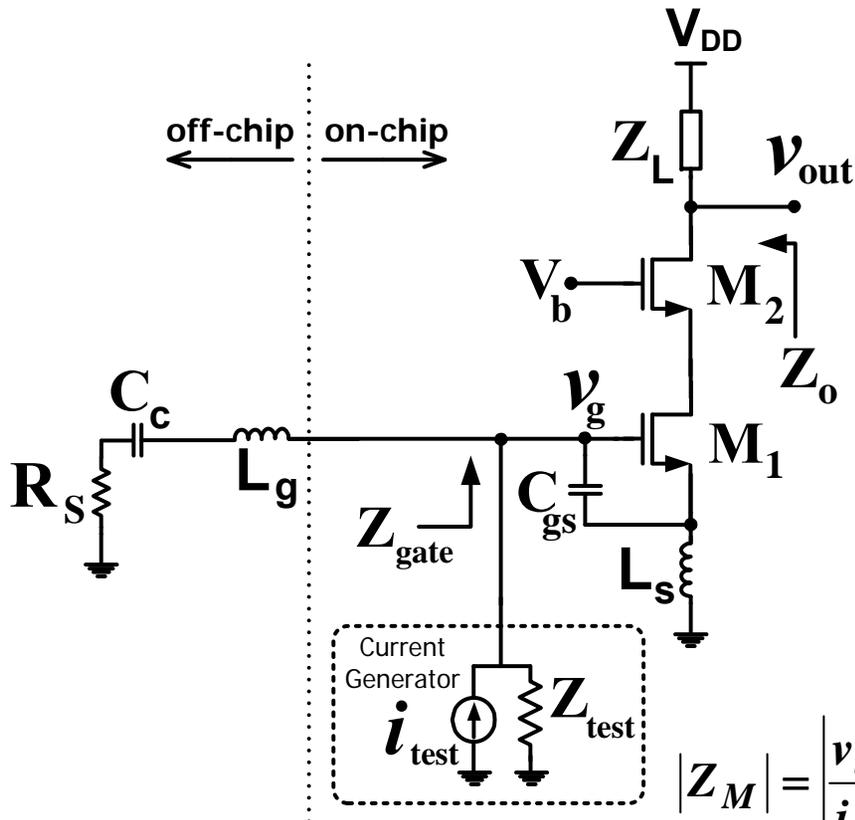

- To avoid impact on impedance matching:
 $Z_{\text{test}} \gg Z_{\text{gate}}$
- Measurement with power detectors:
 $|Z_M| = |v_{\text{out}}/i_{\text{test}}|$


Transimpedance gain:

$$|Z_M| = \left| \frac{v_{\text{out}}}{i_{\text{test}}} \right| = \frac{\left(\frac{1}{\omega C_{gs}} \right) \left(\sqrt{R_s^2 + (\omega L_g)^2} \right) (g_{m1} |Z_o|)}{\sqrt{\left(R_s + g_{m1} \frac{L_s}{C_{gs}} \right)^2 + \left(\omega(L_g + L_s) - \frac{1}{\omega C_{gs}} \right)^2}}$$

Voltage gain estimation:

$$|G| = \left| \frac{v_{\text{out}}}{v_{\text{in}}} \right| = \frac{|Z_M|}{\sqrt{R_s^2 + (\omega L_g)^2}}$$

Current Generator Circuit

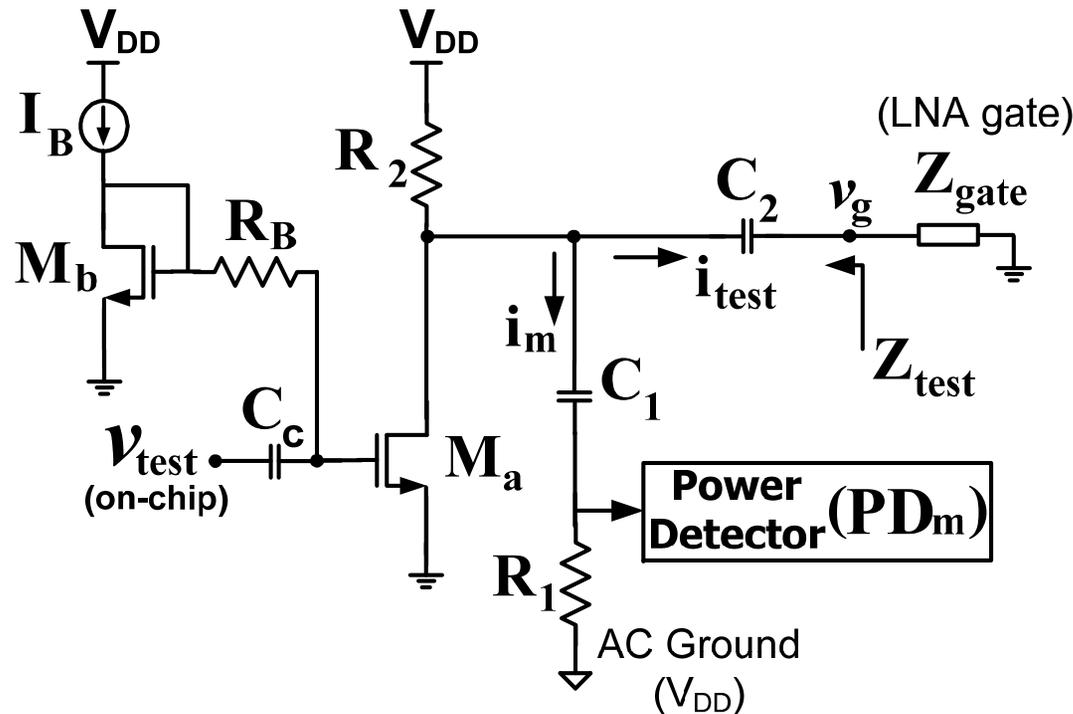

- Designed with:
 - $C_1 = m \cdot C_2$
 - $|1/j\omega C_2| \gg Z_{gate}$
 - $i_m/i_{test} \approx m$
- Indirect measurement of i_{test} with R_1 and i_m

Layout area (without PD_m): 0.002mm^2

$$\frac{i_m}{i_{test}} = \frac{Z_{gate} + \frac{1}{j\omega C_2}}{R_1 + \frac{1}{j\omega C_1}} = m \times \left(\frac{Z_{gate} + \frac{1}{j\omega C_2}}{mR_1 + \frac{1}{j\omega C_2}} \right)$$

- $Z_{test} \gg Z_{gate}$ avoids loading ($Z_{test} > 1.1\text{k}\Omega$ for $f < 2.4\text{GHz}$)


Post-Layout Simulation Results

Voltage-mode gain estimation:

$$G_{V,dB} = 20 \log \left(\frac{V_{out_rms}}{V_{g_rms}} \times \frac{\sqrt{50^2 + (\omega \times 8.1e^{-9})^2}}{2 \times 50} \right) + 6$$

Current-mode gain estimation (error < 1dB):
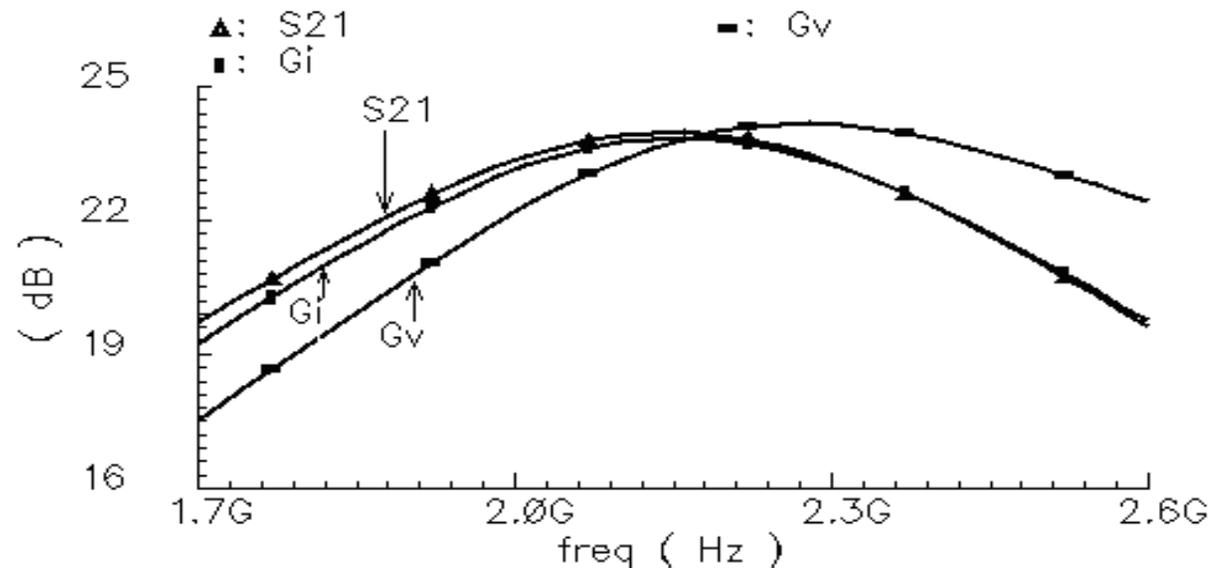
$$G_{I,dB} = 20 \log \left(250 \frac{V_{out_rms}}{V_{m_rms}} \right) - 10 \log(50^2 + (\omega \times 8.1e^{-9})^2) + 6$$



Simulated comparison of S_{21} with G_v and G_i



Thank You.