

High linearity, Low cost SAW-less Radios

Jose Silva-Martinez

Slides provided by H. Mohan Geddada


Texas A&M University



Outline

- Introduction
- Broadband LNAs with non-linearity cancellation
- Fully balanced LNTAs with $P_{1\text{dB}} > 0\text{dBm}$
- A 12 bit, 20MHz, C.T $\Delta\Sigma$ ADC
- Active Antenna
- Conclusions


Introduction

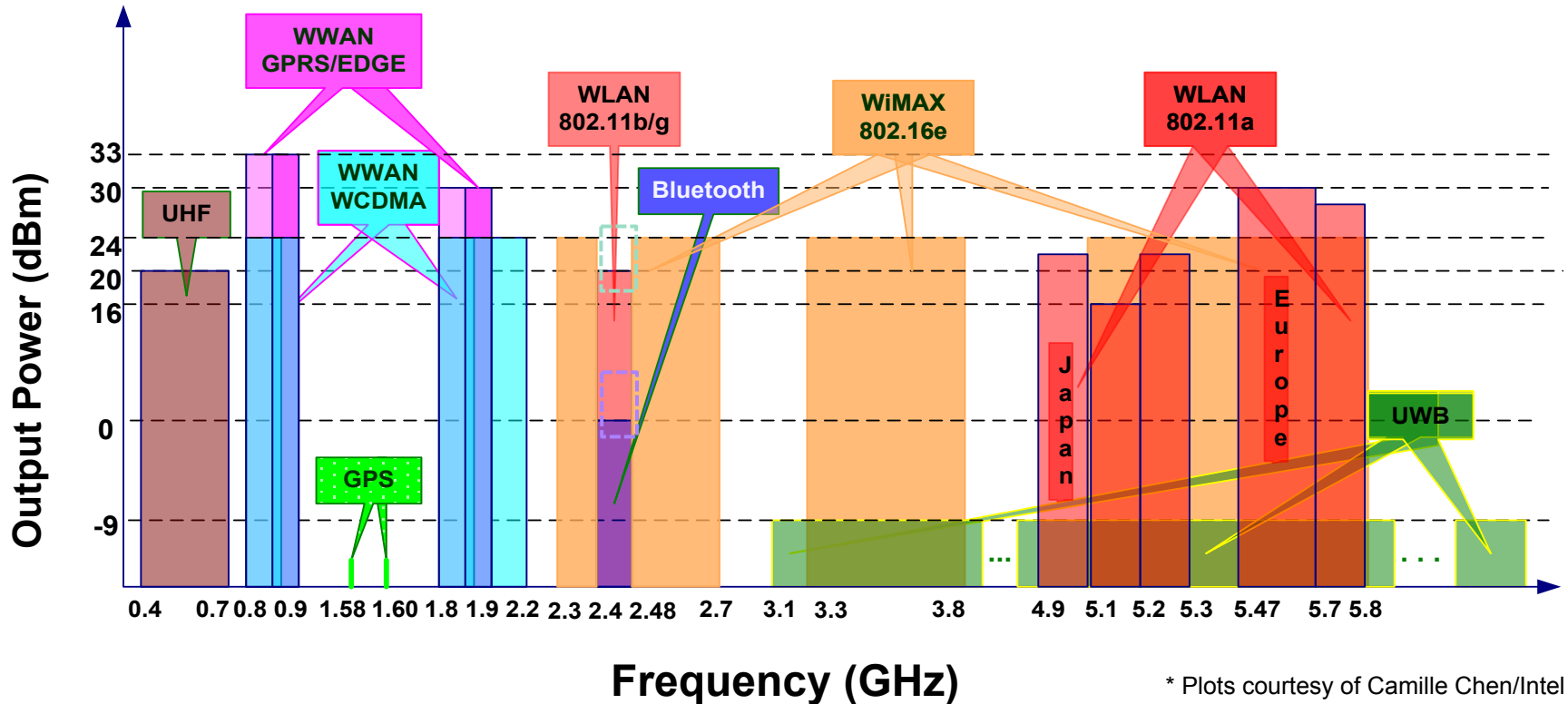

Low cost radio receivers for multi standard co-existence

- Low cost: SAW-less and Inductor-less solution.
- High linearity receivers to deal with strong out-of-band interferers

Targeted system

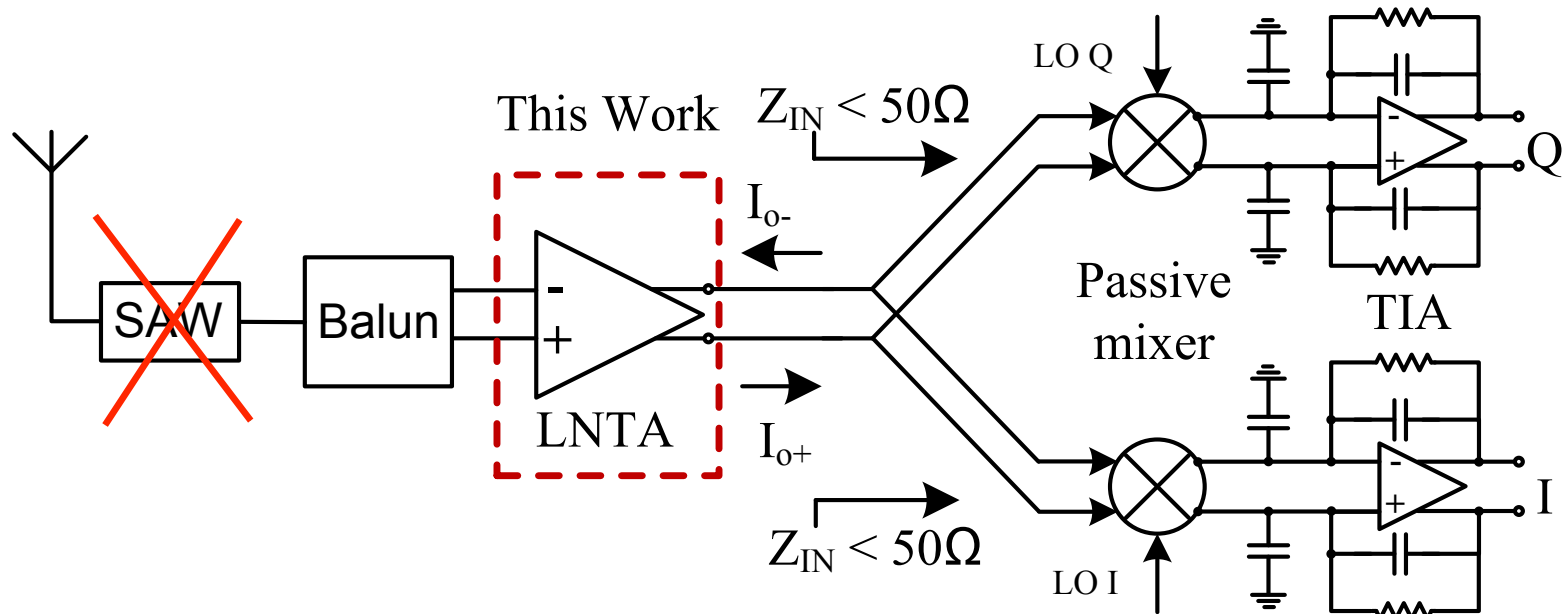

Direct Conversion Receiver Architecture:

Better performance in terms of noise, linearity and power consumption.


Linearity bottleneck \rightarrow LNTA

Broadband CMOS LNAs with Nonlinearity Cancellation

Hemasundar M Geddada¹, José Silva-Martínez¹, and
Stewart S. Taylor²

¹Texas A&M University

²Intel Corporation

 


Outline

- Introduction
- State of the Art
- Proposed Derivative superposition
- Noise and distortion cancellation LNA
- Experimental results
- Conclusions

LNA Linearity Analysis

**Broadband
LNA**

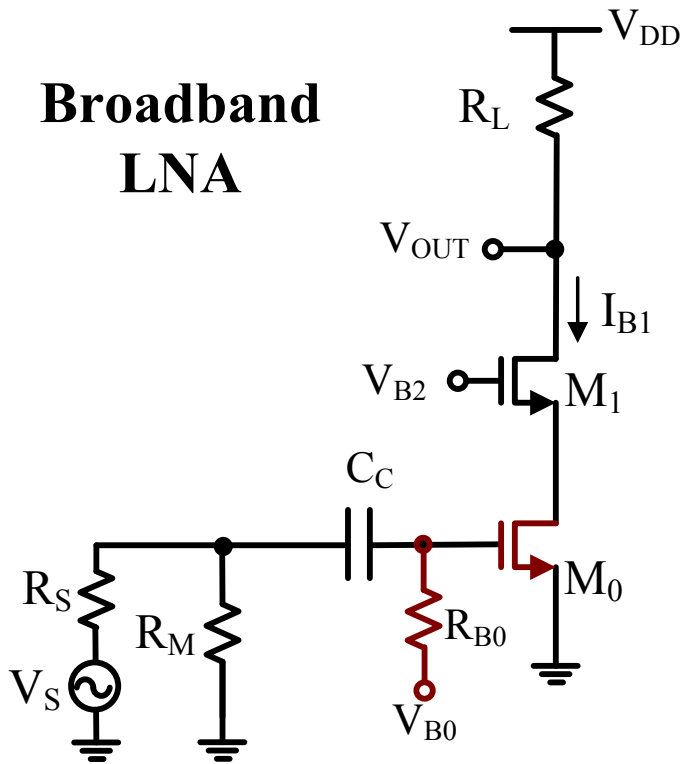



**Resistive terminated
LNA**

$$I_d = I_{B1} + g_m v_{gs} + \frac{g'_m}{2!} v_{gs}^2 + \frac{g''_m}{3!} v_{gs}^3 + \dots$$

$$g''_m = \partial^3 I_D / \partial V_{GS}^3$$

- A simple design for linearization technique path finding.
- Simplify the input matching network.
- g''_m is the dominant 3rd order distortion.



Characterization & observations

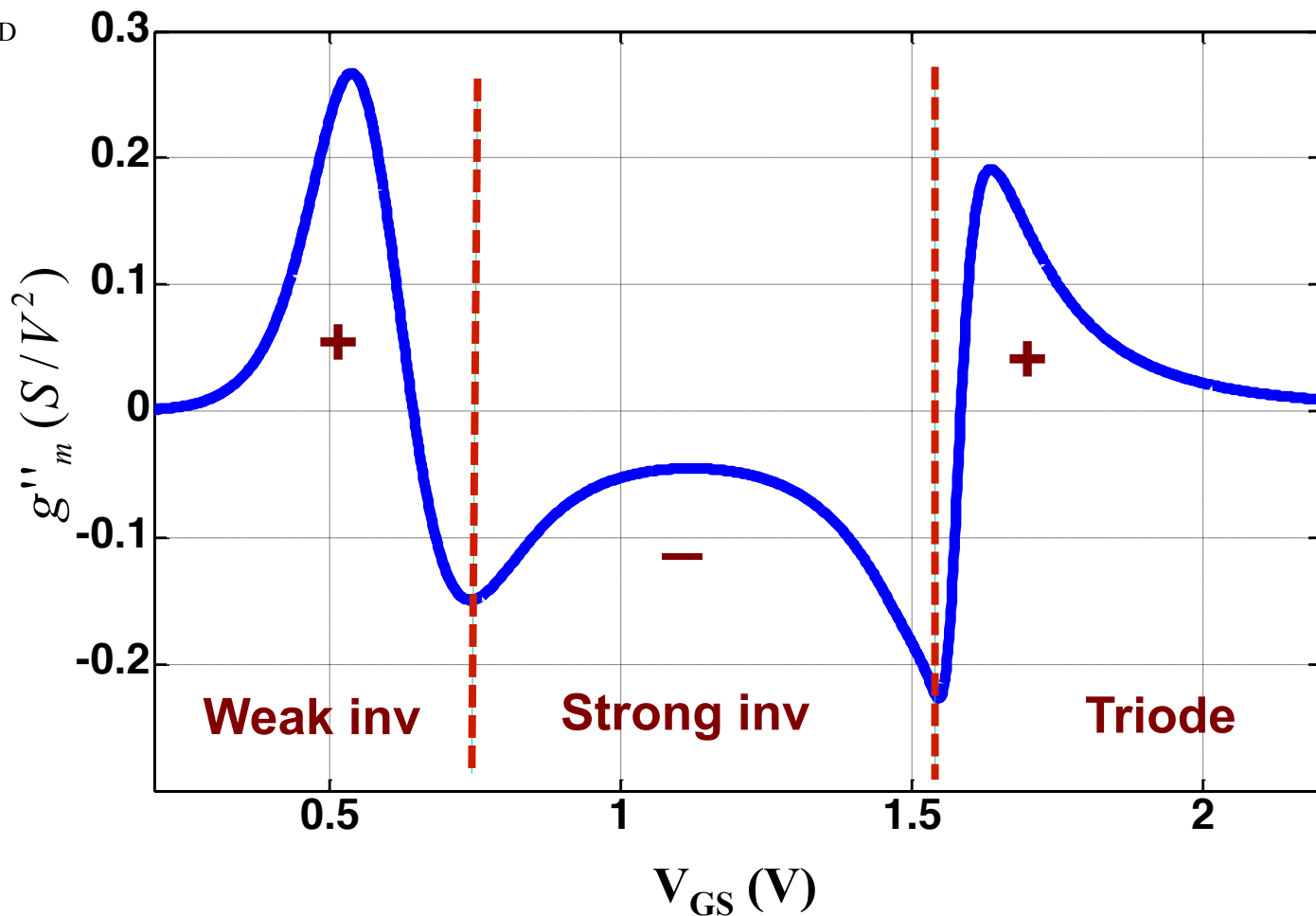 

$$g''_m = \partial^3 I_D / \partial V_{GS}^3$$

Previous work

➤ We want High g_m

  


➤ P.V.T. Sensitive

➤ Low g_m

➤ Good small signal linearity (IIP3), but Poor Large signal linearity (P_{1dB})


Previous work

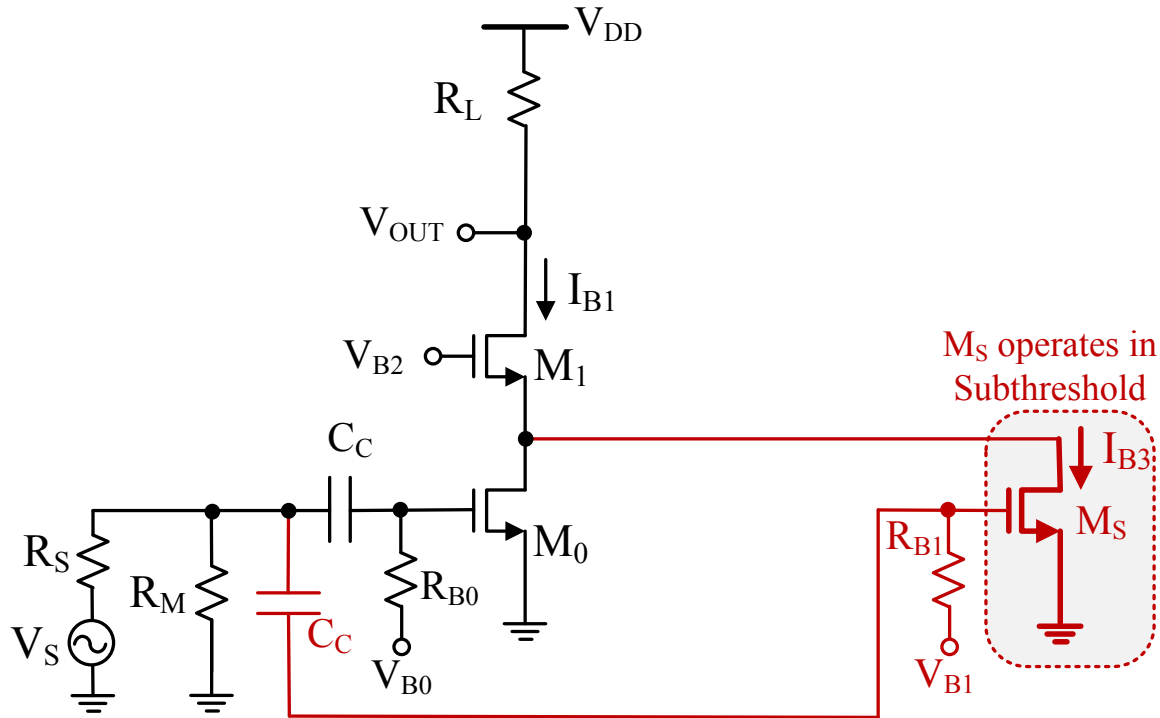

Derivative Superposition (DS):


- M_0 : Strong inversion
- M_S : Weak inversion

Previous work

 



➤ Poor Large signal linearity (P_{1dB})

Previous work

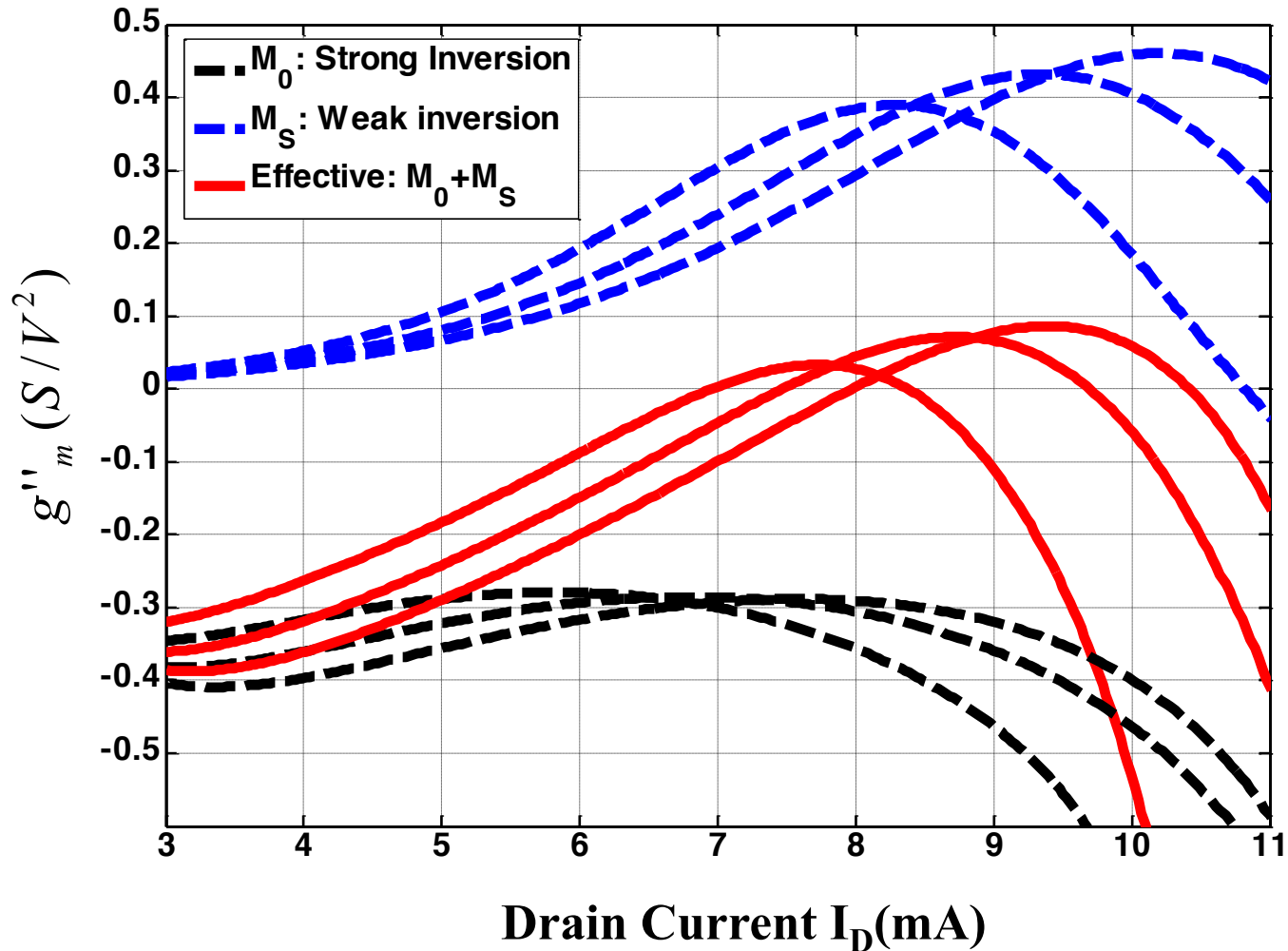


- Poor Large signal linearity
- P.V.T. sensitive

Re-visit Characterization: Fix V_{DS}

  

$$g''_m = \partial^3 I_D / \partial V_{GS}^3$$


Proposed Linearization Technique

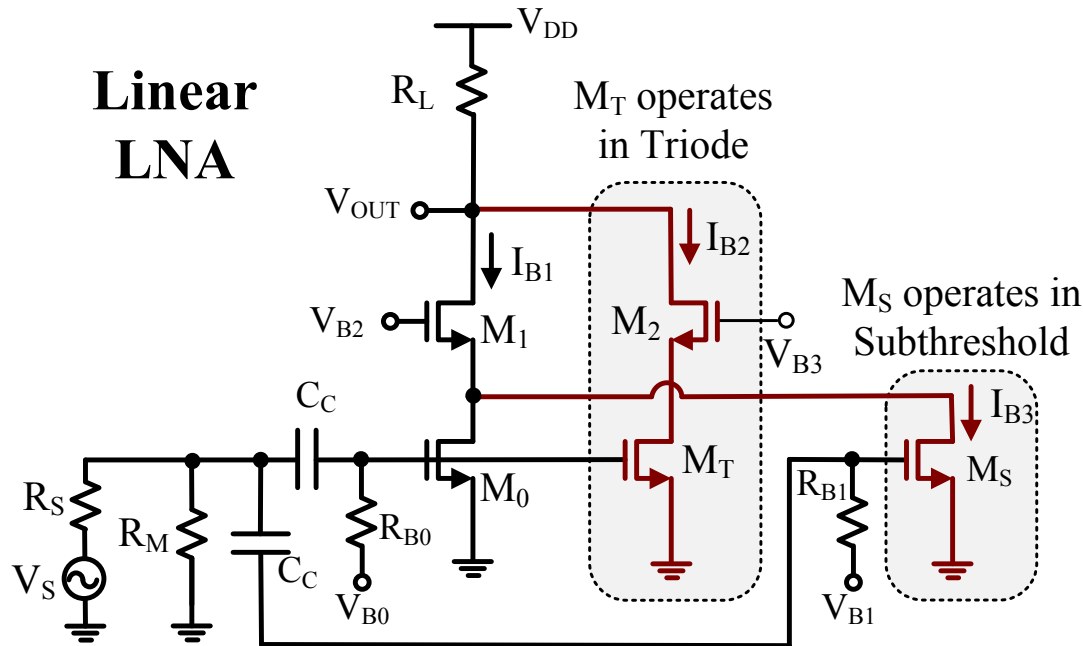

Robust Derivative Superposition (RDS):


	Region	g_m	g''_m
M_0	Strong Inversion	POS	NEG
M_S	Weak Inversion	POS	POS
M_T	Triode	POS	POS

Robust Derivative Superposition

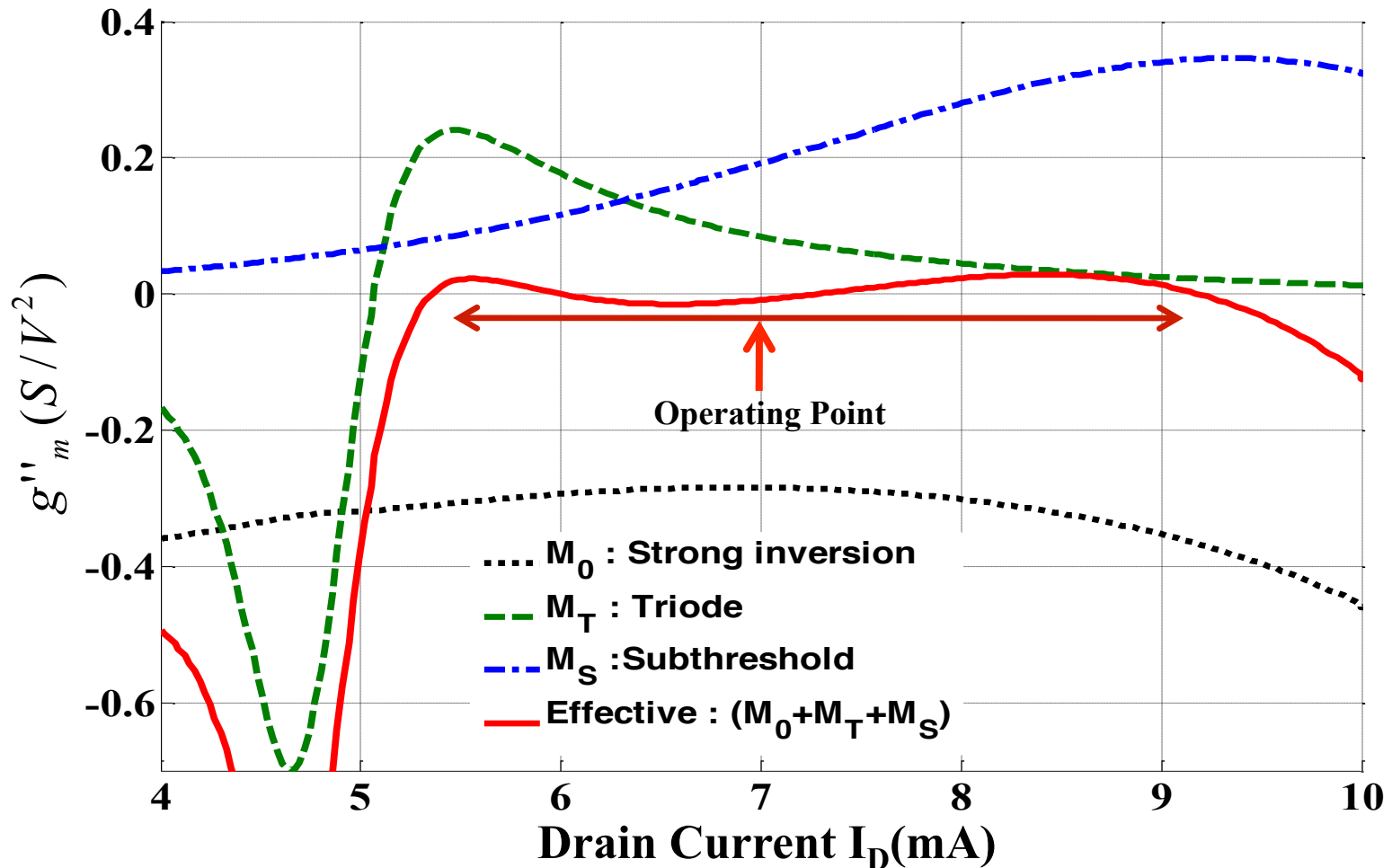


- **Wide range cancellation** of g_m'' → Good Large signal linearity
- Less P.V.T. sensitive

Robust Derivative Superposition

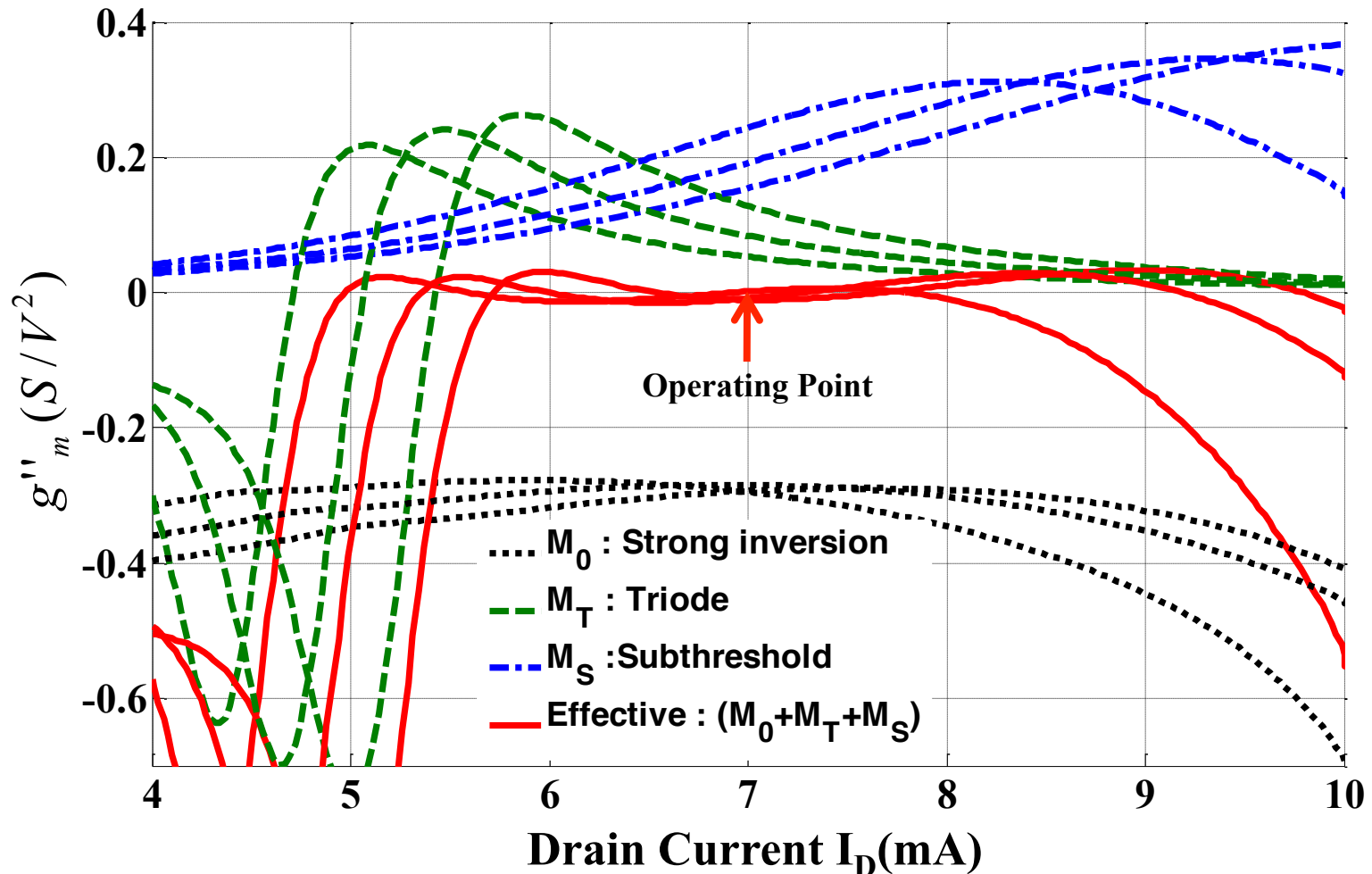


Good **wide range cancellation** of g_m'' at **various technology corners** → **P.V.T. insensitive**

Design Considerations of RDS

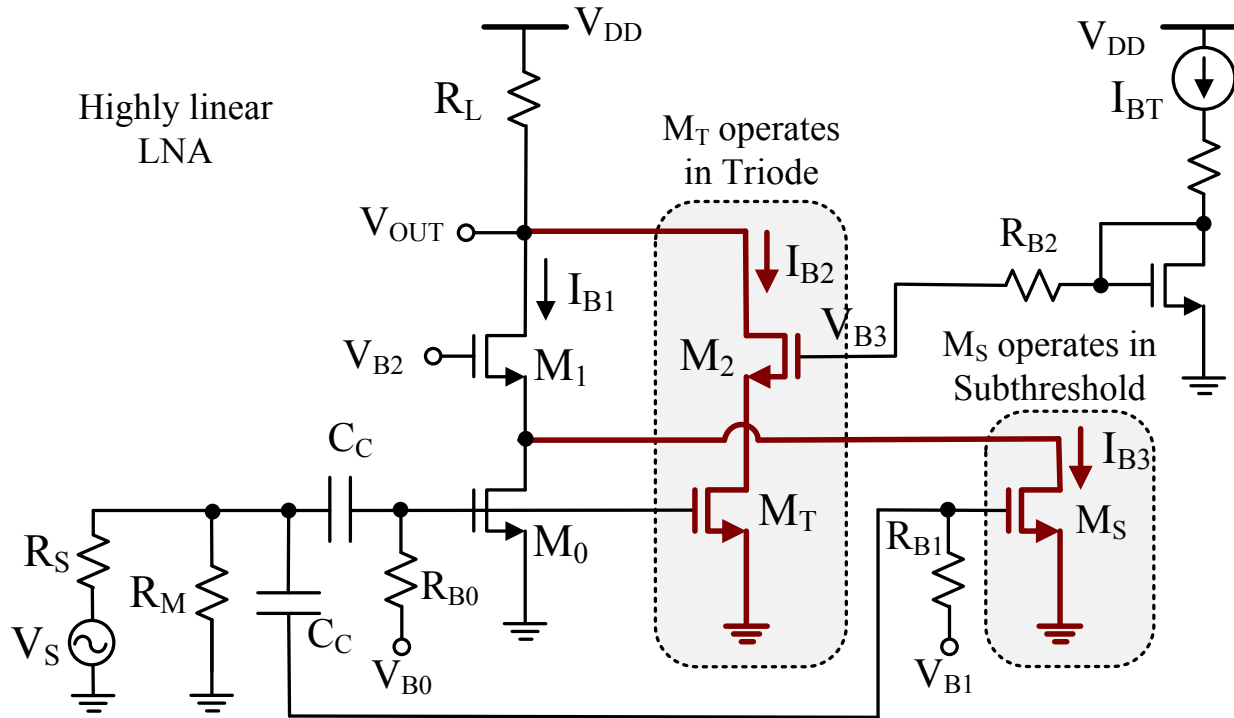

- Fixed V_{DS} of M_T for robust cancellation among corners.
- M_2 avoids output impedance degradation due to $M_T(r_{ds})$.
- Similar delays in main path and the auxiliary paths ensure accurate nonlinearity cancellation.

Advantages of RDS technique

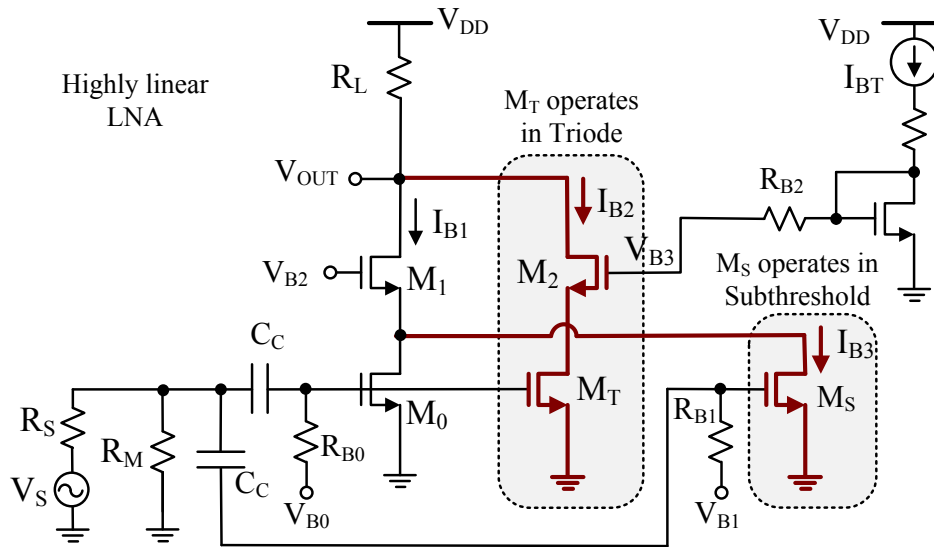


**Best Paper Award:
IEEE MWCAS-2011**

- Feed-forward compensation: **No stability problems**
- M_T and M_S are small transistors: **No BW limitation**
- $I_{B2} + I_{B3} < 8\%$ of I_{B1} : **Little power penalty**
- M_T shares C_C with the M_0 : **No additional coupling cap**

“Robust Derivative superposition Method for Linearizing Broadband LNAs,” H. M. Geddada, J. Won-Park and J. Silva-Martinez. IEE Electronics Letters, Vol. 45, pp. 435-436, April 2009.

Noise/distortion cancelling Balun-LNA

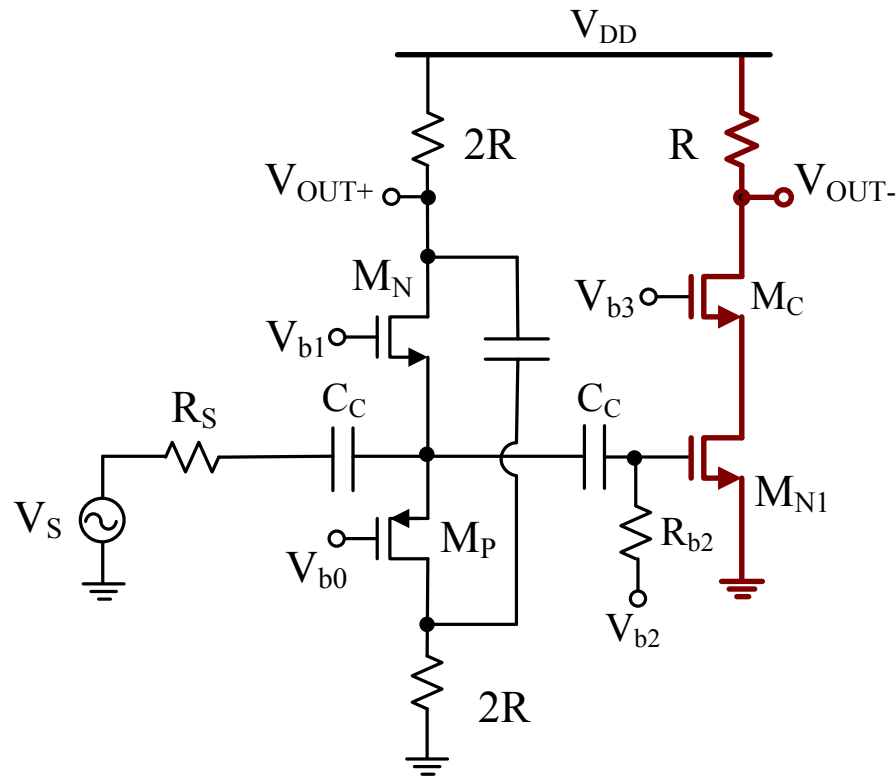


Blaakmeer et al
JSSC 2008

Common-gate common-source topology:


- Significant benefits such as balanced outputs as well as noise and distortion cancellation in the CG stage

Noise/distortion cancelling Balun-LNA

 


- Noise/distortion of M_N (MP) appears as common mode.
- Noise/distortion performance limited by the CS stage.
- Use RDS to improve the linearity of CS stage.

Noise/distortion Cancelling Balun-LNA

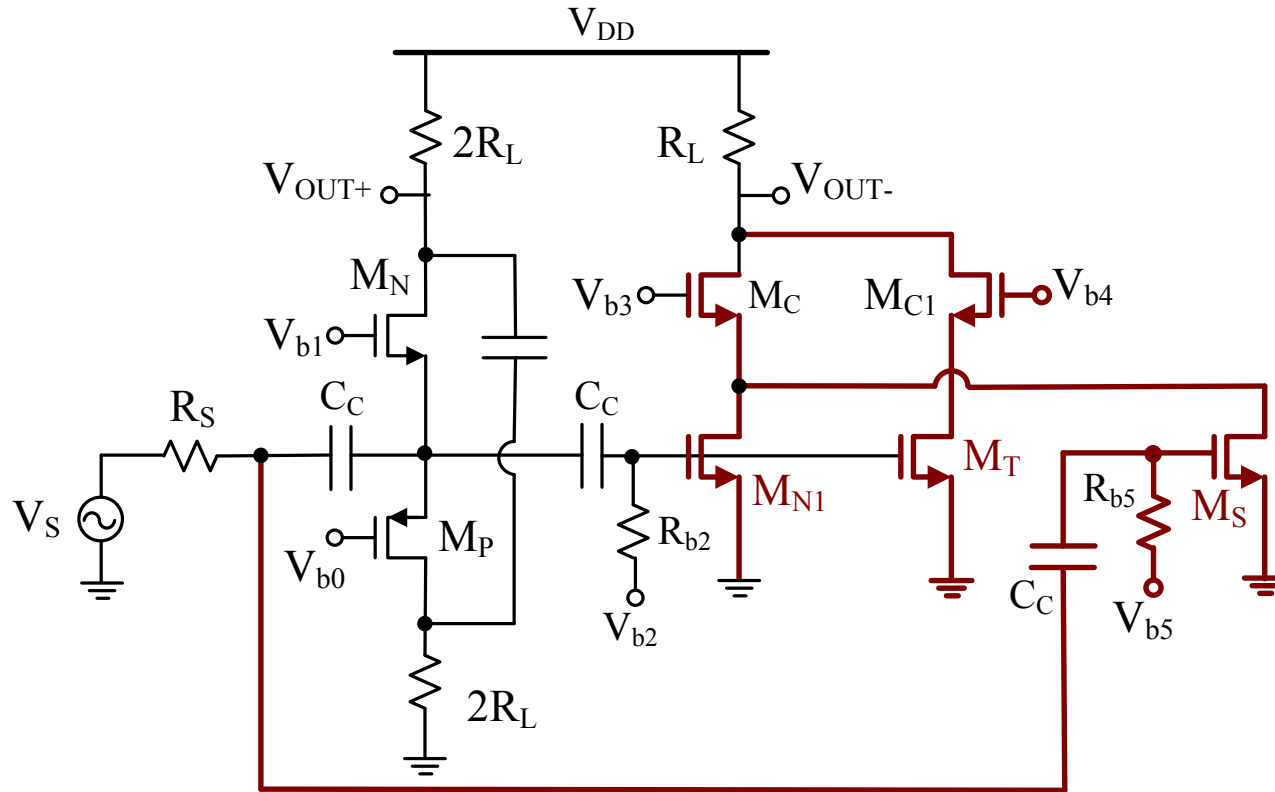

- Distortion in CS stage is reduced by R_{DS} .
- Power overhead $< 8\%$.
- Noise overhead < 0.1 dB.

Chip Microphotograph

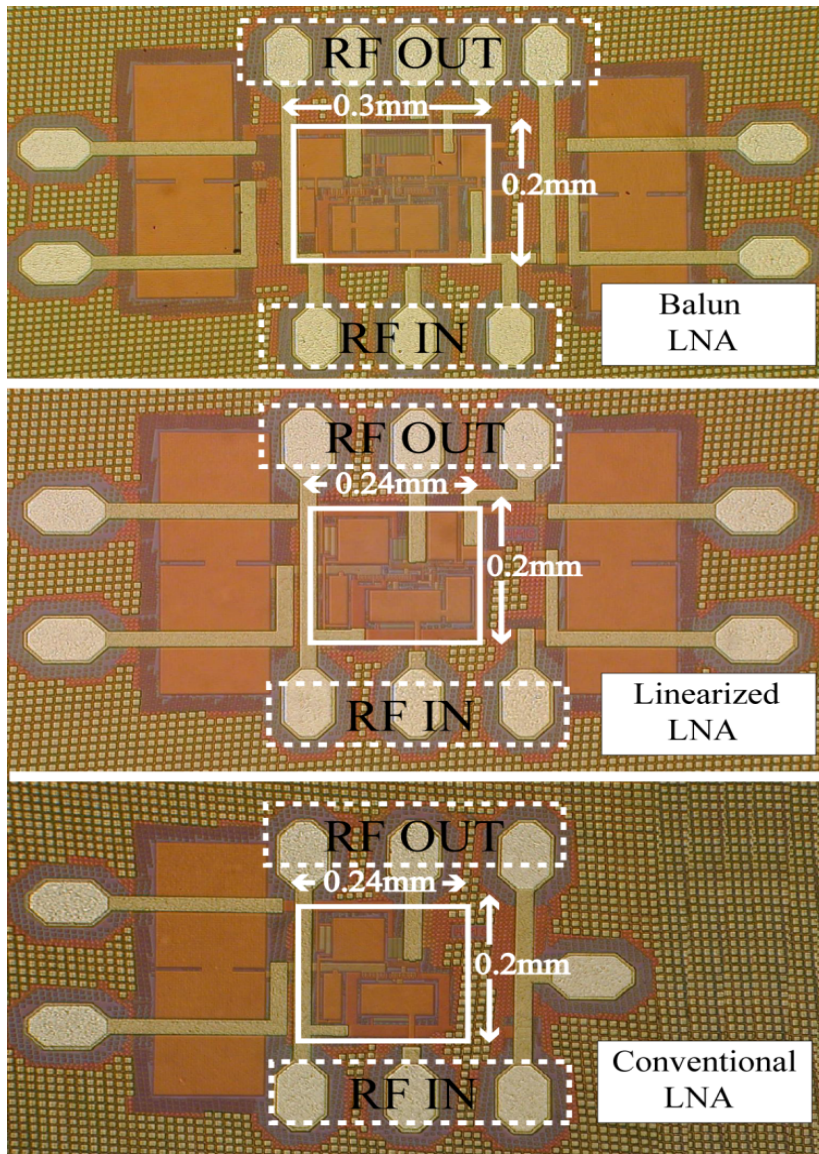


- Jazz 0.18um CMOS Tech..
- Wafer probing test.
- No output buffers.


Silicon area: 0.06 mm²

Measurement results

Test Setup for linearity

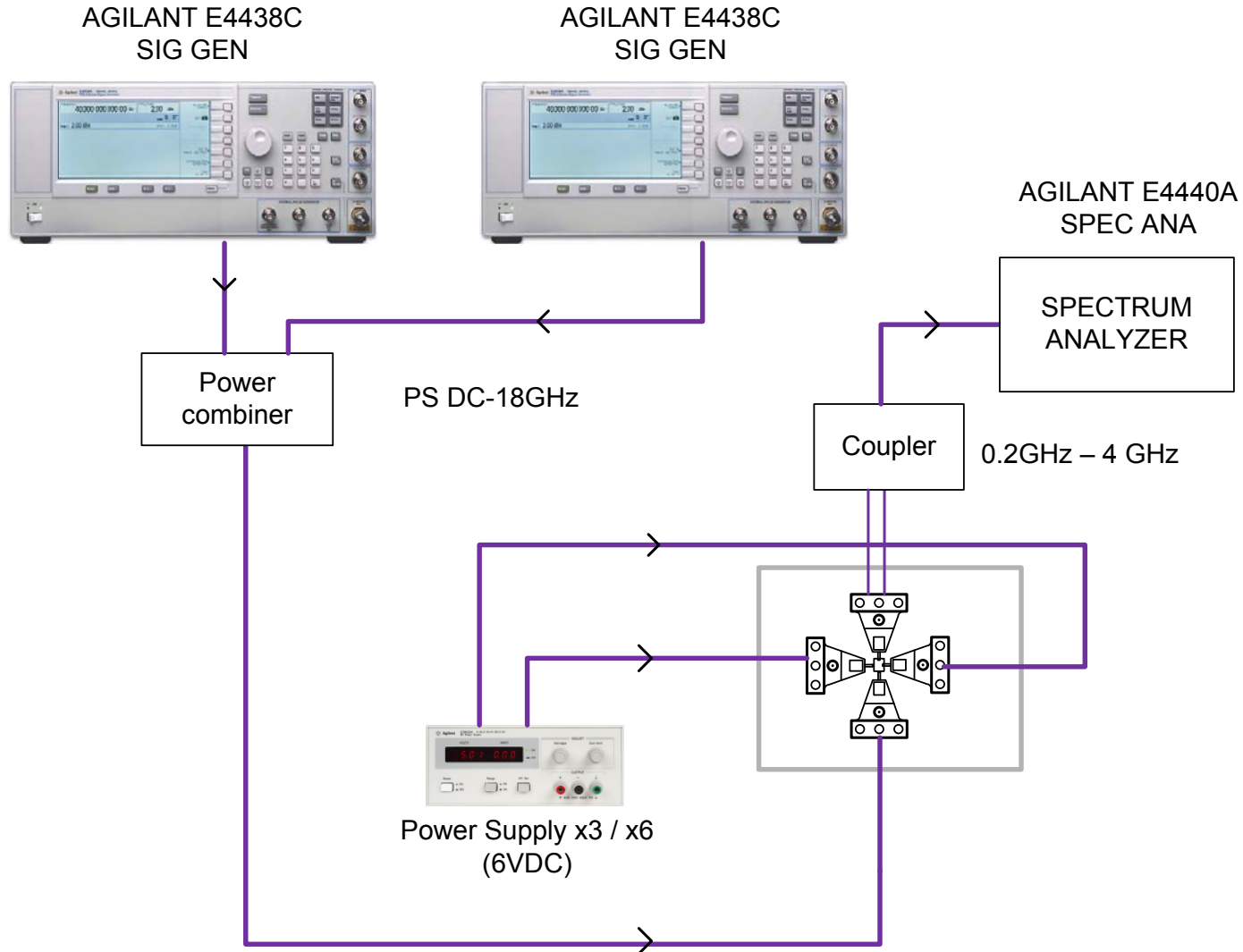


Measured LNA linearity

 


Two-tone test
measurements
with -16.5 dBm
input power per
tone at 1GHz
with $\Delta f = 2$ MHz

Proposed (blue) LNA outperform the linearity of the conventional LNA (red) by 17.5dB


Measured LNA linearity

 


IIP3 vs Frequency

 

Linearity Performance of 5 Chips

 


Input matching & gain Performance

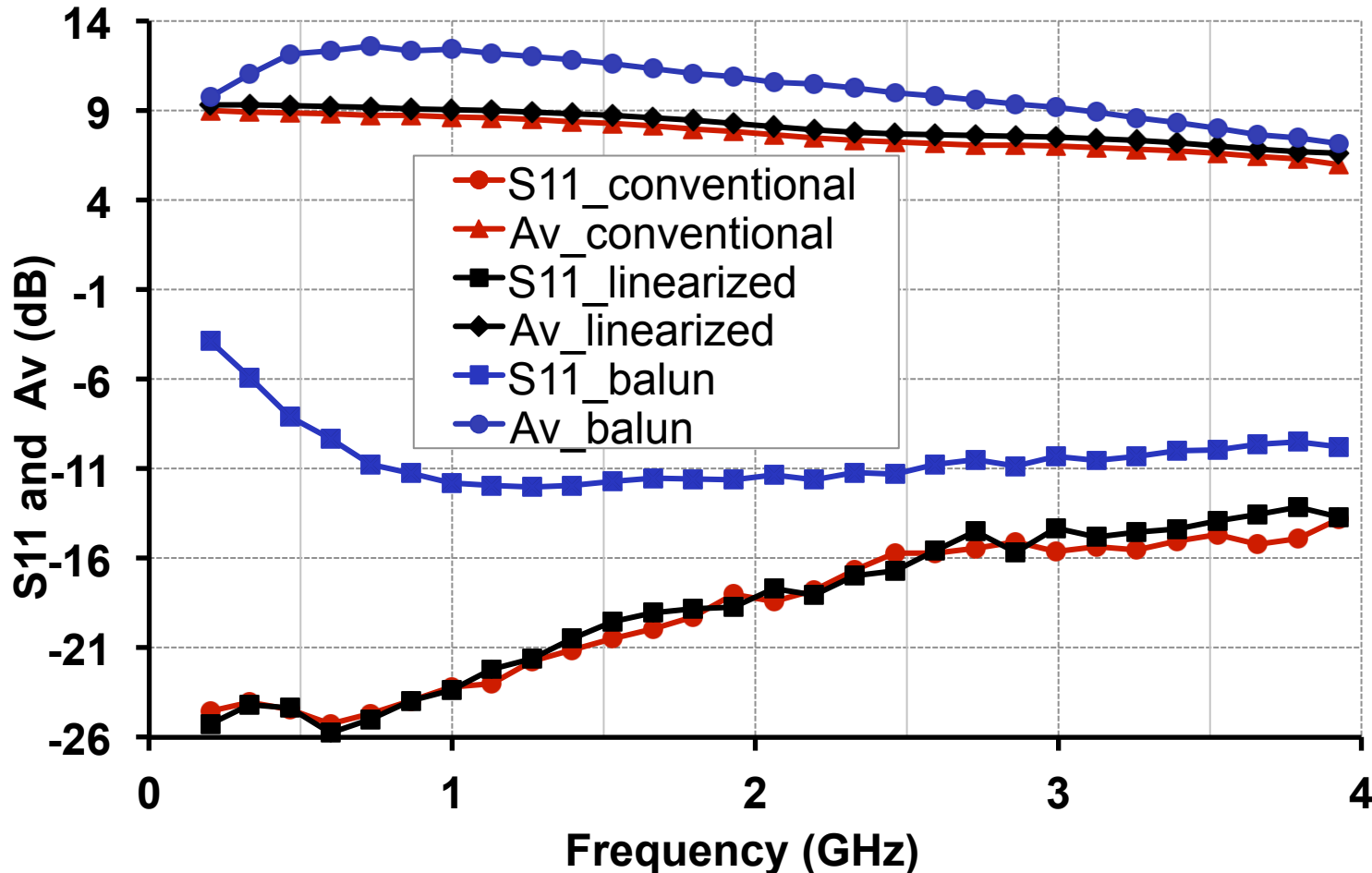

Av = Internal gain:
$$Av = S_{21} * \frac{Z_{22} + Z_{PORT}}{Z_{PORT}} + 3dB(balun)$$

Noise Figure

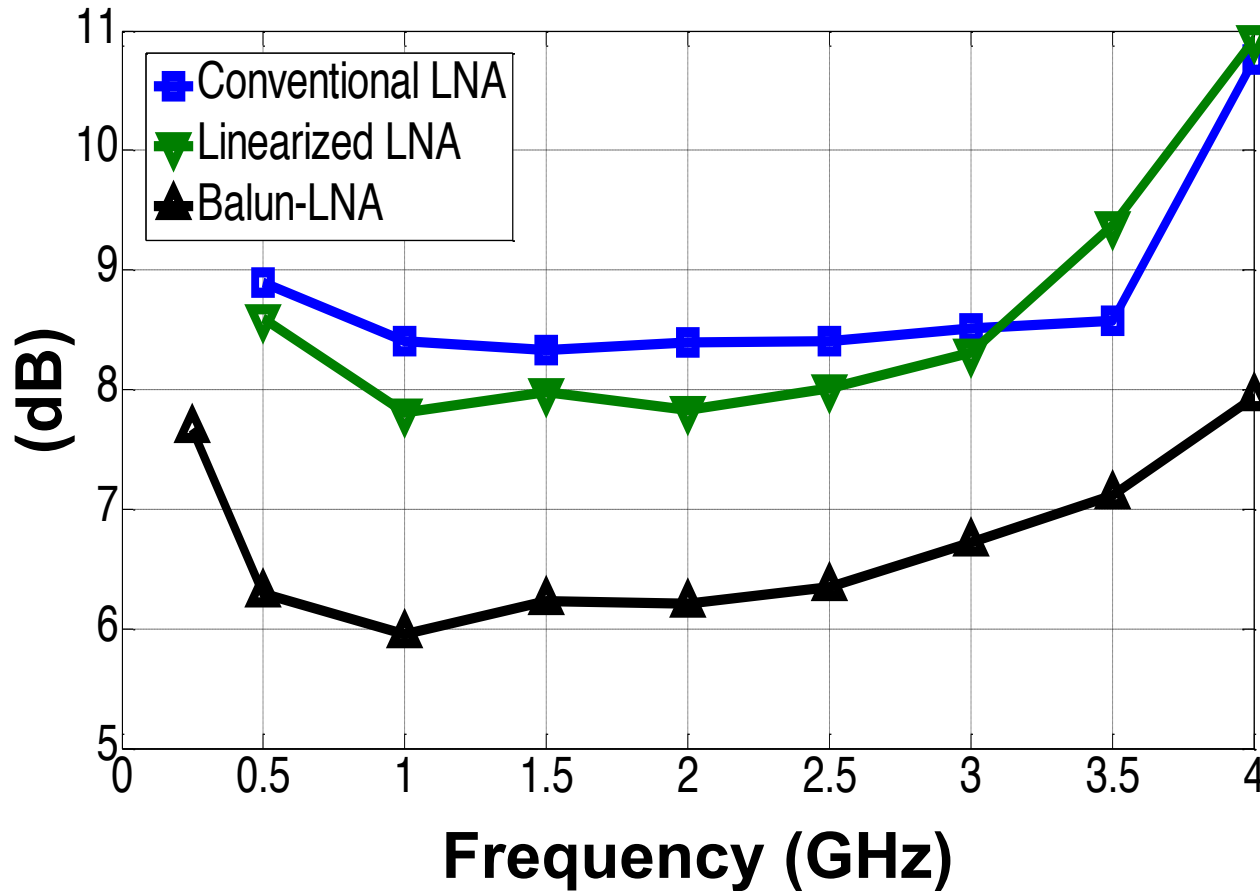

Comparison with Prior Art

	Blaakmeer JSSC-2008	Ramzan ISSCC-07	Chen JSSC-08	Van de Beek ISSCC-08	This work Balun-LNA
Technology	65nm	0.13 μ m	0.13 μ m	45nm	0.18 μ m
BW [Ghz]	0.2~5.2	1~7	0.8~2.1	0.6~10	0.3~2.8
Av [dB]	13~15.6	17	**14.5	10	**9.6~12.5
NF [dB]	2.9~3.5	2.4	2.6	3	5.95~6.5
IIP3 [dBm]	0~4	-4.1	16.0	6.0	16.8
P_{1dB} [dBm]	-	-	-11	-	0.5
Power [mW]	14	25	17.4	30*	14.2
No. of coils	0	0	0	2	0
Area (mm ²)	0.009	0.019	0.0992	-	0.06
FOM	16.22	6.343	102.3		34.3

* Includes V-to-I converter.

**Internal gain (Gain after de-embedding)

$$FOM = \frac{IIP3_{AVG}[mW].PowerGain_{AVG}[abs].BW[Ghz]}{Pdc[mW](F_{AVG} - 1)}$$

Conclusions

- A highly linear LNTA for SAW-less radios is proposed
- A robust derivative superposition technique low-sensitive to the process variations with little penalty in power consumption (< 8%) and wideband frequency effectiveness was proposed.
- The proposed balun-LNA simultaneously achieves impedance matching, noise and distortion canceling, and a well-balanced output.
- The proposed technique was validated in a resistive terminated LNA and a balun-LNA.
- The proposed linearization approach can be extended to most of the existing topologies.

Outline

- Introduction
- Broadband LNAs with non-linearity cancellation
- **Fully balanced LNTAs with $P_{1\text{dB}} > 0\text{dBm}$**
- A 12 bit, 20MHz, C.T $\Delta\Sigma$ ADC
- Active Antenna
- Conclusions

Fully Balanced Low-Noise Transconductance Amplifiers with

$P_{1\text{dB}} > 0\text{dBm}$ in 45nm

Hemasundar M Geddada¹, José Silva-Martínez¹, and
Stewart S. Taylor²




¹Texas A&M University

²Intel Corporation

Outline

- Introduction
- Noise and distortion cancellation LNTA
- Low power LNTA
- Experimental results
- Conclusions


Introduction

 

Low cost radio receivers for multi standard co-existence

- Low cost: SAW-less and Inductor-less solution.
- High linearity receivers to deal with strong out-of-band interferers

Targeted system

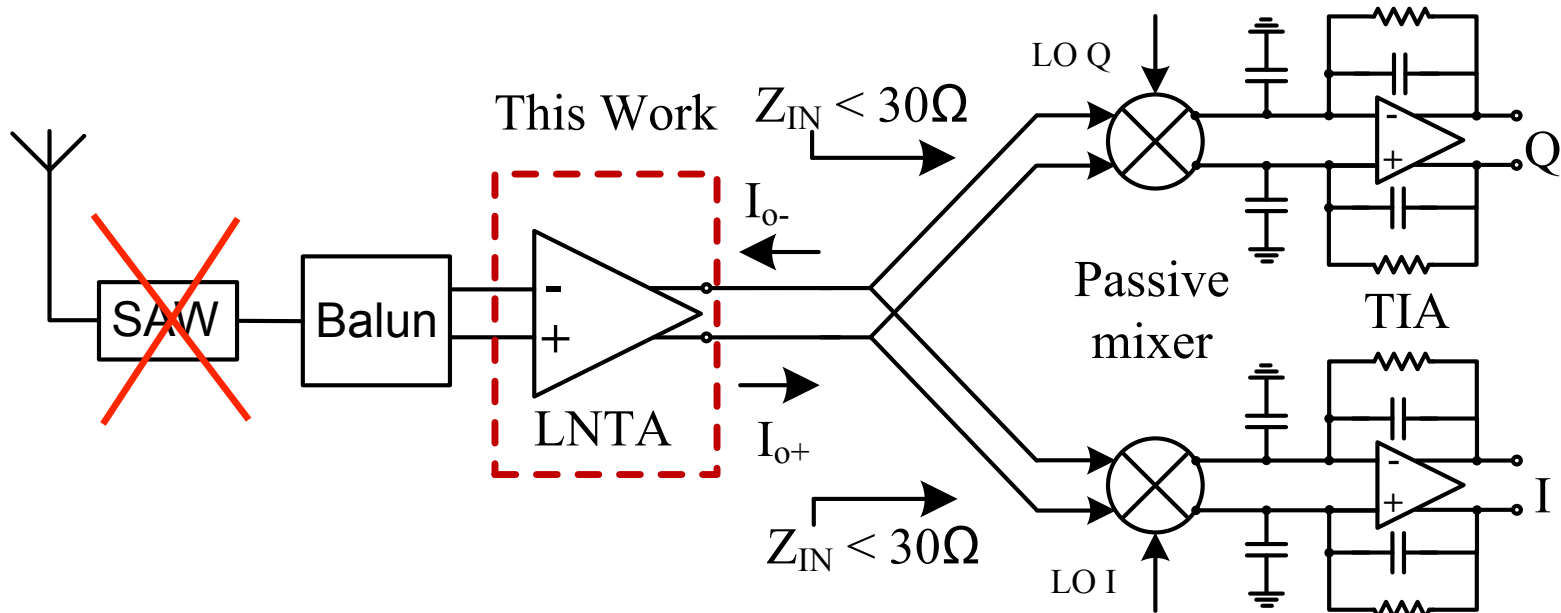


Direct Conversion Receiver Architecture:

Better performance in terms of noise, linearity and power consumption.

Linearity bottleneck \rightarrow LNTA

Low-Noise Balun-LNA

 


B. Gilbert (Micro-Mixer)
Blaakmeer et. al. JSSC 2008

i_n Cancellation condition
for balanced operation

$$g_{mCS} = g_{mCG}$$

- Noise of M_N appears as common mode.
- Noise performance limited by the CS stage and bias.
- Trade off between NF and balanced outputs
- Limited linearity

Low-Noise Balun-LNA

 

$$i_{01} = \frac{V_S - V_X}{R_S}$$

For same $Gm_i = 1/R_S$




$$i_{01} = \sum_j Gm_j (-V_X)^j$$

$$i_{02} = Gm_1(V_X) + \sum_{j=2} Gm_j (V_X)^j$$

$$V_X = \left(\frac{V_S}{2} + C_2 V_S^2 \right) + \sum_{j=3} C_j V_S^j$$




- Non-linearities in i_{01} can be converted in common-mode
- Cross products in i_{02} remain
- V_X is a strong function of the common-gate linearity

   Complementary PMOS-NMOS: DC characteristics



**PMOS-NMOS combination
makes $gm'_{OUT} \Rightarrow 0$ and
Minimizes gm''_{OUT}**

   
Complementary PMOS-NMOS: DC characteristics



Proper PMOS-NMOS combination
makes $g_{m'_{DIFF}} \Rightarrow 0$;


Common Source voltage more
linear!

Noise/distortion cancelling Balun-LNTA

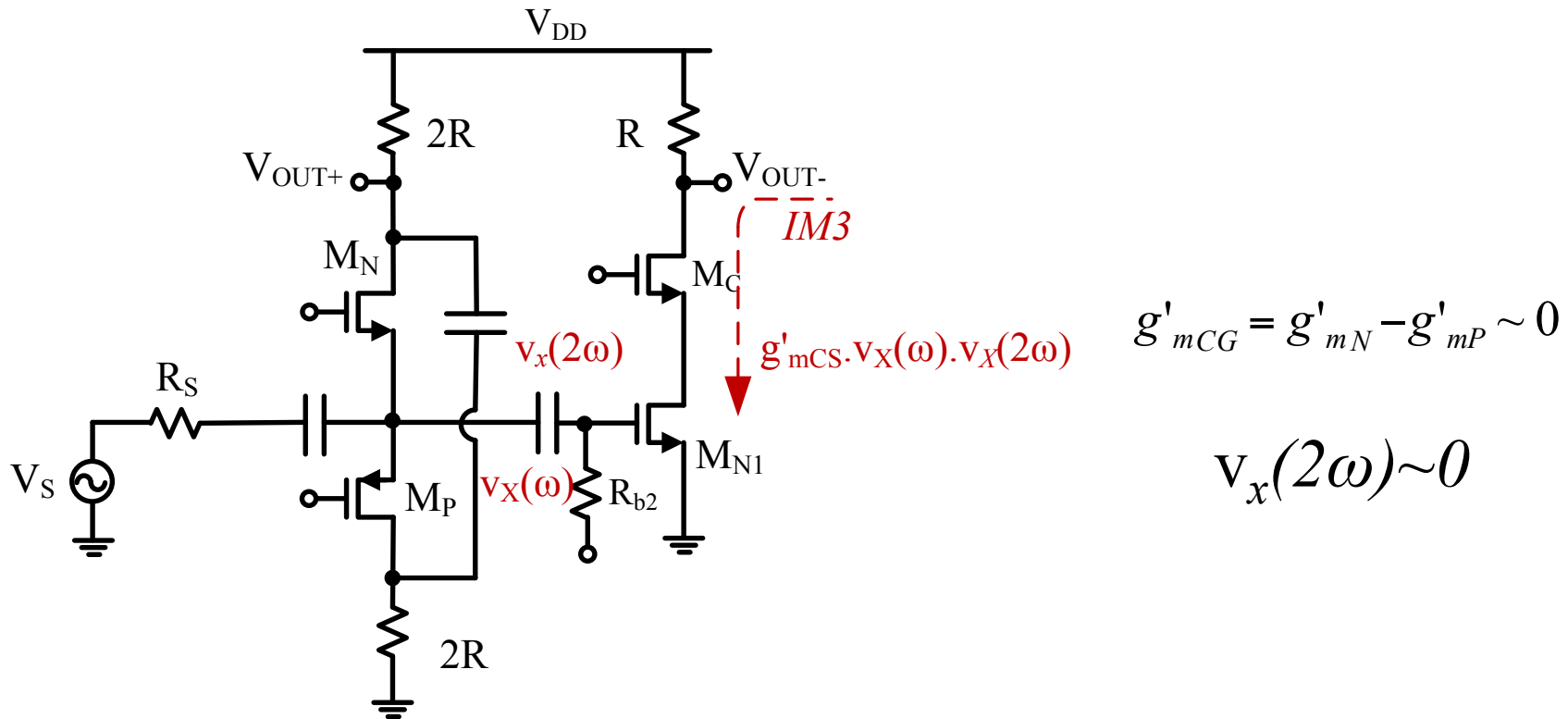

- Input CG stage is implemented current reuse M_N - M_P
- PMOS-NMOS → Even order distortion cancellation.
- IM3 because 2nd order interaction is reduced.


Noise/distortion Cancelling LNNTA

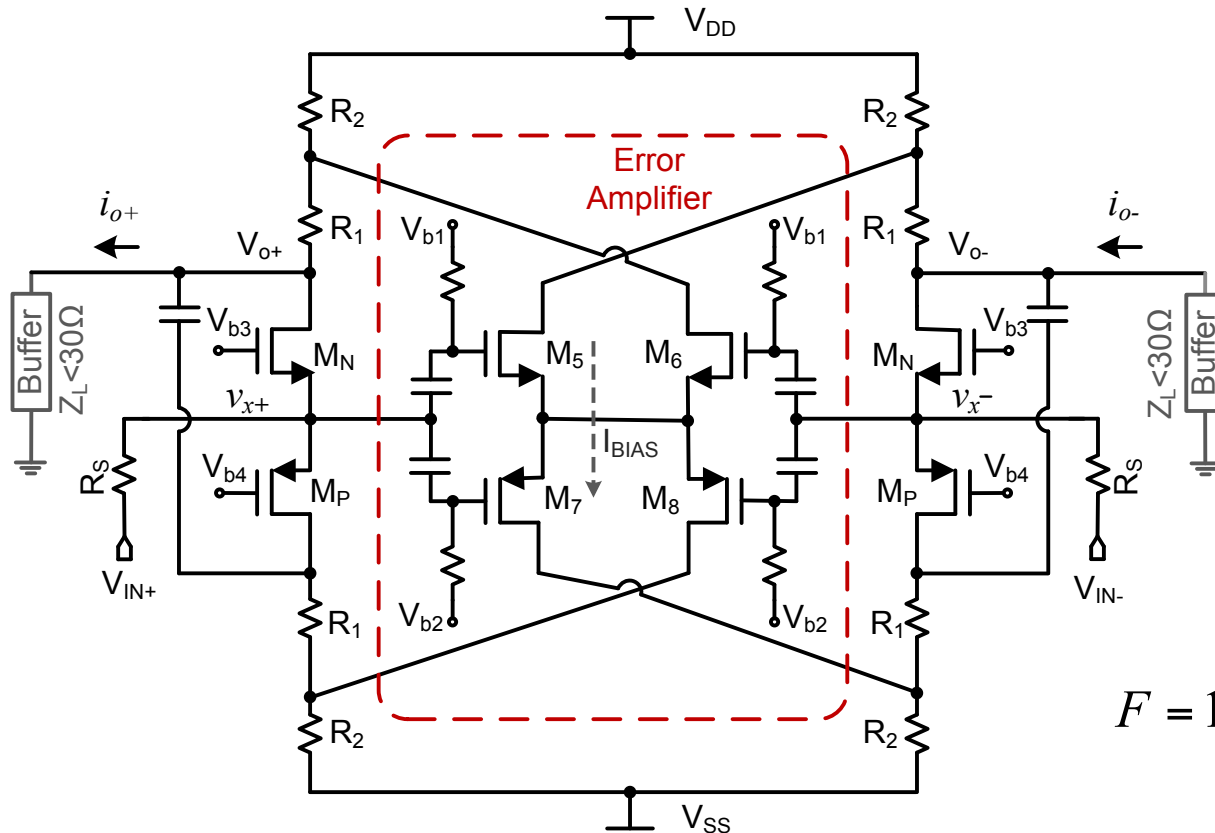

$$F = 1 + \cancel{F_{CG}} + F_{CS} + F_{R1,R2}$$


- Current re-use PMOS-NMOS error amplifier
- Error amplifier is implemented through PMOS-NMOS combination $\rightarrow g'_{mCS} \sim 0$

Large signal linearity, P_{1dB}

 


- Gain compression in the Error (CS) stage is counteracted by the Gain expansion in the CG stage

Low power LNTA

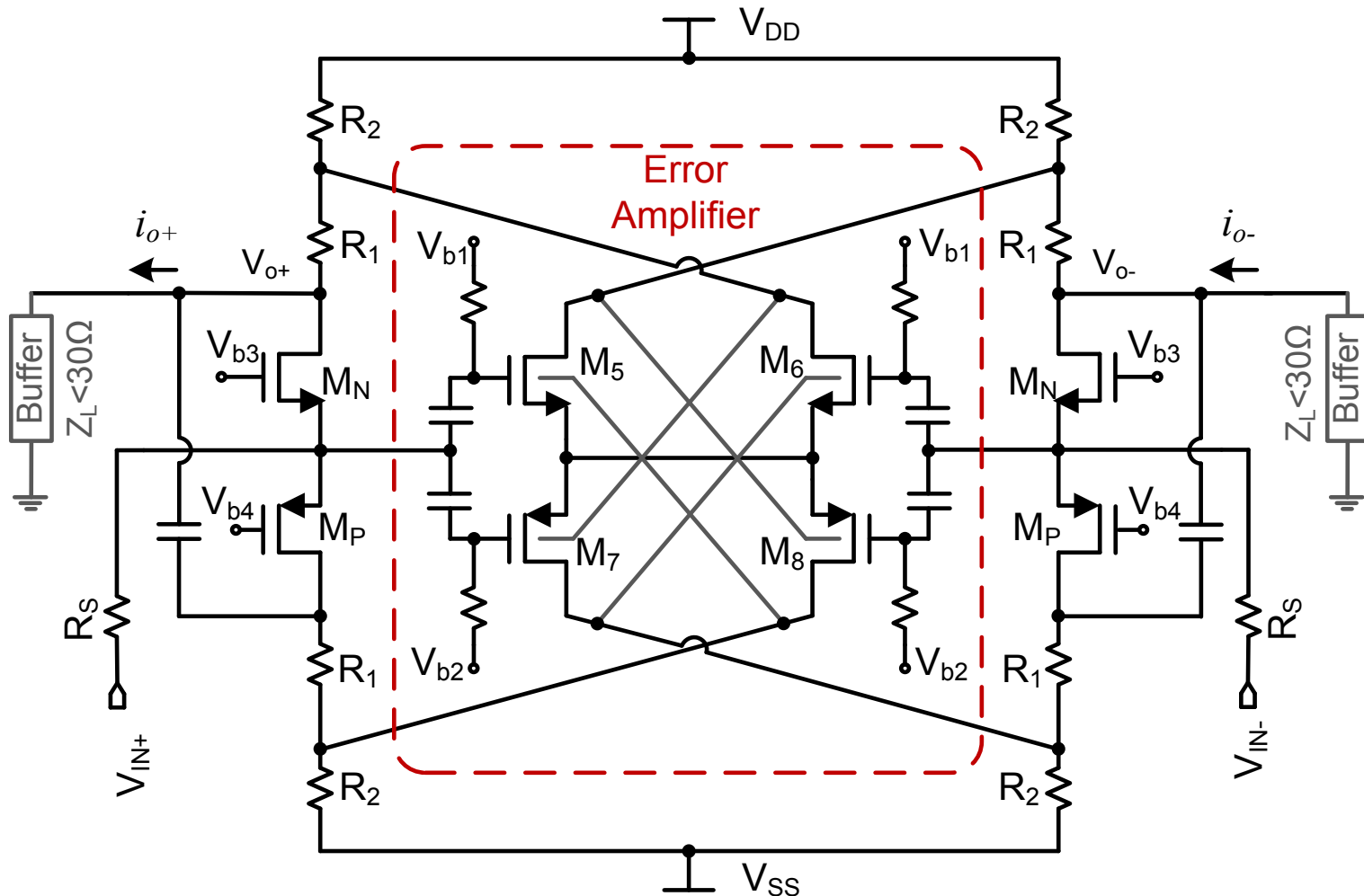

Bulk driven EA: transistor sizes and currents are scaled down to maintain the value of the original transconductance

On chip output buffer

 

$$Z_{IN} = C_P \parallel \frac{R_F + R_{OUT}}{1 + g_m R_{OUT}}$$


$$A_V = \frac{R_{OUT} (1 - g_m R_{OUT})}{R_F + R_{OUT}}$$

$$g_m = g_{m5} + g_{m8}$$

C_P = Input parasitic shunt cap

- Resistive feedback amplifier with $Z_{IN} \sim 30\Omega$
- Programmable A_V in the 6-14dB range and $S_{22} < -10$
- Two gain modes to facilitate NF and Linearity measurement

Chip Microphotograph


 


- 45nm CMOS Technology
- Wafer probing test.


Silicon area: 0.06 mm²

Measurement results

Input matching & Transconductance

  


Noise Figure

 


NF of LNTA (lines: simulations; markers: measurements, L_s = series inductance of 1.5nH at the input).





Measured LNTA linearity: 2-tone test

 

Measured LNTA linearity

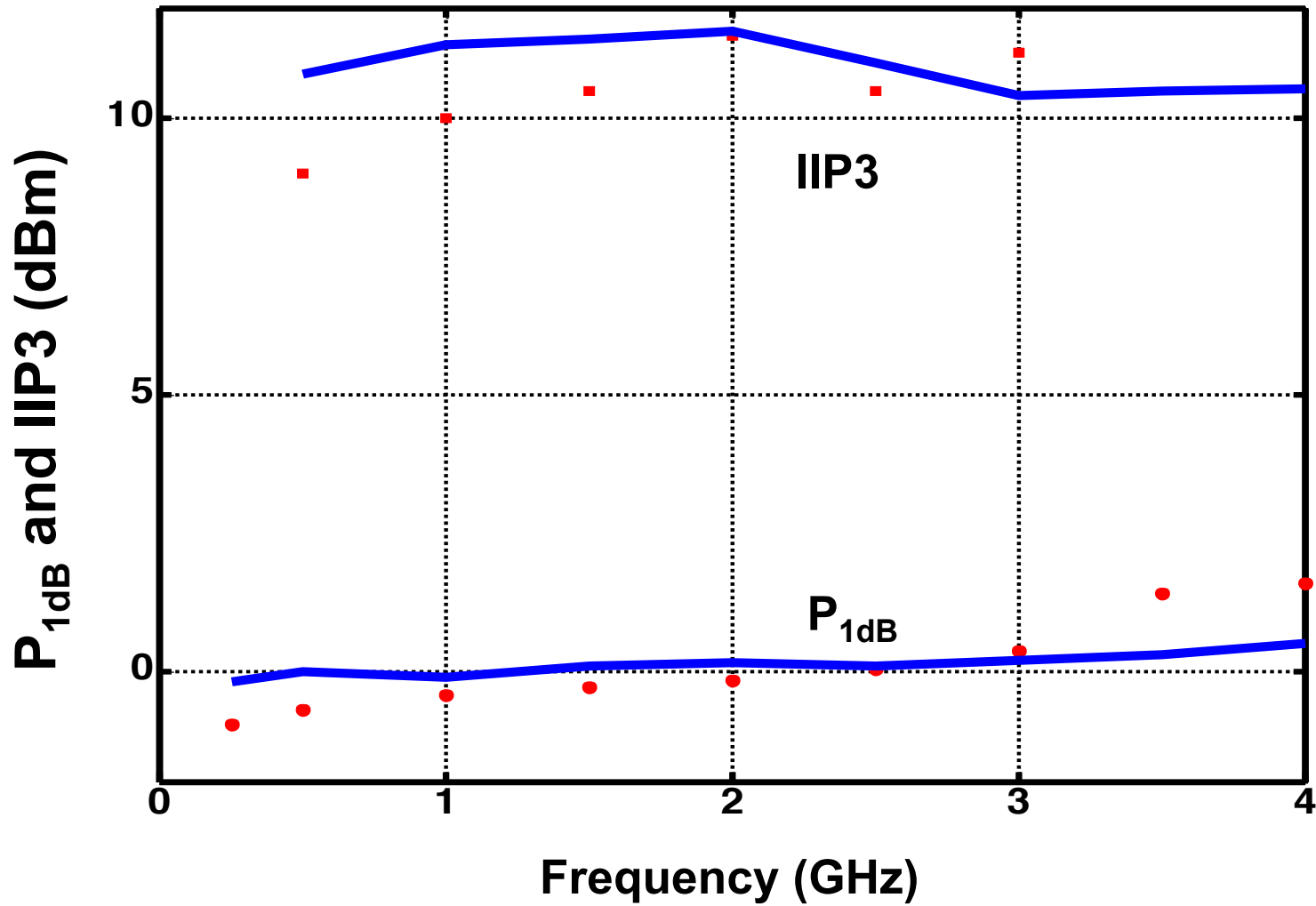

Results for Low-Power LNNTA

    

Comparison with Prior Art

Parameter	JSSC 08	TMTT 10	ISSCC 08	ESSCIRC 10 ⁺	LNTA	LP LNTA
Technology	0.13 μ m	0.18 μ m	45nm	90nm	45nm	45nm
Freq (GHz)	0.8 - 2.1	1-3	0.6 - 10	0.4-3	0.1 - 2	0.1 - 3
S11 (dB)	<-8.5	<-9	-	<-10	< -9	< -9
Gain(dB)/ gm(mS)	14.5 ^φ / NA	16.9/ NA	10/ NA	15/ NA	11*/ 36.5	10.3*/ 34.5
NF _{min} (dB)	2.5	2.6	3	2.3	3	3.4
IIP3 (dBm)	16	-0.7	6	>5	10.8	12
P_{1dB} (dBm)	-11 **	-11**	-	-10	0	0.4
Supply (V)	1.5	1.8	-	2	2.2	2.2
Power (mW)	17.4	12.6	30 ^Δ	-	35.2	20
Area (mm ²)	0.099	0.073 ^θ	-	-	0.06	0.06

* Internal gain (removing the R_L of 30 Ω); ^φ Internal gain ** graphically estimated; ^Δ includes the power of the V-to-I converter; ^θ active area; ⁺ LNA performance de-embedded from receiver front-end

Conclusions

- Highly linear LNTAs for SAW-less radios is proposed
- The proposed architectures achieve $P_{1\text{dB}}$ over 0dBm within the entire 0.2-2(3) GHz frequency band.
- The proposed LNTAs simultaneously achieves impedance matching, partial noise and distortion canceling, and a well-balanced output.
- Room for noise, linearity and power efficiency improvements