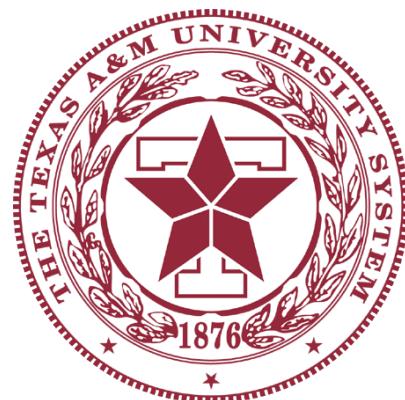


High linearity, Low cost

SAW-less Radios

Hemasundar Mohan Geddada


Texas A&M University



Outline

- Introduction
- Broadband LNAs with non-linearity cancellation
- Fully balanced LNTAs with $P_{1\text{dB}} > 0\text{dBm}$
- A 12 bit, 20MHz, C.T $\Delta\Sigma$ ADC
- Active Antenna
- Conclusions


Introduction

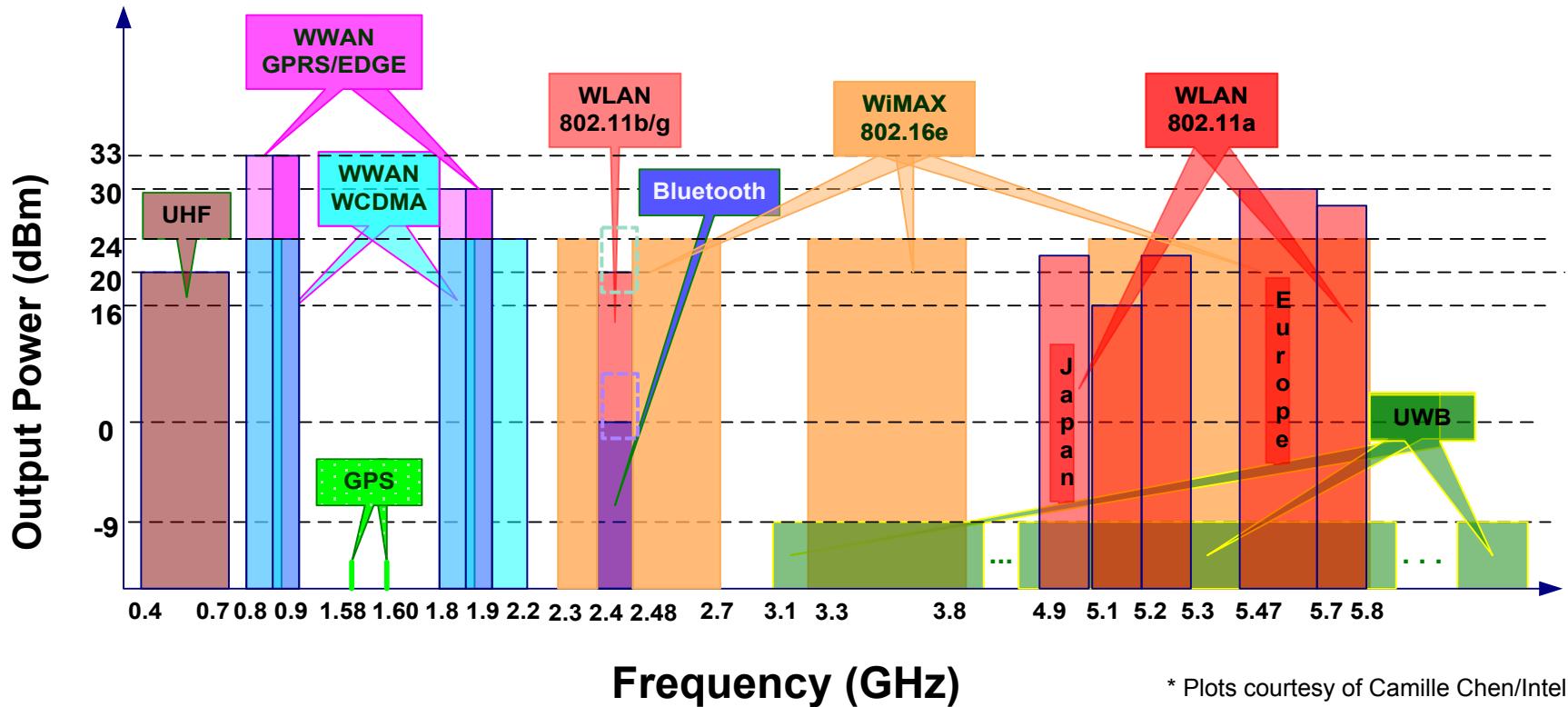

Low cost radio receivers for multi standard co-existence

- Low cost: SAW-less and Inductor-less solution.
- High linearity receivers to deal with strong out-of-band interferers

Targeted system

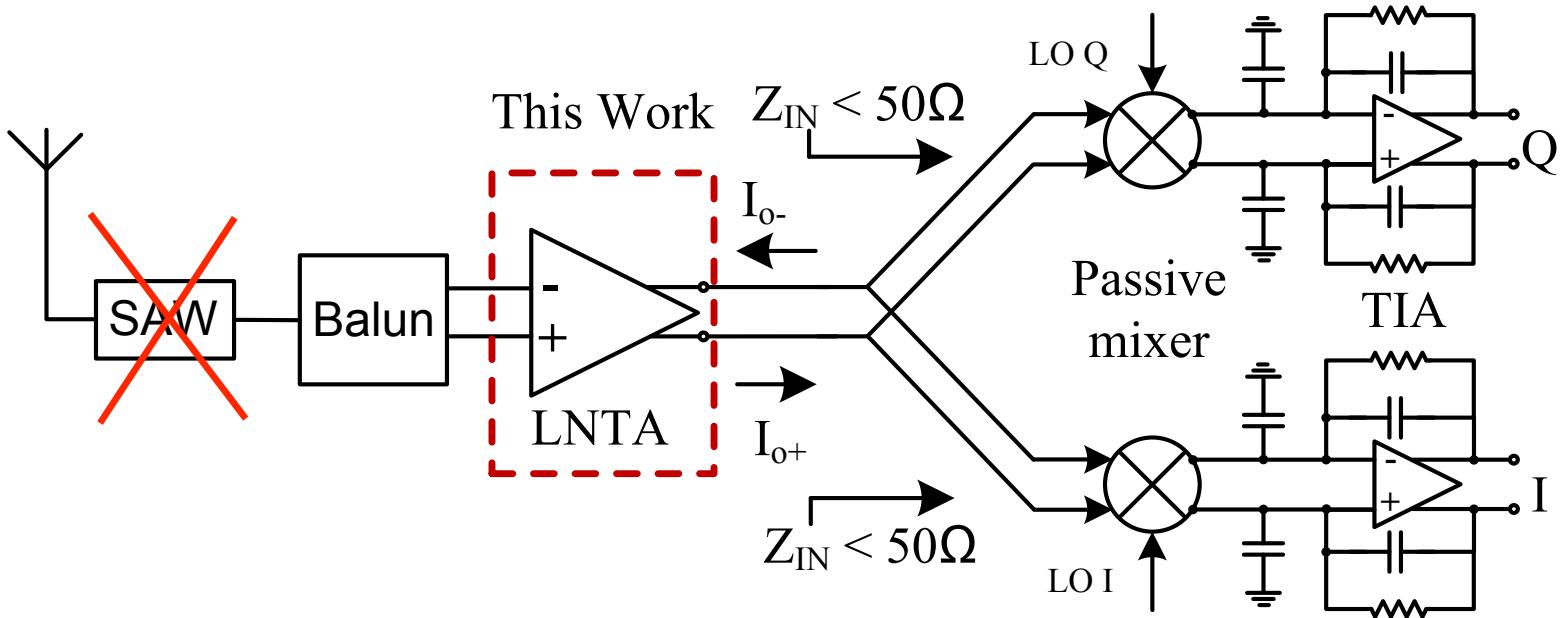

Direct Conversion Receiver Architecture:
Better performance in terms of noise, linearity and power consumption.


Linearity bottleneck \rightarrow LNTA

Broadband CMOS LNAs with Nonlinearity Cancellation

Hemasundar M Geddada¹, José Silva-Martínez¹, and
Stewart S. Taylor²

¹Texas A&M University

²Intel Corporation

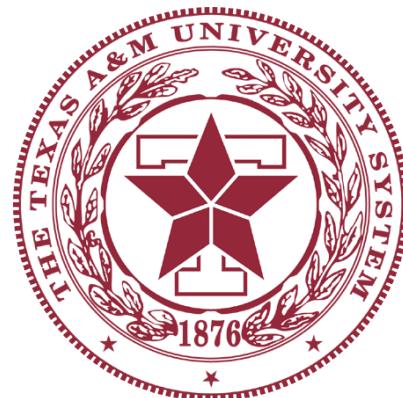

A 12-bit, 20Mhz, Analog-to-Digital Converter for Broadband Applications

H. M. Geddada, C. J. Park, H. J. Jeon,
J. Silva-Martinez, A. I. Karsilayan

SRC sponsored project
Task 1836.038

Outline

- Background and motivation
- Task overview and introduction
- Proposed ADC topology
- Digital current-DAC calibration
- Effect of blockers
- Static blocker filtering
- Saturation detection and attenuation for instantaneous blockers
- Effect of clock jitter
- Clock filtering for improving jitter tolerance
- Complete ADC design, chip floor-plan and performance summary
- Current status and conclusions

Background and Motivation


Key Needs

- Broadband analog-to-digital converters have been identified as a relevant need in the International Technology Roadmap for Semiconductors (ITRS)
- TxACE call for proposals indicates Broadband Analog-to-Digital conversion as a major industry need

Potential Applications

- Broadband wireless networks requiring high resolution analog-to-digital conversion solutions
- Multi-standard receiver applications where the desired signal has to be detected in the presence of strong out of band (OOB) blockers
- Mobile computing devices require low-power solutions

State-of-the-art and Targets

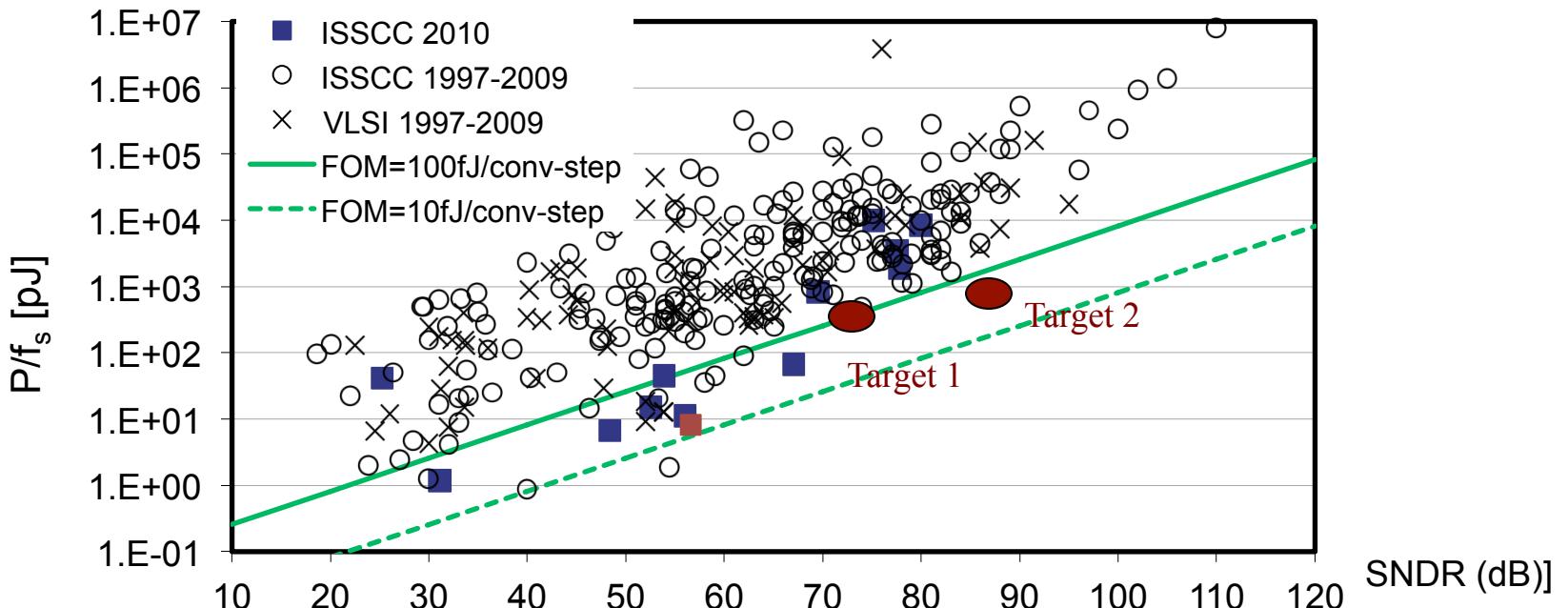

First Task:


B. Murmann, <http://www.stanford.edu/~murmann/adcsurvey.html>.

- 5th order 12 bit, 20MHz ADC in 90nm technology
- Total power consumption of the core ADC < 20 mW
- Figure of merit in the range of 200 fJ/conversion step
- Highly blocker tolerant (blockers up to 0dBFS)
- Second Task:
- 15-bit $\Delta\Sigma$ modulator with quantization noise cancellation

Task Overview

- Efficient techniques for the design of low-voltage low-power $\Delta\Sigma$ modulators in deep-submicron technologies.
 - New digital calibration techniques to improve the linearity of the DAC.
 - A fully calibrated 5th-Order 20MHz 14-bit $\Delta\Sigma$ modulator with low blocker and jitter sensitivity.

DC Broadband Receiver

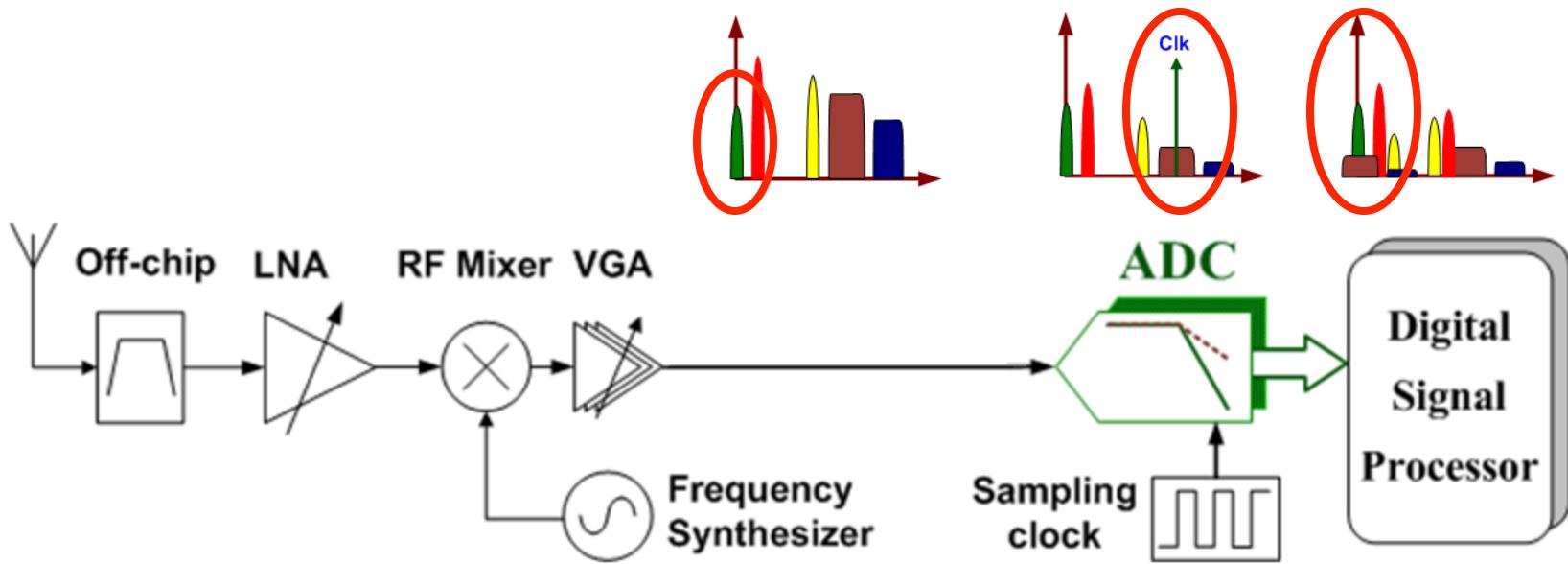


System issues in broadband systems:

- High frequency filtering is especially critical in broadband applications
- Blocker rejection: ADC filtering must be complemented by LP filtering

Trade-offs:

- Light filtering in front demands an ADC with higher Dynamic Range (DR)
- Higher DR ADC implies more power and more circuit complexity


ADC Feed-Forward Architecture

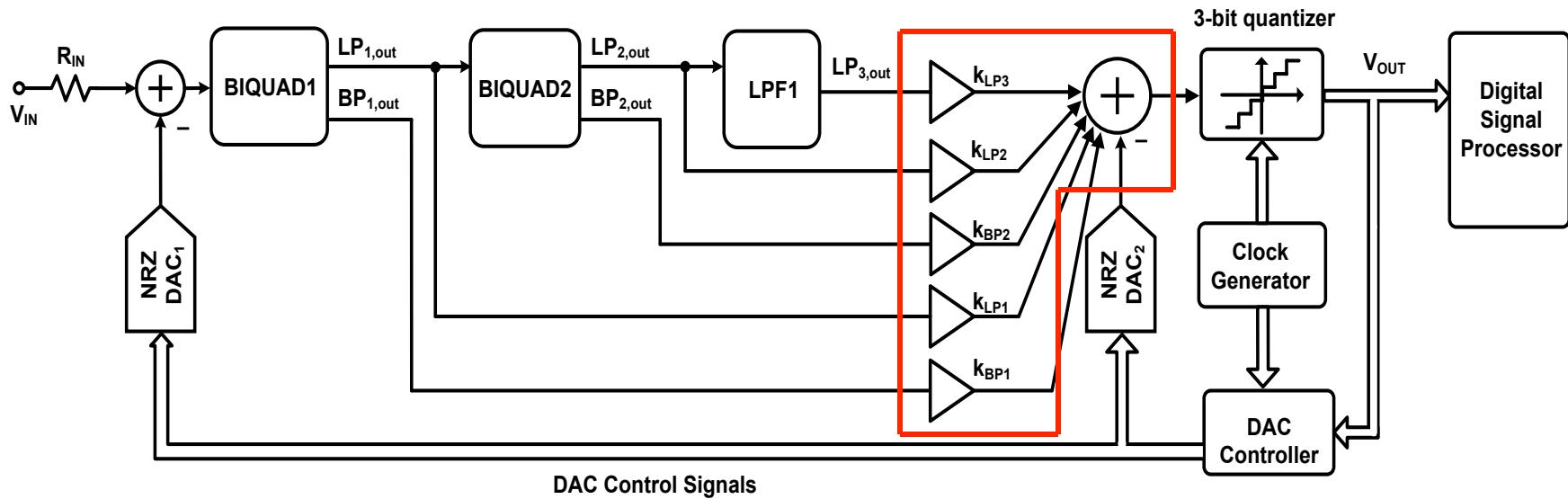

5th Order CT Low-Pass $\Delta\Sigma$ ADC Feed-Forward Architecture


- 👍 **Low power consumption**
- 👍 **Reduced complexity: one critical DAC**
- 👎 **Highly sensitive to DAC errors**
- 👎 **1st order attenuation to OOB blockers and OOB peaking**

Complete $\Sigma\Delta$ Modulator

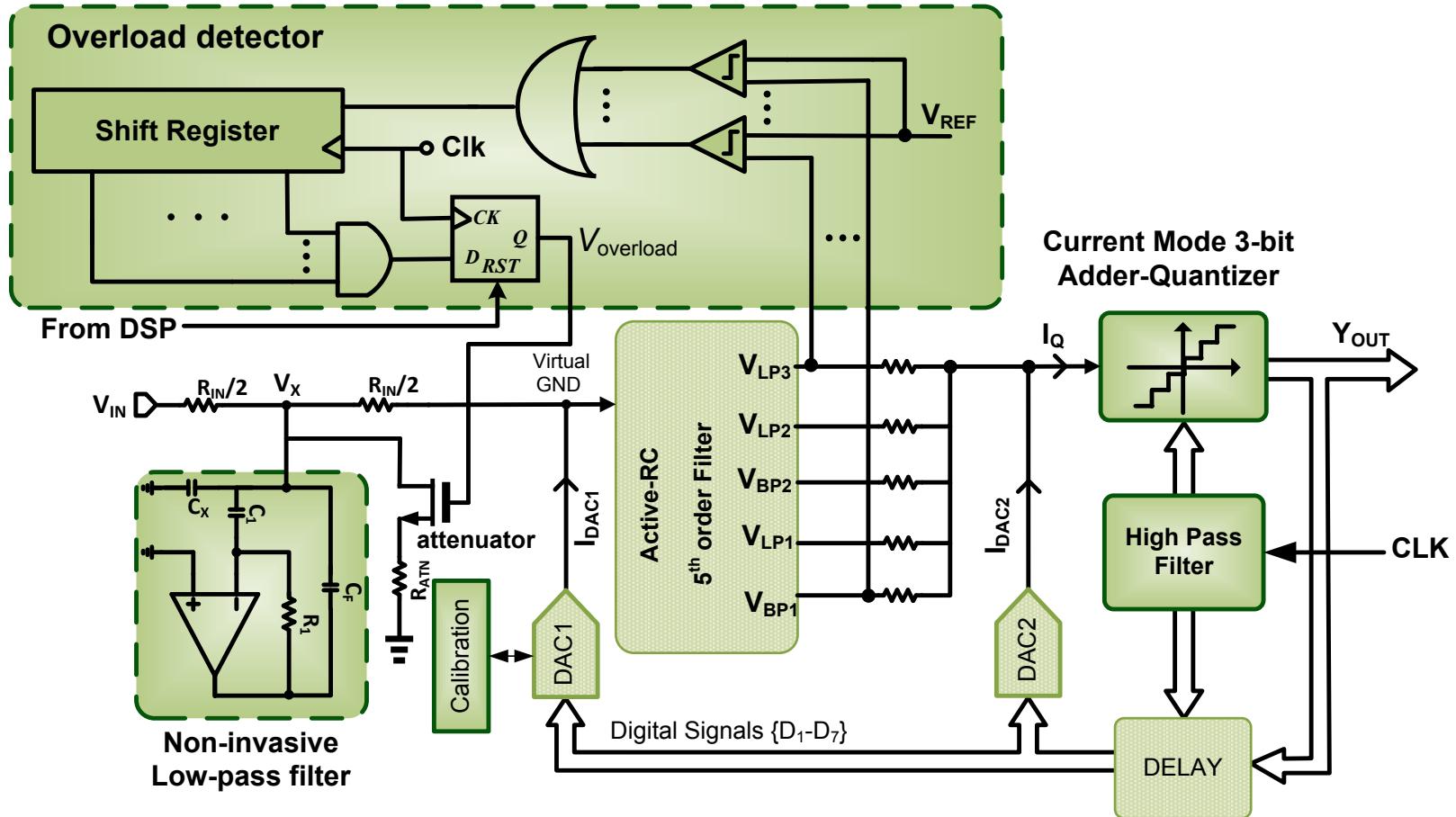


➤ Schematic of the full system


5th Order Loop filter

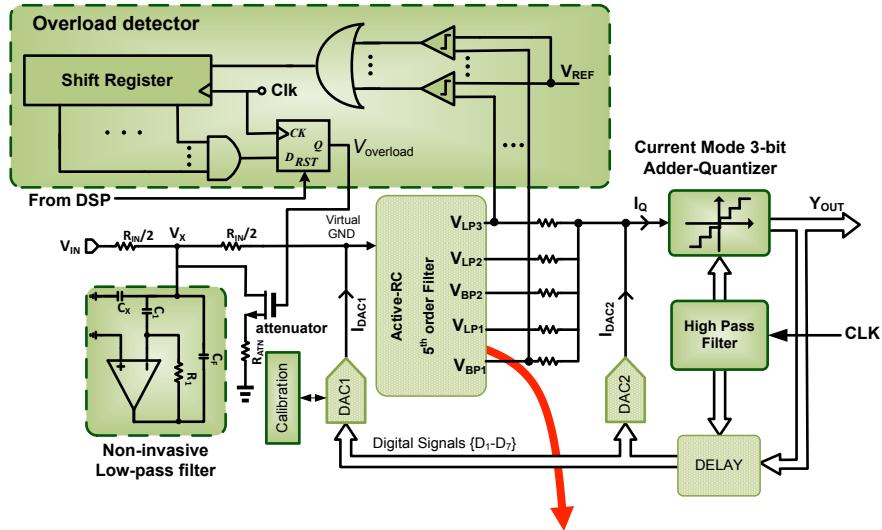


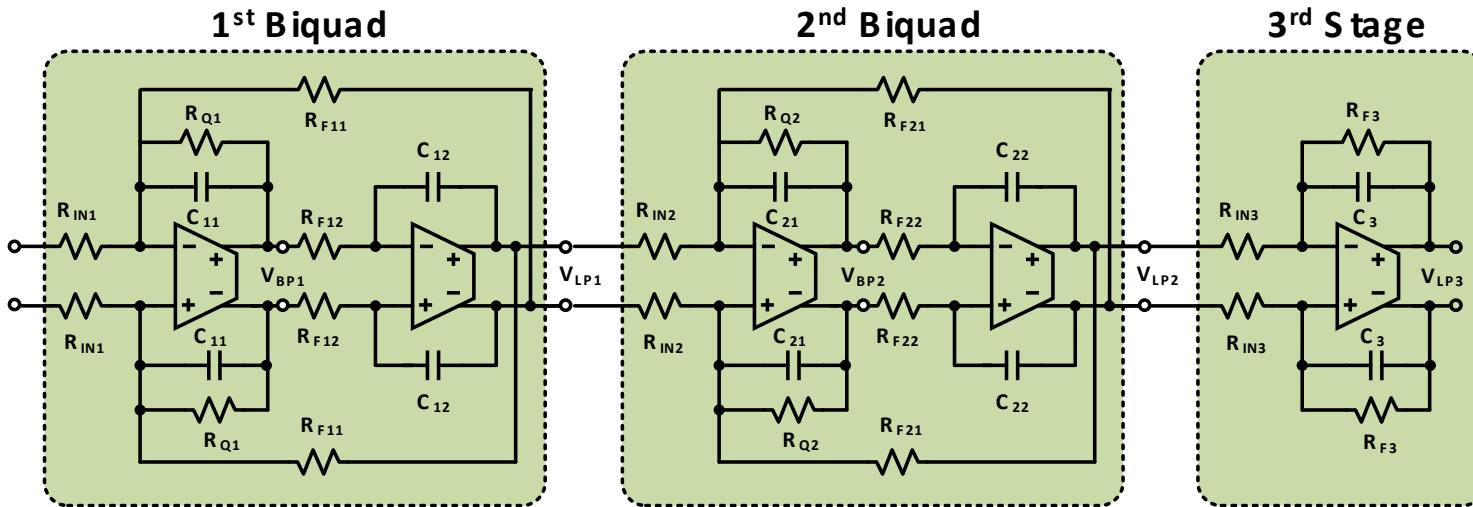
- 5th Order Active-RC loop filter
- Active RC realization to achieve high linearity
- Operational transconductance amplifiers use feed-forward compensation



Current-Mode Adder-Quantizer

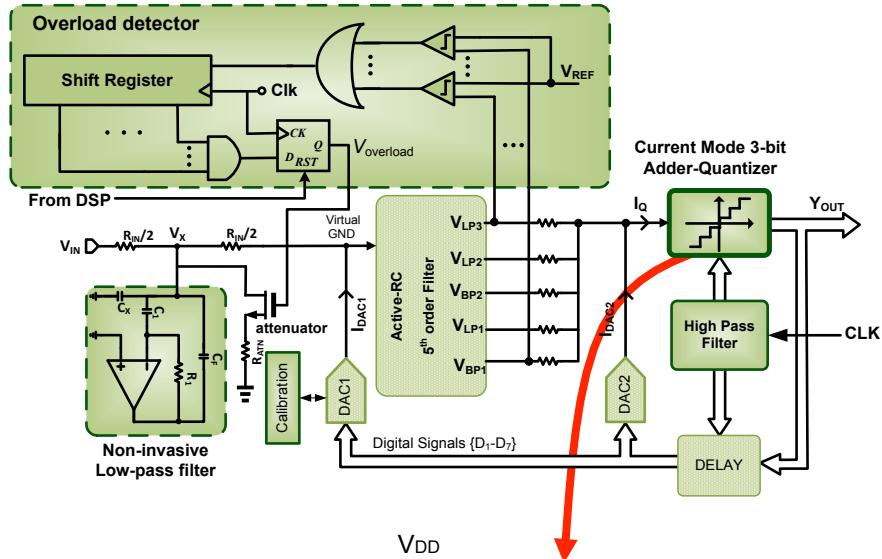

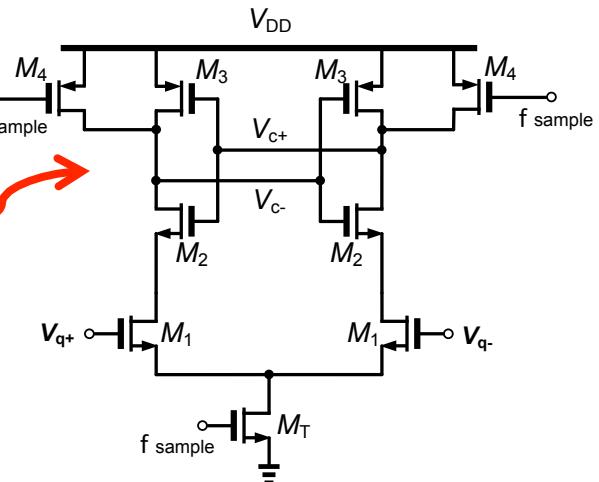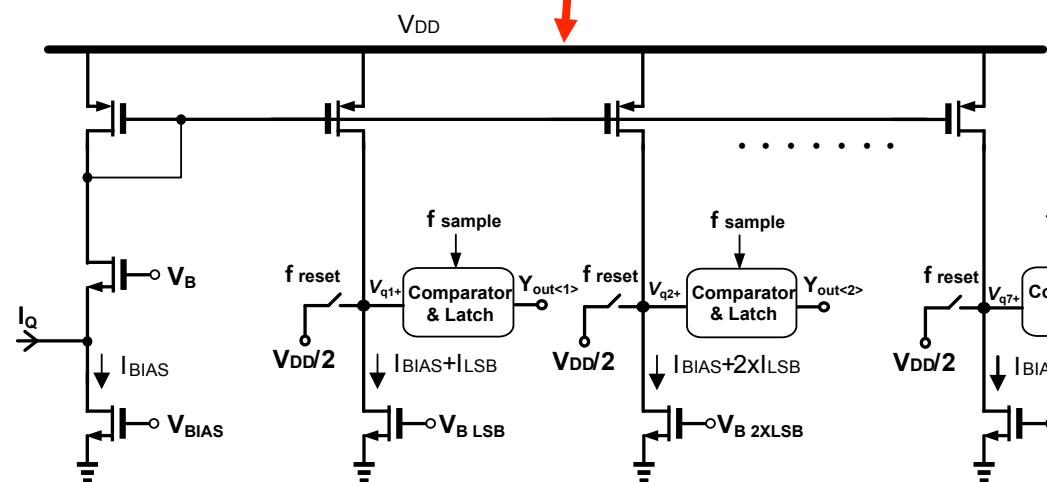
- Current-mode adder-quantizer realization
- Low power solution
- Reduced complexity



Efficient Current-Mode Adder-Quantizer
15


Strong-Arm Comparator

Digital Calibration of DAC₁

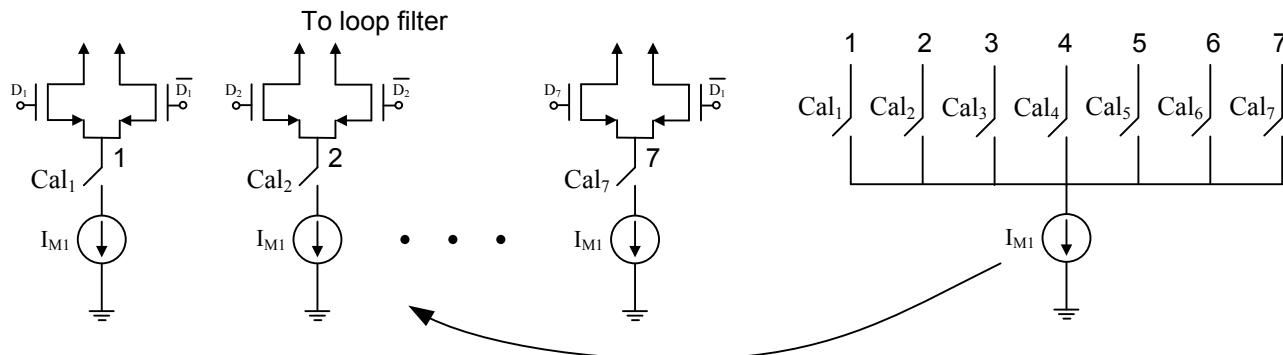

- Online calibration
- Robust to process variations

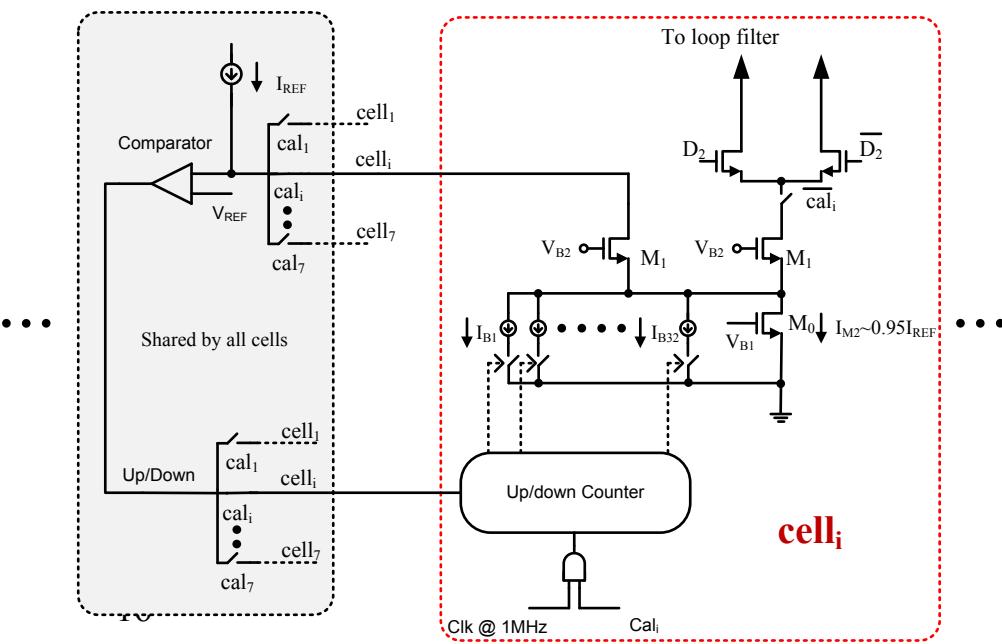Spare current source takes the position
of current source being calibrated



Calibration Properties

- Robust to process variations
- 32 current sources
- Granularity ~ 0.15%
- Calibration is stored digitally
- Glitch free


Effect of Blockers

- **Blocker:**
 - Any unwanted signal that degrades the sensitivity of receiver
- 1. **Steady state:**

Steady state blocker rejection depends on the OOB attenuation of the system
- 2. **Transient:**

Large internal gain stages and finite delay in the feedback of $\Delta\Sigma$ loop makes the system vulnerable to blockers during transient
- **Main issues:**
 1. Filter and/or quantizer saturation make the loop unstable and usually requires reset to be operative again
 2. Higher order ADCs take long time (μ seconds-seconds) to get back to linear operation after reset


Closed-Loop Gain at Internal Nodes

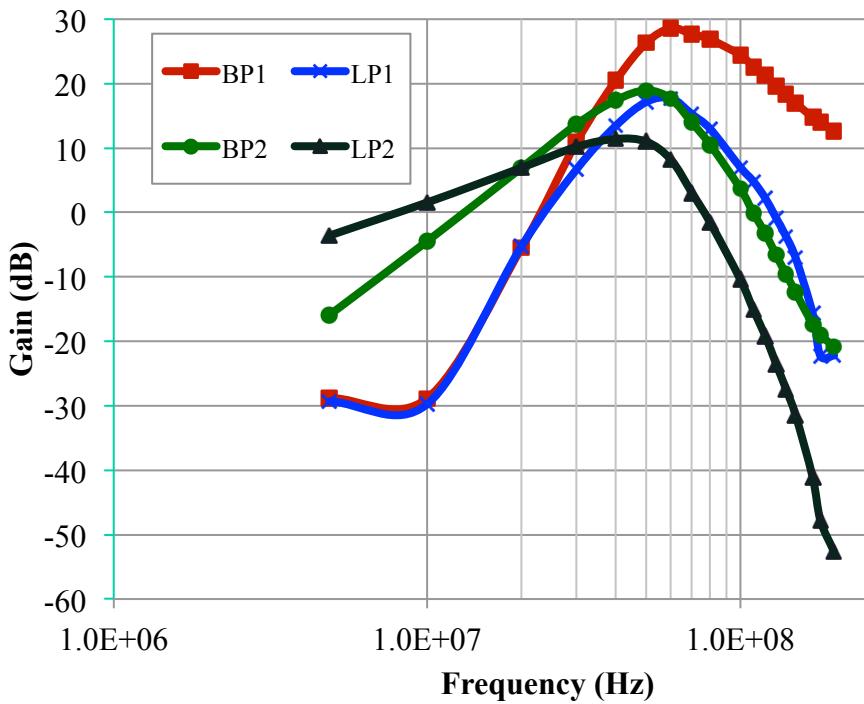

- Feed-forward paths cause peaking at the internal nodes
- Adjacent/alternate channel frequency blockers at ~30-150MHz may overload internal nodes and quantizer.
- Large time constants are associated with the internal nodes for 10Mhz poles. So resetting the system is a slow process and not acceptable in real time communications.


- There is not enough loop gain at critical frequencies to reduce the blockers at internal nodes.
- Improvement in the steady state blocker tolerance can¹⁸ be achieved by filtering critical frequency bands.

High-Frequency Blocker Filtering

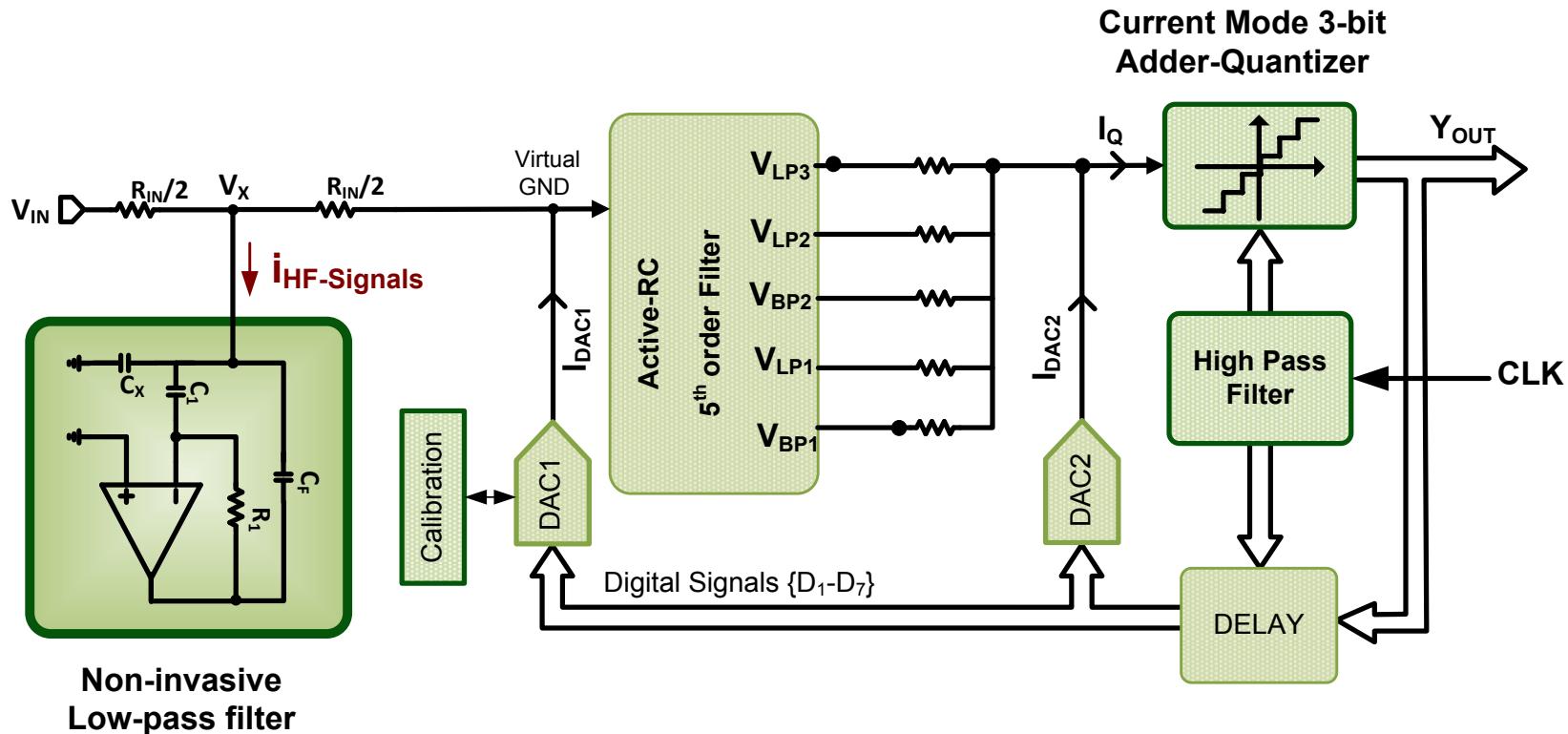

- Non-invasive LPF is implemented outside the loop
- Can also be integrated into the TIA (RF-IC 2011, Perez-Taylor-Silva-Karsilayan)
- In-band noise is not affected
- Low-power solution

Blocker Filtering: Non-Invasive LPF

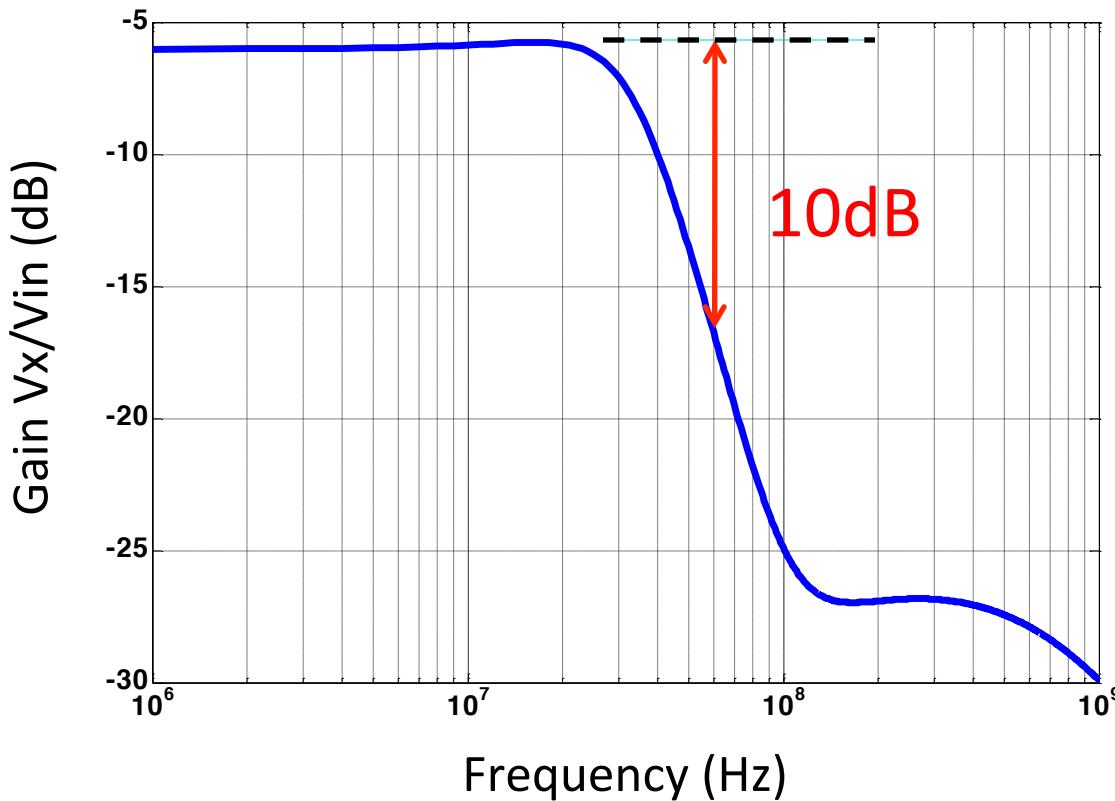


- 10dB attenuation at 60MHz
- Power: 2.25mW
- Area: 0.0816mm^2


$$Z_X = \frac{0.5\omega_0^2 R_{IN}/2}{S^2 + \omega_0 S/Q}$$

$$f_0 = 20\text{Mhz}$$

$$Q = 0.7$$

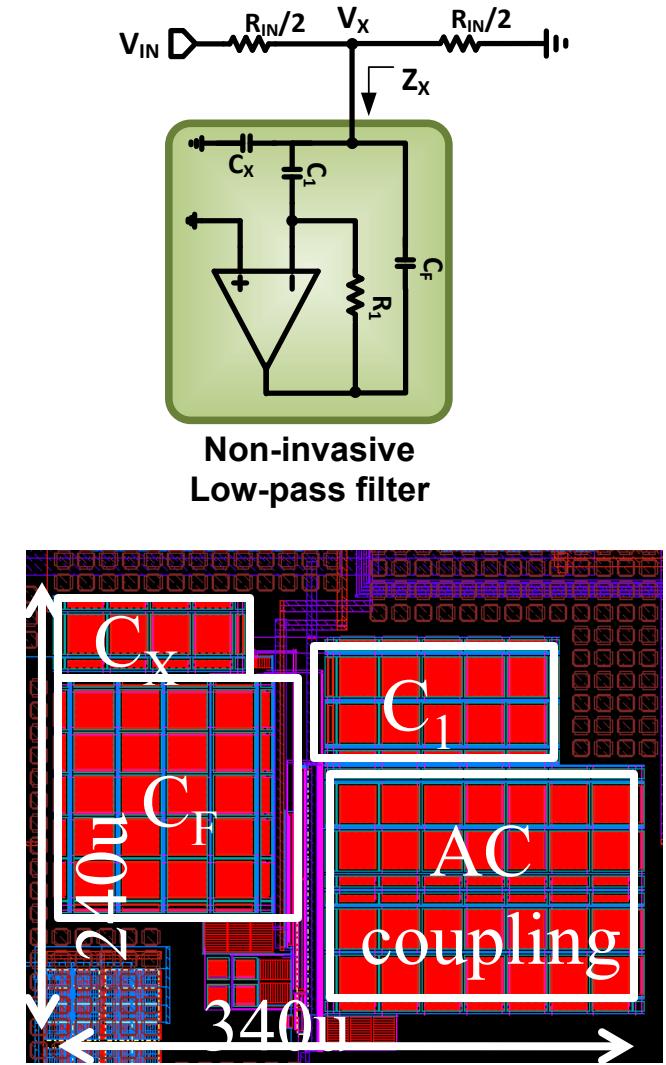


Programmable Non-Invasive LPF

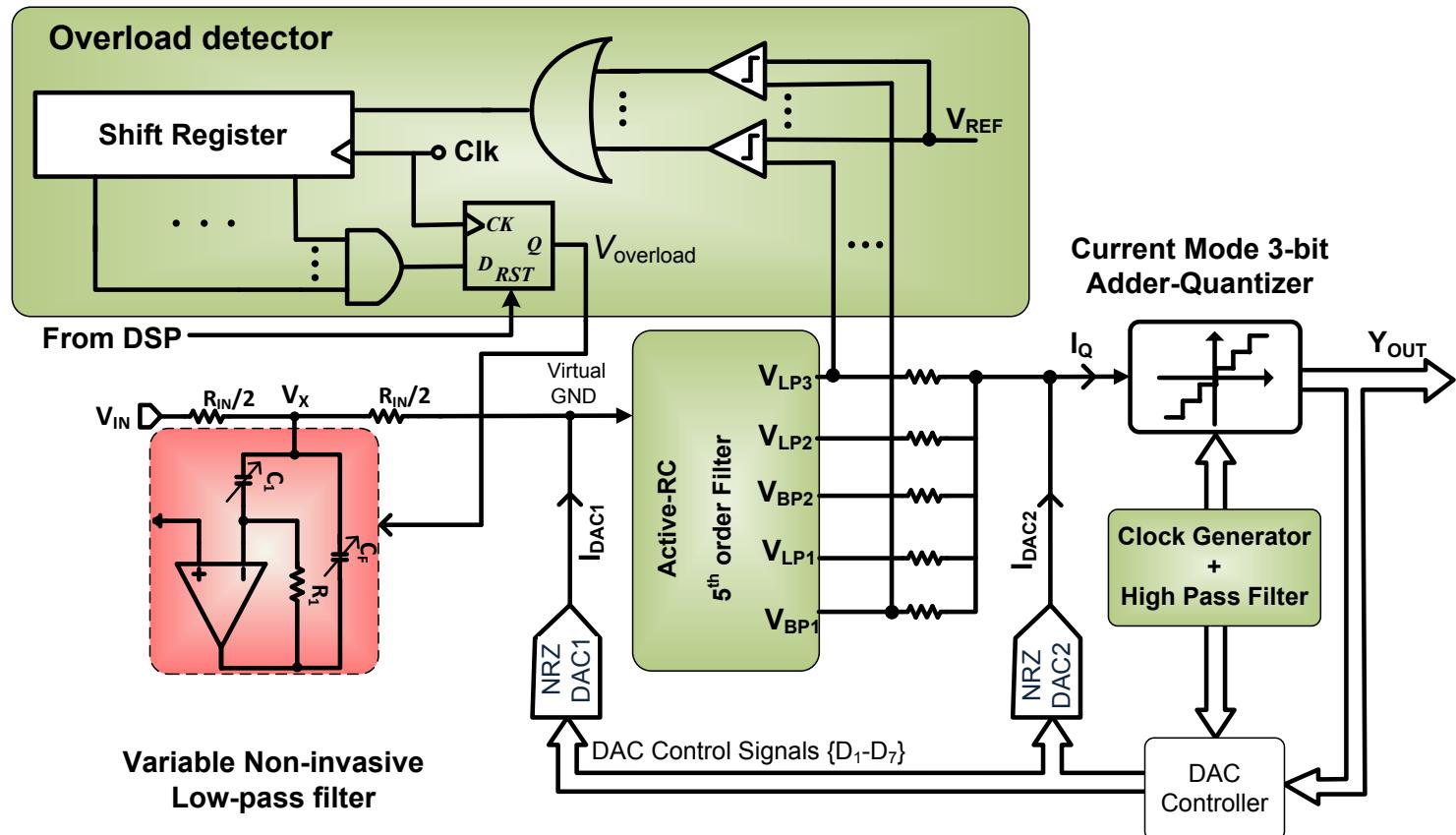

- Programmable BW for the low pass filter
- Overload detector controls the BW of the LPF

Programmable Non-Invasive LPF

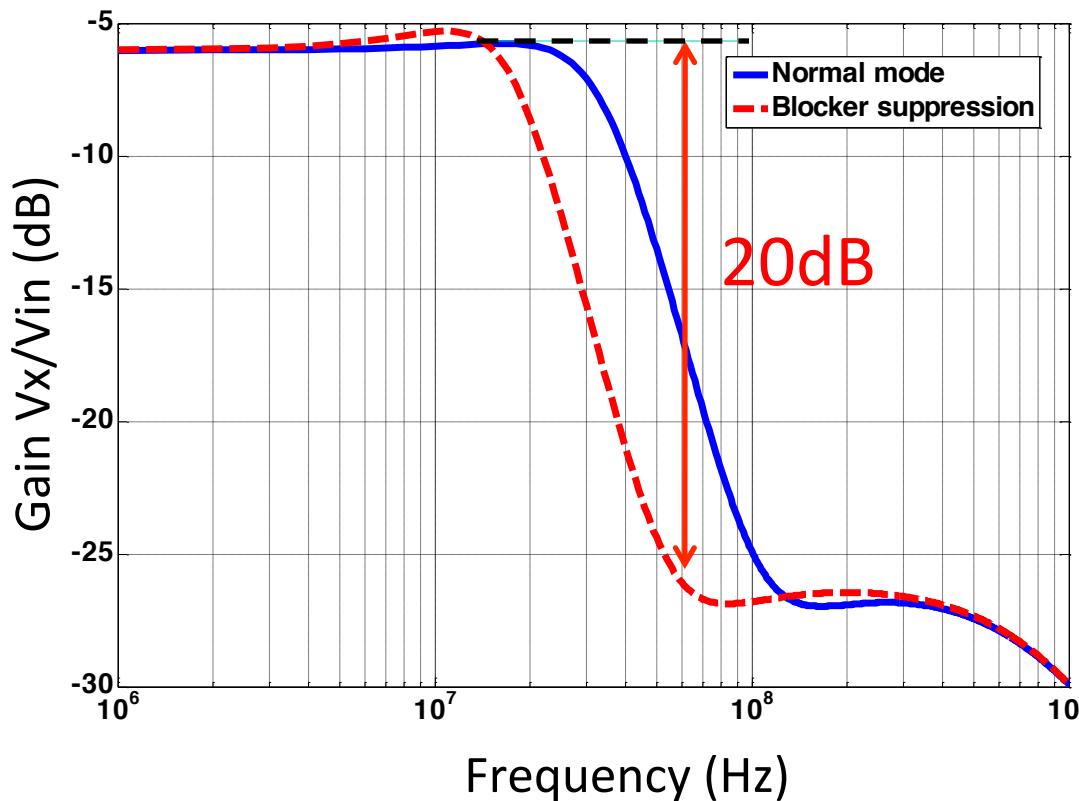


- In blocker suppression mode, LPF gives 20dB of attenuation at (60-80MHz).
- Band-edge droop is maintained to be less than 3dB at 20MHz.
 - can be recovered in post digital processing.

Instantaneous Blockers

What are effects of the agile (fast time variant) blockers?


- Instantaneous blockers during transient may also saturate the ADC and then breaking the communication
- The protection technique must react very fast to avoid loop saturation
- In the case of strong blockers, moderate SNR is better than no communication
- High-frequency loop linearity is critical to minimize the power of inter-modulation products
- Regular feedback is not fast enough to react to the instantaneous blockers. Need a faster feedback to avoid the system from getting overload because of the instantaneous blockers.

Saturation Detector & Attenuator

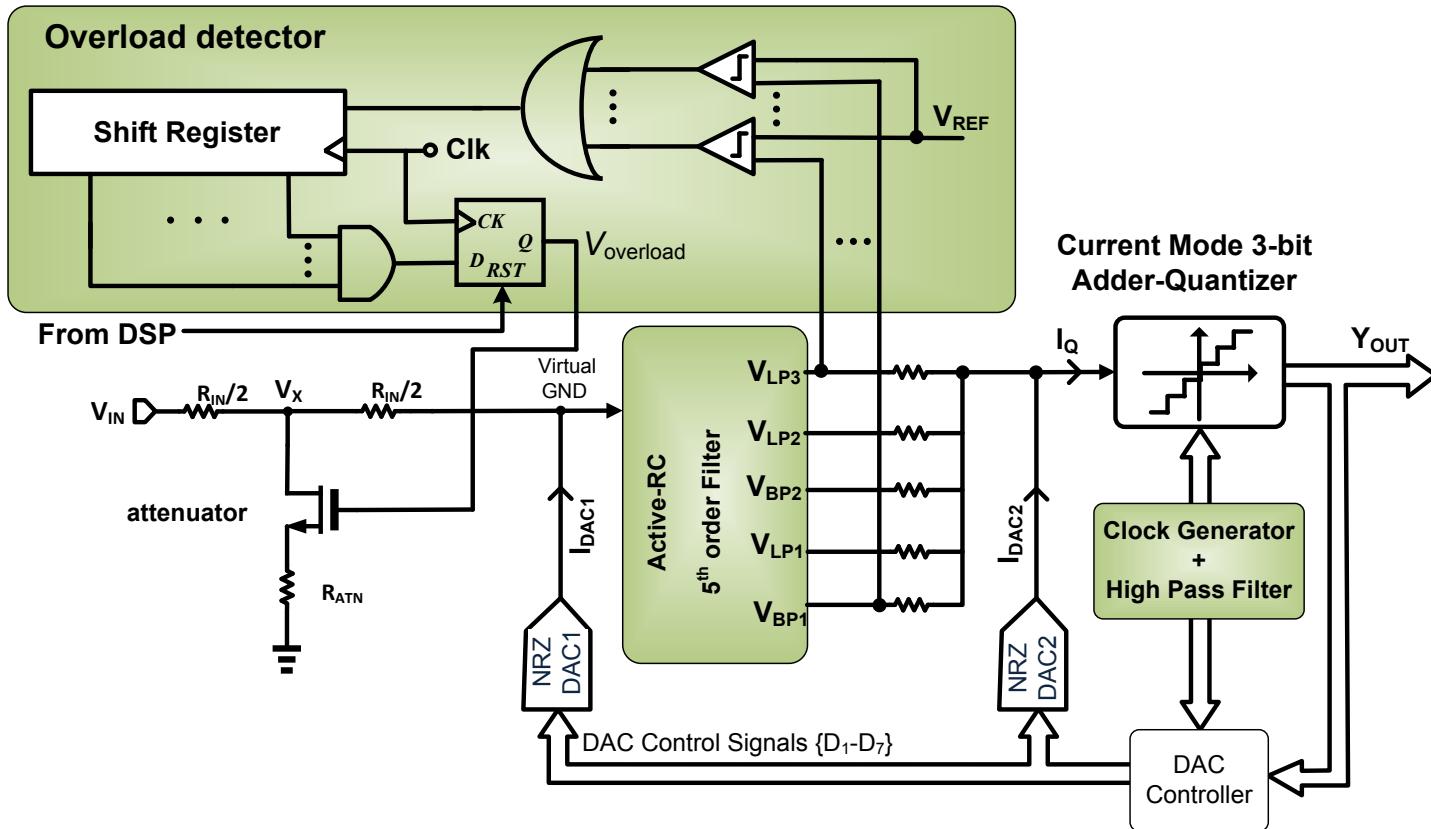


- Filter overload is detected through overload detectors
- The programmable (out of the loop) attenuator is activated when systematic overload is detected
- SNR reduces but loop stability can be guaranteed

Blocker protection

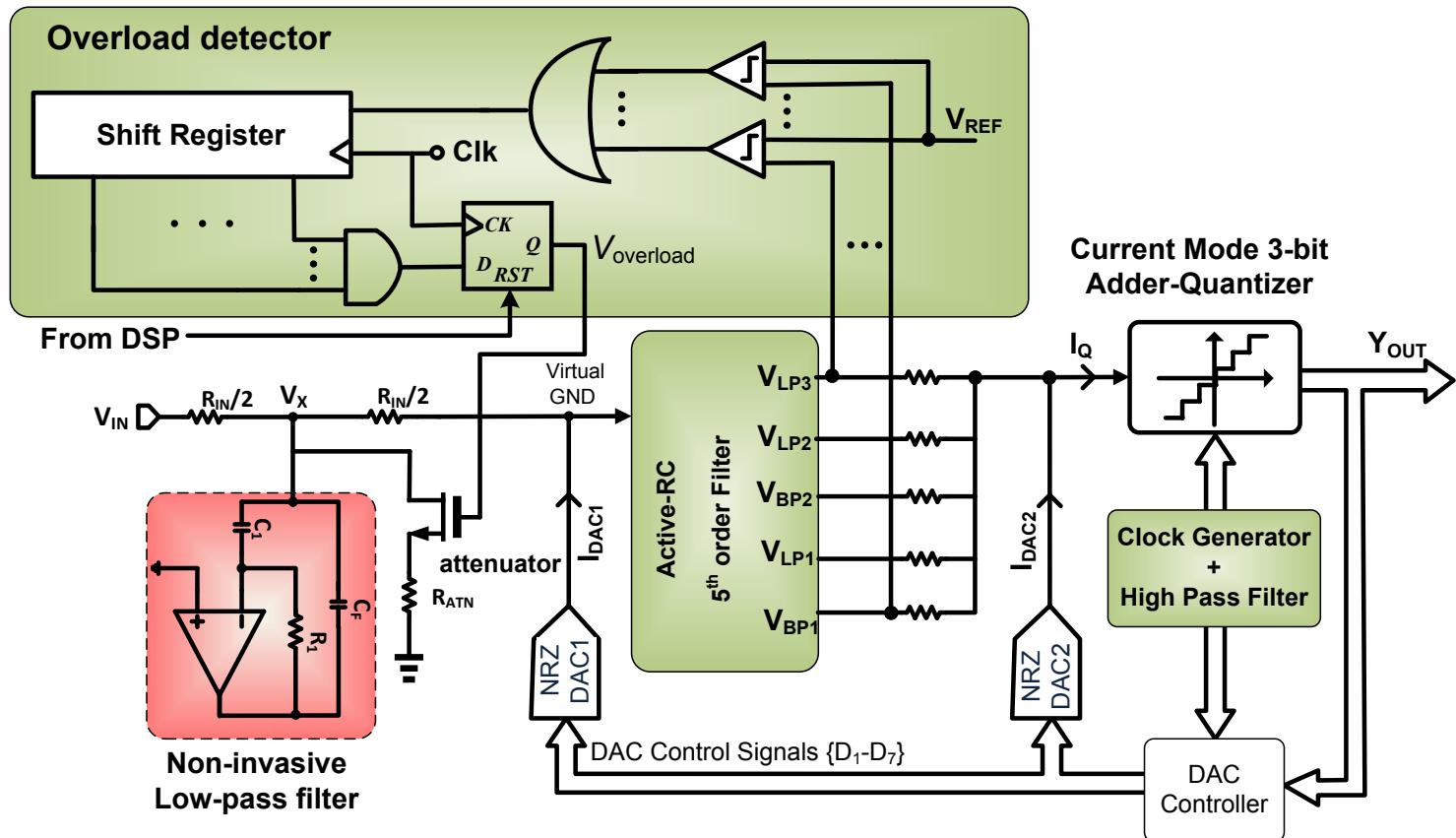


- Static blocker filtering through the Non-invasive LPF
- Agile/fast blockers are attenuated through the Overload detector and attenuator

SNR in the Presence of a Blocker

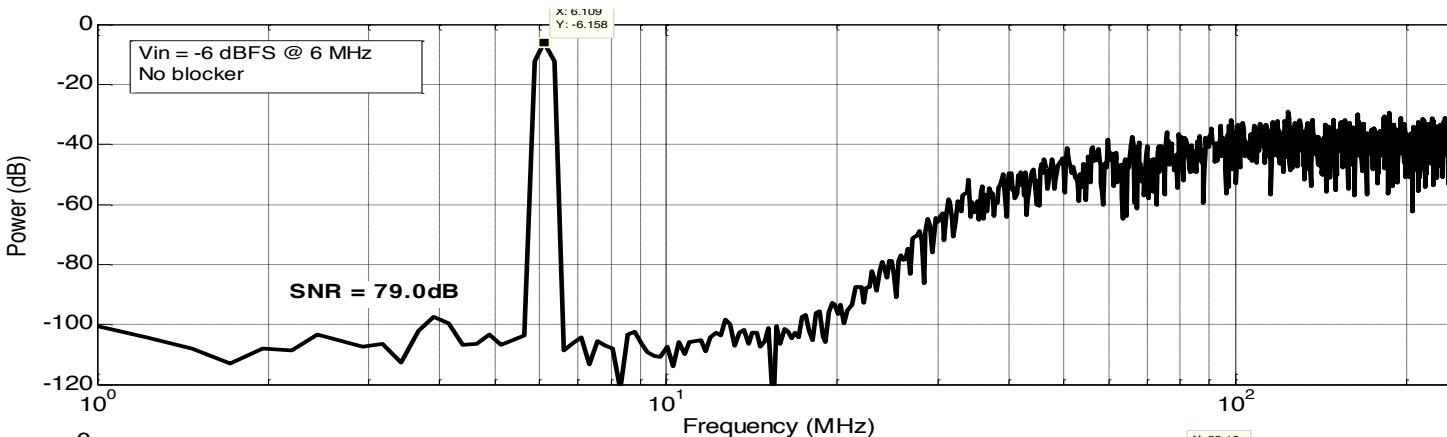

No blocker
Quasi-Linear
system

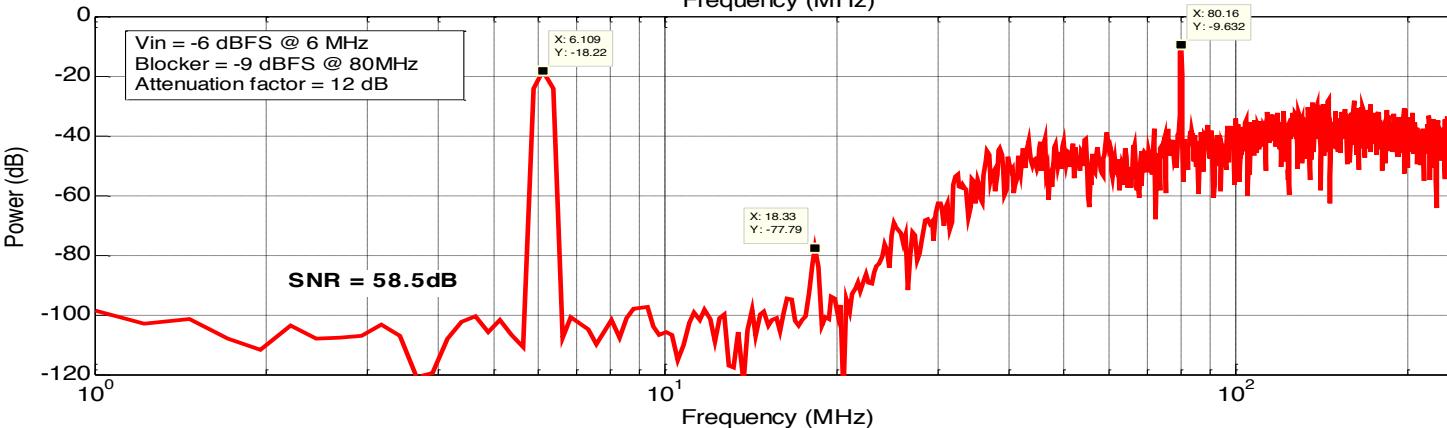


Saturation
detector
attenuates the
input signal by
12dB


- SNR degradation in the presence of blocker is 29dB
- Additional decrement in SNR is due to rise in noise floor
- High internal voltage swings tends to push the system into the non-linear regime.
26

Loop Settling Time = 0.5 μ sec


Input signal

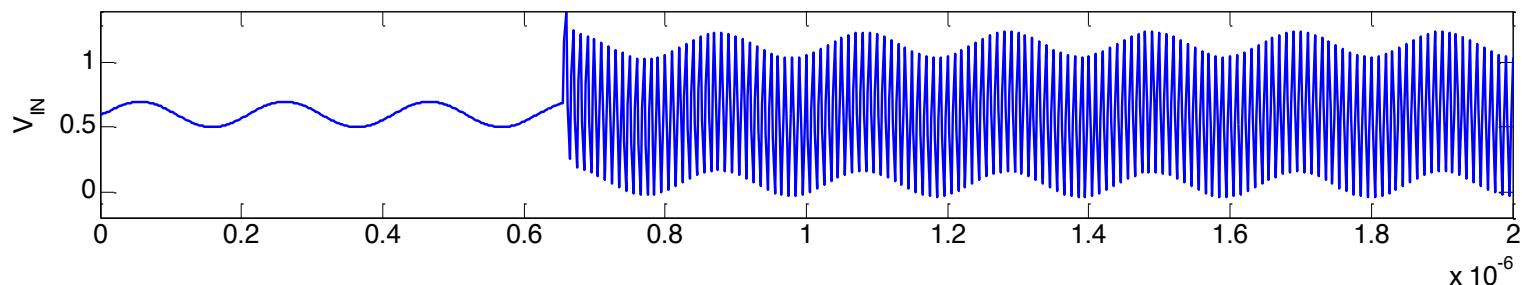

Saturation
detector
output

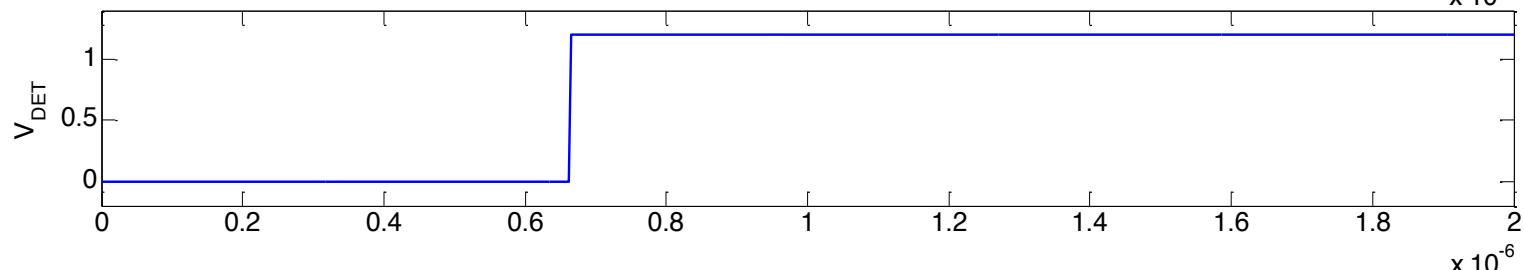


ADC output

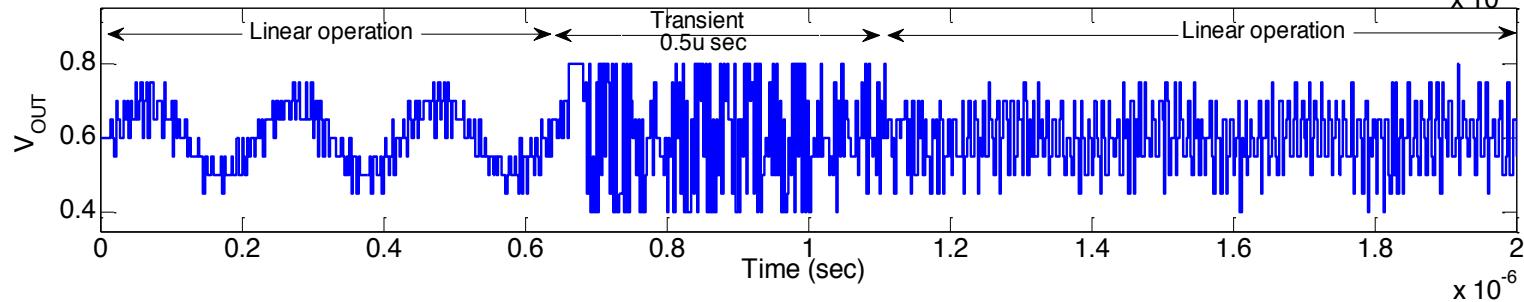


Transient response of the ADC to an 8dBFS blocker at 100MHz in
the presence of a -6dBFS in-band signal at 5MHz
ADC stabilizes again after 0.5 μ secs

Loop Settling Time < 0.2μsec


Input signal

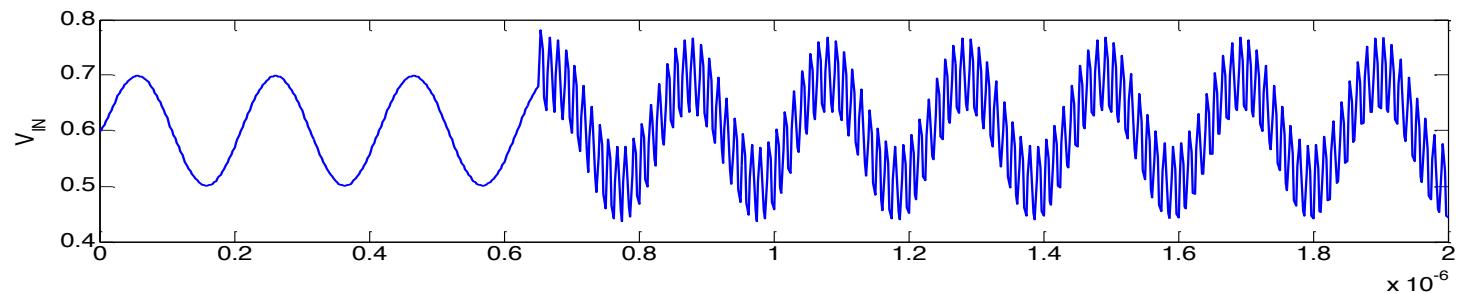

Saturation
detector
output

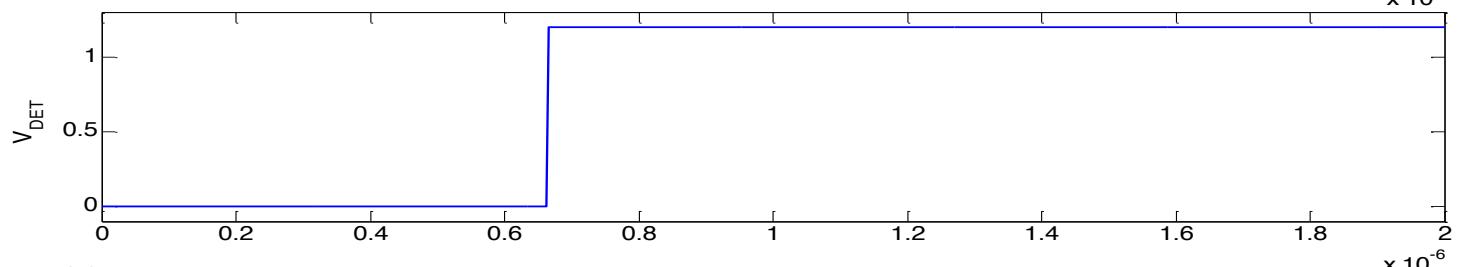


ADC output

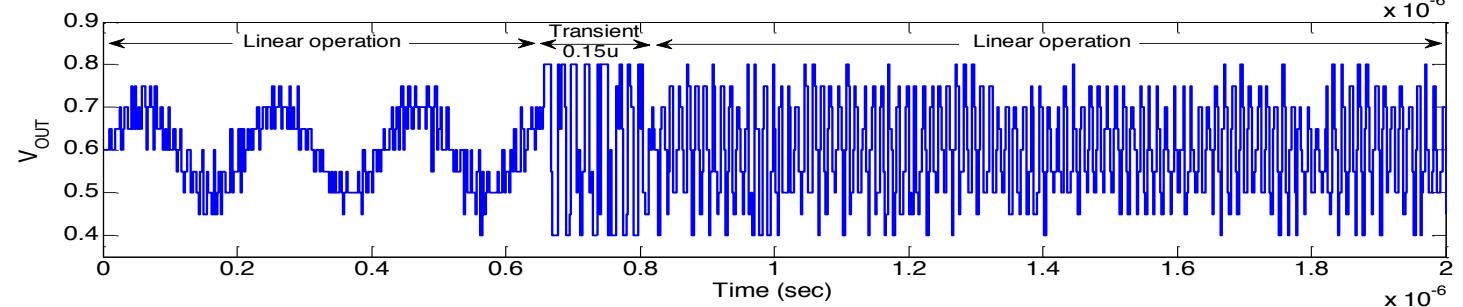


Transient response of the ADC to the -9dBFS blocker at 40MHz in the presence of a -6dBFS in-band signal at 5MHz
ADC stabilizes again after 0.15 μsecs

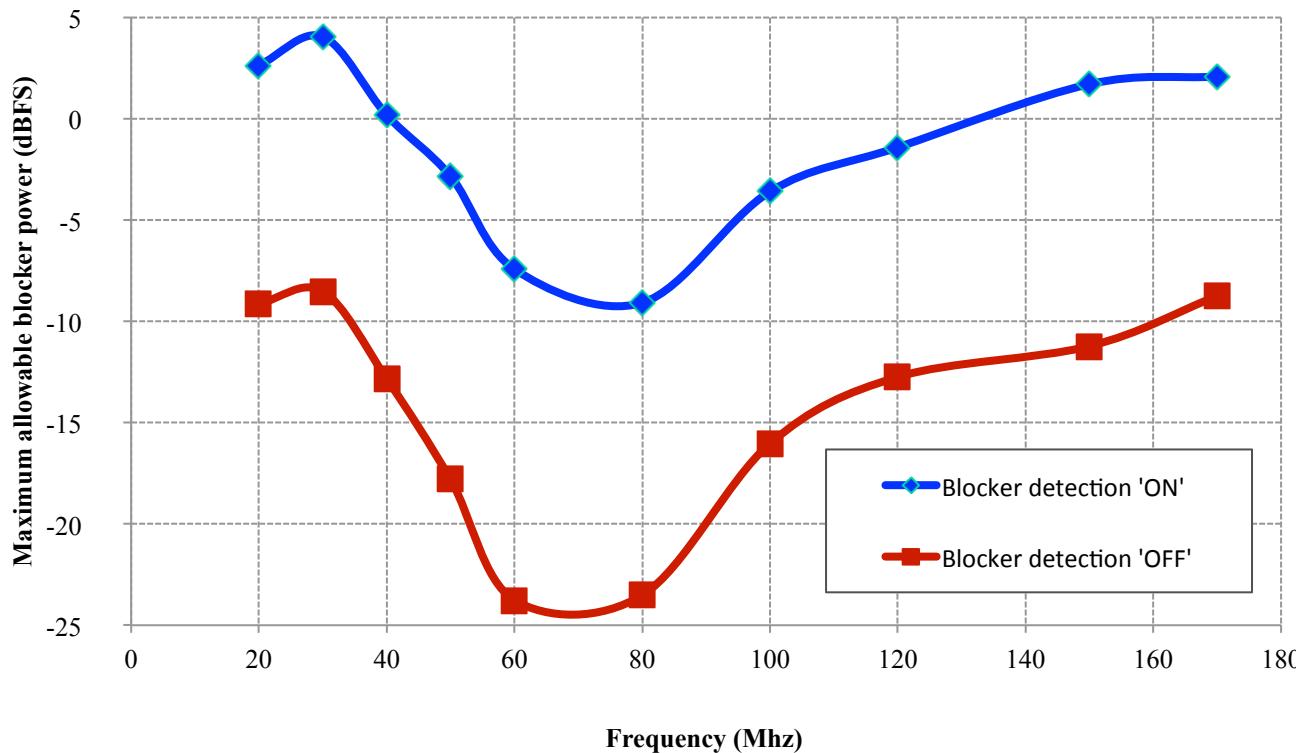Blocker Tolerance with a 0/12 dB Attenuator



- Blocker tolerance performance in the presence of a -6dBFS in-band input signal and various conditions of the blocker signal
- The proposed techniques improve the blocker tolerance of the system by >12dB

Post-Layout Simulation

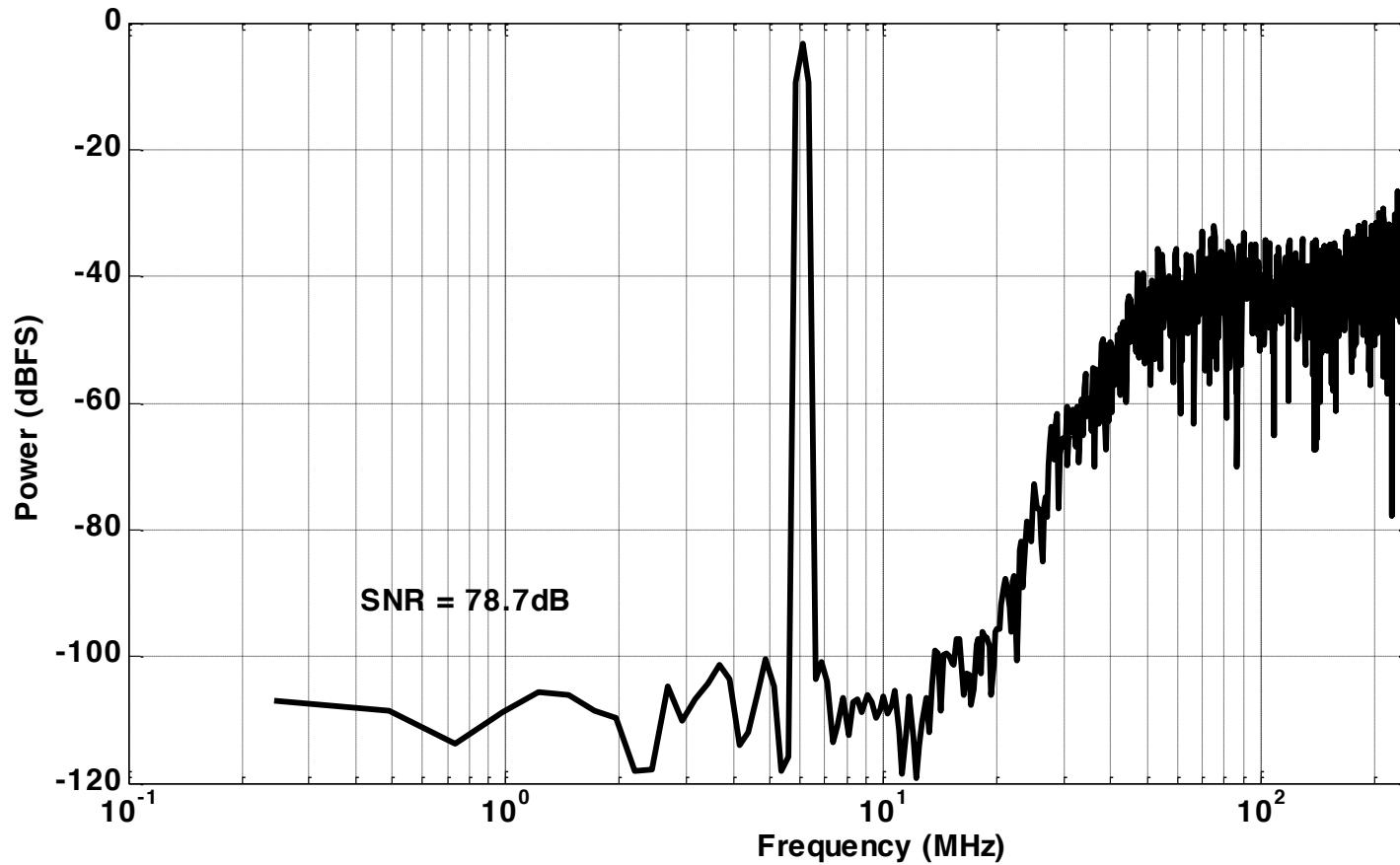

- SNR of the ADC from post-layout extraction
- Expected ENOB > 12 bits
- Tolerant to full-scale blockers



Summary: Blocker Tolerance

- Shunt complex impedance provides static blocker rejection especially at the critical frequencies.
- Overload detector and PGA prevents the ADC saturation during transients.
- Programmable complex impedance receives the signal from overload detector and toggles between Normal and Blocker suppression mode.

Advantages

- 👉 Less power
- 👉 Loop parameters are not disturbed so fast settling times
- 👉 Protects the ADC from instantaneous/temporary blockers
- 👉 Moderate SNR is better than no communication or no SNR

Proposed Architecture and Layout

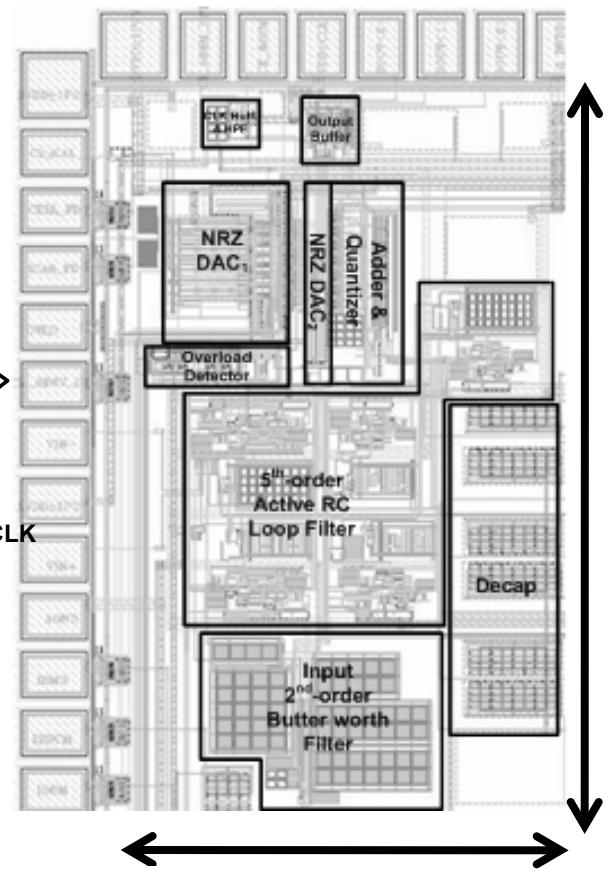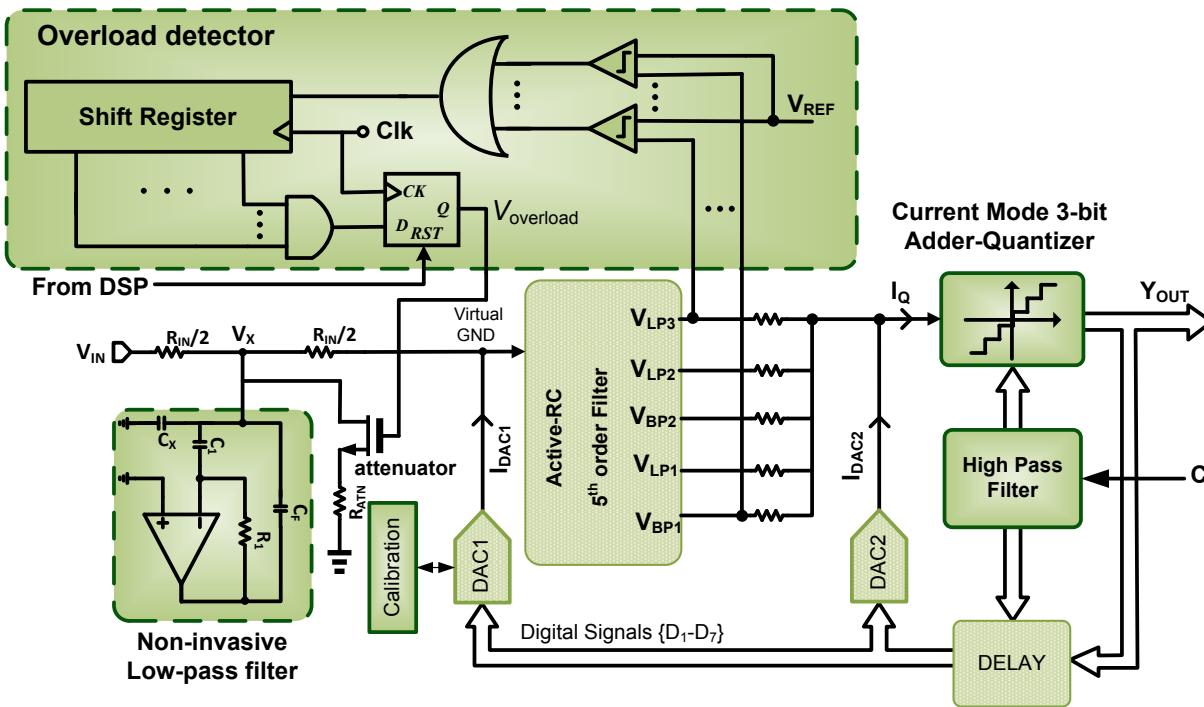

- Layout of the entire ADC using IBM 90nm CMOS process with 1.2x0.6mm² area
- Expected characterization: Late October 2011

Performance Summary of the ADC

Signal Bandwidth	20MHz
Oversampling Ratio	12.5
Order	5
Number of Quantizer Levels	8
Peak SNDR/SQNR	74dB/79dB
Maximum Stable Input Amplitude	-3dBFS
Blocker Tolerance in the Presence of a -6dBFS In-Band Signal	-9dBFS @ 80MHz
Settling Time After Blockers	<0.5μS
Static Power Consumption (ADC Core)	< 25mW
FOM (ADC Core)	154fJ/conv-step

Status of the Project

- Two targets are proposed for the task 1806.038:
 1. 12 bit $\Delta\Sigma$ data converter : Taped out and currently testing
 2. 15 bit $\Delta\Sigma$ data converter : Working on the schematic .
 - Currently developing low-power techniques to improve resolution of 15 bit $\Delta\Sigma$ data converter

Conclusions

- Digital DAC calibration is employed.
- Blocker rejection is achieved by overload detector, attenuator and shunt complex impedance.
- Jitter tolerance is improved by high-pass filtering the clock.
- 12 Bit ADC is implemented in a 1.2V, 90nm CMOS technology.
- 15Bit ADC is currently under design
- Mesh topology improves the SQNR, Embedded quantizer is a low power solution

Acknowledgements

SRC for supporting my PhD program

Analog and Mixed signal centre (AMSC), Texas A&M University,
students

Jazz-Semiconductor support for chip fabrication.

NSF for their partial support

C.T. Fu, H. Xu, J. Duster and R. Bishop of Intel Corporation.

Intel Corporation

Publications

1. **H. M. Geddada**, J. Silva-Martinez and S. S. Taylor, “Fully Balanced Low-Noise Transconductance Amplifiers with $P_{1dB} > 0\text{dBm}$ in 45nm CMOS,” IEEE European Solid-State Cir. Conf., Sept 2011.
2. **H. M. Geddada**, J. Silva-Martinez and S. S. Taylor, “Inductorless wideband CMOS LNAs with non-linearity cancellation,” IEEE MWSCAS. Conf., Aug 2011. **(Best student paper award)**
3. J. Silva-Martinez, A. I. Karsilayan, **H. M. Geddada**, Aravind Padyana, C. J. Park, “A Blocker Tolerant Broadband Analog-to-Digital converter architecture” Techcon conference, SRC, Sep 2010.

Publications

4. **Geddada H. M. ;Park, J.W.; Silva-Martinez, J.** “Robust Derivative superposition Method for Linearizing Broadband LNA’s” IEE Electronics Letters Vol. 45 Issue: 9 April 2009 (**Top 2nd paper accessed for the month of May 2009**).


Q&A

Back up slides

Comparison with Prior Art


	Blaakmeer JSSC-2008	Ramzan ISSCC-07	Chen JSSC-08	Van de Beek ISSCC-08	This work Balun-LNA
Technology	65nm	0.13μm	0.13μm	45nm	0.18μm
BW [Ghz]	0.2~5.2	1~7	0.8~2.1	0.6~10	0.3~2.8
Av [dB]	13~15.6	17	**14.5	10	**9.6~12.5
NF [dB]	2.9~3.5	2.4	2.6	3	5.95~6.5
IIP3 [dBm]	0~4	-4.1	16.0	6.0	16.8
P_{1dB} [dBm]			-11	-	0.5
Vdd[v]	1.2	1.4	1.5	-	2
Power [mW]	14	25	17.4	30*	14.2
No. of coils	0	0	0	2	0
Area (mm ²)	0.009	0.019	0.0992	-	0.06
FOM	16.22	6.343	102.3		34.3

Target 2: 15bit $\Sigma\Delta$ Modulator

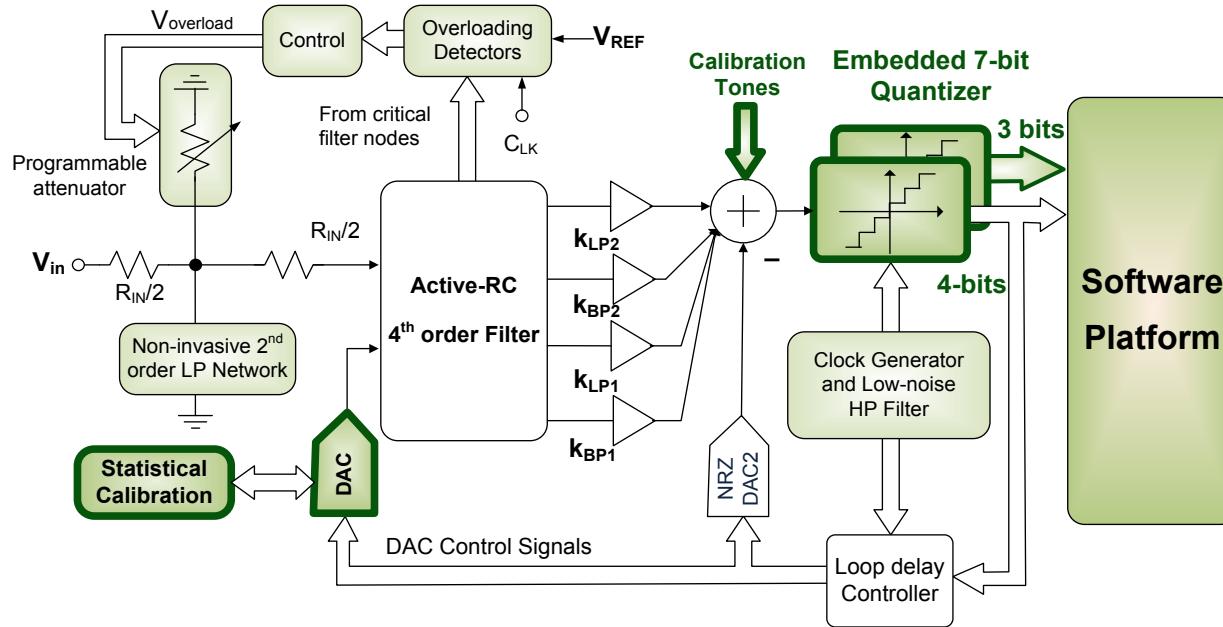

- Embedded 7-bit quantizer to improve the SQNR
- MSB 4 bits are used for the feedback
- Entire 7-bits are used to process modulator's output.


Target 2: 15bit $\Sigma\Delta$ Modulator

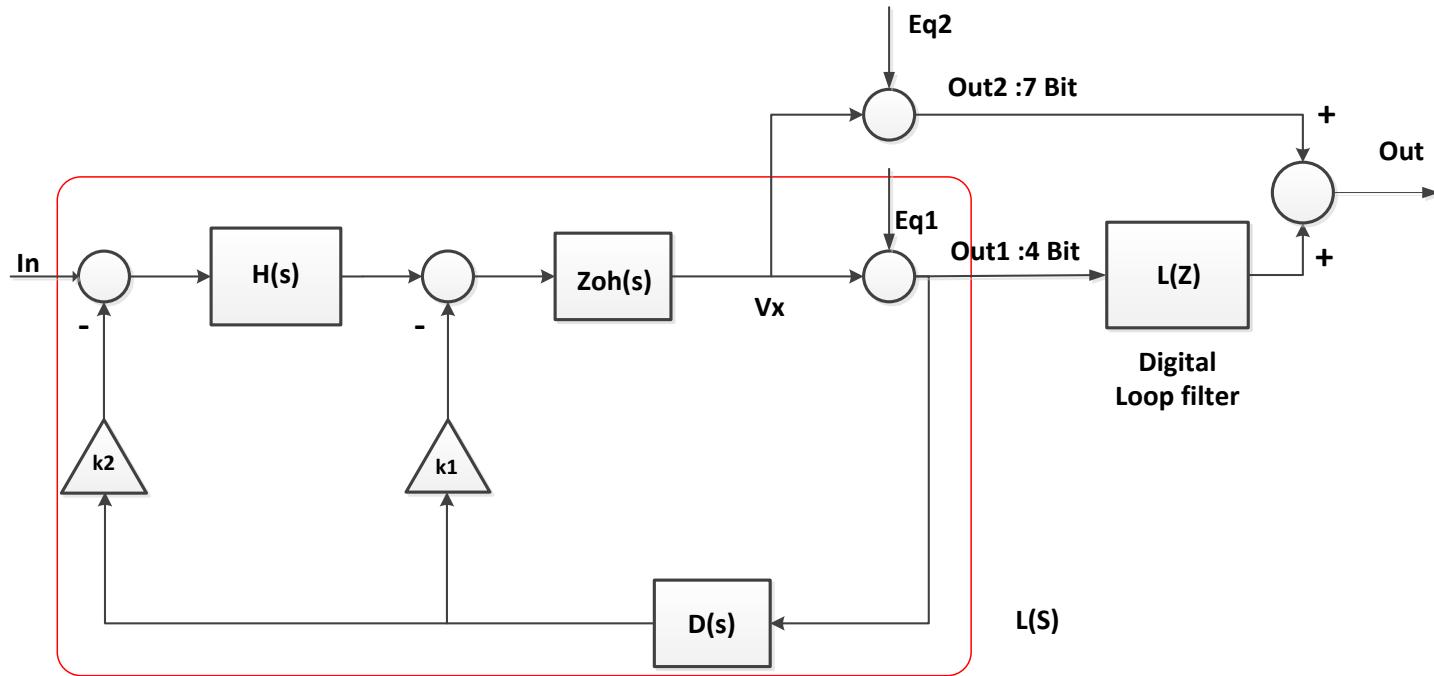

- Model showing quantization noise ($Eq1$) cancellation through Mesh topology.
- Embedded 7-bit quantizer to improve the SQNR


$$L(Z)|_{z=e^s} = L(S) \text{ for proper cancellation of } Eq1$$

Target 2: SQNR improvement

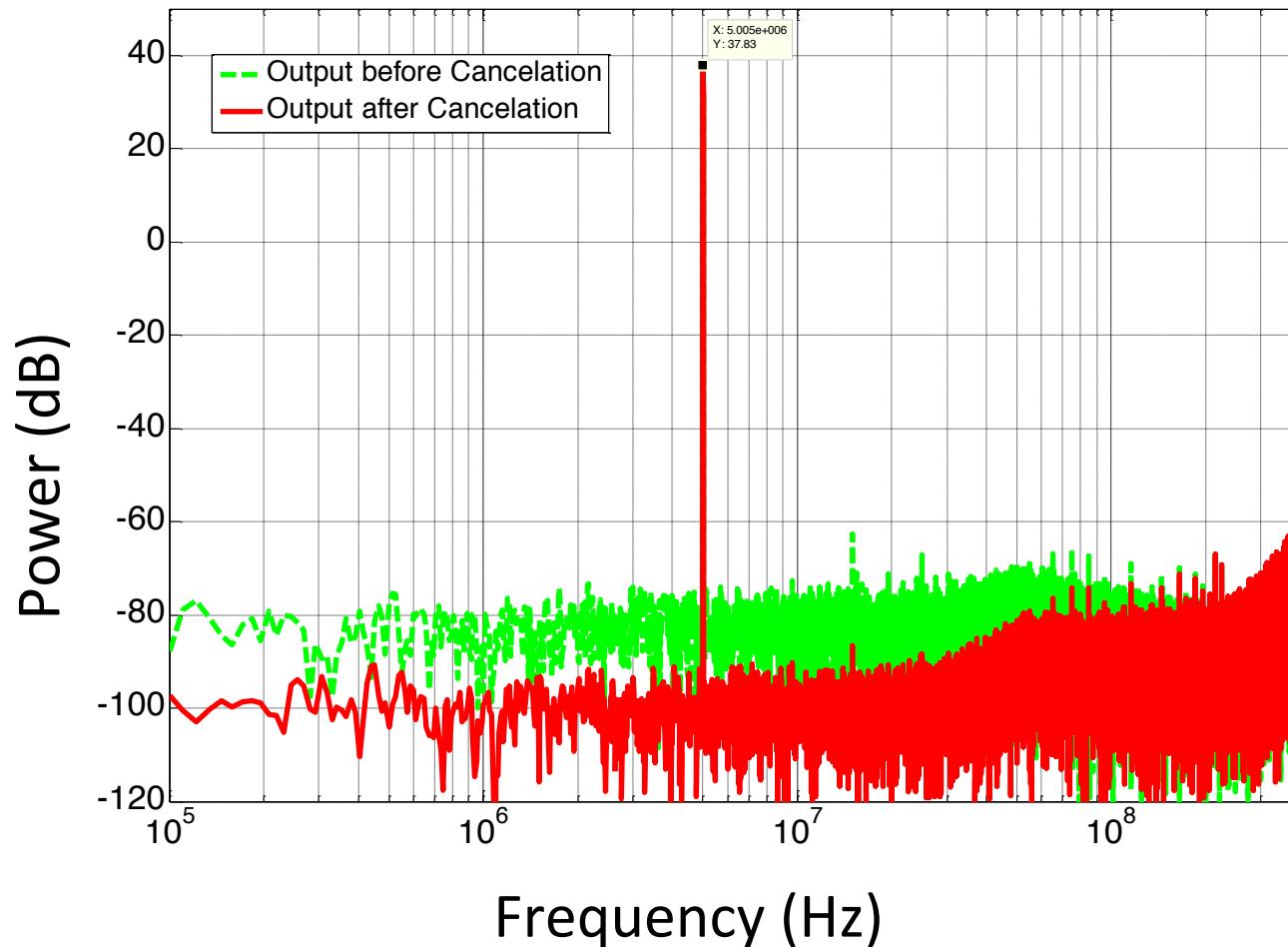


- SQNR improvement > 20dB

Sensitivity

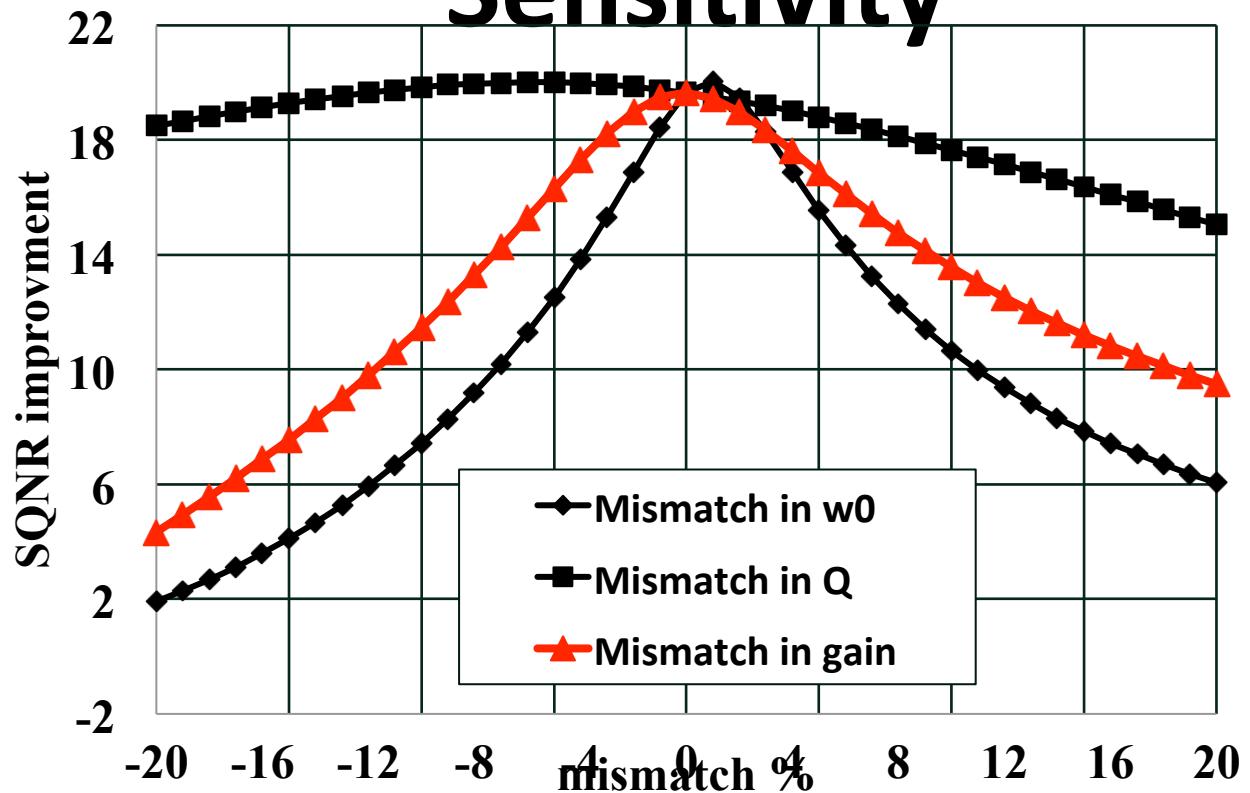

- SQNR sensitivity to mismatch in $L(Z)$ and $L(S)$.


Embedded 7 Bit Quantizer

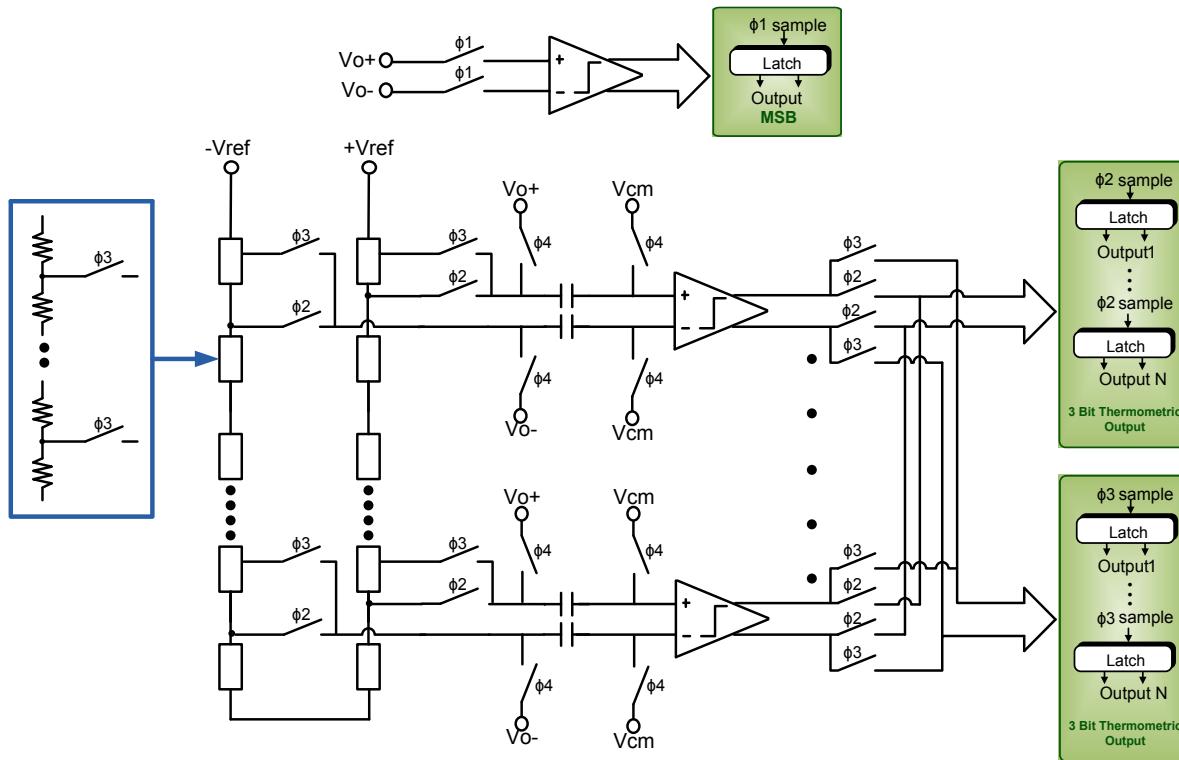

- 3 Step quantizer
- Low power solution


- **ϕ_1 Solve MSB**
- **ϕ_2 Depending on MSB, place the sampling capacitors in the proper location and solve 3 coarse bits**
- **ϕ_3 Move the capacitors to the proper segment and solve 3 fine bits**
- **ϕ_4 Sample the signal for the next iteration.**

Closed-Loop Transfer Functions

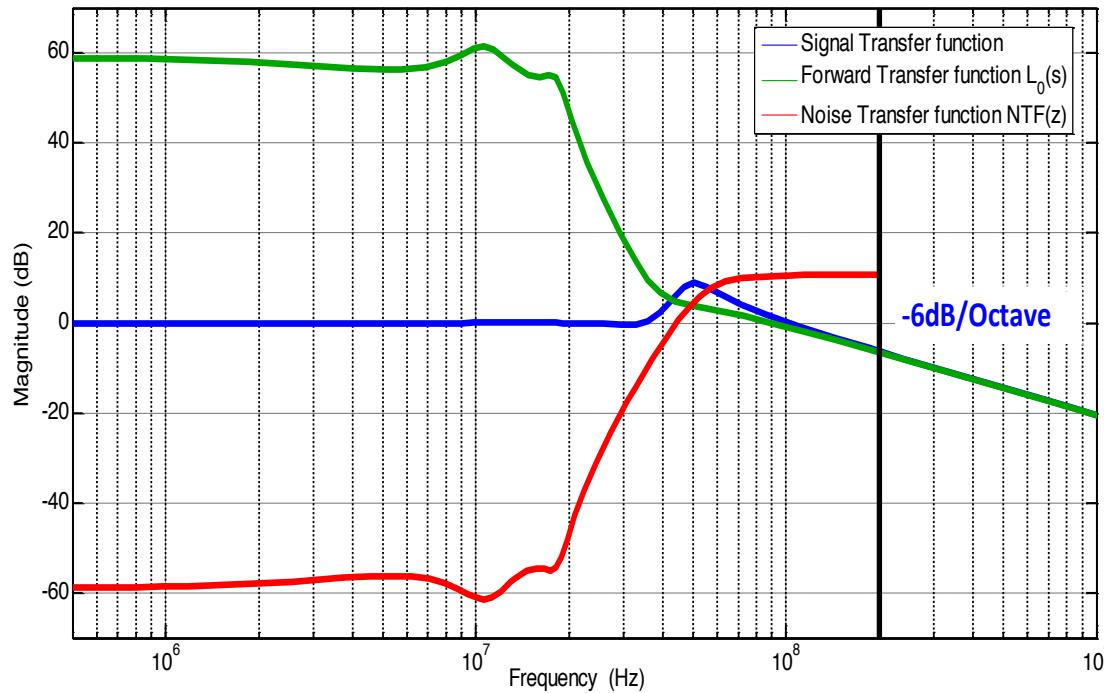

- First-order high frequency roll-off for both STF and Filter transfer function
 - Out of band peaking in the STF
 - Around 10 dB NTF gain
-
- Potential saturation issues around 30-100 MHz

Target 2: SQNR improvement

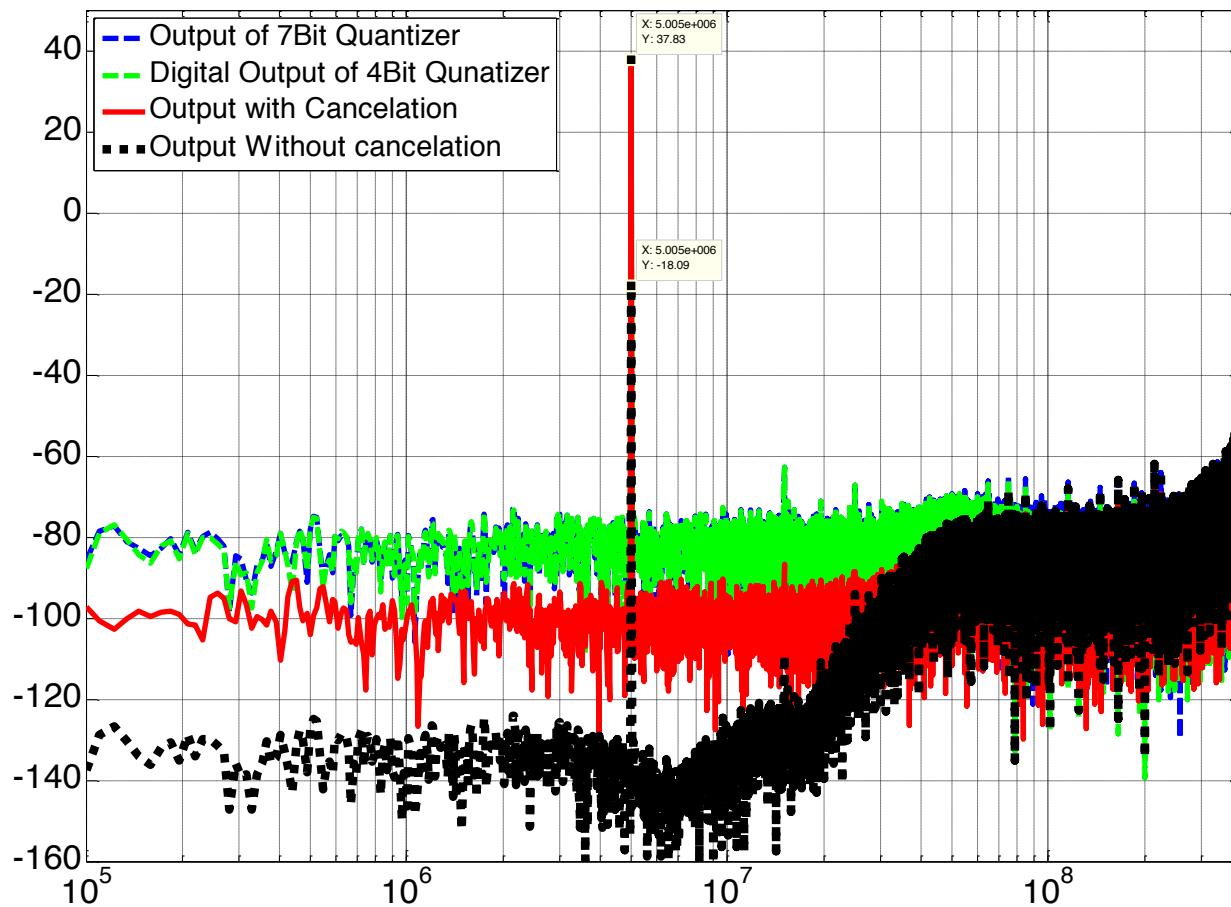

- SQNR improvement